RADIO & TELEVISION

NEWS

JULY 1954 as cents



IN THIS ISSUE

PIONEER AMATEUR STATION

A 35-WATT "MFINITE FEEDBACK" AMPLIFIER

A SIMPLE GEIGER COUNTER

INSTALLING A COLOR TUBE

2-METERS IN THE FAMILY CAR

TROUBLESHOOTING

FUNDAMENTALS OF COLOR TV

THE CURVE THAT CONFORMS

AERIAL "PRIVATE EYE" TRACES TV SIGNALS
(See Page 45)



GET OFF THE SPOT





AND INTO THE SPOTLIGHT


WITH THE

RAYTHEON

BONDED ELECTRONIC TECHNICIAN PROGRAM

Once you gain the confidence of customers, you're on your way to increased volume and profits. The Raytheon Bonded Electronic Technician program is designed to help you do just that. The Raytheon Registered Bond Certificate, the Raytheon Creed Display Decal and Identification Cards, featuring your bonded status and the fine Raytheon "Code of Ethics", inspire customer confidence. And a recent survey proved that wherever Raytheon Bonded

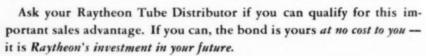Technicians took full advantage of their Bonded status — used it to inspire customer confidence — business improved by at least ten per cent.





RAYTHEON MANUFACTURING COMPANY

Asserting Table Divinto

Mann, Chingen, Ill., Atlanta, Co., Co. Avantos, Cul-

RAYTHEON MAKES ALL THESE:


RAYTHEON

Demoklation to DI- A - In

WILL TRAIN YOU AT HOME GOOD PAY JOBS 2 FREE BOOKS

America's Fast Growing Industry Offers You Good Pay-Bright Future-Security

SE

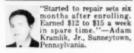

op to our necks in Radio-Television work. Four other NRI men work here. Am happy with my work."— Glen Peterson, Bradford, Ont., Canada. 'Up to our necks in Radio-



"Am doing Radio and Television Servicing full time. Now have my own shop. I owe my success to N.R.1."—Curtis Stath, Ft.

"Am with WCOC. NR1 course can't be beat. No trouble passing 1st class hone license exam." W. Parker, Meri-




"By graduation, had paid for course, car, testing equipment. Can service toughest jobs."—E. J. Streitenberger, New Bos-

Training plus opportunity is the PERFECT COMBINATION for job security, good pay, advancement. In good times, the trained man makes the BETTER PAY, GETS PROMOTED. When jobs are scarce, the trained man enjoys GREATER SECURITY. NRI training can help assure you more of the better things of life.

Start Soon to Make \$10, \$15 a Week Extra Fixing Sets

Keep your job while training. I start sending you special booklets that show you how to fix sets the day you enroll. Multitester built with parts I send helps you make \$10, \$15 a week extra fixing sets while training. Many start their own Radio-Television business with spare time earnings.

My Training Is Up-To-Date

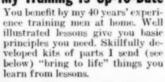



Television Making Good Jobs, Prosperity—Even without Television, Radio is bigger than ever. 115 million home and auto Radios to be serviced. Over 3000 Radio-broadcasting stations use operators, technicians, engineers. Government, Aviation, Police, Ship, Micro-wave Relay, Two-Way Radio Communications for buses, taxis, trucks, etc., are important and growing fields. Television is moving ahead fast.



on the air. Hundreds of others being built. Good TV jobs opening up for Technicians, Operators, etc.



Radio-TV Needs Men of Action-Mail Coupon

Act now to get more of the good things of life. Actual lesson proves my training is practical, thorough. 64-page book shows good job opportunities for you in many fields. Take NRI training for as little as \$5 a month. Many graduates make more than total cost of training in two weeks. Mail coupon now. J. E. SMITH, President, National Radio Institute, Dept. 4GE, Washington 9, D. C. OUR 40TH YEAR.

	with	1 Pa	rts l	Sen	d
	That's why	y NRI trainin	g is based of I furnish to	AL EXPERIENC n LEARNING build many circ	BY
	cations Cou	arse, you build shown at left.	many things, You put it "	art of my Commi including low po on the air," perfo operators. With	we
	procedures	O	Servicing modern titester	Course you be Radio, etc. Use M you build to m	uile Iul ak
100	C	THE	dents extra	xing sets. Many a make \$10, \$15 w fixing neighbors' a re time while tra	reel
الله			ing. (bring equipm	Coupon below to book showing of nent you build.	wil
Bo	00	33	1.00	Tested W	/a

You Learn by Practicing

Good for Both-FREE	The ABC's of SERVICING
MR. J. E. SMITH, President, Dept. 4GE National Radio Institute, Washington 9, D. C.	200
Mail me Sample Lesson and 64-page Book, FREE. (No salesman will call. Please write plainly.)	LoRe 8
NameAge	Success .
Address	PLEIDE
CityZoneState	195
VETS of disheres	-

RADIO & TELEVISION NEWS is published monthly by Ziff-Davis Publishing Company, William B. Ziff. Chairman of Chicago 1, Ill. Entered as second-class matter July 21, 1948, at the Fost Office, Chicago, Ill., under the act of Marment, Ottawa, Canada, as accond-class matter, SubSCRIFTION RATES: Radio & Television News-one year U. S. and Union countries 84.50; all other foreign countries 85.00. Radio-Electronic Engineering Edition—one year U. S. and Union countries 87.00. Pastmaster—Please return undelivered copies unside form

Editor and Asst. Publisher OLIVER READ, D.Se., WIETI

Managing Editor WM. A. STOCKLIN, B. S.

> Technical Editor H. S. RENNE, M. S.

Service Editor CHARLES TEPFER

> Assistant Editura P. B. HOEFER M. C. MAGNA

Television Consultant WALTER H. BUCHSBAUM

> Short-Wave Editor KENNETH R. BOORD

> > Art Editor FRANK SAYLES

Draftsmen A. A. GANS, W2TSP J. A. GOLANEK

Advertising Manager L. L. OSTEN

Midwest Adv. Manager JOHN A. RONAN, JR.

> Western Adv. Manager JOHN E. PAYNE



COVER PHOTO: Part of the measuring equipment used by Tele-Beam Industries in making their aerial surveys to determine television station signal strength and service coverage. (Ektachrome by Peter J. Samerjan)

ZIFF-DAVIS PUBLISHING COMPANY

B. O. DAVIS

Vice-Presidents H. J. MORGANROTH M. H. FROELICH

> Secretary-Treasurer G. E. CARNEY

Circulation Manager M. MICHAELSON

BRANCH OFFICES CHICAGO (1)

LOS ANGELES (14) Statler Center, 900 Wilshire Blvd., Mich. 9850

First in radiotelevision - audio - electronics Average Paid Circulation over 230,000



Reg. U. S. Pat. Office o Television News Trademark Reg. U. S. Pat. Office.

CONTENTS

JULY, 1954

From Catswhiskers to Color—An Editorial	Oliver Read
A Pioneer Amateur Station	Paul G. Watson
A Simple Geiger Counter	. Fechter & Dr. M. R. Boyd
Troubleshooting 3-Way Portables	James A. McRoberts
2 Meters in the Family Car	Walter S. Rogers, W1DFS
A 35-Watt "Infinite Feedback" Audio Amplifier	Charles P. Boegli
Aerial "Private Eye" Traces TV Signals	
Elimination of R.F. Interference in Audio Systems	
Installing a Color Picture Tube	
The Curve that Conforms	*********************************
P.A. Rentals—A Profitable Sideline	Oliver Berliner
A Bass-Boost Control	Allan M. Ferres
1954 TV Receiver Specifications	************
TVI Troubleshooting (Part 3)	
Servicing Hi-Fi	David Fidelman
Certified Record Revue	
Magnetic Recording 1888 to 1954	Leon A. Wortman
Fundamentals of Color TV—Chrominance Circu	its (Part 5) Milton S. Kiver
Mac's Radio Service Shop	John T. Frye
The ARTSNY Story	
Save That Rectifier	John P. Fath
New TV Stations on the Air	
New TV Grants Since Freeze Lift	
Radio-TV Service Industry News	

DEPARTMENTS

Spot Radio News	12	What's New in Radio	82
Within the Industry	26	Technical Books	101
Short-WaveK. R. Boord	64	New Audio Equipment	118
Manufactu	rers'	Literature 126	




COPYRIGHT 1954 (All Rights Reserved) ZIFF-DAVIS PUBLISHING COMPANY WILLIAM B. ZIFF (1898-1953) FOUNDER Editorial and Executive Offices 366 Madison Ave., New York 17, N. Y. VOLUME 52 • NUMBER 1



SUBSCRIPTION SERVICE: All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Leas St., Chicago I, III. Subscribers should allow at least four weeks for change of address. Contributions and evident contributions of address. Contributions should be malled to the New York Editorial Office and test and test of the New York Editorial Office and test of the St. Contributions of the New York Editorial Office and test of the New York Editorial Office of the New York Editori



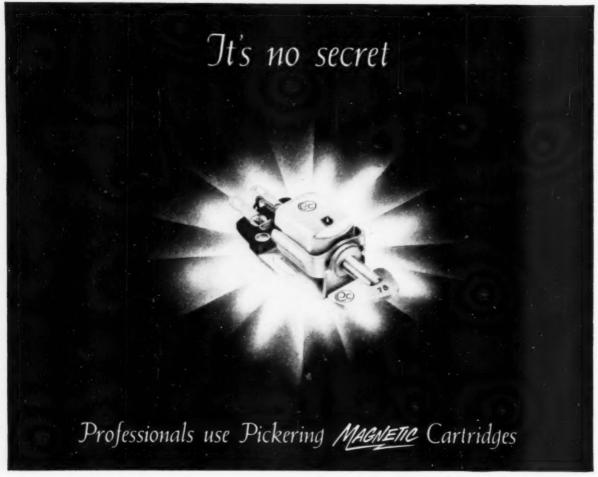

You're in the best of company if you use a Pickering Magnetic Cartridge. You have this in common with:

- 1. Leading record companies who use Pickering Cartridges for quality control.
- 2. Leading FM/AM good music stations and network studios.
- 3. Leading manufacturers of professional equipment for radio stations, recording studios, wired music systems and automatic phonographs, who install Pickering Cartridges for the maximum performance of their equipment.

Why Pickering Magnetic Pickups are the Choice of Recording and Broadcast Engineers!

"All modern disc recordings are made with MONETIC cutters. Within the geometrical and mechanical limitations of recording and reproducing equipment, a Pickering Pickup will re-generate an exact replica of MONETIC cutter response to the original program of music, speech or sound. This is a fundamentally inherent characteristic of the Pickering Pickup, supported by basic electromagnetic theory and countless

precise laboratory measurements. This is why Pickering Mastelle Pickups provide the most nearly perfect coupling possible, between reproducing equipment and original program. This is why they sound cleaner...less distorted.

"Through the medium of the disc material, the reproducing system is effectively driven by the cutter electrical response itself."



PICKERING and company incorporated • Oceanside, L. I., New York


PICKERING PROFESSIONAL AUDIO COMPONENTS

"For those who can hear the difference"

. . . Demonstrated and sold by Leading Radio Parts Distributors everywhere. For the one nearest you and for detailed literature write Dept. C-5



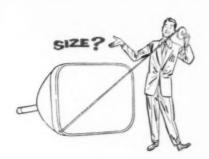Make old sets like new...have more satisfied customers!



Interested in new sales records? You'll be heading in that direction when you replace old picture tubes with new Sylvania Aluminized Tubes.

Sylvania Aluminized Picture Tubes give terrific performance. They make old sets better and brighter than new by providing whiter whites—blacker blacks . . . a 6-times better picture contrast.

Sylvania Aluminized Picture Tubes are now available in most sizes for all popular TV sets. In other words, with Sylvania Aluminized Picture Tubes, you give your customers the best possible buy and the best possible service, including a full one-year warranty.

Remember, millions of set owners see and hear about Sylvania Picture Tubes on the nation-wide weekly television show "Beat The Clock." They know that they are famous for quality and dependability. For full details about aluminized tube replacement, write for Sylvania's "Aluminized Picture Tube Replacement Guide." Address: Dept. 4R-3507, Sylvania NOW!





SYLVANIA

Sylvania Electric Products Inc.

1740 Broadway, New York 19, N. Y.

In Canada: Sylvania Electric (Canada) Ltd. University Tower Building, St. Catherine Street, Montreal, P. Q.

LIGHTING . RADIO . ELECTRONICS . TELEVISION



50 Years of Setting Standards

Ray L. Triplett with the first commercial tube tester a Triplett production—and Triplett Model 3423, the leading tube tester of today and tomorrow. See it at your parts jobber. Model 3423 Mutual Conductance Tube Tester. Dealer's net \$199.50



The only tube tester designed with 50 years experience. Two important lessons are learned, from experience, by the manufacturer of test equipment. First, the value of test equipment to a service man is in direct proportion as it reduces his necessary labor and increases his profit for the same span of work time. Model 3423 will give you no false readings to waste time—the patented circuit for tube testing employs actual signal (4KC) for grid signal. It also has a complete coverage of all tube types—six plate voltages (including 0-10 variable). Micromhos scales read 0-1800, 0-6,000, 0-18,000 and 0-36,000.

Secondly, test equipment costs money and the purchaser must be protected against quick obsolescence. In Model 3423 the multiple switches allow making any combination of tube connections and is protection against such obsolescence.

Ask your jobber to demonstrate the many other extra features of this tester.

Only Triplett offers you a ten day free trial on all test equipment.



Electrical Instrument Co. Bluffton, Ohio

ADVANCE! Raise your earning power-learn RADIO-TELEVISION-ELECTRONICS by SHOP-METHOD MASTER ALL PHASES! OME TRAINING

GOOD JOBS AWAIT THE TRAINED RADIO-TV TECHNICIAN

There is a place for you in the great Radio-Television-Electronics industry when you are trained as National Schools will train you at home!

Trained technicians are in growing demand at good pay -in manufacturing, broadcasting, television, communica-tions, radar, research laboratories, home Radio-TV service, and other branches of the field. National Schools Master Shop-Method Home Training, with newly added lessons and equipment, trains you in your spare time, right in your own home, for these fascinating opportunities. OUR METHOD IS PROVED BY THE SUCCESS OF NATIONAL SCHOOLS TRAINED MEN, ALL OVER THE WORLD, SINCE 1905.

EARN WHILE YOU LEARN

Many National students pay for all or part of their training with spare time earnings. We'll show you how you can do the same! Early in your training, you receive "Sparetime Work" Lessons which will enable you to earn extra money servicing neighbors' and friends' Radio and Television receivers, appliances, etc.



National Schools Training is All-Embracing

National Schools prepares you for your choice of many job opportunities. Thousands of home, portable, and auto radios are being sold daily-more than ever before. Television is sweeping the country, too. Co-axial cables are now bringing Television to more cities, towns, and farms every day! National Schools' complete training program qualifies you in all fields. Read this partial list of opportunities for trained technicians:

Business of Your Own • Broadcasting Radio Manufacturing, Sales, Service • Telecasting Television Manufacturing, Sales, Service Laboratories: Installation, Maintenance of Electronic Equipment **Electrolysis, Call Systems** Garages: Auto Radio Sales, Service Sound Systems and Telephone Companies, Engineering Firms Theatre Sound Systems, Police Radio And scores of other good jobs in many related fields

TELEVISION TRAINING

You get a complete series of up-to-theminute lessons covering all phases of repairing, servicing and construction. The same lesson texts used by resident students in our

modern and complete Television broadcast studios, laboratories and classrooms!

FREE RADIO-TV BOOK AND SAMPLE LESSON! Send today for

National Schools' new, Illustrated Book of Oppor-tunity in Radio-Television

Electronics, and an actual Sample Lesson. No costno obligation. Use the coupon now-we'll answer by return alrmail.

APPROVED FOR VETERANS AND **NON-VETERANS** Check coupon below

Resident and **Home Study** Courses Offered!

ATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA . ESTABLISHED 1905 IN CANADA: 811 W. HASTINGS STREET, VANCOUVER, B.C.

VETERANS: Give Date of Discharge...



uperheterodyne Receiver LEARN BY DOING

You receive and keep all the

modern equipment shown above, including tubes and

valuable, professional quality Multitester. No extra

charges.

Home Training from an Established Practical Resident School with its own Training

Shops, Laboratories, Studios — almost 50 Years of Successful Experience in Training Ambitious Men.

You also

receive this

Multitester

We Bring National Schools To You!

GET FACTS FASTEST! MAIL TO OFFICE NEAREST NATIONAL SCHOOLS, Dept. RH-74 323 West Polk Street 4000 S. Figueroa Street or Los Angeles 37, Calif. Chicage 7, III.

Send FREE Radio-TV Electronics book and FREE sample lesson. No obligation, no salesman will call.

NAME	BIRTHDAY 1	9
ADDRESS		
CITY	ZONE STATE	-
Check here if intereste	ed in Resident School Training at Los Ana	eles



Now, National — world's most respected maker of professional radio receiving equipment — brings you a new concept in high-fidelity!

For 40 years, National has designed and manufactured extremely critical circuits for the armed forces (9 out of 10 Navy ships are equipped with National receivers), for the world's largest airports, for communication services, industry, radio amateurs and all those who demand optimum reception even under the most adverse operating conditions.

Only this hard core of radio experience could produce the New "Criterion" AM-FM Tuner, the heart of National's new

HORIZON line in high fidelity!

HORIZON *line in high fidelity*

On the entire line, National has lavished all the advanced engineering techniques and latest research available.

The result is an integrated high-fidelity system so unique in circuitry, so far ahead in performance and styling, it obsoletes present equipment on the market today!

Look for the new HORIZON line at your high fidelity headquarters this month! Meantime, write for complete specifications to Dept. RN 754, National Co., Inc. Malden, Mass.

HORIZON 20 20-Watt Amplifier

Incorporates a revolutionary new National circuit featuring "unity coupling"
— first major improvement in amplifier design since the Williamson circuit! \$84.95

HORIZON 5 Preamplifier-Control Unit

Lowest distortion (less than 1%) at highest output (15 volts). Distortion virtually unmeasurable at 1.5 volts output. Compensation for choice of 7 recording characteristics. Unique bass and treble controls permit compensation for speaker deficiencies and suppression of turntable rumble without affecting middle range. \$49.95

HORIZON 10 10-Watt Amplifier

The National "unity-coupled" circuit — new amplifier standard — in a 10-watt amplifier. Incorporates built-in preamplifier and complete equalization and tone control networks. \$79.95

HORIZON "Criterion" AM-FM Tuner

Simultaneous AM and FM reception with separate volume and tuning controls for individual or binaural listening. Exclusive new Mutamatic Tuning eliminates all hiss and noise between FM stations—
stations come in out of velvety silence, stay locked in. \$169.95 (less pre-amp)















Public Address Loudspeaker System

setting new standards for **VOICE PENETRATION** AND MUSICASTING

- Greatly outperforms comparably sized
- Tremendous penetrating power and coverage at very low unit energy cost
- Exclusive E-V coaxial design and diffraction principle
- Peak-free response ±5 db to 10,000 cps
- Delivers 21/2 octaves more musical range
- Weather-proof, blast-proof, splash-proof Virtually indestructible


Model 848 CDP. 25 watts, 16 ohms. List Price, \$69.50 Net, \$41.70

COMPARE POLAR PATTERN Sound distribution

at all frequencies up to 10,000 cps. COMPARE

RESPONSE AND EFFICIENCY Note extended high

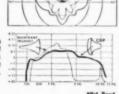frequency range of CDP. Response is smooth, peak-free ± 5 db to 10,000 cps.



Write for Free

410 CARROL ST. . BUCHANAN, MICHIGAN Export: 13 E. 40th St., New York 16, U.S. A. Cables: Arlab



* Presenting latest information on the Radio Industry.

By RADIO & TELEVISION NEWS' WASHINGTON EDITOR

THE BRIGHT HOPES, forecast for the ultra-highs, (which began to lose some of their iridescent luster a few months ago when v.h.f power boosts began sprawling signals over to areas earmarked for the high-band channels, network ties became more difficult to obtain, and low powers stumped u.h.f. coverage and audience appeal) were routed to the witness stand in Washington, in the late Spring, during one of the most unusual technological trials ever authorized. Here, for the first time, a Congressional body sought to find out why these new channels were in such trouble and what might be done to help.

Under the skilled guidance of Senator Charles Potter, members of an ultra-high association, telecasters, network operators, and even manufacturers set up a plan to review the variables that obtain on the higher bands and what might be applied as a prac-

tical solution.

As the trial convened, the number of upstair-station casualties continued to grow. WTAC-TV in Flint reported that they had to suspend operations because ad agencies and advertisers refused to accept the station, and this despite a 62 per-cent conversion rate in that city. According to the general manager of the station, the agencies and sponsors have just developed a "blanket aversion" to the use of a u.h.f. outlet if a v.h.f. station covers the market, even with an inadequate signal. It was noted that the Flint station had begun operating from a new \$125,000 building on Thanksgiving Day, 1953, and had been losing a minimum of \$10,000 a month, even though it was affiliated with ABC. The low-band signals, causing the economic problem, come from Detroit, Lansing, and Bay City.

In Atlantic City, WFPG-TV also reported it had run into trouble and was temporarily suspending operations, until Washington and others could provide a satisfactory solution. A statement released by management said that the station had, with the advent of superpower, lost 33 half-hours weekly of network and other topnotch programs. The program cancellations were received because the high-power metropolitan market v.h.f. stations 60 miles from Atlantic City had established a concept of coverage generally satisfying TV viewers. Con-

tinuing, the complaint added: "Therefore, extreme audience and economic loss compels suspension at this time, because WFPG-TV cannot now render a service of pride to the south Jersey area, for which it was planned, built, and dedicated."

St. Louis was also up in arms over the grant of a low-band permit to a second station owned by a newspaper. It was felt that this new grant would seriously upset ultra-high interest. The area had been assigned channels 14, 30, 36, 42, and 54, but because of economic problems 30 and 42 were not on the air, and 14 went off the air because the operators couldn't obtain network programs. Commenting on the upheaval caused by the low-band approval, one association spokesman said that the Commission must do something to prevent failure of the high-band system, and keeping new low-band operators off the air until u.h.f. is firmly established is one an-

swer.

Spartanburg, South Carolina, was also faced with a problem, according to the operators of two u.h.f. stations in that area. The condition appeared when the Commission permitted a station to shift its channel to 7 and move its transmitter atop a mountain. The u.h.f. owners claimed that this move hit their market, since the new site and channel will provide a stronger signal over the areas they now serve. The majority of the Commission held that the high-band owners advanced no substantial reasons against the change; the economic-injury allegations were called purely speculative. However, Madame Commissioner Frieda Hennock disagreed with her colleagues, and asked for a further inquiry. She felt that the shift would affect the high-band stations, for it . . "will bring into these two markets another competitor for the advertising revenue, and will seriously curtail the conversion of sets to receive u.h.f. programs.

The Commission received one proposal for a solution to the u.h.f. snarl from a California attorney. Recommended was the establishment of a subscription TV service restricted to u.h.f.; permission to telecast stills with sound for more than one hour daily, to give dealers and technicians more time to work with u.h.f. sets and converters; a requirement that networks

new values releases **Popular Knight** Portable Radio Knight **Build-Your-Own Kit** Super-Thin ortable Radio

It's easy to build this powerful 3-way superhet portable for AC, DC or battery operation. Tunes 535-1650 kc broadcast

80 J 651. Battery Kit. Only \$2.74

An ideal battery-operated personal portable, hardly thicker than a book. Advanced superhet circuit features low-drain tubes for 100 hours of battery life. Includes built-in loopatick antenna, PM speaker, easy-tuning thumbwheel controls, automatic volume control. Develops surprising power and wonderful tone quality. Housed in beautiful red plastic case, 6 x 9 x 2 ½ deep. With tubes (less batteries). Shpg. wt., 4 lbs. 54K717. Only. \$17.95 5 4K 717, Only

80 J651. Battery Kit. Only \$2.74

Ward Economy Auto Aerials

Word Economy Avis Aeriels
Low-cost top cowl auto antenna. Fits any model car;
easily and quickly installed
completely from outside of car.
Has 3 sections; telescopes to
56°. Of sturdy, durable tubing;
chrome-plated; with "8-ball"
mounting insulator. Complete
with 36° high. "Q" lead-in and
coaxial-type connector. A
value sensation; makes an
ideal auto serial replacement.
Spng. wt., 1 lb.
92 CX 000. Only......\$2.32
92 CX 001. As above, but with

92 CX 001. As above, but with 54" lead-in. Only \$2.54

Sav-A-Battery Rejuvenator—Plays Portables from A.C.

Permits the operation of portable radios using single $1\frac{1}{2}$ v. "A" and single $67\frac{1}{2}$ v. "B" batteries from AC outlet. Fits into battery compartment of set. Also serves as "B" battery rejuvenator. Easy to install. $3\frac{1}{2}$ x $2\frac{1}{2}$ x $1\frac{1}{2}$ ". For 105-125 v., 50-60 cycles AC. Shpg. wt., $1\frac{1}{2}$ lbs. 80 P 190. Only \$5.85



Exceptional value in a powerful, well-balanced drill. Has \(^{1}\)gear-type chuck with key. Heavy-duty universal series-wound motor; self-aligning ball thrust bearings; trigger switch. No-load speed, 2400 rpm; full load, 1500 rpm. Capacity in steel, \(^{1}\)gen in hardwood, \(^{1}\)gen Goverall length, \(^{9}\) to ILL approved. For 110-120 v., \(^{1}\)C or DC. Shpg. wt., 4\(^{1}\)gel lbs. \(^{1}\)Label{eq:13} (No. 100).



PE-101-C Dynamotor Buy



Ideal for control of room air con ditioners, etc. SPST type; turns equipment on or off once in 24

hours; minimum time between settings, I hour. Manual

78 § 323. Adapter Kit to make above unit portable. Consists of 6-ft. cord, plug. etc. Shpg. wt., 1 lb. Only... 986

New Fisher "50" Horn Speaker Enclosure

#1 DX 711. Korina Blonde. Net...... ALLIED RADIO



send for ALLIED'S

Latest Free Supplement

WITH ELECTRO-VOICE PROJECTORS. As above, but with two E-V 848 compound diffraction projectors in place of University trumpets, Features extended frequency response. 93 SX 633. Only \$182.50 3-SPEED PHONO TOP. Plays 78, 331/4 and 45 rpm records. Highest quality; with turnover crystal cartridge. 93 SX 640. Only ... \$17.45

Best Buy Knight Push-Button Tape Recorder

Top Recorder Value-NOW with **Remote Control Provision**

Remote Control Prevision

Latest model—acclaimed "best buy" by recording fans. Five push-buttons select all operating functions: fast forward, playback, stop, record and fast reverse. Now with provision for remote control. Takes up to 7" reels. Two-speed dual-track for wide range of recording times. At 3.75° per second, 7" reel records for 1 hour—and additional hour on second half of tape; st 7.5° per second, records 3/4 hour continuously, 1 hour overall. 7" reel revinds in 3 minutes. Response: a crase system; "lock" prevents accidental erase. Festures: two seon recording level indicators, 2-wait built-in amplifier; 5 x 7" oval speaker. Records from mike, radio, tuner or phono. Handsome 2-tone portable case, 14 x 12 x 9". Complete with mike, take-up reel and 609-ft. roll of tape. For 110-120 v., 60 cycles AC. U.L. Approved. Shpg. wk., 29 lbs. 96 RX 673. Only. \$104.50 REMOTE CONTROL. For remote starting and stopping of recorder, 18-ft, cable

Special Value Knight Recording Tape

Top-quality, highly dependable ¼° recording tape at exceptionally low cost. Plastic base, smoothly coated with red oxide. Manufactured to meet rigid specifications. Features very low poise level, uniform output, and excellent response characteristics. Type "A".
96 R 698. 600 feet. Net each, \$1.37. 5 or more, each... \$1.24

96 R 699. 1200 feet. Net each, \$2.10. 5 or more, each....\$1.89





New Centralab Compentral—Improves Tone Quality
Dual shaft combination volume control and tone compensator—assures full range music, even at low volume levels. Accentuates bass and treble as volum is reduced. Level-set feature "customizes" control foindividual room acoustics. For hi-fi amplifiers, radios TV sets, etc. 30 ft 436. Only. 34.4

	LLII																							_	_		(R				-	•	
□ 8	end	F	RE	E	-	L	LI	EC)	S	u	pp	ol	eı	m	eri	ŧ	N	la		1	3	9.					•								
E	nter	0	rd	le	r	fo	F.							*															 							•
							0 0			0	0 1				\$				0			. 0			. 4		a				. e	n	cle	08		d
Name	•						* 1					. 1							*					*		. *			 							
Addr	ess.																												 							
City.																			Z	0	ni					SI	a	le								





Make this test yourself. Compare Perma-Tube with any other masts—steel or aluminum.



have u.h.f. stations for at least onehalf of their affiliates within two years of the new rule; and special permission for ultra-high stations only, initially, to multiplex their sound to provide stereophonic sound transmission.

The lawyer pointed out that the use of stills and sound was very important, because most u.h.f. stations cannot undertake extensive daytime programming and therefore dealers and technicians cannot convert, test, or demonstrate receivers, unless the signals are available. Multiplexing would, it was said, provide an additional advantage to the service that would be attractive to sponsors; it might be applied to low-band transmission, too, once the u.h.f. service was firmly established.

"THE RUMORS OF U.H.F.'s death are exaggerated." So declared FCC's chief economist Hyman Goldin during a meeting of educators in Columbus. He said that no one was denying that there were a long list of woes for u.h.f., but those high-channels will eventually be used, because . . . "this country is too big and too diverse in its interests to be satisfied with only v.h.f. stations." The fact is, he added, that . . . "many substantial communities must look to u.h.f. for their only local station and many others need u.h.f. to obtain an adequate number of program choices."


Reviewing the brighter side of the high-channel picture, the economist pointed out that we must remember that there are now 125 u.h.f. stations on the air, and most of the drop-outs have only been paper grants. He felt that the establishment of a higher power minimum and the extension of the multiple-ownership rule to permit five-station owners to acquire two more u.h.f. stations would help solve the current problem.

AEROELECTRONICS continues to receive accolades on the military and civilian fronts. In Bedford, Massachusetts, the Air Force played host, a short while ago, at a brilliant ceremony dedicating a \$5-million research center.

The wing, part of a new center, which will eventually replace the famed quarters at Cambridge, will house the Command's electronic-research directorate. Over a hundred national, state, and local dignitaries were at the ceremonies. Washington was represented by Air Force Secretary Harold E. Talbott. Main speaker for the event was Lt. General Thomas S. Power, Commander of the USAF Air Research and Development Command in Baltimore.

A formation flight by a group of jet aircraft and B-29 bombers high-lighted the ribbon-cutting affair.

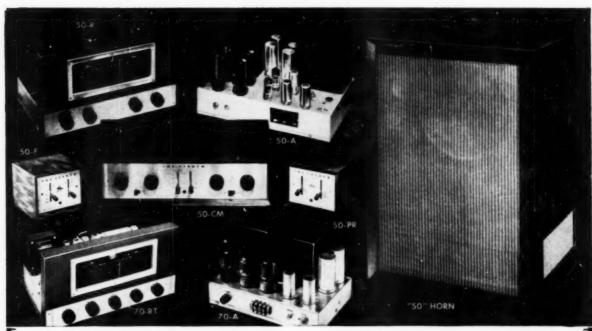IN WASHINGTON, the subject of aeroelectronics served as the basis of an interesting report by the Radio Technical Commission for Aeronautics (Continued on page 18)



The Best Costs Less When You Buy

THE FISHER

Custom Audio Components

■ If you are buying 'for keeps' buy the best first! Buy FISHER, quality leader for seventeen years. Engineered for the professional, functionally designed for home use. "Of the very best!"—High Fidelity.

FM-AM TUNER, Model 70-RT

Features extreme sensitivity, low distortion and low hum. Armstrong system, adjustable FM-AFC and AM selectivity. Preamplifier-equalizer, 2 inputs, 2 cathode follower outputs. Six controls. Self-powered. \$184.50

FM-AM TUNER, Model 50-R

Same features as 70-RT above, but designed for use with external preamplifier-equalizer such as 50-C. Hum level better than 100 db below 2 volts output. Fully shielded and shock-mounted. Self-powered. **\$164.50**

MASTER AUDIO CONTROL, Series 50-C

16 choices of record equalization, plus separate bass and treble tone controls, loudness balance control. Five inputs and input level controls, two cathode follower outputs. Chassis only, \$89.50 • With cabinet, \$97.50

25-WATT AMPLIFIER, Model 70-A

50-watts peak! More clean watts per dollar. Less than ½% distortion at 25 watts (0.05% at 10 watts.) Response ±0.1 db, 20-20,000 cycles; 1 db, 10 to 50,000 cycles. Hum and noise virtually non-measurable! \$99.50

50-WATT AMPLIFIER, Model 50-A

100-watts peak! World's *finest* all-triode amplifier. Uniform within 1 db, 5 to 100,000 cycles. Hum and noise 96 db below full output. IM distortion below 2% at 50 watts. Highest quality components thruout. \$159.50

SPEAKER ENCLOSURE, Series 50

NEW! Regardless of the speaker or enclosure you are now using, the "50" Horn will revolutionize its performance. For use with 12" or 15" speaker systems. 50-HM (Mahogany) \$129.50 • 50-HB (Blonde) \$134.50

PREAMPLIFIER-EQUALIZER, Model 50-PR

Professional phono equalization facilities at low cost! Independent switches for LF turn-over and HF roll-off. Output lead up to 50 feet. Can accommodate any low-level, magnetic pickup. Self-powered. \$22.95

HI-LO FILTER SYSTEM, Model 50-F

Does what ordinary tone controls cannot do, for it suppresses all types of noise with an absolute minimum loss of tonal range. High impedance input; cathode follower output. Use with any equipment. \$29.95

Prices slightly higher west of the Ruckies

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORPORATION · 39 EAST 47th STREET · NEW YORK, N. Y.

CAN YOU HANDLE

TOAYS' WORK




G.E. SHOWS YOU HOW—with a field-tested plan that has helped hundreds of other TV-radio service dealers. Only plan of its kind in the industry!

Authorities agree that the normal growth of the TV-radio service industry can bring an increase in your business next year equal to one extra day's work a week. To get your full share of this new business, and at the same time boost your profits, you need to organize now for top efficiency.

- How to begin, what to do, and how: these questions are answered for you in G.E.'s new Successful Service Management. It's a complete plan for improving and strengthening your methods, with accounting, merchandising, and technical helps that service dealers from coast to coast have tested and found successful. If available commercially, this plan would cost you a substantial sum.
- General Electric, however, has made the investment in money and research—its purpose, to help you help yourself by becoming a better businessman. Know where you stand financially! Make every advertising and promotion dollar pay ample returns! Stay ahead of competition in technical knowledge! You can do these things with the aid of SUCCESSFUL SERVICE MANAGEMENT. See your G-E tube distributor! Tube Department, General Electric Co., Schenectady 5, N. Y.



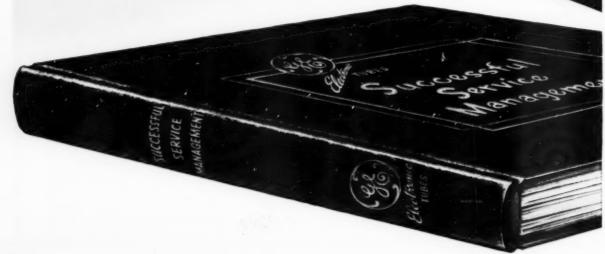

IN 6

NEXT YEAR?

EVERYTHING you need to set up an organized and efficient service business is included in G.E.'s Successful Service Management. You learn step-by-step how to manage your—

BUSINESS PRACTICES... Are you sure you're making money? ... Accounting for the TV-radio service dealer (a complete course, with all records and how to keep them) ... Preparing your income-tax return.

MERCHANDISING . . . Why advertise, why promote? . . . Identification . . . Advertising . . . Direct-mail . . . Window and store display . . . other effective ways to increase your business.

TECHNICAL ACTIVITIES . . . TV trouble-shooting with an oscilloscope . . . Alignment techniques . . . U-h-f servicing . . . other technical instruction, all detailed in its treatment and fully illustrated.

Plenty of operating examples make it easy to understand and apply SUCCESSFUL SERVICE MANAGEMENT. Instruction is down-to-earth and practical throughout. For the first time, you have in compact form both an aid to scientific operation of your business, and a guide to its healthy future growth.

Your G-E tube distributor has SUCCESSFUL SERVICE MANAGEMENT. See him today! "We find the business practices material especially good, and use the forms 100% in our bookkeeping." Silverton TV Service & Sales, Cincinnati, Ohio

"Plan is very helpful and appreciated.
We like the technical section especially

Cecil N. Chaney, Humansville, Ma.

"I have been delighted with the information sent us, and cannot at this time think of anything that would improve it."

David S. Hyae, Bloomfield, N. J.

"Information has been excellent and valuable, with the technical data especially useful."

Phil Miller, Kansas City, Mo.

"I have been pleased with the service. It has been very beneficial."

Ralph Moore, Leavenworth, Kan.

"This has been the most helpful material we have yet encountered. It is simply written and easy to understand."

Central Radio & TV Service, Inc., Hastings, Mich.

"This material is the finest I have ever

J. C. Wightman, Akran, Ohio

"Your manual has been a wonderful help."

Sterling Electronics, Lincoln Park, Mich.

GENERAL ELECTRIC



(RTCA) on the operational objectives for long-distance navigation aids.

RTCA is a non-profit cooperative association comprising both industrial and governmental agencies. It consists of four major elements; the assembly, executive committee, special committees and the secretariat. The assembly governs the RTCA. It meets twice a year and directs the activities of the group by establishing broad policies and operating procedures. The executive committee manages the affairs of RTCA, and meets monthly. The assembly is composed of approximately 100 U.S. aeronautical telecommunication organizations. Membership in the assembly is wholly voluntary and is open to any organization in the country actively identified with any phase of the air art. The executive committee comprises a representative from the Departments of State. Treasury, Army, Navy, Air Force, and Commerce, FCC, CAB, Aeronautical Radio Inc., Air Transport Association of America, Aircraft Industries Association of America, Inc., RETMA, Air Line Pilots Association, National Business Aircraft Association, and Aircraft Owners and Pilots Association. The Air Transport Association is the organization of the scheduled airlines. Aeronautical Radio is primarily concerned with the radio communication services of the airlines. Technical advisers to RTCA include Congressman Carl Hinshaw, Admiral S. C. Hooper USN (Ret.), Admiral Charles F. Horne, USN (Ret.), FCC Commissioner Edward Webster, Howard Morgan, and Delos Rentzel.

Discussing the uses of the navigation aid system, the report said that a ground-based radio aid to long-distance navigation performs services which are useful in flight control, airtraffic control, search and rescue, and marine navigation.

In ocean navigation, the report disclosed, a system of electronic navigation aids provides a useful function. Primary reliance is placed on celestial navigation procedures. These are supplemented by dead reckoning. In certain parts of the world, adverse weather conditions may prevent use of celestial navigation for extended periods of time, thereby requiring reliance on dead reckoning. In either condition, a radio navigation system provides fixing information which furnishes a useful check upon the accuracy of other navigation procedures.


ELSEWHERE ON THE AVIATION front, the communications division of the International Civil Aviation Organization, issued an important bulletin summarizing its radio-aid meeting in Montreal recently.

At this session the group disclosed that there appeared to be no practicable solution, at present, to the problem of providing air-to-air collision warning by means of airborne radar. But radar could be used, it was said, for storm-cloud detection, terrain mapping, and high-ground indication. It was felt that presently efforts

HEAVY-DUTY

LIMITED OFFER

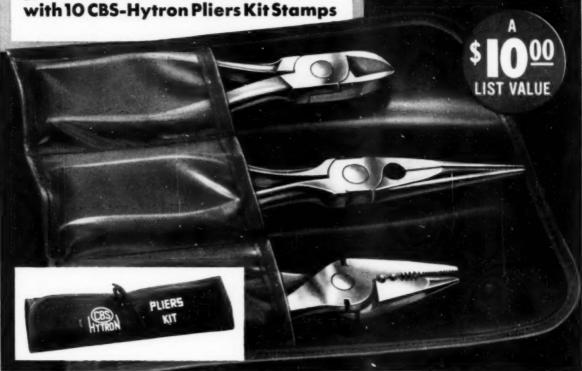From July 1 through August 31 . . . Your CBS-Hytron distributor will give you 1 Pliers Kit Stamp with your purchase of 25 CBS-Hytron receiving tubes.



PICK UP THESE FINE IMPORTED TOOLS. Examine the beautiful finish of their drop-forged tool steel. Try their comfortable handle grips. Feel the precise balance . . . the powerful leverage. Go ahead! Cut some eight-penny nails. Like cutting cheese, wasn't it? And not a trace of a nick in the tough, carefully matched jaws.

You will be proud to own these husky, quality pliers. Tested . . . guaranteed . . . they can take it. And did you notice that two are unique? Nothing else just like them . . . they are "musts" for your tool kit. Yes sir, this free Pliers Kit (packed in an attractive, handy plastic case) is an offer you cannot afford to miss!

The 61/2-Inch Diagonals are husky, box-joint, fully polished side cutters with precisely matched jaws. Size is right: Compact, but big enough ... with comfortable, full-fashioned, full-polished handles ... to do repeated, tough cutting jobs with ease.

The 8-Inch Long-Nose is unique. Extra-long (2¾ inches), spring-tempered jaws combine with extra-long, knurled handles for powerful leverage. Hand-honed cutting knives. Beautifully chrome-plated.

The 6-Inch All-Purpose is also unique. Combines: Flat and round nose. Jaws shaped for positive gripping. Two wire strippers. Two side cutters. Finish of handles is gun-metal; jaws are fully polished. This tool has everything.



CBS-HYTRON Main Office: Danvers, Mass.

A Division of Columbia Broadcasting System, Inc.

A member of the CBS family: CBS Radio - CBS Television . Columbia Records, Inc. - CBS Laboratories .

CBS-Columbia · CBS International · and CBS-Hytron

RECEIVING July, 1954 TRANSMITTING

SPECIAL-PURPOSE

TV PICTURE TUBES

. CRYSTAL DIODES AND TRANSISTORS

Get This Pliers Kit Stamp Book . . .

and stamps from your CBS-Hytron distributor: One Pliers Kit Stamp for 25 CBS-Hytron receiving tubes. Each Stamp is im-

printed with your CBS-Hytron distributor's

code number. Redeen, your Stamps with him. This offer is valid only in areas where such offers are legal . . . and it is limited: July 1 through August 31. Don't miss it. Be sure to get your free CBS-Hytron Pliers Kit. See it at your CBS-Hytron distributor's . . . today!



C900 FM TUNER

Finest FM Tuner regardless of cost. Highest in Sensitivity . . . Lowest in Distortion.

Another craftsmen first . . . Photo-etched 20.6 mc. transitionally-coupled IF coils insure life-long uniformity and stability of performance under all conditions.

In every performance test by high fidelity experts the C900 has established its outstanding superiority.

FEATURING

Extreme Sensitivity: 1.0 pv for 20db quieting provided by advanced circuitry of cascode rf amplifier. Minimum Distortion: 0.1% IM throughout entire receiver. Amplified AFC with front-panel control, assures accurate tuning for minimum distortion.

Entirely new 20.6 mc. IF system rejects spurious images, reduces oscillator radiation.

See your Hi-Fi Dealer or write to

The Radio Craftsmen, Incorporated, Dept. R7
4403 North Ravenswood Avenue, Chicago 40, Illinois





should be concentrated on the development of a satisfactory storm-cloud detection radar.

Covering the use of secondary radar frequencies, the committee said that it agreed that 1030 megacycles should be used for interrogation and 1090 for reply.

To improve air-ground communications, several new methods were recommended. In areas subject to disturbances in the ionosphere, groundwave propagation could provide a valuable supplement to the established networks for over-water communications. Congestion on radiotelephony channels could be relieved by taking certain routine traffic off these channels and providing for it by alternative means; for example, the use of ground-to-air teletype equipment of-fered considerable promise as a vehicle for meteorological broadcasts and other routine information. It was also pointed out that under suitable conditions, the application of selective calling principles-by which an aircraft radio operator listens only to messages directed to his own aircraft and not to any other broadcast on the same channel-would make it simpler for the air crew and result in an improved efficiency of air-to-ground communications.

The division also revealed it felt, in the not-too-distant future, that it may be necessary to develop a means of transferring information from ground to air and from air to ground at a much greater speed than can be done by the use of wireless telephony or telegraphy.


SUBSCRIPTION TV has once again become a see-saw affair in Congress, with some asking for immediate consideration of the matter and others declaring that the subject is not too important, now.

Representative Carl Hinshaw, who offered a bill which would make subscription TV a common carrier, said that the House Interstate Foreign Commerce Committee certainly ought to begin considering this pay method, because it is . . . "being agitated."

Referring to a talk on pay-TV by Dr. Millard C. Faught in New York and Washington, the Congressman said that some very interesting facts on the systems, as they exist now, were disclosed.

According to Dr. Faught, who is a management consultant, in the new techniques, it is possible to make "an unholy mess" of the scrambled signal. Not only is the signal coded, he said, but its code is coded, and the whole business is what one might call randomized. There are available about 5000 different electronic symbols for any given letter of the alphabet; and altogether the system offers 20,000 codes. "Since each customer literally has his own code," the specialist added, "the odds against two neighbors swapping useful information could be one chance in 10, followed by forty zeros."

(Continued on page 100)

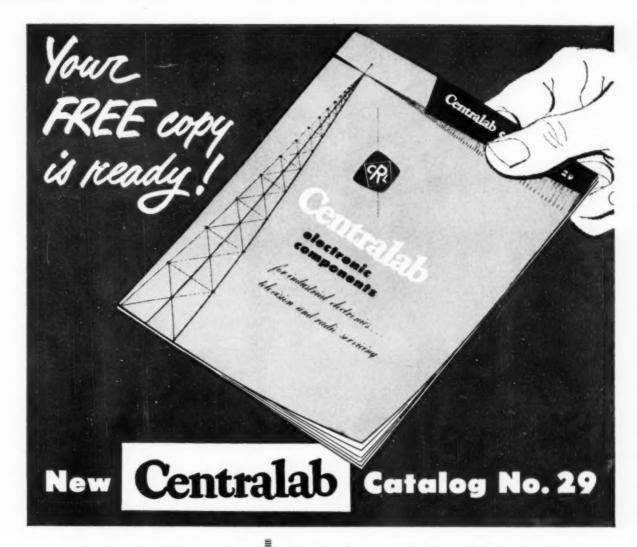

Keeps you up to date on Centralab's latest developments for faster, more profitable servicing

New values in Adashaft* Radiohms

New Adashaft shafts

New Snap-Tite Controls

New Fastatch* Dual Concentric Controls

New Senior Compentrol*

New miniature rotary phenolic switches

New Phenolic Switch Kit

New complete line of standard DD disc capacitors

New miniature disc capacitors

New 3000-VDCW and 6000-VDCW Hi-Vo-Disc* Capacitors

New arrangement of capacitor kits

New Precision Attachable Terminal Hi-Vo-Kaps®

New Negative 330 and Negative 1500 TC Tubular Capacitors

New easier-to-read listings on CRL Printed Electronic Circuits

New P. E. C.* Kits

*Trademark

Revised, 48-page edition of handy reference book on America's most complete line of volume controls, switches, capacitors, Printed Electronic Circuits*, steatite insulators

Centralab Catalog No. 29 pictures and describes hundreds of CRL components, with exact specifications and details.

Ask your Centralab distributor for your free copy. Or send the coupon to us today.

Centralab

CENTRALAB, A Division of 910G E. Keefe Avenue, Milwaul	
Send me free copy	of Centralab Catalog No. 29.
Name	
Company	
Company	



THESE QUALITIES HAVE BEEN COMBINED INTO THIS SINGLE ANTENNA -THE ULTAMATIC . .

- * LOW VOLTAGE STANDING WAVE RATIO . . . the mis-match between antenna and transmission line is lower than four competitive types tested, an attribute to its broad band quality.
- * FRONT-TO-BACK RATIO . . . higher than multi-element, yagi-type antennas, minimizing co-channel interference.
- GAIN . . . expressed in decibels, is a ratio of signal voltage developed by an antenna over that of reference folded dipoles. It is not a quality sold by the pound or achieved by the addition of meaningless elements. The curves shown accurately describe the gain of the Ultamatic. Loss of sound or picture due to erratic antenna response is eliminated.

MECHANICAL FEATURES


- * Aluminum screen reflector of exclusive fold-out design, assembled in seconds with adequate stability for years of trouble-free service. Longer elements insure maximum front-to-back ratio on channels 2 - 6 and are more closely spaced for increased performance on channels 7-13.
- * Dipole and boom assembly are of heavy gauge, seamless tubing. Dipoles fold out and are rigidly supported and reinforced to minimize sag and sway.
- * Specifically designed mechanically by stress analysis of each unit and sub-assembly to provide a low vibrational period of all elements — your assurance of troublefree installations.


MODEL UM-213 . . . double stacked UM-213-2

for the FIRST time ... the FIRST Antenna with which You Can See the fference perfectly synchronized for

monochromatic and color TV

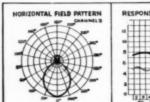Most Uniform Gain Response The gain response DOES NOT VARY MORE THAN 3 D. B. ON ANY CHANNEL across the band. This quality is exceedingly important in color reception to insure adequate color synchronization without resetting.



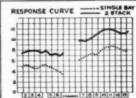



THE RADIART CORPORATION

CLEVELAND 13, OHIO

TV ANTENNAS * AUTO AERIALS * VIBRATORS * ROTORS * POWER SUPPLIES

RADIO & TELEVISION NEWS




These RCA types today give you...

LONGER LIFE

SUPERIOR PERFORMANCE

AT NO EXTRA COST

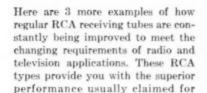

RCA-6J6 features pure tungsten heaters for improved life . . . uses a special cathode material to help maintain characteristics throughout the life of the tube. Each tube mount is adjusted to provide increased uni-

higher priced specialty designed types.

formity of characteristics of each triode unit.

RCA-6CB6 uses a No. 2 grid of improved design, resulting in lower grid operating temperature and longer tube life. Special controls on materials and processing improve uniformity of plate cutoff and reduce variations in characteristics when heater voltage fluctuates.

RCA-6AU6 uses a double helical heater, resulting in an extremely low hum level. Inverted pinched cathode reduces possible motion of tube elements thus minimizing microphonics.

The superior performance of regular RCA receiving tubes—at regular prices—eliminates unnecessary callbacks, assures you of greater customer satisfaction, results in increased profits for you.

1 1 1

When you sell a receiving tube, your reputation and profit depend on its performance and reliability. So, you can't afford to buy anything less than the best in receiving tubes . . . and the best are RCA.





RADIO CORPORATION of AMERICA

ELECTRON TUBE:

HARRISON, N. J.

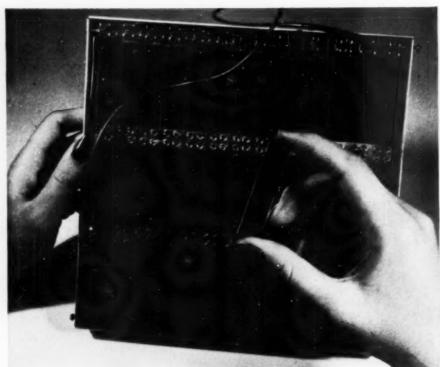The Bell Solar Battery.
A square yard of the small silicon wafers turns sunshine into 50 watts of electricity.
The battery's 6% efficiency approaches that of gasoline and steam engines and will be increased. Theoretically the battery will never wear out.
It is still in the early experimental stage.



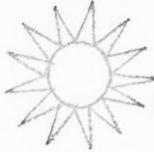

Bell Solar Battery

Bell Laboratories scientists have created the Bell Solar Battery. It marks a big step forward in converting the sun's energy directly and efficiently into usable amounts of electricity. It is made of highly purified silicon, which comes from sand, one of the commonest materials on earth.

The battery grew out of the same long-range research at Bell Laboratories that created the transistor—a pea-sized amplifier originally made of the semiconductor germanium. Research into semiconductors pointed to silicon as a solar energy converter. Transistor-inspired techniques developed a silicon wafer with unique properties.

The silicon wafers can turn sunlight into electricity to operate low-power mobile telephones, and charge storage batteries in remote places for rural telephone service. These are but two of the many applications foreseen for telephony.

Thus, again fundamental research at Bell Telephone Laboratories paves the way for still better low-cost telephone service.



Inventors of the Bell Solar Battery, left to right, G. L. Pearson, D. M. Chapin and C. S. Fuller – checking silicon wafers on which a layer of boron less than 1/10,000 of an inch thick has been deposited. The boron forms a "p-n junction" in the silicon. Action of light on junction excites current flow.



BELL TELEPHONE LABORATORIES

IMPROVING TELEPHONE SERVICE FOR AMERICA PROVIDES CAREERS FOR CREATIVE MEN IN SCIENTIFIC AND TECHNICAL FIELDS



Train for a secure career -not just another job! Success ahead for trained men only in



Radio-T

Stop Dreaming! Start Planning! Start Doing! Start Your

CREI CAREER TRAINING AT HOME TO INSURE MORE INCOME!

WHAT YOU DO NOW-today, tomorrow, next week-will decide your success in the electronics field. Every day counts because the trained technicians are the ones who get the "plums" when promotions are handed out. How can you be sure to step ahead of competition, to earn more money, to get the position that carries more responsibility and the pay that goes with it? The answer is contained in a CREI booklet called "Your Future in the New World of Electronics."

ERA OF COMMUNICATION

This is the era of Communication: aeronautical, marine, police and fire, industrial, land transportation. This is the era of defense orders and a manufacturing industry which last year alone sold billions of dollars worth of electronic equipment, which will top ten billion dollars (without military) this year. This is the era of electronic development, research, design, production, testing, inspection, manufacture, broadcasting, telecasting and servicing. This is the era of electronic careers well-paid, interesting, and secure.

CREI resident instruction (day or night) is offered in Washing-ton, D.C. New classes start once a month.

VETERANS: If were discharged after June 27, 1950—check the coupon for full information about the new G. I. Bill of Rights.



COLLEGE DEGREE NOT ESSENTIAL—You don't have to be a college graduate to benefit from CREI's famed courses. You do have to be willing to study at home. You can do it while holding down a full time job. Thousands have. No matter what your level of electronics experience, CREI has a course for you.

CREI's professional guidance is recognized all over world. Since 1927 CREI has trained technicians; you find them in radio and television stations; you find them in electronics planning and manufacture; you find them everywhere and, generally, near the top. During World War II CREI trained men for the Armed Services. Lead-

ing firms choose CREI courses for group training in electronics (among them are United Air Lines, Canadian Broadcasting Corp., Trans-Canada Airlines, Bendix Products Division, RCA Victor Division and Canadian Marconi).

PRACTICAL COURSES

CREI's practical courses are prepared by recognized experts. You get up-to-date material. Your work is under the supervision of a regular staff instructor who knows and teaches what industry needs. Training is accomplished on your own time, during hours chosen by you,

KEY TO SUCCESS As a graduate you'll find your CREI diploma the key to success in the entire field of electronics. At your service is the Placement Bureau which finds positions for advanced students and graduates. No short cuts are promised; no jobs are guaranteed— but requests for CREI-trained personnel far

exceed current supply.

This can be your big year! Write today for complete Tuition is reasonable, terms are easy, information is free. Fill out the coupon and mail it at once.

WHO WILL GET AHEAD?



There's a vacancy coming up. It means a boost in pay, prestige and responsibility. Can you fill it? The answer is NO if you postpone your self-training. The answer is YES if you're trained in elec-

CAPITOL RADIO ENGINEERING INSTITUTE

An Accredited Technical Institute 3224 16th St., N.W., Washington 10, D. C.



		-	
-3	r.	М	1
2	Ł	ы	ĭ
		-	۵
7	d	4	Ē

MAIL COUPON F	OR FREE BOOKLET
---------------	-----------------

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 117-A 3224 16th St., N.W., Washington 10, D. C. Send booklet "Your Future in the New World of Electronics" and course outling

CHECK
FIELD OF
GREATEST
First Advanced AM Servicing Aeronautical Radio
Engineering Engineering
Broadcast Radio Engineering (AM, FM, TV)
Practical Radio Engineering (AM, FM, TV)

Street

Check Residence School □ Veteran WORLD'S LARGEST MANUFACTURER OF CUSTOM BUILT TELEVISION

SILVER ROCKET 630 CHASSIS Featuring Syncromatic Tuning

NO DRIFT UHF-VHF-DX

ONLY THE MATTISON 630 ELIMINATES DRIFTING APART OF PICTURE AND SOUND ON UHF, VHF and DX RECEP-TION. SELECT YOUR CHANNEL SOUND IS AUTOMATIC. (Syncromatic tuning is on exclusive Mattison 630 Cir-

Tube Complement: 29 tubes 3 rectifiers 1 CRT SILVER ROCKET 630 Chassis with built in UHF Tunor



All Channel JUHF Tuner

UHF Cascode I.F. amplifier adds additional I.F. stage. Very important because UHF transmitters operate with moderate power and RECEIVER must be sensitive to give top noth UHF performance.

SILVER ROCKET 630 CHASSIS . with TUNEABLE . BUILT-IN BOOSTER for Better DX Reception Tube Complement: Select Your Channel

Tube Complement: 28 tubes 3 rectifiers 1 CRT

SOUND IS AUTOMATIC!



Tuneable J Booster

cause regeneration and attenuation of signal.

ONLY THE MATTISON 630 CHASSIS
HAS AN ALL CHANNEL TUNEABLE BUILTIN BOOSTER THAT INCREASES SIGNAL
STRENGTH UP TO 10 TIMES.

ALL CABINETS MADE IN MATTI

ALL CABINETS MADE IN MATTISON'S OWN CABINET FACTORY. AVAILABLE IN EVERY FINISH AND STYLE. WRITE FOR COMPLETE CATALOG.

DEALERS! SERVICE MEN! Here is your DEALERS: SERVICE MENI Here is your opportunity to become the "important" TV Dealer in your area for THE FINEST CUSTOM-BUILT LINE OF TV RECEIVERS, FREE! Write for Matilson's merchandising portfolio explaining the "UNASSEMBLED PLAN" and Write for Mattison's merchandising portfolio explaining the "UNASSEMBLED PLAN" and explaining the "UNASSEM"\$1,000,000 FLOOR PLAN.



When you buy from Mattisin you need enly one source of supply? You can buy a Mattison Chassis, a Mattison Cabinet or a complete Mattison TV Set?

Mattison Television & Radio Corp. 10 West 181st St., Dept. RN, N. Y. 53, N. Y. ******************

Within the

JOHN D. VICKREY has joined the engineering department of International

Rectifier Corporation as a sales and application engineer for selenium rectifiers.

He was formerly assistant manager for Lee Electric Mfg. Company and prior to that was sales and application engineer with the

Vickers Electric Division. He received his degree in electrical

engineering from USC, is a registered professional engineer, and a member of the AIEE.

WESTERN ELECTRONIC SHOW & CON-VENTION (WESCON) has been scheduled for August 25-27 at the Los Angeles Pan-Pacific Auditorium.

Sponsored jointly by the West Coast Electronic Manufacturers' Association and the San Francisco and Los Angeles sections of the IRE, show officials anticipate the greatest exhibitor participation in the history of the show.

An interesting program has been planned for those attending the convention including social events for delegates and women guests.

The Ambassador Hotel in Los Angeles will be convention headquarters.

EDWARD C. BONIA has been appointed manager of dealer relations for Emer-

son Radio and Phonograph Corporation. He will function as the coordinator of factorydealer relations on a national level.

Mr. Bonia has 25 years' experience in the radio and tele-

vision field, including a period during which he served as general sales manager of radio and television for Bendix. He was most recently president of E. C. Bonia, Inc., a national sales organization marketing TV receivers and appliances.

He was associated with Sparks-Withington Company for 19 years, advancing from the position of distributor salesman to vice-president for radio sales.

NORBERT F. DERR COMPANY, a manufacturers' representative firm, has been established at 937 S. Ashburton Road, Columbus 13, Ohio. It will represent electronics accounts in Ohio and Ken-LEVINTHAL ELECTRONIC tucky PRODUCTS, INC., a new company, is occupying a newly-constructed building

at 2821 Fair Oaks Ave., Redwood City, California. The firm will manufacture electronic medical instruments and do research, development, and merchandising work on other products relating to the fields of applied physics and elec-. . DAGE ELECTRONICS COR-PORATION of Beech Grove. Indiana has announced its affiliation with THOMP-SON PRODUCTS, INC. of Cleveland. DAGE will operate as a decentralized division of the parent firm's electronics division.

FCC has announced the assignment of amateur call sign prefix KC4 to Navassa Island in the Greater Antilles in the Caribbean. In case any U.S. amateur station is ever established on that island, the call sign will be selected from the block KC4AA through KC4AZ.

C. CHANDLER COLE has been named general manager of the Ward Products Division of The Ga-

briel Company of Cleveland.

He was formerly a top executive with several industrial firms in the Chicago area. His background in finance. manufacturing, and

sales has brought him into contact with a number of firms in the scope of activity of reorganization and revitaliza-

Mr. Cole will divide his time between the company's offices in Cleveland and the antenna plant in Ashtabula, Ohio.

TRAV-LER RADIO CORPORATION is now in production in its new 70,000 square foot addition to its plants in Orleans, Indiana. Designed to handle production of TV, hi-fi products, and color sets, the new addition now gives the firm 210,000 square feet of production space in Orleans . . . SYLVANIA ELEC-TRIC (CANADA) LTD., has announced plans to construct a new television receiver plant at Dunnville, Ontario. The 68,000 square foot plant is scheduled to begin production August 1st . . . JEN-SEN MANUFACTURING COMPANY of Chicago has acquired a new plant in Guttenberg, Iowa where a standardized line of speakers for volume industrial customers will be manufactured RADIO CITY PRODUCTS CO., INC. of New York has moved its engineering department and development laboratories to its factory location at Easton, Pa. The general and administrative offices were moved to Easton some time ago . . . ELECTRONIC MARKETERS, INC., electronic parts distributor, has moved

to new and larger quarters at 25-27

The BACKSTOP

STOPS co-channel and adjacentchannel interference caused by rear signal pick-up!


- Highest front-to-back ratio ever built into an antenna!
- No rear pick-up; eliminates "venetian blinds"!
- Largest screen area: 70 square feet!
- Very high all-channel gain. Incorporates basic Champion design, including Tri-Pole, with additional elements!
- Completely preassembled!

Table of Front-to-Back Ratios (Relative Voltage)


Channels	Front-to-Back Ratios
2	9:1
3	10:1
4	11:1
5	20:1
6	18:1

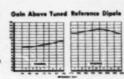Only Low Band channels shown, since ca-channel interference is not encountered on High Band channels.





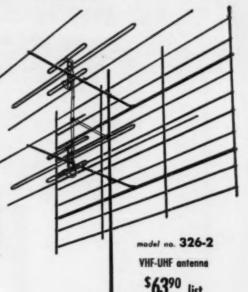IMPORTANT . . . don't be misled by polar patterns representing relative POWER. Remember, power is the square of voltage. All Channel Moster polar patterns are presented in relative VOLTAGE.



2 radical new antennas by CHANNEL MASTER

The most beautiful antenna ever made! The only indoor antenna featuring powerful outdoor design principles — Bow-Tie and Screen. Wonder 30W

VHF-UHF indoor antenna

DESIGNED FOR POWER!

On **UHF:** For primary and secondary areas. In many cases, performance is equal to actual outdoor installations. Good directivity on all channels.

On VHF: Ideal in areas of strong VHF signals.

STYLED FOR BEAUTY!

Designed by a well-known industrial designer, the WONDER BOW is proof that indoor antennas can be beautiful as well as powerful. Wins customer approval on beauty alone!

Gain Above Tuned Reference Dipol-

The first gain figures ever to be published for an indoor antenna!



ilver and bla



5835 list



CHANNEL MASTER CORP.

The World's Largest Manufacturer of TV Antennas

Write for complete technical literatur

Copyright 1954, Channel Monter Corp

*Pot No. D 17156

NEW! BERLANT BROADCAST RECORDER



\$545.00

EXCLUSIVE FEATURES

UNISYNC DRIVE

This radical improvement in design brings a new standard of quality to sound recording. An integral unit, consisting of an "inside out" hysteresis synchronous motor, fly-wheel and blower provides a cooler, lighter, smoother drive than has been previously possible.

FIVE HEADS

Instead of the usual three heads, the BR-1 can accommodate up to five. This permits playback of a delayed broadcast while recording an incoming program on the same tape. Single and dual track operation of one recorder is also possible.

UNIFIED CONTROL

All operations of the recorder are combined in a single, convenient error-proof lever system. Tape handling in fast forward and rewind can be at any speed from zero to full spooling. This permits rapid location of any desired section of tape.

A-B TEST FADER

An exclusive method of fading from the incoming signal to playback from the tape eliminates all clicks and noises previously inherent in such A-B tests.

Best Beslant
WRITE FOR BROCHURE NUMBER 24

BERLANT CONCERTONE
BERLANT ASSOCIATES
4917 WEST JEFFERSON BLVD.
LOS ANGELES 16, CALIFORNIA
MANUFACTURERS OF CONCERTONE
WORLD'S FOREMOST HIGH FIDELITY
TAPE RECORDERS AND ACCESSORIES

Hoyt St., Newark 3, N.J. . . . RAY-THEON MANUFACTURING COMPANY has opened its ultra-modern electronics laboratory at Bedford, Mass. The \$2,-000,000 plant has 100,000 square feet of floor space on two floors and will house approximately 700 workers.

NORMAN C. OWEN has been named president of Webster-Chicago Corp. fol-

lowing the annual meeting of the company. He was formerly vice-president in charge of sales.

E. J. Moritz, general manager of the laminations division was elected vice-



president in charge of manufacturing. Other officers who were re-elected include R. F. Blash, chairman of the board; Walter P. Altenburg, vice-president and general counsel; G. W. Wallin, vice-president in charge of engineering; C. B. Dale, vice-president in charge of research; Herman Biechele, secretary; and Edward R. Johnson, treasurer.

BRUCE A. COFFIN, formerly vice-president and a director of Columbia Broad-

casting System, has been elected to the post of chairman of the board of directors of Victoreen Instrument Company of Cleveland.

The board also reelected Cyrus W. Haller president of

the firm and renamed Harold S. Carter vice-president and Raymond F. Shima the secretary-treasurer.

The firm manufactures radiation detection instruments, color television, and electronic components.

JOHN BENTIA has been promoted to the post of executive vice-president of Alliance Manufacturing Company by the firm's board of directors . . . RALPH H. G. MATHEWS, veteran radio and electronics engineer, has joined The Magnavox Company as general sales counsel for the high-fidelity division. He will make his headquarters in Fort Wayne, Ind. . . . Kierulff Sound Corporation has named FRANK GONZALEZ, JR., to the post of sales manager. He has been with the firm since 1948 . . . JAY T. NICHOLS is the new chief engineer of Pentron Corp. His job will include the development of magnetic recorders for both commercial applications and government services . . . NEL-SON B. SHERRILL has been appointed sales manager of the electrical division of Olin Industries, Inc. He will maintain offices at the division's headquarters in New Haven, Conn. Chester Cable Corp. has appointed JOHN LACHMANN to the post of executive technical director. He was formerly with E. I. du Pont de Ne-J. LEONARD COHEN, formermours . . . ly with DeWald Radio Mfg. Co., has



ANSWERS THE NEED

In a nation-wide questionnaire the chief engineers of radio stations and recording studios were asked to set the specifications for the ideal professional tape recorder.

They did ... THIS IS IT!

PERFORMANCE

Every requirement of frequency response, freedom from distortion, stability of motion, dynamic range, timing accuracy and tape handling ability is met and exceeded by this recorder at both tape speeds.

DEPENDABILITY

Designed and built for continuous operation under the most rigorous conditions, this recorder combines rugged components and advanced engineering to guarantee maximum dependability with minimum maintenance.

SIMPLICITY

New concepts in design, construction and operation result in a functional simplicity that is reflected in the recorder's performance, dependability and last, but not least — economy.

TO THE ENGINEER

Compare this machine, point by point, with any other recorder on the market, regardless of price. You will find it the ideal recorder for your needs.

RADIO & TELEVISION NEWS

(Continued on page 116)

Home Study Courses in TELEVISION SERVICING offered by RCA INSTITUTES



Study Television Servicing—from the very source of the latest, up-tothe-minute TV and Color TV developments. Train under the direction of men who are experts in this field. Take advantage of this opportunity to place yourself on the road to success in television. RCA Institutes, Inc. (A Service of Radio Corporation of America), thoroughly trains you in the "why" as well as the "how" of servicing television receivers.

FIRST HOME STUDY COURSE

IN COLOR TV SERVICING


Now you can train yourself to take advantage of the big future in Color TV. RCA Institutes Home Study Course covers all phases of Color TV Servicing. It is a practical down-to-earth course in basic color theory as well as how-todo-it servicing techniques.

This color television course was planned and developed through the combined efforts of instructors of RCA Institutes, engineers of RCA Laboratories, and training specialists of RCA Service Company. You get the benefit of years of RCA research and development in color television.

Because of its highly specialized nature, this course is offered only to those already experienced in radio-television servicing. Color TV Servicing will open the door to the big opportunity you've always hoped for. Find out how easy it is to cash in on color TV. Mail coupon today.

SEND FOR FREE BOOKLET

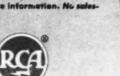High coupon in envelope or paste on postal card. Check course you are interested in. We will send you a bookiet that gives you complete information. No salesman will call.



RCA INSTITUTES, INC.

A SERVICE OF RADIO CORPORATION of AMERICA 350 WEST FOURTH STREET, NEW YORK 14, N.Y.

HOME STUDY COURSE IN BLACK-AND-WHITE TV SERVICING

Thousands of men in the radio-electronics industry have successfully trained themselves as qualified specialists for a good job or a business of their own—servicing television receivers. You can do this too.

This RCA Institutes TV Servicing course gives you up-tothe-minute training and information on the very latest developments in black-and-white television.

As you study at home, in your spare time, you progress rapidly. Hundreds of pictures and diagrams, easy-to-understand lessons help you to quickly become a qualified TV serviceman.

There are ample opportunities in TV, for radio servicemen who have expert training. Mail coupon today. Start on the road to success in TV Servicing.



Color

Television

MAIL COUPON NOW

RCA INSTITUTES, INC. Home Study Dept. RN-754 350 West Fourth Street, New York 14, N. Y. Without obligation on my part, please send me copy of booklet on:

☐ Home Study Course in Television Servicing.
☐ Home Study Course in Color TV Servicing.

Mome Study Course in Color TV SERVICING.

Name_____(please print)
Address

City______ Zone___ State_____

NOW... 2 SENSATIONAL EICO SCOPE VALUES!

NEW AMAZING FEATURE PACKED 7" PUSH-PULL OSCILLOSCOPE

Only **EICO** Has All These Features

- VERTICAL FREQ. RESPONSE: flat ± 2 db 10 cps 1 mc VERTICAL SENS.: .01 voits

- rms/inch
 HoR. FREQ. RESP.: flat ± 0 db
 10 cps 200 kc, -4 db at 500 kc
 HOR. SENS.: 3 voits rms/inch
 SWEEP RANGE: 15 cps-100 kc
 3-STEP FREG.-COMPENSATED
 ATTEMUATOR eliminates freq.
- CATHODE FOLLOWER inputs to

- both amplifiers
 PUSH-FULL outputs in both amplifiers
 RETURN TRACE BLANKING
 INT. VOLTAGE CALIBRATOR
 V & M TRACE EXPANSION & CENTERING:
 1.5X full screen without distortion.
 BIRECT CONNECTION to vert. CRT plates.
 PHASING CONTROL of internal 60 cps line wave sweep
- AT FRONT PANEL: intensity mod. input; 60 cps, aswtooth outputs.



WIRED \$129.50

EICO EXCLUSIVE! 5" PUSH-PULL SCOPE, 425K, Amazing feature-packed

economy-priced KIT, \$44.95. Wired, \$79.95.

SCOPE VOLTAGE CALIBRATOR KIT 495K KIT \$12.95. WIRED \$17.95.

■ Sq. wave output at power-line freq. with full-scale readings of 1, 1, 16 or 100 V. peak-to-peak ■ Accuracy ± 5% of full-scale

on each range.

V & 12V BATTERY ELIMINATOR KIT 1050K KIT \$29.95, WIRED \$38.95,

 DC output: 0-8 V or 0-16 v.
 Continuous current rating: 10 A at 6 V. 6 A at 12 V.
 intermittent current rating: 20 A at 6 V. 12 A at 12 V.
 Separate Voltmeter & Am-DC output: 0-8 V or 0-16 V.

SWEEP, 15

221K VTVM KIT \$25.93. WIRED

AC & DC voits:
0-5, 10, 100, 500,
1000 V (30 KV with
HVP-1 probe). • 5
ohm ranges from .2
ohm to 1000 megs.

BC input Z 26
megs. • 4½" meter
movement in can'tmegs. • 4½" meter movement in can'tburn-out circuit. • 1% mult. resis-

HIGH VOLTAGE PROBE SE 95 ● Extends range of VT & voltmeters to 30 KV.



360K SWEEP GEN. KIT \$34.95.

● Continuous coverage of all TV & FM frees. from 500 kc to 228 mc.

● Sweep width variable 0-30 mc.

● Crystal marker oscillator, variable amplitude.



WIRED \$49.95.

CATHODE RAY TUBE CHECKER 630K, WIRED \$24.95 KIT \$17.95



 Checks all types of TV picture and C.R. tubes in the set or certen. Bridge neasurement of neak to screen brightness). Detects shorted & open

825K TUBE TESTER KIT \$34.95. WIRED \$49.95.



 Illum. gear-driven
 "Speed Rollchart."
 New lever-action switches for individual testing of avery

• Tests all conventional & TV tubes. PIX TUBE ADAPTER for Tube Testers \$4.50. Checks TV picture tubes while in set.

214K YTVM KIT \$34.95. WIRED \$54.95. 249 K P-P KIT \$38.85 WIRED \$58.85



e Large 7½" meter, can "-burn-out circuit. e AC/DC volts: 0-5, 10, 100, 500, 1000 (30 KV with HV Probe). e 5 ohms ranges from .2 ohm to 1000 megs. • DC input Z 26 megs.

• 1% mult. resistors.

Large 745" meter

950A-K R-C BRIDGE & R-C-L COMP. KIT \$19.95. WIRED \$29.95.



Measures & tests all resistors; .5 ohm to 500

megohms.

Every type condenser, 10 mmf to 5000 mfd.

O-500 DC voltage source for capacitos leakage testing

NOW! ONLY VEICO - KITS & WIRED INSTRUMENTS Gives You

LIFETIME SERVICE & CALIBRATION GUARANTEE

at less than our cost of handling (See EICO Guarantee Card enclosed with each Kit & Instrument).

BAR GENERATOR 352K, WIRED \$19.95 KIT, \$14.95

 Enables rapid adjustment of TV picture V&H linearity without hard-to-find station transmitted test pattern.

• Produces 16 V or 12 H bars. Operates on TV chan-nels 3, 4, or 5.



Prices 5% higher on West Coast, Specificati and prices subject to change without notice

SASK MULTIMETER KIT \$24.95 WIRED \$29.95.

555K MULTIMETER KIT \$29.9\$ WIRED \$34.95. (1% precision resistors)

20,000 Ω/V; 31 ranges.
 DC/AC/Output volts:
 0-2.5, 10, 50, 250, 1000,

5000. • DC Current: 0-100 ua; 10, 100, 500 ma; 10 A. • Ohms: 0-2K, 200K, 20

EICO SCOOPS!

232 K PEAK-to-PEAK VTVM with DUAL-PURPOSE AC/DC Uni-Probe WIRED \$49.95



KIT 129.95 Measures directly p-p voltage of complex and sine waves: 0-4, 14, 42, 420, 1400, 4200 V p-p. DC/RMS sine voltage range: 0-1.5, 5, 15, 50, 150, 500, 1500 v. Ohms: 0-1000 megs. 7 non-skip ranges on every function. Calibration without removing from cabinet. Zero center. Freq. Resp. 30 cms. 3mg. 1v. presisting security multi-Resp. 30 cps-3mc. 1% precision ceramic multipliers. Exceptional stability and accuracy. Compact, portable (8 / x5x5"), smart, rugged

NEW! UNI-PROBE! Terrific time-saver! Only 1 probe for all functions-a half-turn of probe-tip selects DC (Pat. Pend.) or AC-OHMS!

249 K PEAK-to-PEAK VIVM with 732" METER KIT \$39.95 WIRED \$59.95

844 K FLYBACK TRANSFORMER AND YOKE TESTER Wired \$34.95 Kit \$23.95

Tests all flybacks and yokes, in or out of TV set in just seconds! Detects even 1 shorted turn!

Exclusive separate calibration for air-and ironcore flybacks assures utmost accuracy. Large 414" meter, 3 colored scales. Compact, portable (81, x5x5"), smart, rugged.

1171K RES. DECADE BOX NIT \$19.85 WIRED \$24.95 DECADE CONDENSER BOX AIT 11808 HIT \$14.95 WIRED \$19.95 BTMA RESISTANCE SUBSTITUTION BOX 1180K WIRED \$9.95 KIT \$5.50 315K DELUXE SIG. GEN. KIT \$39.95. WIRED \$59.95.



● Covers range of 75 kc to 150 mc. ● 7 calibrated scales:

accuracy better than

1%.

Bandspread vernier tuning.

4-step RF shielded output multiplier: constant output Z.

377K BINE & SQUARE WAVE AUDIO GEN. KIT \$31.05. WIRED \$40.05.



· Complete sine wave coverage, 20-200,000 cps in 4 direct-reading

ranges.

• Complete square
wave coverage, 6050,000 cps.

• Cathode follower
output circuit.

536K MULTIMETER KIT \$12.90. WIRED \$14.90. SISK MULTIMETER KIT \$13.99, WIRED \$16.90.



- 1000 Q/V; 31 ranges
 DC/AC volts: Zero to
 5, 10, 50, 100, 500,
- DC/AC Current: 0-1, 10 ma; 0.1, 1 A. Ohms: 0-500, 100 K,

145K SIG. TRACER KIT \$19.95. WIRED \$28.95.



e Audibly signal traces all IF, RF, Video & Audio circuits from ANT to SPKR or CRT in all TV, FM, AM, etc. without switching. Germanium crystal

de probe responsive over 200 mc. Integral test speaker.

320K SIG. GEN. KIT \$19.95. WIRED \$29.95. 322K SIG. GEN. KIT \$23.95. WIRED \$34.95.



Fundamentals 150 kc 34 mc, harmonics to 102 mc.

102 mc.

• 5-step band switching.

• Colpitts audio oscillator generates 400 cps pure sine wave voltage.

• Permits pure RF, modulated RF, or pure

Write NOW for FREE latest Catalog R-7

Ask your jobber for FREE EICO business building decals.

Seperate Assembly & Operating Manuals supplied with each EICO KIT!

SAVE OVER 50%! See the tamous alCO line "ODAY at your ocal obber

ELECTRONIC INSTRUMENT CO., Inc., 84 Withers Street, Brooklyn 11, N. Y.

CATSWHISKERS to CO



AN EDITORIAL by OLIVER READ

ADIO & TELEVISION NEWS (titled "Radio Amateur News," July 1919) was in existence long before the first broadcast station went on the air, as it was not until November 2, 1920, that KDKA, the world's first broadcast station, was put into operation. Dr. Frank Conrad, 8XK, radio amateur, and prominent engineer of Westinghouse had been consistently experimenting with voice transmission, occasionally sending out programs of phonograph music and talks over his ham station. A newspaper carried the advertisement of a Pittsburgh store offering radio receivers which would enable one to tune in the broadcasts of 8XK. The rest is history. Westinghouse officials decided that radio should be developed as a publicity medium rather than a straight communications service and early in 1920 plans for the operation of KDKA were made.

Mirroring the development of radio for the past 35 years, RADIO & TELEVI-SION NEWS has recorded the progress of radio virtually from the "stone age" of reception when the crystal receiver was titillating the imagination of the amateur up to the high standards of communications now in existence, R&TN not only has acted as a historian of radio progress, but the various departments of amateur radio, television, and broadcasting have been crystallized, based on the pioneering of many articles which have appeared in early issues. Such developments as television, synchronization of two or more stations on the same wavelengths, and the first radio musical instruments were all pioneer developments of our writers.

During the initial year of R&TN's publication, crystal sets costing from \$15.00 to \$25.00 were in vogue. One-tube sets were too expensive for the average purse, considering how slightly better they were than crystal sets. Soon the regenerative receiver made its appearance. Dr. de Forest, for example put out the MR-6 which sold for approximately \$150.00 without accessories. It consisted of a honeycomb coil tuner and two stages of audio-frequency amplification. Shortly there-

after, Radiola came out with a model that resembled a small table radio phonograph having a lid and concealed horn. It operated from dry batteries and used four WD-11 tubes. It was considered a luxury to have accessories in those days. Some horns, to which a headset could be attached, sold for around \$15.00. Even grid leaks and rheostats cost as much as \$2.50 each, while other components were similarly high priced. When the famous 201A tube came out, dealers were getting premium prices for them as there were no "ceilings" in those days. Many hams paid ten dollars apiece for these cherished "bottles."

The entire progress of broadcasting is due largely to the efforts of the amateur, even though he seldom got a break from the authorities who regulated activities in those early days. All broadcast stations were operating on 360 meters while the hams were found from 200 meters and below. They were then putting on amateur talent shows from their own stations and most of the entertainment was by means of phonograph records and musical instruments.

The Department of Commerce then relegated them to the short waves and banned entertainment directed to the public. Their transmissions were confined thereafter to code and voice. They bowed gracefully to the decree and pushed on to explore the new realms which were opened to them despite the premonition that as soon as these were developed they, too, would be taken from them.


Throughout the years, RADIO & TELE-VISION NEWS has recorded the ever growing development of the radio amateur since the early trail-blazing days of such prominent hams as the late Major Edwin H. Armstrong of regenerative, superregenerative, and superheterodyne fame; John Grinan; Dick Richardson, the Princeton boy who had one of the few operator's licenses during World War I; J. O. Smith, the first amateur to install c.w. in place of spark; Ralph Waldo Emerson Decker; Frank Conrad; Lloyd Hammarlund; and a host of others.

The first issue of this magazine (15.-000 copies) included a release to the effect that amateur stations were permitted to re-open on April 15, 1919 following World War I. Approximately sixteen times as many copies of Radio & TELEVISION News are now printed monthly. In this same year, a young man by the name of A. H. Grebe was working on an amateur apparatus after analyzing the outstanding features of the new types of equipment that were being used by the radio amateurs in government service and who were returning to their peacetime vocations following the signing of the Armistice. Dr. Lee de Forest, in his article "The Audion and The Radio Amateur" told of the advantages of using the vacuum tube and the superior performance that it was capable of providing over existing detector methods.

On October 1, 1919, all restrictions on amateur radio stations were removed. A warning was issued by G. K. Thompson, American Radio and Research Corp., to amateurs that unless they cultivated at once a conscientious respect for Federal radio regulations, the liberties of amateur radio would be doomed. Considerable work was being done with underground antenna systems, but this method was soon discarded in favor of flat-top and cage systems. Maj. Gen. George O. Squier, then Chief Signal Officer, United States Army, in his article "Tree Radio Telephony and Telegraphy," August, 1919, RADIO NEWS, described further experiments, which he had started as early as 1904, in the use of growing trees for antenna systems for radio telegraphy Amateurs were using loop antennas commonly in their shacks. In fact, many of them were attempting to take advantage of their directional properties by using them for transmission as well as reception. Moulded and oilimmersed condensers were finding wide acceptance in amateur stations. Crystal detectors of many varieties were still popular.

During the year 1920, considerable work was done by amateurs on the development of audio amplifiers. Sev-

(Continued on page 105)

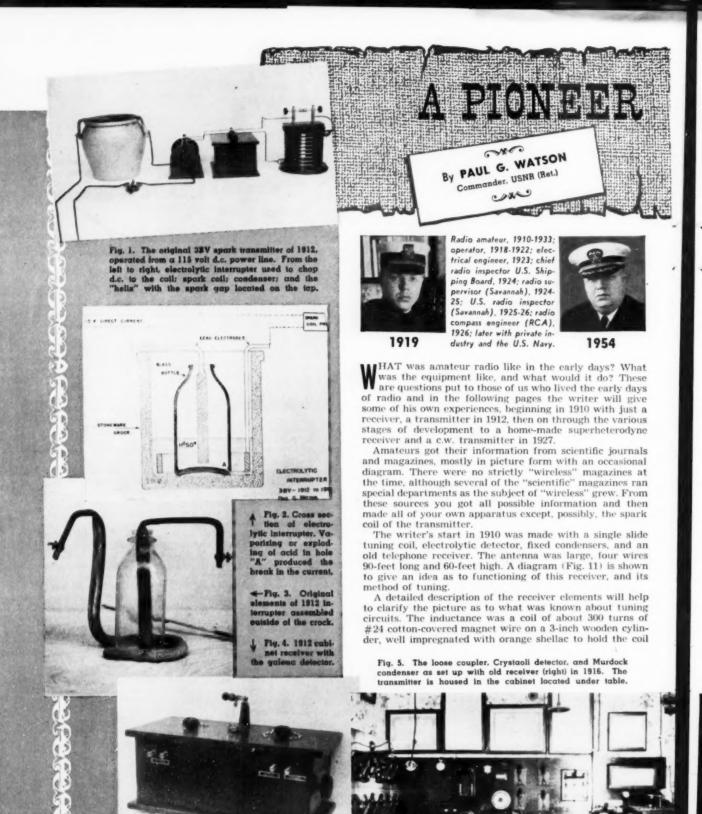

A trip to 'nestalgia' for the old timer and a glimpse into the past for today's hom. Amateut radio has come a long way! Fig. 7. The 1919 transmitter in display cabinet, oscillation transformer, rotary gap and motor, "send-receive" switch and

key.



Fig. 8. Station in June, 1922—all home-made gear. Left to right, honeycomb coll receiver, various ter receiver in rear center, detector panel with "Audotron" tube at right, two-stage audio amplifier in corner, and the enough on the floor at the end of the table.



Fig. 9. 4EO, 4ED, 4XX 100 watt transmitter with honeycomb cell secretary at Savannah, Georgia in 1923.

Fig. 10. 4XX station in Sevennah, Ga. in 1837. The 180 wait transmitter is at right, then CM 284 Navy receiver, e.w. regenerative receiver under callsign, and (left) the 20 to 800 moter. 10-tube superhat,


in place. A bare strip was carefully sanded down the top center of this coil, and a sliding contact arranged on a square bar to contact the individual turns of the coil and provide its inductance variation as one of the tuning elements.


The three condensers and switch shown in the center section of the diagram, with the inductance described, complete the tuning circuit. This capacity unit consisted of a four-point switch and three fixed condensers of wax paper and tinfoil. The first condenser had five leaves, the second ten, and the third twenty leaves, all in a wooden box with the switch on top. Now we come to what would today be called balancing the "L" and "C" values of the circuit. On the first contact of the switch no capacity was across the coil. When the slider tuned to the end of the coil (maximum number of turns), the switch was moved to the second point and the first condenser cut in. Its capacity had been so arranged that it re-established resonance at the same frequency with the slider near the center of the coil, and so with the other two progressively larger condensers, as the slider neared its maximum, cutting in the next larger condenser would bring it back to center position for best tuning adjustment.

The electrolytic detector was, at the time, considered the best and most reliable means of rectifying signals, with the possible exception of de Forest's "Audion" tube. The electrolytic detector used here was composed of a microscopic platinum wire, silver plated, known as "Wollaston wire," the tip end of which was immersed in a small cup of dilute nitric acid. When the cup and the wire were connected in the radio circuit, slight gas polarization collected on the tip of the wire, giving unilateral conductivity and rectification of signals which became audible in the headphones.

Today, all this sounds very crude, but it was a reasonably close copy of *United Wireless'* Type "D" receiver, the best of its kind in the commercial field at the time, and differed only as to the type detector and condenser, and the fact that it had only one slide instead of two.

So we listened on the air for a year or so with this gear, when the urge to "get on the air" hit with a bang. Early in

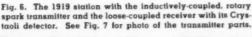

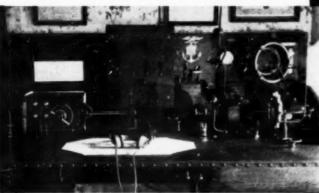

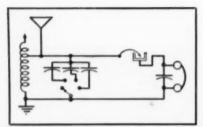


Fig. 11. Single slide tuner circuit as used in the author's 1910 receiver. The early version used an electrolytic detector which was later replaced by a galena crystal.

1912 a one inch "Bull Dog" spark coil was purchased and, along with a fellow experimenter, we set out to build a "sending set." This first transmitter was very simple, an old Western Union telegraph key was connected between eight dry cells and the primary of the coil, a spark gap was connected across the secondary, one side of the gap was grounded, and the other side connected to the antenna. After fixing up the antenna insulation several times, signals were heard a quarter mile away (in dry weather). The entire antenna insulation consisted of unglazed porcelain tubes and cleats used in house wiring, and the station was put on an "all weather" basis by boiling all the porcelains in red sealing wax and paraffin.

Now we were on the air, with a little squeaky spark note generated by the coil vibrator. We listened to a lot of the "big boys" growl and gurgle with notes resembling everything from a bad power leak to a rusty gate hinge, but they had "power" to get through. (Sounds like something I heard on 80-meter phone this past week.)

We were all "power" minded and when an article came to hand showing a de Forest station with plate glass condensers and a "helix" to tune with, that was for us, as it was supposed to double your range.

A condenser was made by cleaning off several glass photo plates, shellacking tinfoil on each side an inch from the edge, and when the stack was completed tying the whole bundle with cotton tape and immersing it in mineral oil, then placing the whole unit in a box.

The "helix" previously mentioned was the tuning inductance, 10 turns of #6 bare copper wire spaced % inch between turns on an 8-inch diameter wood column support. It was used as a common inductance in both the antenna and the spark circuit, tuning being accomplished by moving either the spark circuit clip, or that of the antenna, or both if needed after the proper number of condenser plates had been determined.

What an improvement this made. My friend and I could now tune out each other's signal by moving our sliders forty turns either side of the maximum point.

In 1912, alternating current was available in very few places and certainly not in the little town of West Chester, Pa. where all this "scientific" development was taking place. We wanted "power" and we had power available in the form of 115-volt direct current for house lighting. We already had tuned transmitters so during the summer of 1912 an electrolytic interrupter was made to work the transmitter directly from the 115-volt d.c. line. The only change necessary in the apparatus was the bridging out of the mechanical vibrator on the spark coil and the connection of the key and the coil primary through the electrolytic interrupter to the power line.


Fortunately all of the original apparatus of this transmitter has survived the 42-year gap since it was first assembled and is shown in Fig. 1 wired as it was in 1912 for use on the 115-vold d.c. line. The only thing missing from the picture is the two clips in the helix for antenna and ground connection.

In 1912 we did not have TVI, but if anybody except ourselves thought our connecting a transmitter, drawing 10 amperes, to the power lines was a good idea they did not say so. In fact the local paper ran an editorial on how we had ruined Edison's wonderful invention. People, not scientifically minded, who lived within a block of our home objected to their lights blinking. When the power company checked a house on our street they found the voltage dropped from 115 to 90 when we opened up. In our own home, in addition to the blinking lights, there was the problem of odor from the decomposition of sulphuric acid, and on one occasion a broken crock dumped a gallon of acid solution on my bedroom floor at 2 a.m. This gradually worked through the floor and dripped on the kitchen range below. My mother did not like the beautiful orange color of her range the next morning.

What was this devilish device that caused so much trouble? It is shown at the left of Fig. 1 as it was used in 1912. Fig. 2 is a cross-section view, and Fig. 3 a picture of the actual elements used in 1912 to pulsate the 115-volt direct current to the coil. It consisted of a stoneware crock of about two gallons capacity, filled to a depth of 4 inches with a sulphuric acid solution. A quart milk bottle was drilled with a file end at point "A" (Fig. 2) to about 1/16th inch diameter and was then placed in the acid in the crock. A lead pipe electrode contacted the acid inside the bottle and another electrode was placed in the acid in the crock. By this arrangement, the only electrical connection between the two electrodes was through the small column of acid in hole "A" of the bottle. When the 10 ampere current passed through this column of acid it promptly vaporized (exploded is a better word) and thereby opened the circuit. The acid then fell together, closed the circuit, and the cycle repeated itself as long as current

In spite of all the difficulties, we got going with the interrupter setting in a lead-lined box and by operating only in daylight or early morning hours. Just

(Continued on page 89)

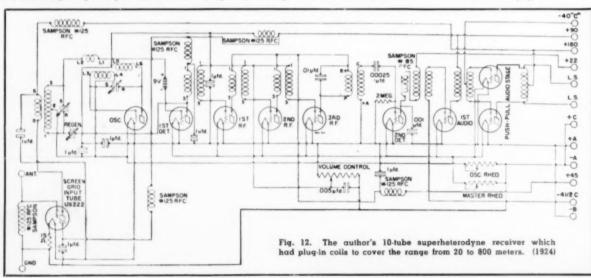

A SIMPLE GEIGER COUNTER

By

DR. HARRY R. FECHTER Stanford Research Institute

DR. M. R. BOYD General Electric Research Lab.

CCASIONALLY one has need of a simple, convenient counter to get a qualitative idea of the presence of radiation. On the other hand, one may be interested in the Geiger counter as a system. This counter may be built inexpensively from parts found in most experimenters' homes. We have used this counter to measure activity in the experimental physics area at the Hansen-High-Energy Physics laboratory (Stanford University) after conducting electron scattering experiments. It has also been an interesting companion on several prospecting trips.

There are several unique features of technical interest (Fig. 2). The high voltage supply uses a minimum of parts. It is built with a Microswitch (or equivalent), an ordinary speaker output transformer, an easily-made spark gap, and a 1.5 volt flashlight cell which is also used to heat the amplifier filament. With simple mechanical switching it delivers 700 to 1000 volts for the Geiger tube. The substitution of manpower for expensive batteries is a special convenience if one is using the counter for prospecting.

The spark gap construction is somewhat arbitrary. We found it convenient to cut an inch of lucite from a 1" diameter cylindrical rod. A quarter inch hole in the side allowed room for the gap which was made by tapping in at right angles to the quarter inch hole for two 6/32 bolts. The 6/32 bolts were filed and stoned to pin point sharpness (see Fig. 4). The points are set about .2 mm apart, but this adjustment is not too critical and should be experimented with. The base of the lucite cylinder is tapped for mounting.

To operate, one closes the Microswitch 10 or 12 times. The large induced voltage in the secondary of the output transformer breaks down the gap and adds charge to the condenser C1 at each switching. This gap action is also self rectifying and we thus eliminate a rectifier tube. One listens in the phones for the appearance of counts either from cosmic ray mumesons, or electrons, or the gamma rays from a watch with a luminous dial. The charging process is discontinued before the voltage builds up beyond the Geiger plateau (see Fig. 3). If the tube is over-voltaged, one hears




A compact and light counter in which a flashlight battery is used in a new circuit to generate 1000 volts for the Geiger tube. A storage system is used to permit operation with very small current drain. Standard parts are used.

many more than normal counts during the charging. Repeated over-voltage shortens the tube life (approximately 109 counts) or damages it. The condenser C_1 is fairly well isolated on the Geiger tube side and the charge in it will now run the counter from 5 to 30 minutes, depending on the quality of components and, somewhat, on the humidity. An occasional push on the Microswitch will allow operation to continue. C, is a .05 µfd., 600 volt Sprague unit; the tube socket is Isolantite. When a particle passes through the counter, a current flows in the direction of the arrow (Fig. 2) and a fairly loud click is heard in the phones.

The counter can be housed in any convenient way, keeping the high voltage circuit well insulated from other parts. It can be built in a very small space if desired (Fig. 1).

Fig. 2. Complete schematic of Geiger counter. It requires few parts and is small.

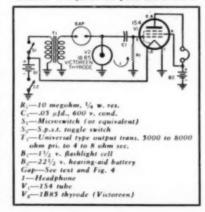



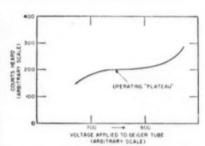


Fig. 3. Geiger tube operational curve.

Fig. 4. Mechanical details of the "gap."

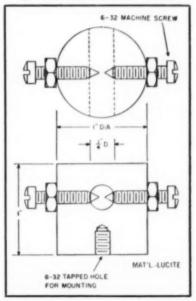

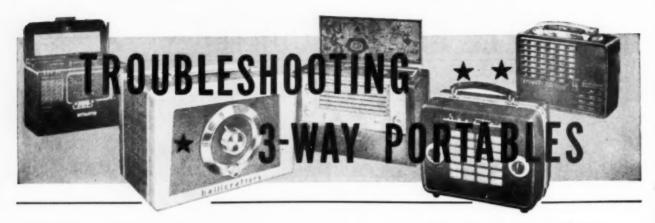

By JAMES A. McROBERTS

The greatest single source of trouble in portable radios is the power supply. Here are some helpful hints for servicing and checking the major types.

THREE-WAY portable radios have some fundamental peculiarities which the troubleshooter should bear in mind, namely:

 On power-line operation, a halfwave rectifier rectifies a.c. if used or passes d.c. if the polarity is correct.
 The rectifier may be a tube type or a selenium type.

 The rectified output feeds a filter which may be disconnected for battery operation. Batteries act as electrolytic condensers if in good condition.

3. The filaments of the signal tubes are series-connected for power-line duty, but the plates and screens are fed with d.c. from the rectifier via a filter and dropping resistor. The rectifier is fed with power for its heater from the power line directly or through a dropping resistor such as a line cord or ballast.

 Battery voltages are ordinarily less than those supplied by the power supply. Signal pickup is aided by the power-line connection; the loop only is available in portable service.

A schematic of a typical 3-way portable is shown in Fig. 1. In Figs. 2 and 4 this same circuit is shown with battery supply only and with power-line operation only, respectively. The reader should note that the rectifier and filter circuits are cut out of the circuit in battery operation. The set is strictly a portable only in battery service; even the "A" and "B" batteries have their own sections on the "on-off" switch.

Switching to power-line operation brings into existence two separate "A" circuits—the "A" circuit of the signal tubes and the rectifier heater circuit.

Series-filament operation has another peculiarity. The bypass resistors R_1 , R_2 , R_3 , and R_4 serve to shunt the "B" current drawn by each tube directly to "B—" so that this current does not pass through the other fila-

ments and overheat them. Always replace these resistors with others of the same wattage and resistance. The filaments also have definite plus and minus terminals, and the negative is connected internally to the suppressor grid; therefore, do not interchange connections. Note, too, that the series arrangement is in a definite order with the audio output being the most positive, the i.f. next, then the r.f. stage if present, with the converter and detector-first audio following in order.

Troubleshooting


A major key to troubleshooting 3way portables is the different power supplies. Test on a.e. and on battery. You will have the following cases:

1. The set does not work on either power or battery. Something is wrong in the signal part of the set or the series-filament chain is broken. Test by tube substitution or by voltmeter measurement with the set on. Do not use an ohmmeter; the result may be more burnt-out filaments. Other possibilities are bad "on-off" switch or power changeover switch, or broken connections.

First get the filament string lighted (check with the voltmeter); then check the "B+" bus, fixing any breaks or shorts. After this, repair the signal portion as in any standard set.

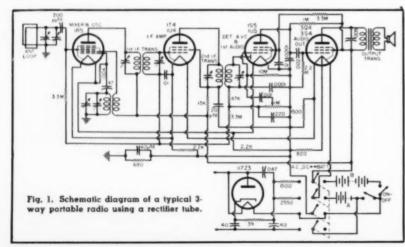2. The set works on battery but not on power. Here you must get your rectifier in operation and delivering an output as the first step. If the rectifier does not light up, test its heater or try another tube. If the heater is OK, trace back the heater line (see Fig. 4) which is directly across the power line except for passing through the changeover switch and a section of the "on-off" switch. In tracing this circuit, you can use an ohmmeter.

Once the tube lights up, the next step is to see if there is an output at its cathode. This should be about 90 to 100 volts ordinarily. If the voltage is low, a new tube may be needed or there may be a short circuit in the filter. After the filter is checked and found to have an output, check for "A+" at the set end of resistor R. The voltage here should equal the total series-filament voltage—generally 6 to 9 volts, the voltage of the "A" battery.



The next test is at the set side of the changeover switch for both "A" and "B" voltages; lack of either means an open or short.

3. Battery operation unsuccessful but power OK. Apart from bad batteries, the "on-off" and changeover

switches may be at fault.

Note: The electrolytics are cut out in many sets on battery operation and old batteries can cause oscillation. Oscillation on power-line operation usually points to bad electrolytics.

Fig. 3A shows a typical selenium rectifier circuit used in 3-way sets. Test this circuit for voltage from the input of the filter (point X) to common line (point Z). This should be done with the set on. If no "B+" voltage is present, check for a.c. from point Y to point Z.

Another type of rectifier in which the rectifier heater circuit includes a dropping resistor or ballast is shown in Fig. 3B. Continuity checking with the ohmmeter will show up any trouble in this circuit; of course, the rectifier heater must be operating to secure an output from it. Also shown in Fig. 3B is a pilot lamp in series with "B+". This serves as a pilot light and surge limiter. If there is a short circuit in the set, this pilot lamp will also act as a fuse—so check for a short before putting in a new bulb and hoping! Fig. 3C shows an alternate arrange-


ment for the pilot lamp.

Quite a number of 3-way sets use the series connection of filaments for power-line operation, but switch all signal-tube filaments to parallel connection for battery duty. Probably the best method of troubleshooting this type of circuit is to test it on power with the voltmeter. Starting from the rectifier cathode, proceed to the switch side of the "A+" dropping resistor and from there to the set side of the changeover switch, to the first filament, to the second filament, and so on to "A-" and back through the changeover switch to the power-supply common, usually negative. With the filament string working, the "B+" can be straightened out and then the signal part of the set. The signal part of the set will be easier to repair (in most cases) when operating from a battery supply.

The same rectifier variations may be expected in parallel-on-battery types as in the series-on-battery types. The use of a pilot lamp as a surge-limiting resistor will also be encountered in many of these sets. Naturally, if the set operates on battery the trouble is

in the power supply.

To summarize then, first find out if the set will operate on either power supply. Then get the filament chain going on battery operation if possible. Next, test out the power supply starting with the rectifier tube heater circuit. Follow by the testing of (and repair if needed) the "B+" supply and the "A+" supply in the power part of the set and the changeover switch. From this point, test out the "B+" supply to each electrode, and thence,

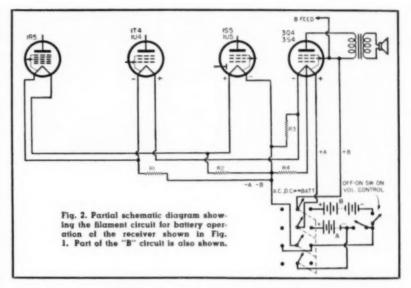



check the purely signal troubles like mistuning, shorted turns in an i.f. can. etc.

Many portable 3-way receivers use printed circuitry, and it is important when servicing such sets to consult the manufacturer's service notes (where available) for peculiarities in the circuit wiring. Also, when changing components on printed-circuit chassis, never use a large wattage soldering iron (or gun), and never apply heat to any component for too long. This is particularly important with chassis using copper-clad wiring where heat may cause peeling.

—30—

Fig. 3. Rectifier variations used in 3-way portables. (A) Circuit using a selenium rectifier, probably the most common today: (B) circuit using a rectifier vacuum tube with a dropping resistor in series with the heater to provide the proper operating voltage for the tube. (C) shows an alternate hookup for the pilot lamp in circuit (B).

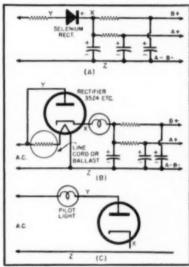

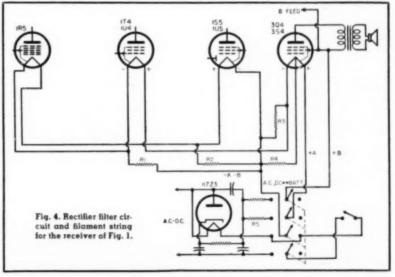

2 METERS IN THE FAMILY CAR

By WALTER S. ROGERS, WIDES

T IS an imposition for a ham to mutilate the family car with a two-meter mobile installation since it is not at all necessary to make structural changes on the auto with the system to be described here. One ham who made a thorough, police-like installation sacrificed \$400.00 when he came to trade in his car. In addition such jury rigs certainly do not add to the convenience and beauty of the family bus—which must serve many purposes other than housing radio gear.

Two meters is becoming one of the principal CD city communications bands. When W1DFS was to go on with a relatively new car, many possibilities were investigated and what was finally adopted by W1DFS, W1FBI, W1MAR, and others has proved to have many advantages over a per-

manent installation.

There are two major considerations involved antenna and power take-off. We have Gonset "Communicators" which are compact, single-cabinet units that work well on 117-volt, 60cycle a.c. as well as on 6-volt d.c. No matter how good the rig, it won't get out worth a darn without a good antenna. The usual hole in the roof was ruled out. Complicated brackets are too slow to move from car to car as are those mounted on the bumpers, etc. Forcing of the rubber in the door jamb might make the car leak cold air during the winter as well as permit the antenna to drop every time the door was opened.

These restrictions led to the idea that a lead must be made from the outside to the rig, thus a window must be opened just a bit to allow for a small window adapter which is made to fit the nearly-closed door glass. This is surprisingly easy to do, as shown in Fig. 1. As for the antenna, the author's Navy experience showed that the ground plane has certain characteristics which are particularly valuable for mobile operations. Mechanically it makes possible a most compact antenna, thus a vertical quarter-wave ground plane antenna was adopted.

RG/8-U was chosen as the feed cable since the losses are a bit less than the smaller RG/59-U. This 52-ohm impedance suggested that rather than four radials offering an antenna impedance of about 34 ohms, two radials would give a slightly higher value as well as offering less antenna to hit passing branches or the door of the garage. The general dimensions, given in Fig. 2, are not critical and work over the entire band.

For power, it was decided that the rig should operate in any car' with a 6-volt electrical system. Thus special



Fig. 1. The vertical ground plane in operating position—note lead through front window. Above is close-up of the metal bracket and fitting which must be stiff enough to retain shape in use.

Avoid mutilation of the family car by adopting this means of installing your two-meter rig and its antenna system.

or permanent fittings would not be required. During an emergency my car might go dead. Since almost every car has a cigarette lighter, why not use one of those emergency drop light plugs—or trickle charger plugs—such as the "Monowatt." This plug, attached to the *Gonset* 6-volt d.c. cord, is all that is necessary.

To build the antenna using the Gonset whip requires a few parts. A piece of aluminum, brass, or stainless steel, in my case about 2" x 15" x 1/16", plus two fittings—one 83-1R (SO239) for the antenna and one 83-1SP (PL259) cable connector to match the Gonset was needed. In addition you will need some #10 or #12 copper wire (the author used tinned copper because it looks better), about 6-feet of RG/8-U,

a few 4-48 machine screws and nuts, and some plastic electrician's tape. Fig. 3 shows the mounting for the antenna connector. The RG/8-U is grounded to one of the connector screws and taped after the center lead is fastened to the connector.

The flat metal strip is then care-

The flat metal strip is then carefully bent to fit the car. The antenna and ground plane rods should just clear the car top so that they will not hit—thus serving to make the metal car top part of the ground plane. It may be desirable to add some tape where the metal passes through the door so that the paint will be protected from scratches. The RG/8-U may be led in through the same window or through the forward section, as shown in Fig. 1.

In use, the equipment is either set on the seat alongside the driver so that he or a passenger can operate it or set into a light frame made of wood which rests on the floor of the car. Two parallel pieces of light wood, about ½" x 6", keep the equipment from rolling.

This flexible installation is so easy to shift to any car and to dismount for an a.c. installation that it fits into CD operations most conveniently. Resistor plugs were installed in my car, but any car with broadcast radio receiver quieting is usually all that is needed for city operation.

Our operations with this type of installation have been surprisingly good. We can more than cover our city. Above all, it is an efficient installation with no mutilation of the car which might, and usually does, affect its trade-in value.


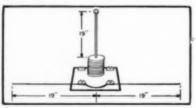


Fig. 2. Over-all dimensions of antenna. For Gonset whip, mount thread up. With home-built whip mount below for 90 degree elbow and a RG/8-U feed cable connector.

Fig. 3. Mechanical details of antenna bracket.

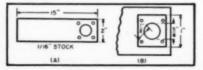



A rather novel circuit—it incorporates, in a single compact design, both positive and negative feedback.

DURING the last six years advances in high-quality sound reproduction have been most marked. Phonograph pickups now available at modest cost track with forces that would have seemed impossibly low only a short time ago, and have responses wider and smoother than those obtainable from the most expensive units of earlier days. Speakers and their enclosures are being developed at almost as rapid a rate.


As far as amplifiers are concerned. several recent noteworthy circuits have frequency responses much wider and distortion levels much lower than were afforded even by laboratory amplifiers of a decade ago. The excellent performance of these circuits is generally obtained by relatively large amounts of negative feedback over at least three stages. Instability is usually avoided by various novel means, such as the direct coupling of several stages within the loop. The resulting circuits often need to be constructed with accurately calibrated components and sometimes require some adjustment for best performance; these extremes are necessary for reasons that will become evident later in this article.

In any amplifier employing large amounts of negative feedback over several stages, the frequency response of that part within the loop must be very carefully controlled. Almost without exception, the final circuits display over-all frequency responses much wider than are required for top-quality reproduction. The object is to attain low distortion and low output impedance-the penalty is the wide frequency response. As a matter of fact, an entire reproducer system does not need a flat response below 16 cps or over 30,000 cps but the distortion must be quite low and the output impedance must be small-the latter especially if the speaker is one of low efficiency.

Actually, the frequency response and output impedance of an amplifier are not independent when the unit is loaded with a speaker. An amplifier of high output impedance and flat response with a resistance load will show a very uneven response, particularly in the bass region, when connected to a speaker.

The lower limit to the output impedance of the amplifier would seem to be a negative resistance equal to the d.c. resistance of the speaker voice coil in series with the speaker lines and the output transformer secondary. Even with this negative resistance the speaker cone could conceivably make some undesirable excursions because the speaker is not 100% efficient in converting electrical to mechanical energy and vice versa. In practice, such large negative impedances are difficult to realize with an amplifier of low distortion and good stability. Granting that they might be obtained, they might nevertheless be undesirable, for the large error-correcting voltage appearing within the amplifier in case the cone made undesirable movements would undoubtedly overload the amplifier (unless it had enormous reserve power) and cause considerable harmon-

Fig. 2. Block diagram of amplifier with two feedback loops. See discussion in article.

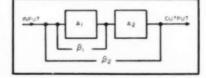

ic distortion. A lower limit to the output impedance seems necessary, but the magnitude of this limit depends upon many factors, among them the power-handling capacities of the amplifier and the efficiency of the speaker.

The amplifier covered in this article was originally intended to have approximately zero output impedance along with negligible distortion and adequate frequency response. These goals have been accomplished with a simple and trouble-free circuit, requiring no precision components or delicate adjustments, and making use of both negative and positive feedback. The principle is well known but the manner of utilizing it in this amplifier is considered to be novel and simpler than that of previously-designed circuits.

The Amplifier

The reduction of distortion effected by negative feedback in any amplifier is, to a first approximation, directly proportional to the gain reduction:

$$\frac{A'}{A} = \frac{1}{1 - \beta A} \cong \frac{D'}{D} \quad . \quad . \quad (1)$$

where β is the feedback factor (negative for negative feedback), A and D are the amplification and distortion of the amplifier without feedback, and A' and D' are the same characteristics with feedback. Distortion reduction is thus dependent not only upon the feedback factor but also on the original amplification A. The output transformer of an audio amplifier acts as a step-down unit as far as voltage is concerned; if it is to be part of the

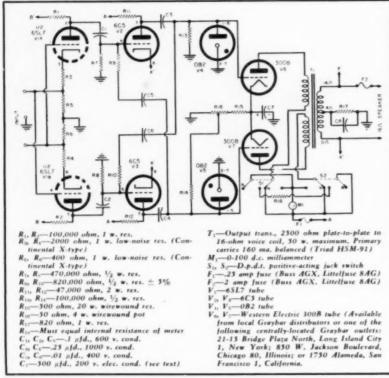


Fig. 3. Complete schematic of the "infinite feedback" amplifier. See Fig. 5 as well.

feedback loop a worthwhile reduction in distortion can be effected only by including a fairly large number of amplifier stages within the same loop. Avoiding oscillation in multistage amplifiers with over-all feedback, however, poses a very difficult problem, which is solved in such circuits as the Williamson by using direct coupling between at least two of the stages to eliminate part of the phase shift caused by ordinary RC interstage coupling.

The amplifier to be described accomplishes the same result with just two stages, namely, driver and power output. By means of positive feedback the gain of the driver stage is increased approximately to infinity; that is, if the negative feedback were removed the driver would oscillate. This principle has certainly been used before but generally in the design of cheap amplifiers. Its application to high-quality amplifiers seems largely to have been overlooked.

The gain of an amplifier of this type is2:

$$A = \frac{A_1 A_2}{1 - A_1 \beta_1 - A_1 A_2 \beta_2} , \dots$$
 (2)

where the symbols A and β represent the amplification and feedback factors shown in Fig. 2. If the driver stage is caused to oscillate, then $A_1\beta_1$ is equal to 1.0 and the equation simplifies to

$$A = -\frac{1}{\beta_i}$$

For negative feedback β_1 is negative so that the over-all amplification is

the reciprocal of the negative feedback factor. In a single-loop amplifier this result could be obtained only with an infinite gain within the loop. The feedback would then be infinite (in terms of decibels) and for that reason the present amplifier is called the "infinite feedback" amplifier.

The output impedance is : $Z_z =$

$$Z_L = \frac{1}{\left(1 + \frac{Z_L}{Z_{p2}}\right) \left(1 - \frac{A_1 A_2 eta_2}{1 - A_1 eta_1}\right) - \left(1 - A_1 eta_1\right)}$$

where Z_2 is the observed output impedance, Z_L is the load impedance, and $Z_{\mathbb{P}^2}$ is the output impedance without feedback. If $A_1\beta_1=1.0$ then $Z_2=0$; or the amplifier has zero output impedance. The rate of change of Z_2 as $A_1\beta_1$ is varied slightly from 1.0, however, depends upon β_2 , the amount of negative feedback, and will be smaller as the negative feedback becomes greater.

If the output of such an amplifier is subjected to some voltage disturbance δ (which might arise, for instance, from an unwanted oscillation of the speaker cone or the introduction of distortion in the output stage), then a correcting output of magnitude

$$E_{\circ} = \frac{A_{1}A_{2}\beta_{2}}{1 - A_{1}A_{2}\beta_{2} - A_{1}\beta_{1}} \delta (4)$$

also appears at the output terminals. When $A_i\beta_i=1.0$, $E_*=-\delta$, which means that the correcting voltage is equal in magnitude but opposite in sign to the disturbance, or that all dis-

tortion in the output stage is removed and unwanted speaker excursions are eliminated to an extent dependent solely upon the characteristics of the speaker. If $A_i\beta_i$ is slightly greater than 1.0 then any disturbances to the output are actually overcorrected. While the speaker damping is improved the distortion becomes worse. When $A_i\beta_i=2.0$ the distortion is equal to that resulting if the positive feedback were removed entirely.

An amplifier of this type will be unstable (it will oscillate) when the denominator of equation (2) becomes equal to or less than zero, that is, when $A_1\beta_1 + A_1A_2\beta_2$ becomes equal to or greater than 1.0. The stability of the amplifier increases as the quantity $A_i\beta_i$ + A₁A₂β₂ becomes smaller. Maximum stability is thus achieved by using as much negative feedback as is conveniently possible. At very low or very high frequencies where, as a result of phase shifts in the negative feedback loop, instability may tend to exist, the positive feedback can be reduced and shifted in phase to keep the sum $A_1\beta_1$ + $A_1A_2\beta_2$ less than 1.0. It should be noted, however, that with sufficient negative feedback the midrange positive feedback can be greater than unity without instability, which means that within certain limits a perfectly stable negative output impedance can be obtained. In the amplifier to be described the quantity $A_1\beta_1$ is made slightly greater than 1.0 and 100% negative feedback is employed. This combination insures minimum distortion and maximum stability, together with an output impedance near zero and an over-all voltage gain near unity. The power gain, however, is quite large.

Since in this type of circuit instability is avoided primarily by regulating the positive feedback, the response of the entire circuit within the negative feedback loop need not be controlled very closely, and the final amplifier may display an extremely low output impedance without necessitating excessively wide frequency response.

Aside from reasons of stability there is a significant advantage in using 100% negative feedback, and this is that the response of the entire amplifier is almost completely independent of the response of that part within the loop. Rather drastic measures may then be employed to eliminate any tendency toward oscillation without effect on the over-all frequency response.

The low output impedance is, of course, limited by the power handling capability of the output stage, which is not affected by the negative feedback. Only a limited amount of power can be drawn by very small load impedances without overloading the output stage, whereupon distortion sets in. The amplifier is thus unable to correct for errors in the output voltage when these errors are large and the load impedance is small, which means that overdriving the speaker will generally result in considerable distortion or other undesirable effects.

Circuit Design

The theoretical reduction of distortion is seldom attained in practice, so every possible step must be taken to improve the quality of the amplifier prior to the introduction of feedback. In this particular version the output tubes are 300B's in straight class-A push-pull operation with 460 volts on the plates. The drivers are 6C5's with a plate supply of approximately 550 volts. To develop full amplifier output each 6C5 must deliver a signal of about 100 volts peak to the grid of the following 300B; the gain of the 6C5 is about 14 so the peak grid signal at the 6C5 is about 100/14 or 7.1 volts.

Some speculation may arise as to why such expensive tubes as 300B's have been used in this amplifier (they cost approximately \$9.00 apiece). It was the object of this work to provide an amplifier of around 30 watts output and 300B's are the only triodes capable of supplying this output in the desirable class-A operation. No doubt some available power tetrodes or pentodes could have been used, connected as triodes, but it has been the writer's observation that results are never as satisfactory as when triodes are used. Part of the problem probably arises from the difficulty of balancing two tetrodes when they have been so connected and making each tube do its share of the work. 6C5's were selected as drivers because they are capable of delivering the required output voltage with very low distortion even in the absence of negative feedback; in this respect they seem to be slightly superior to the more common 6J5's.

Push-pull negative feedback is taken from the secondary of the output transformer to the cathodes of the 6C5's. The entire secondary of the transformer is thus at a d.c. potential of about 8 volts above ground, so the speaker lines must not be grounded at any point. Positive feedback from the plate of each 6C5 to the grid of the other 6C5 is adjusted so the driver stage is oscillating weakly when the negative feedback is removed. A lowcut filter comprised of R_2C_3 in the positive feedback network prevents oscillation at very low frequencies where the over-all negative feedback loop gain begins to fall off and a high-cut filter made up of R_sC_s and R_sC_b (where R_* is the output resistance of the 6C5, C. is the capacity at the grid of the 300B, and C_b is the total capacity at the grid of the 6C5) performs the same functions at high frequencies. Such simple precautions are insufficient unless an output transformer of very high quality is employed, and the sizes of the components in this loop are largely dependent upon the characteristics of the output transformer. Because push-pull negative feedback is taken from two ends of the voice-coil winding of the transformer, the capacities to ground at the two ends must be about equal.

This circuit was constructed with a standard output transformer having 4, 8, and 16-ohm taps on the secondary.

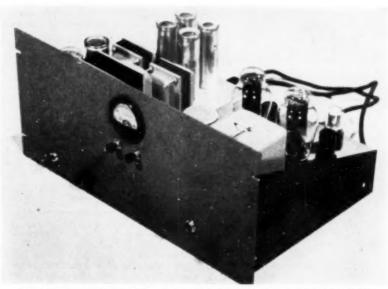


Fig. 4. Front panel view of 35-watt amplifier. The meter is permanently in circuit.

The 4-ohm tap was used as a centertap and a balanced output was taken from the 0 and 16-ohm taps. This arrangement has been quite adequate, since the d.c. resistances and the output voltages each side of the "center tap" were very well balanced with the transformer used. An 8-ohm speaker, however, is necessarily connected in an unbalanced manner, which may be less satisfactory than when a 16-ohm speaker is attached. For this reason it would be desirable to have a transformer with 4, 8, and 16-ohm balanced secondary windings; at present such a transformer is not commercially avail-

The inverter is an essential part of the amplifier because it prevents vari-



Fig. 5. Response of "infinite feedback" unit.


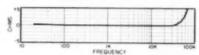


Fig. 6. Output resistance of the amplifier at .78 volt into a speaker of 16 ohms.

ous input sources from influencing the positive feedback. The circuit is the writer's simplification of the crosscoupled amplifier developed by Van

Fig. 7. Power supply diagram. Connections C and D are used for preamp power supply.

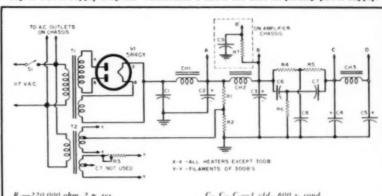

-220,000 ohm, 2 w. res.

-10,000 ohm, I w. res.

R₃-1 ohm, 5 w. wirewound adj. res. Set tap so that 300B filaments are supplied with 3 volts.

Ri, R.-1950 ohm, 4 w. res. (Each resistor

6040 31

, C₃, C₄, C₇-20 μfd., 600 v. elec. cond. (Mallory HS-696)

 C_0 , C_1 , C_2 —1 μfd ., 600 v. cond. C_0 —10 μfd ., 450 v. elec. cond. T_1 —Plate trans. 550-0-550 v. @ 250 ma.; 5 v. @ 4 μm μr (Friad F-5A)

Ty-Fil. trans. 6.3 v. c.t. @ c.t @ 3 amp (Triad F-32A) 1 amps; 6.1 r.

-4 hy. @ 250 ma. filter choke (Triad C-15A) CH -12 hy. @ 75 ma. filter choke (Triad

C-5X1 -50 hy. @ 15 ma. filter choke (Triad C.30X1

S .- S.p.s.t. switch V .- 5R4GY tube

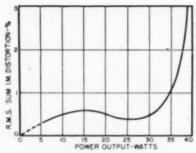


Fig. 8. Intermodulation distortion of the "infinite feedback" amplifier. The resistive load is 16 ohms and input is balanced.

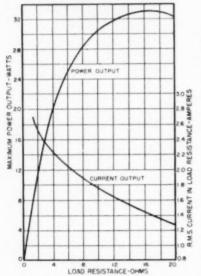


Fig. 9. The calculated maximum power and current delivered by the amplifier into various load resistances. Refer to text.

Scoyoc3 and performs essentially the same function as a line-to-push-pull grid transformer. It has been fully described in a previous article.4

The circuit of the complete amplifier is shown in Fig. 3; the parts list describes the components that were used in the experimental model, with a few exceptions. Only one generally unavailable part has been used in the experimental construction, namely, the 500-µfd., 200-volt bypass on the 300B cathodes. This condenser may of course be eliminated but it is desirable to use as large a condenser here as possible. A 300-µfd., 150-volt unit, which is commercially available, would be quite satisfactory.

The circuit diagram of the power supply designed for the experimental model is shown in Fig. 7. It is built on a 7" x 12" x 3" chassis which is a twin to the amplifier chassis. Fig. 1 is an over-all view of the completed amplifier and power supply.

Performance

Fig. 5 shows the frequency responses at various power outputs into a 16-ohm resistive load. The response, particularly at high frequencies, is dependent upon the power that must be supplied. It may be remarked at this point that this amplifier falls outside the class of minimum-phase structures; that is, the phase curve cannot be computed from the frequency-response curve. The response curves show that 3 db less than full power is delivered ±0 db over a range of 16 to 40,000 cps; a tribute to the high quality of the output transformer. Fig. 6 shows the output resistance of the amplifier on the 16-ohm tap as related to the frequency.

The r.m.s. sum intermodulation distortion for frequencies of 60 and 3000 cps (4:1) at different power levels is shown in Fig. 8. Below the point at which the grids of the 300B's are starting to be driven positive, the intermodulation distortion of the entire amplifier is substantially the same as that of the inverter, from which it might be concluded that the poweramplifier stages are practically distortionless. The intermodulation distortion is less than 2% for power levels less than 37.5 watts.

The r.m.s. sum intermodulation distortion is almost always greater than the harmonic distortion, and is a fairly good measure of the cleanness of the output. For advertising purposes some manufacturers have published figures for various other types of IM distortion measurements (such as the level of the first-order difference tone only) which are much lower than those for r.m.s. sum IM distortion and must not be confused or compared with them.


The output tubes in this amplifier are operated very near their maximum ratings. For this reason a plate-current meter should be provided and the plate currents balanced carefully. The single balancing control designed into the amplifier, when rotated, increases the plate current of one tube at the same time it decreases that of the other. It is sometimes necessary to interchange the positions of the 300B's to arrive at a balance. The zero-signal plate currents of the output tubes are approximately 94 ma, per tube. If the output leads of the amplifier are shorted together the negative feedback is removed and the oscillation of the drivers then tends to drive the grids of the output tubes well into the positive region. 300B's are not intended for operation in this region and will quickly be destroyed by this eventuality. same type of destruction will occur if the output is effectively short-circuited such as by severely overdriving the speaker. A number of protective devices have been employed to prevent this type of destruction. Not only the plate supply but also the speaker line is fused and 0B2 voltage-regulator tubes are placed across the 300B grids. Of these three precautions the 0B2's are the most effective.

The power-handling capabilities of the output stage are not influenced by negative feedback, which simply attempts to keep the output voltage constant irrespective of changes in the load resistance. Fig. 9 shows the theoretical maximum output power this amplifier can deliver into various load resistances and also the maximum current that will flow in the load. When the output is shorted the current rises to a very high value, and the quickacting fuse in the output will blow.

The unit requires .43 volt balanced or unbalanced input to be driven to full output. The noise level of the experimental unit measured .005 volt, or 74 db below 35 watts, with input shorted. The damping factor of the amplifier is, of course, infinity.

Because of its low input impedance the amplifier cannot be driven by many of the preamplifiers now in use without special precautions. Fig. 10 illustrates several schemes by which existing preamplifiers may be employed or new units designed.

Fig. 10. Several methods of connecting preamps to the "infinite feedback" amplifier.

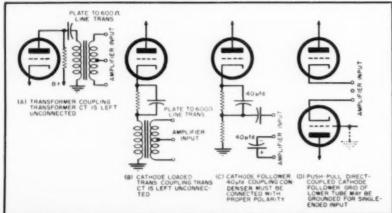

REFERENCES

1. Langford-Smith, F. (ed.): "Radiotron Designer's Handbook," Amalgamated Wire-less Valve Ca. Pty., Ltd., Fourth Edition, 1952, page 369. 2. Miller, J. M., Jr.; "Combining Positive and Negative Feedback," Electronics, March

1959.
3. Van Scoyoc, J. N.: "A Cross Coupled Input and Phase Inverted Circuit," Radio-Electronic Engineering Edition of RADIO & Television News, November 1948.
4. Boegli, C. P.: "Simplified Cross-Coupled Amplifier," Radio & Television News, May

30-


AERIAL "PRIVATE EYE" TRACES TV SIGNALS



(Left) Pilot-General Manager Raiph Bykerk at the controls and (Below) Bykerk and Ray Mitchell go over findings with John Kelley. KTNT-TV's assistant engineer.



By TELE-BEAM INDUSTRIES

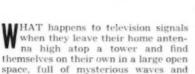

cross currents? Why are some signals received clear as life 75 miles away while others arrive pale, weak, and ghostlike on nearby screens?

To try and get the answers to these old-as-video questions, a team of TV troubleshooters has taken to the air and actually tracks down signals as they are being telecast. Their findings are proving of great value to television stations, and to jobbers and dealers, as well as to their own business, which is the manufacture of antennas and TV accessories.

The airborne team is composed of Ralph O. Bykerk, owner, and Ray J. Mitchell, sales manager, of Tele-Beam Industries. Napa, California—both radio-TV engineers. The air survey was the last resort in a series of tests to find out why, in areas equidistant from telecasting stations and with the same terrain, they would find one town with high signal levels, while in the other direction from the station there was barely enough signal to give a reading on a field strength meter.

First, Tele-Beam engineers designed their antennas to go higher in the air to get difficult signals, but this wasn't the answer. Then they mounted 50-foot masts on their station wagons, with antennas, field strength measuring equipment, and even the full equipment of a local amateur station, to make radiation patterns of the TV stations. On a survey in the Puget Sound area they used a boat to fill in the area not accessible by vehicle. Unusual radiation patterns were found, and the great extent of terrain effect was realized, but still the engineers were not satisfied. Then somebody got a brainwave-why not test the signals in the air, using the Cessna 170 which the firm maintains for business transportaHow two enterprising engineers increased receiving antenna sales by supplying TV stations with data on their markets.



Tele-Beam's technical staff swarmed over the aircraft making and spacing antennas, checking ignition noise, static effect, and all the complications of aircraft radio. With completion of the onemeter folded antenna spaced properly under the fuselage, field strength meter, and power converter, the Tele-Beam pioneers took off into the blue. While in the air, CAA was contacted regarding the flight plan, and the altitude and pattern of flight. Eventually special permission was obtained for aircraft, pilot, and passengers, and a whole new field was opened.

The company's aerial survey service has, since its first flight over a year ago, proved of great value to many West Coast TV stations in programming for their areas as well as the company. The firm has learned what merchandise to recommend in a given region in the reception area of any TV station tested, and both the company and its dealers can be pretty sure it will stay sold. These aerial surveys are made gratis at the request of TV stations. Wholesalers and dealers may participate in the surveys at the discretion of the station.

Here's how an aerial survey would work on hypothetical station USA-TV, channel 10, which is located at an altitude of 904 feet with a 500-foot tower and a 55-foot, 12-bay turnstile—total, 1432 feet above sea level (but to be exact, the pilot flies a course straight toward the center of the turnstile and checks the altimeter):

Disregarding the terrain below, which sometimes rises to 1350 feet or falls off to 600 feet, the pilot flies out the time required at his rate of speed, to be five miles from the tower. Prior

to take-off, aeronautical and topographical maps have been checked to set up local identification marks such as water towers, grain bins, small towns, or even rifle ranges and golf courses.

Starting at the north of the station, or at zero degrees, the pilot flies the five mile circle, calling out every ten degrees-350, 340, 330, etc. Readings are taken at each of these ten degree positions while flying in concentric circles. The second time around, the ground effect is observed and charted. Similar readings are taken at distances of one mile, three miles, 10 miles, and, many times, at 40 miles. Then, when the plane is back on the ground, polar plots are drawn. These polar plots are superimposed in order to develop the final plot or radiation pattern of the station. Actual deviation has been found to be as much as 14 db, while other stations were found to conform very well to design.

Vertical plots are made every 90°, or if the station's chief engineer desires, every 45°, this being done by going to 2000 feet above the center of the turnstile—or in the case of station USA-TV—to an altitude of 3350 feet. At this height the plane turns toward the station and dives earthward at a rate of 2000-feet-per-minute (until the surveyers can almost see the barbs of the barbed wire fences), all the time reading the meter every 100 feet.

All of the information gathered on these aerial survey flights is plotted both on polar paper and aeronautical and topographical maps, so that just what and where the station is transmitting can be checked. In some cases

(Continued on page 104)

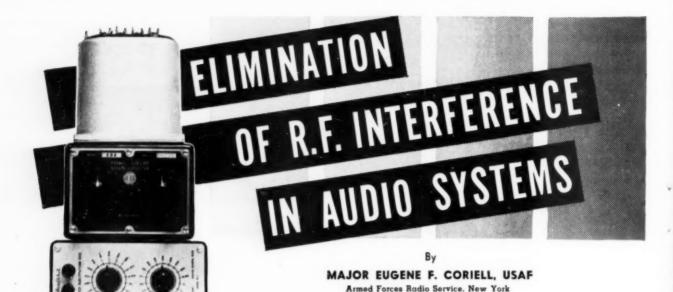


Fig. 1. Some of the equipment used in eliminating r.f. pickup in audio gear. From top to bottom: W.E. or Altec 111C repeat coil, Cornell-Dubiller CDA5 decode condenser, and Heathkit RS1 resistance substitution box. See text for application data.

ence warrants the cost, such circuits can be converted to balanced conditions by interposing 1:1 isolation transformers, preferably with electrostatic shields. Also see the section "Miscellaneous Remedies" for other

data on unbalanced equalizer circuits.

2. Microphone, turntable pickup head, and other low-level lines should be as short as possible to reduce their antenna action. In portable and field setups where some leeway exists, the microphone cables can be oriented for minimum r.f. interference.

3. For all low-level lines in conduit or in cable bundles, use two-conductor (stranded) shielded cable with insulation over the shield, and with a bare ground wire inside of and in contact with the shield. This wire facilitates connection of the shield to the ground lugs of the various terminating connectors. Typical cable of this type is the Whitney-Blake CBS-3-22F. cables used for this purpose should have minimum capacitance per foot, and equal capacitance from each circuit conductor to shield in order to maintain optimum balance to ground. The two conductors should be twisted. of course, to reduce electromagnetic pickup.

4. When interference is expected or experienced from higher frequency sources such as communications transmitters (as compared to broadcast plants), try to avoid low-level line lengths which are multiples or submultiples of the interfering wavelength. Otherwise, they may become resonant to the r.f., with resulting maximum pickup.

5. Run low-level and line-level cir-

and cables, amplifiers and power supplies, prevention of rectification; and miscellaneous remedies to be tried.

warrants the cost, such circuits—cuits—in grounded electric conduit.

Part 2. Concluding article covers suppression in lines

which has some r.f. shielding effect if all the joints are electrically tight. Rigid conduit is probably better in this respect than "thin-wall" as the former uses threaded connections.

6. Try small r.f. chokes in each leg of the affected low-level and line-level pairs. This is a matter of experiment, as the exact value depends on the circuit impedance and the frequencies to be suppressed. Values upwards of .3

cuit impedance and the frequencies to be suppressed. Values upwards of .3 millihenry are suggested. Variable chokes such as the *Grayburne* V-6 and V-25 simplify the necessary selection by trial. Don't overlook the possible effect of chokes on the audio frequency response and other performance characteristics. Remember also that chokes are highly inductive and may require electromagnetic shielding against hum.

7. Use an LC low-pass filter in low-level lines. One very effective form of this device is shown in Fig. 2 and consists of two closely-coupled coils, one in each circuit leg, with condensers across the circuit.² The inductances add for r.f. voltages which, being longitudinal, travel in the same direction on both conductors. The coils and condensers form a low-pass filter which greatly attenuates the r.f. Since audio signal currents travel in opposite directions on each circuit leg, the inductances cancel and have little effect on program material. The filter should be enclosed in a shielded case.

8. Wave traps may also be used in audio lines. Traps differ from low-pass filters in that the former attenuate a narrow band of frequencies and their cut-off frequencies are, therefore, more sharply defined. A trap might be pref-

AST MONTH the problem of r.f. interference in audio systems was discussed as to origins, suppression at the source, and, in part, suppression at the affected gear. It was also pointed out that professional audio installations designed and built in accordance with the best engineering practices should experience little or no trouble from transmitter interference. These two articles are intended to serve as a construction guide as well as a list of corrective measures and it is honed they will also be useful for non-professional equipment such as home tape recorders and high-fidelity music systems. Part 1 concluded with a listing of construction precautions and remedies under the heading "Shielding and Grounding." This article describes r.f.-elimination measures under the headings "Lines and Cables," "Amplifiers and Power Supplies." "Prevention of Rectification," and "Miscellaneous Remedies."

Lines and Cables

1. Keep as many as possible of the low-level and line-level circuits balanced to ground. This applies, of course, principally to low impedance circuits. A two-wire line in the presence of r.f. may have a longitudinal voltage impressed between each wire and ground. When the impedance to ground is different for each leg, an r.f. voltage may appear across the pair and therefore across the input of the following circuit element. Reference¹ gives a detailed analysis of longitudinal pickup in audio lines. Some circuits, such as filters and equalizers, are traditionally unbalanced. Where the severity of interfer-

erable to eliminate an interfering frequency near the desired upper audio limit with minimum effect on the frequency response. This would involve careful and probably experimental determination of component values

9. It is important to use patch cords with the shield bonded to the plug body at one end only, to avoid troublesome

ground loops.

10 Use repeat coils (audio transformers) having an electrostatic shield between windings, to isolate low-level and line-level circuits from their amplifiers. This shield, which should be tied to the main audio ground, reduces the capacity between the primary and secondary windings, which is the principal means whereby r.f. passes through an audio transformer. Examples of this type of unit are the Western Electric or Altec 111C and the UTC A21 transformers.

11. For the same reason, use 1:1 power transformers with electrostatic shields in the a.c. lines feeding amplifiers or complete rack assemblies. An example of this unit is the Stancor type P6415. Since this may involve considerable expense in a large installation, such devices should be used only on circuits for which this need is clearly

demonstrated

12. Use line-filter condensers in amplifiers and/or power supplies between each leg of the a.c. power circuit and

13. It may sometimes be necessary to install r.f. filters in a.c. power lines to amplifiers and power supplies. Occasionally a small plug-in filter of the type used to suppress electric shaver and fluorescent lamp noise can be inserted in the wall socket with fair results. Sometimes a larger unit such as the Cornell-Dubilier NF 10325 or the one diagrammed in Fig. 1 of Part 1 will do the trick. There may be times when a heavy-duty filter in the main a.c. feeder to the audio equipment room is the best answer. Units of this size may have to be made to order, and in any case, filter manufacturers should be consulted beforehand. These devices reduce the r.f. conducted directly along the power lines to the affected amplifiers. An additional benefit is that lines so filtered re-radiate less r.f. (beyond the filter) to be picked up by inductive elements and internal wiring of the audio equipment. Filters should therefore be placed as close to the wall socket or distribution panel as possible, to reduce the radiating length of a.c. wiring between the power outlet and the filter. Installation of filters at distribution panels may require approval of the local authority administering the electric code.

Amplifiers and Power Supplies

1. Use input transformers and filament-plate power transformers having an electrostatic shield between their windings and ground the shield. Power transformers are also available with inverted windings which, like the electrostatic shield, reduce the interwinding capacitance and thereby provide an r.f. barrier. However, the need for

such power transformers is remote in a well-designed audio system except in cases of exceptionally severe interfer-

2. Keep the internal r.f. impedance of plate power supplies to a minimum. Electrolytic filter condensers may have appreciable inductance at radio frequencies, which may be reduced by paralleling the filters with small mica condensers.3 This will reduce the magnitude of any r.f. voltages that may appear in the plate circuits as a result of r.f. drops across the supply.

3. Keep grid and plate leads short

and well shielded.

4. Bypass tube heaters to ground with perhaps a 100 micromicrofarad condenser.

5. Bypass the output tube plate to ground with a small condenser. Bypass each push-pull plate separately.4 A condenser decade box may be useful in determining the optimum capacity, but be on the look-out for possible disturbing effects from the decade unit.

6. Insert a resistor in series with the input tube grid, using a calibrated volume control or a resistance substitution box to determine the best value, which may be around 10,000 ohms. (A resistance decade box may introduce additional noise difficulties.) The grid lead inductance and the grid-to-cathode capacitance may form an LC circuit resonant at or near the interfering frequency. Adding the resistor reduces the "Q" of the circuit.5

7. Insert a small, perhaps 2 or 3 millihenry, choke in the grid lead of the input tube at the socket pin. It may be necessary to shield the choke, and in any case, the possible effect of the choke on the frequency response and other performance characteristics

should be checked.

8. Try bypassing the input tube grid to ground with a very small condenser, possibly 50 µµfd., or try a very high resistance between these points, and check for possible resulting degradation of audio performance.

9. Keep gain controls in "off" position on unused microphone and turntable channels on consoles and other amplifiers. A partially-opened attenuator is an invitation to r.f. pickup when wired to a long pair running out

the studio.

to an empty microphone receptacle in Prevention of Rectification

In spite of all precautions, some r.f. may reach the audio equipment. The problem is not only to keep this to a minimum, but also to prevent detection or rectification of this residual r.f. whereby it becomes audible. Following are precautions against some of the most common causes of rectification.

1. Clean all connector and receptacle contacts, especially in low level circuits and make sure mating elements seat

firmly.

2. Clean all tube base prongs and their mating socket contacts.

3. Clean grid caps and their connecting clips and make sure their shielding hats make good contact with the tube

4. Tighten all screw-type plugs and connectors

5. Re-solder all questionable connections, particularly those in low-level circuits.

6. Clean jack contacts by rapidly inserting a plug five or six times, and polish the patch-cord plugs.

7. Check bias on tubes and hold the input signal to the grid below the overload point to prevent nonlinear opera-

Miscellaneous Remedies

1. Try reversing the a.c. line plug at the wall socket.

2. Relocate, re-orient and/or ground any large metal objects in the equipment room or adjacent rooms which

may be re-radiating r.f.


3. Use resistive pads instead of transformers for impedance matching, if there is enough gain available to make up for the pad loss. This reduces the number of inductive elements which may serve as r.f. pickup coils. However, the power level should never be allowed to fall below microphone level (approximately minus 60 dbm) since this would degrade the signal-to-noise ratio

4. Re-locate affected audio equipment which does not respond to other measures. The writer recalls the case of a limiter amplifier in a rack adjacent to a transmitter. The limiter was saturated with r.f. due to extremely difficult field conditions existing and it was necessary to remove the unit to the control room in another building. This was admittedly an unusual situation; ordinarily, properly shielded grounded audio equipment can be operated in a transmitter room without interference.

5. Turntable equalizers are generally unbalanced and should therefore look into unbalanced preamplifier inputs. Otherwise, r.f. or other stray fields may appear as noise in the preamplifier output. The writer has found this to be one cause of the so-called "contact noise" in attenuator-type volume controls following turntable preamplifiers.

6. Sometimes r.f. noise in a volume (Continued on page 117)

Fig. 2. An r.f. filter for 30-50 ohm microphone lines. For higher impedances, the inductances would be greater and the capacitances smaller. The two coils are wound together in the same direction so that their close-coupled inductances add. thereby blocking r.f. currents which travel in the same direction in both colls. For audio signal currents which travel in opposite directions in the coils, the inductances cancel and offer little attenuation of the signal. The filter should be mounted in a shielded case. Adapted from "Elements of Sound Recording" with the assistance of Dr. Halley Wolfe, the book's coauthor. Courtesy of John Wiley and Sons.

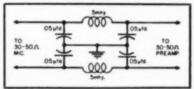



You may not install a color picture tube tomorrow, but you will need to know these facts when you do.

OW that some manufacturers have started to ship the first color TV receivers to their dealers, information on installation problems is becoming available. The majority of these early TV receivers use the shadowmask type color tube and this is usually shipped in a separate carton. Assuming that all circuits have been adjusted properly at the factory, the main job is to mount the color picture tube and adjust the various components and controls for proper pictures.

This article presents a detailed setup procedure for both the 15GP22 (RCA) and the 15HP22 (CBS-Hutron). as well as the new 19-inch tubes, based on manufacturers' instructions and the personal experience of the author. It might be mentioned here that a full day was spent for the first setup, but it took less than an hour the third time to produce acceptable color pictures. Installation procedures are presented here in hopes that they will save service technicians from many errors they might commit when they come in contact with color sets.

Before unpacking the picture tube, the color receiver should be air-tested for sound reception. Also check the "B+" and heater voltages. Next, check off the following items which go on the picture tube:

- 1. Mumetal shield.
- 2. Deflection yoke.
- 3. Purity-coil assembly.
- 4. Convergence-coil assembly and blue magnet for 19-inch tubes.

5. Field-neutralizing coil (omitted in some models).

The major test equipment required is a dot generator or a bar generator. If neither is available, a monochrome or color station signal can be used. For final testing, both monochrome and color signals should be used, although a lot can be accomplished with monochrome only. In addition to a conventional multimeter, a high-voltage probe or meter having a range up to 30 kv. should be available. A mirror will greatly help in some adjustments.

Since the high-voltage supply furnishes up to 27 kv. at 1 ma., the ordinary safety precautions should be increased. Wearing rubber soles and heels, plenty of space to move in, and some privacy, are a great help to the technician in his first encounter with the new color TV monster.

Preliminary Adjustment

Remove the color picture tube from the carton and place it face down on a padded spot. Figs. 1 and 2 show the location of the various items mounted on the 15-inch color picture tube. The Mumetal shield does not fit directly on the tube envelope, but contains foam rubber pads which cushion and center it. A plastic insulating ring, similar to the ones used on metal-envelope tubes, fits over the metal flange which connects internally to the 2nd anode or "ultor." Fig. 3 shows the components on the 19-inch color tube. The major differences between it and the 15-inch

Line the inner tube mask up with the cabinet escutcheon. Before connecting power to the receiver, be sure all plugs are in their respective sockets.

Turn the set on, allow for warm-up time, and tune in a monochrome or color telecast. Check fine tuning, contrast, brightness, and sync for best reception. In most color TV receivers, the high voltage is regulated, and this regulation as well as the actual voltage should be checked. The voltage at the kinescope "ultor" terminal—the metal flange near the face of the tube should remain at 20 kv. (27 kv. for the 19-inch tube), with either a bright or dark raster. Check this by watching the meter and varying the master brightness control.

To improve regulation or increase the voltage to the correct value, adjust the high-voltage regulator control shown in the simplified diagram of Fig. 4. This control is usually located inside the high-voltage compartment.

Next, turn the color or chromaticity control counterclockwise for minimum color video and adjust the contrast or brightness control for a fairly clear picture. At this stage of adjustment, the coloring of the screen can be neglected and adjustments for a.g.c., horizontal and vertical sync, linearity, size, and centering should be made. Do not attempt to oversweep the edges of the internal screen mask, but rather leave the left and the top edge visible

For these adjustments, especially for linearity checks, a station test pattern is very helpful. If none is available, the bar generator can be used. In color TV it is absolutely essential that both vertical and horizontal linearity be near perfect. Later adjustments will affect such other criteria as focus and convergence. Incorrect linearity will greatly complicate the dynamic focus and convergence adjustments, so be sure to get the proper aspect ratio, size, centering, and linearity before adjusting any of the color controls. Good synchronization, especially in the hori-

RADIO & TELEVISIO: NEWS

zontal section, is also essential. Most receivers use a modified synchroguide circuit, requiring both locking and phasing adjustments for which standard black-and-white adjustment procedures

apply.

The cylinder located near the picturetube socket, as shown in Fig. 2, is the purity coil assembly. It consists of the purity coil, three small permanent magnet screws, and the magnetic shield cover. See Fig. 3 for the position of the purity coil on the 19-inch tube. Adjusting color purity involves orienting the three electron beams with respect to the center line of the picture tube. It is necessary to vary the location, direction, and magnitude of a transverse magnetic field for each of the three beams and, finally, optimize for best combined operation. One satisfactory method for doing this is outlined below.

1. Remove the video signal and turn down the green and blue screen controls. (See Fig. 5.) Adjust the red screen control for a screen color of

almost pure red.

Slide the deflection yoke as close to the purity coil as possible, and screw the three permanent magnet screws out from the center for minimum effect. For the 19-inch tube, turn the d.c. convergence controls to minimum.

3. Rotate the purity coil and adjust the current through it until the center of the screen is a deep pure red. Consider only the center and disregard the edges. It is possible to obtain good purity with several combinations of coil current and position; select the one using the least purity-coil current.

4. Slide the deflection yoke forward until the entire screen is a uniform red. Now the neck shadows and color contamination along the edges should be eliminated by proper yoke placement. It may be necessary to touch up the purity-coil adjustment if it is not possible to get a clean red raster with the yoke placement.

5. Turn the red screen down and the blue screen up. If the screen color is not a uniform blue touch up the puritycoil current and rotation slightly.

Turn the blue screen down and the green screen up. It may again be necessary to touch up the purity adjustment.

Check purity again on red and blue. In some receivers a compromise must be made between best purity on all three colors.

8. It may be that all preceding adjustments cannot be made as smoothly and simply as described. Occasionally some stray magnetic field may interfere and this would be noticeable by sudden rather than gradual variations in purity or by stubborn color contamination at a particular spot on the screen. Such external magnetic fields may be due to a magnetized screwdriver, a permanent magnet speaker, or other magnetic device located near the receiver. Some color sets use a field neutralizing coil located near the screen as shown in Fig. 2, and this coil can be adjusted to overcome the effect of stray

fields. In general, the field neutralizing coil is rotated and the current through it adjusted to aid the purity assembly in its operation. The adjustment procedure described appears quite complex and time consuming, but after some practice it is possible to perform the purity alignment in five minutes.

Convergence Adjustment

In order to get sharp and clear color pictures it is necessary for all three electron beams to strike the screen simultaneously at adjacent dots. For the 15-inch tubes, three separate forces make the beams converge and each of these must be carefully adjusted. The first consists of three small magnets located on the purity coil shield around the neck of the picture tube. Each magnet has its major effect on the electron gun lying underneath it, but also affects the beam from the other two guns. The purpose of the magnets is to position the three beams so that the three colored rasters coincide.

In addition to the magnets there is an internal, electrostatic-lens type element in the 15-inch tube which controls the beam convergence at the screen. It receives a high d.c. voltage, adjustment of which determines the convergence at the center of the screen. The convergence element also receives a horizontal and vertical dynamic convergence voltage which, when superimposed on the d.c. potential, determines the convergence at the edges of the screen. This dynamic convergence signal is reguired to compensate for the variation in electron beam path length as the beam moves from the center of the screen to the edges. Fig. 6 shows the wave shape of the dynamic convergence voltage.

It should also be pointed out that the beam focus must be varied as well. In

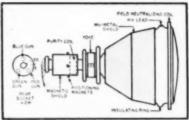


Fig. 2. Shown here are the various focusing and deflection components that mount onto a 15-inch color picture tube. The field neutralizing coil may be omitted in some receivers.


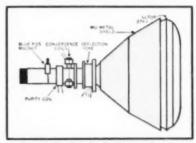


Fig. 3. A 19-inch shadow-mask type color TV tube shown with the various deflection and focus components. Note that here electromagnetic convergence is used rather than electrostatic.

the 15GP22 and 15HP22 there are three electrostatic focus elements connected together which receive a d.c. focus voltage, plus a portion of the dynamic horizontal and vertical convergence signal. The schematic presentation for this connection is shown in Fig. 4.

Before adjusting for convergence and focus, the screen should be tuned for a low-brightness white. This is done by turning the chromaticity control down and adjusting the red, blue, and green

Fig. 4. Focus, high voltage, purity, and convergence adjustments for color set.

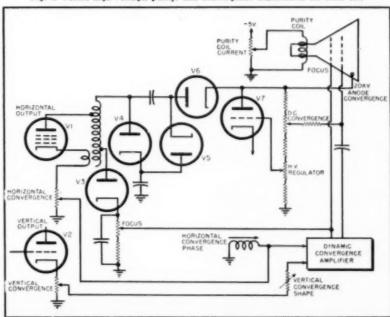

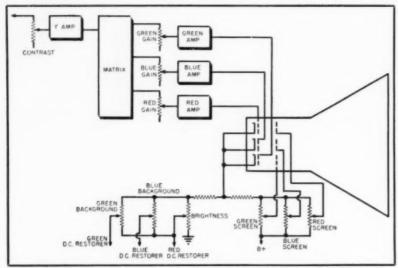


Fig. 5. Brightness, contrast, and color controls of a color TV receiver. Not all of these controls are adjusted by the service technician when he installs the tube.

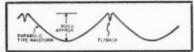


Fig. 6. Waveshape of the horizontal convergence voltage for a 15-inch tube.

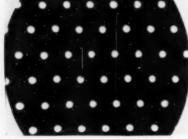


Fig. 7. Dot pattern generated by a dot generator and observed on the screen of a color picture tube when the three guns are in good convergence. Each dot actually consists of three different colored ones, so close they look like one.

screen controls until a neutral white or light gray is obtained. It should be pointed out that this will not be achieved when all three controls are set to exactly the same point. To get white some experimentation is required

Fig. 8. The pattern appearing on the face of a color tube when a dot generator is used and the d.c. convergence voltage is lower than normally required.



which usually provides a demonstration of the principles of colorimetry. When the blue screen is turned down and the red and green turned to about equal brightness, yellow will appear. Red and blue only will result in shades of purple. With some practice it is quite easy to get a neutral light gray quickly.

To set the three positioning magnets roughly, adjust the centering controls until a corner of the raster appears. Usually this corner will show some of the colors even when the rest of the screen is white. It will appear that the three rasters do not overlap completely. Where all three overlap, white will appear. Where red and green overlap the screen will appear yellow. Red and blue give magenta, and blue and green produce cyan (a greenish blue color). At this stage it is best to "make haste slowly."

Turn each of the three permanent magnet screws inward one turn at a time, and observe the effect of each one on all three colors. It will become apparent that each of the magnets has major control over one color but also has considerable effect on the other two electron beams. In other words, the adjustment of each magnet must be followed by adjustment of the other two magnets until a good compromise set-ting is reached. The aim of this compromise is to get all three colors to coincide as well as possible. It should be pointed out here that perfect corner registry is not essential nor easily attainable.

The convergence adjustments must be made with some kind of video signal, otherwise lack of convergence is not apparent. The best type of signal consists of a number of very sharp pulses, producing a dot pattern on the screen. Other usable patterns consist of vertical and horizontal bars, preferably in a grid pattern, or a regular monochrome video signal. In the last instance it is preferable to use a station test pattern if available.

Poor convergence will give the ap-

pearance of three colored pictures out of register. When the monochrome video signal is used, the edges of objects will appear in three colors, rather than uniform gray. If the d.c. convergence is good, this poor registration effect will be most noticeable at the sides. This is somewhat tricky to check especially on moving scenes. For this reason the use of a grid or dot pattern is better. Adjusting convergence with a dot generator is fairly easy.

1. Connect the dot generator and adjust the brightness and contrast controls to avoid blooming and obtain sharp dots, locked in with the sweep circuits. Fig. 7 shows the screen of a color tube with a properly converged dot pattern.

Referring to Fig. 4, turn both vertical and horizontal dynamic convergence controls to minimum.

3. Turn the d.c. convergence voltage control to a low value until three separate dots are visible as in Fig. 8. The green dot is at the left, the red next to it, and the blue below.

4. Turn the d.c. convergence voltage control up until the three colored dots merge into a white dot at the center of the screen. If the convergence voltage is too high the pattern of Fig. 9 will appear where the blue dot is on top and the entire color sequence reversed from Fig 7.


5. It may not be possible to obtain perfect convergence at the center of the screen with the d.c. convergence control. In this event the positioning magnets must be reset. Every change in the positioning magnets will require some further change in the d.c. convergence setting. At the same time the focus control must be set each time for best focus. All these adjustments are interdependent to some degree and the best approach is to perform each step slowly, not advancing any control too far and carefully observing the dot pattern on the screen. In some picture tubes it may appear that the magnets should be positioned quite close to the guns, but this means that the optimum position has already been passed and the magnets should be withdrawn several turns.

6. After the center of the screen shows clear white dots without color fringing, the dynamic convergence controls are adjusted. The vertical dynamic convergence controls, see Fig. 4, are set first to make the top and bottom misregistration equal. Observe the dots going down the center line and when top and bottom dots appear equally misregistered, touch up the d.c. convergence control to converge the entire vertical center line of dots.

7. Now adjust the horizontal dynamic convergence control for equal misregistration of the left and right dos on the horizontal center line. As in step 6, touch up the d.c. convergence control to converge the entire center line.

8. If it appears impossible to converge both left and right edges, the horizontal dynamic phase control, as shown in Fig. 4, should be adjusted. Similarly, if vertical convergence cannot be achieved properly, the vertical

(Continued on page 92)

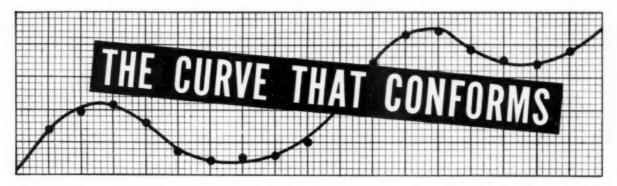

VER since the advent of the longplay record and high-fidelity reproduction, music lovers have been plagued by a thing called "record equalization." No one questioned the merits of equalization but many decried the lack of standardization in the recording industry.

Before the LP era everything was relatively simple. There was one curve (Columbia-NAB) and for six or seven dollars you could buy a neat little preamp with the curve built in and unvariable. Since the advent of LP discs, however, it seems that every engineer in every record company has a different idea about record equalization. Before you could say "turnover," music lovers were overwhelmed by such curves as NAB, AES, ffrr, Orthophonic, and others. The preamp? It has become a bloated monster, replete with many knobs and dials for the production of the widely varying curves. Needless to say, the price of participation in this exotic and fascinating game of "match the curve" has gone up too, from six to fifty dollars and more.

After several futile attempts at standardizing the equalization curve, most manufacturers gave up and continued the status quo. At this point the powerful and influential Record Industry Association of America (RIAA) entered the fray, and now, happily, it is possible to report that the new "RIAA Standard Record-Playback Curve" is Record manufacturers have now agreed not to disagree with the new record-playback curve. Here are the details.

being adopted throughout the record industry

Essentially, the new RIAA curve is the same as the RCA Victor "New Orthophonic." The bass turnover point is 500 cycles, the same as the old NAB. but with a 3 db flattening at 50 cycles. Treble roll-off is 13.75 db at 10,000 cycles. It is interesting to note that the old AES curve falls within ± 2 db of the new curve above 40 cycles.

Now, what does all this mean to you, the record consumer?

First, you will want to know what companies have agreed to standardize on this one curve. The answer is, virtually everyone. A little later on in this article we will give you the comments of responsible people at most of the major companies regarding the adoption of the new curve. The next thing you will undoubtedly want to know is how this new curve will affect. your playing equipment. Is your expensive preamp now obsolete? The answer is a qualified "no." While very few preamps have the RIAA curve incorporated in its circuitry, most have the AES curve which, as noted previously, is within the tolerance limits of the new curve above 40 cycles.


If you are trying to duplicate the

RIAA curve on a unit with provision for NAB and AES curves, set the bass turnover on the NAB curve, treble equalization set at AES and cut the bass and treble tone controls slightly. If you have a one-knob equalization control on your unit, set it at either the AES curve, in which case you cut the treble and boost the bass a little (on your tone controls) or NAB curve in which you boost the treble and cut the bass slightly on the tone controls. Of course, if your unit has the RCA "Ortho" curve, you are all set, since it is identical with the new RIAA curve.

In all this adjusting for equalization remember this, your acoustic environment is an important factor. Use your tone controls to make the music sound right to your ears. That is what tone controls are for. You may have a 'hard" room with many reflecting surfaces in which you'll probably want to cut your treble somewhat. Then again, you may have the reverse situation with many absorptive bodies like drapes, rugs, and upholstered furniture, which might call for some bass and treble boost.

Still another factor in this business (Continued on page 78)

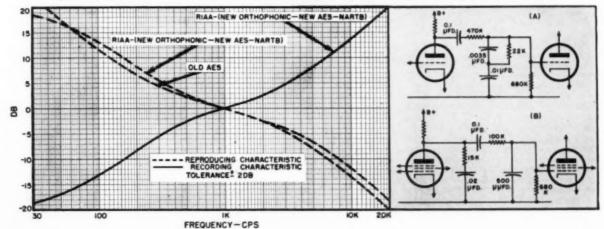New RIAA recording and playback characteristics. The triode and pentode amplifier equalizer circuits (Figs. A and B respectively) when used with a high quality amplifier and pickup are recommended by RCA to obtain the desired basic reproducing characteristics. Minor tone-control adjustments may be required to compensate for pickup characteristics.





Branch out for year-round income. Public address work offers new opportunities for both sales and service.

THE radio-television service shop interested in a money-making sideline should give some thought to public-address system rentals. These could easily grow into a worthwhile venture which could lead to permanent installations and equipment sales. Here is how to go about getting started in this lucrative field.

The first thing to do is analyze the needs of the community and the extent of your competition. The latter point you will have to determine for yourself but the potential market can be discussed here.

A great deal of all sound rental service work is performed evenings and weekends. For example, there are school and club dances, public dances, private parties, banquets, meetings, sporting events, stage attractions, ground breakings, civic events, etc.—all of which are elements of the vast potential in this field.

To a certain extent, the type of work you do will determine the type of equipment you will use so for this reason alone it is essential that you analyze the activities and needs of your potential customers.

Equipment and Systems

Although every technician knows that an amplifier is, essentially, simpler than a television set or a radio and that he will probably have no difficulty in repairing one, unfortunately the average technician's knowledge drops off abruptly at this point. Do not think that because one is an expert in television repairs, he is equally capable of designing, installing, and operating a sound system. Public address work is an art in itself and requires a great deal of trial and error. knowledge of room noise levels and acoustics, and a knowledge of equipment features and limitations before one is able to do satisfactory work at the right price and with a minimum of equipment, effort, and time.

Devote some time to studying manu-

facturers' catalogues as a great deal of knowledge can thus be obtained at no cost and little effort. For example, University Loudspeakers publishes "Technilog" and Masco offers its "Sound Surveyer"—both of which provide invaluable information on loudspeaker characteristics and usage. Similarly, other manufacturers of sound equipment have handy tables, pamphlets, and manuals available at nominal or no cost.

In order to keep the amount of equipment at a minimum, a proper selection of components, determined by the needs of the community, must be made. Two principal types of jobs present themselves—one in which the customer merely rents the equipment and operates it himself and the other in which you install and operate the equipment.

You should be prepared to allow the customer to operate some of the equipment himself for many affairs do not warrant the services and expense of a paid operator. Under these circumstances the customer should be prepared to come and pick up the equipment, receive brief instructions on how to set it up and operate it, and bring it back at the required time.

A number of manufacturers make this type of portable outfit and you should select one capable of handling from 15 to 30 watts of normal audio power output. Perhaps an outfit incorporating a record player would be desirable. At first buy just one of these outfits, adding more units as business expands. One or two microphones with a floor stand for each should be included in the system. The rental can be upped in cases where the customer requires two microphones instead of one.

A portable sound system having two 12-inch PM speakers should be used. The speakers should be self-supporting and also be capable of being hung on a wall. The microphone connectors should be so different from the loudspeaker plugs that their hookup becomes obvious to the layman and no mixup can occur. All controls and connectors on the amplifier should be properly labeled.

The list of suggested components comprising a small, basic public address system rental outfit is given in Table 1. This outfit will provide two complete sound systems. If all the equipment is combined into a single installation you would be able to feed six loudspeakers with 45 to 60 watts of power, using three microphones and two record players, all separately controlled.

Let us examine the characteristics of the components more closely. The author has used virtually every principal brand of microphone with every high quality feature and has found that for price, ruggedness, compactness, reliability, feedback reduction, output level, good looks, and ease of operation, the straight pressure (dynamic) microphone can't be beat. An important feature of this type of unit is that it takes the breathing and banging of the layman and is foolproof in use. The author recently attended a gigantic stage show in Hollywood where a group of top movie stars appeared. The show was almost ruined by the fact that these professionals were speaking into the wrong part of a new type microphone recently released by a major manufacturer.

The high impedance microphone system is often lower in price than its low impedance equivalent, principally because no input transformer is required. The limitation, of course, is that cable lengths in excess of 20 to 25 feet will result in drastic reduction of high-frequency response. Although the beginner may wish to start out with a high-impedance unit, he will soon find, as business increases and installations become larger and more complicated, that he will have to convert to low impedance microphones-a change that will cost between \$8 and \$15 per microphone, not counting the cost of changing to low impedance cables, input transformers, connectors, and the corresponding "down time" of the equipment. Try the Electro-Voice 630 or Turner 22D microphone.

The portable sound system needs are described in Table 1. Look over the features of units like the Newcomb TR-25AM.

The three-section microphone floor stand specified is useful as a banquet table stand and also where a microphone must be placed close to the floor. It of course functions as a regular floor stand when required. The boom attachment is excellent where the stand has to be a few feet from the performer, but where the microphone must be very close to him. The Atlas BB-1 or similar units meet this requirement inexpensively.

For the regular p.a. work that you will do involving one or two microphones, you will want to use a 25 to 30 watt basic amplifier with preamplifiers. Any one of the principal brands will

probably do nicely. The input impedances must match those of the microphones. You may wish to build your own amplifier but before doing so carefully determine the parts and labor cost. You may find that you are better off purchasing completed amplifiers.

The choice of a loudspeaker is probably more important than that of a microphone. You will probably need at least one set of outdoor horns. These particular units should be, at least, semi-weatherproof. Such horns are needed in order to make up for the immense amount of power lost in the open air. The new CDP speaker by *Electro-Voice* is well suited for this work as it is weatherproof, has good frequency response, good dispersion angle, and will handle a lot of power. This same speaker can be used indoors for long throws or noisy areas.

For normal indoor work, and sometimes outdoor applications, a cone speaker gives the best quality service. Unfortunately, a large baffle is often required, however both Altec and Stephens offer excellent compact portable cabinets which give rather good results. RCA offers its MI-12448 series floor cabinet which is light weight and can be moved around fairly easily. A bracket should be fastened to your portable, full-range speaker cabinet so that it may be attached to a collapsible speaker floor stand when it is necessary to raise the speaker above the heads of the crowd.

Most cone-type public address loudspeakers are of 8 ohms impedance as contrasted to the usual 15 ohms of horns. This is unfortunate for only two speakers can be driven from the 4 ohm output tap on the amplifier. If the speakers were 15 ohm units you could connect four of them to the 4 ohm tap without the need of matching transformers. A higher impedance is also advisable so that the resistance of the cable will not introduce noticeable power attenuation.

The microphone and loudspeaker cables should be equipped with the type of connectors which will allow the cable to be connected to the amplifier or used as an extension. If not, you will be plagued with the constant need for resorting to wasteful adapters.

Headphones are handy for monitoring installations where the operator cannot easily hear the loudspeakers. A jack and volume control can usually be mounted on the amplifier with the control bridged across the 500 ohm or 70 volt output tap to ground. A volume indicator meter is also handy and is sometimes a necessity.

As mentioned previously, it is often necessary to utilize matching transformers when connecting large numbers of speakers to an amplifier. Basically, these transformers merely connect to one of the higher impedance taps on the amplifier output transformer and convert it to the impedance of the speaker. A separate transformer is required for each loudspeaker, with the combined primary impedances of all the transformers in parallel equal

to that of the amplifier output tap to be used. The matching transformers should be located near their respective speakers so that the longer cables are in the higher impedance part of the transmission line. Equip your matching transformers with the proper input and output connectors and impedance selector switch so that they may be put into service as required without hurried calculations and connections.

A tape recorder is a handy "accessory." On many occasions you will be called upon to provide sound reinforcement and simultaneously record the proceedings. The recorder should be capable of recording directly from a microphone as well as taking a "feed" from the p.a. amplifier. Although the recorder could be connected to the headphone outlet built into the amplifier, it is best to connect it to one of the first audio stages so as to keep hum and distortion on the recording to a minimum.

Standardization

In order to insure complete and instantaneous interchangeability and intermixing of equipment, it is important that connectors be standardized. This means that if the various amplifier have different microphone connectors you will have to replace some of them, otherwise a large array of adapters will be required. This also applies to phonograph and loudspeaker connectors.

On applications requiring large amounts of audio power it may be necessary to parallel the inputs (and sometimes the outputs) of two or more amplifiers. In most cases a high impedance jumper or "patch cord" between the first audio stages will do nicely. Then, a single set of input gain controls on one of the amplifiers will control everything as though only one amplifier is in use.

What About Prices?

A careful study of your competition will undoubtedly reveal a little about your competitors' prices and pricing methods. This should not be too difficult on rentals but may pose a problem on permanent installation sales as many cost and bidding formulas prevail and list prices are often disregarded.

A new entrant into the field will probably have to keep his prices relatively low until customer confidence and acceptance permit a reasonable profit to be realized. An interesting facet of the sound rental business is that once you have a satisfied customer you won't have much trouble keeping him, for service is as important as price in this business. Newspaper or mail advertising as contrasted with recommendations of satisfied customers, will not be too helpful. An ad in the "classified" telephone directory and personal calls on prospective customers will be your next best bets.

Tricks of the Trade

After you have provided equipment for several p.a. rentals, a number of helpful ideas will occur to you. Certain accessories, such as separate loud-speaker "T" pads, low-level monitor amplifier/speakers, broadcast-type mixer/line amplifiers, bridging and distribution transformers, etc., will find their way into your equipment line-up. You may wish to outfit a truck with sound equipment, allowing all operations to be from the truck when possible. You may wish to go in for mobile operations to ballyhoo conventions, political candidates, etc., or specialize in battery-operated equipment for picnics, sports events, etc.

Many permanent installations are actually rentals, that is, the equipment is permanently installed where the customer desires it and most of it is never removed. The customer pays so much a year or a season for you to supply, operate, and maintain the equipment. If you are planning a long-run sound operation, this type of business is worth your consideration as the customer benefits by paying relatively small amounts for current usage while you actually have made a sale which is virtually impossible to lose. This is also helpful to you incometaxwise as it allows you to spread your income over a

(Continued on page 88)

Table 1. Suggested components for a small basic p.a. system rental outfit.

QUANTITY DESCRIPTION

- 3 Pressure microphones, unidirectional, 250 ohm impedance
- 1 Pertable sound system: 15-30 watt amplifier with phono turntable, two 12-inch loudspeakers with 25 ft. cables, two low-impedance microphones and one high-impedance phonograph separately controlled inputs, tone control, pilot light
- Microphone floor stands, two-section, heavy base
- 1 Microphone floor stand, three-section
- 1 Microphone boom attachment 3 50 ft. microphone extension cables with connectors
- 1 25-30 watt amplifier with two 250 ohm microphone inputs and one highimpedance phono input, tone control. pilot light
- 2 Re-entrant trumpet-type loudspeakers

- with a collapsible floor stand for each.

 15 ohms impedance
- 2 Bass reflex type loudspeakers/cabinets, 20 watts, light weight, 15 or 8 ohms impedance
- 2 50 ft. detachable loudspeaker cables. No. 16 or No. 18 wire with connectors
- 2 100 ft. detachable loudspeaker cables. No. 16 or No. 18 wire with connectors
- 2 100 ft. No. 16 or No. 18 a.c. power extension cords
- Record changer attachment, threespeed, crystal cartridge
- 1 Pair high-impedance headphones 1 Set of loudspeaker matching trans-
- formers

 2 Special "multiple" cables to allow speaker wires to be extended from loudspeaker to loudspeaker in order to eliminate doubling up of cables
- 1 Tape recorder

A BASS-BOOST Fig. 1. A preamp which includes an improved bass boost control. The unit, as shown, can be used as a preamp driving a power am-plifier or it could be used between a conventional preamp and a power amplifier.

Details on a separate control unit designed to provide a maximum of ten transition frequencies.

OO many bass-boost controls muffle music and speech. It is a simple matter to change such a control to a better one, or to build a new ampliffer using an improved circuit.

The trouble with the usual control is easily explained. Fig. 2 shows the conventional bass-boost circuit and its response curves. The frequency at which the response is increased 3 db is called the "transition frequency" and is that frequency at which the reactance of the condenser is equal to R_1 . As neither the condenser nor R_1 is adjustable, this frequency remains constant.

The total boost available depends upon the value of R_1 , R_2 , and R_3 . As R_1

is the only adjustable element, then a flattening or "shelving" of the response curve occurs when the bassboost control (R_1) is set at less than its maximum-boost position. (Shelving also occurs at very low frequencies at maximum boost, but this need not be considered here.) Curve A shows the response at full boost, and curve B shows how the curve flattens out at about one-half boost.

This circuit is widely used due to its simplicity, but has two drawbacks which should be given consideration.

The first is that at moderate listening levels, at which, let us say, 8 db of boost at 100 cycles sounds about right, 3.5 db of boost is also obtained at 600

cycles, as shown in curve B. This tends to make a speaking voice sound muffled and upsets the tonal structure of the music produced by instruments whose fundamental tones lie in the mid-frequency region. This causes the type of sound referred to as "muddy" or "indistinct" by laymen.

The second objection is this. Of necessity, the bass-boost control is used in most systems to compensate for a falling-off of the over-all lowfrequency response due to deficiencies of the speaker, baffle, or room acoustics. As these deficiencies usually exist at fairly low frequencies only, the boost produced at the mid-frequencies by the conventional control tends to emphasize speaker, baffle, and room resonances and make the system sound much less satisfactory than it should.


A more satisfactory control would be one which provided a continuallyvariable transition frequency. With such a control, the extreme low frequencies could be boosted as desired without disturbing the flatness of the response curve in the mid-frequency region.

The control and associated amplifier to be described here does not provide a means of compensation for all low-frequency-response troubles, but it does go a long way toward providing a better control of the bass response of a home radio/phonograph system. This control and amplifier was designed to provide a wide choice of transition frequencies as simply as possible.

As it has been found in practice that a choice of seven or eight transition frequencies is as satisfactory as a continually variable frequency, and as it results in certain circuit simplifications, a tap-switch type of control is used. In this case, a choice of ten frequencies is provided, but the number can be reduced if desired.

As mentioned previously, the transition frequency depends upon the values of the condenser and resistor, $R_{\rm in}$ of Fig. 2. Varying either one would shift the frequency. In the improved control, the condenser is varied. At first glance, it would seem easier to

Fig. 2. A conventional control circuit and the resultant response curves. See text.

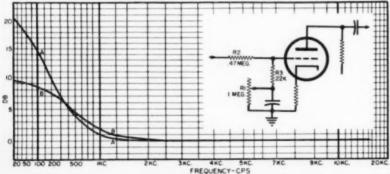

vary R_z , but as the amount of boost is also dependent upon R_z , and as there is a fairly limited range over which R_z can be varied, the capacity variation is the better method.

The chart, Table 1, lists the condensers and the corresponding transition frequencies used by the author. If the reader wishes to experiment with other transition frequencies, the proper value of capacity in microfarads can be found by dividing 7.25 by the frequency desired. Similarly, with a given condenser, the resultant transition frequency in cycles is equal to 7.25 divided by the capacity of the condenser, in microfarads.

The transition frequency is that at which the reactance of the condenser equals R_t . The reactance of the condenser, X_C , equals $1/2\pi fC$, where f is in cycles and C is in farads. Transposing, C equals $1/2\pi X_C$. Substituting 22,000 ohms for X_C , and multiplying by 10^6 , C equals 100/13.8f. Solving the equation produces C equal to 7.25/L.

Similarly, the frequency in cycles equals 7.25/C, C being in microfarads. It should be noted that ordinary paper condensers can be expected to be as much as 20% off from their rated value. This will affect the response curves obtained in the completed amplifier, as will be seen from the curves of Fig. 4. However, it has been found satisfactory to select condensers from the chart or by formula. The reason is that the exact frequency itself is not too important as long as there is a wide enough choice of frequencies available. After the amplifier is completed and tests indicate that one or two curves need correction, then a change can be made in the responsible condenser. If the transition frequency is too low, a condenser of lower capacity is substituted and if

used. R_{I} should be selected by testing with an accurate ohmmeter to be sure that it is as close as possible to 22,000 ohms. If it is not close to this value, all of the transition frequencies will be off even though the condensers used are accurate. The regular commercial tolerances are satisfactory for the other resistors and condensers in the circuit as they have little effect upon the over-all frequency response.

too high, a larger condenser can be

In order to provide an adjustable treble boost, R_i and C_{ii} are included in the circuit of Fig. 3 and a 500,000ohm pot is used for R_2 . When the arm of R_z is rotated to the end of the pot that is connected to R_3 and R_4 , its counterclockwise position, Cn is effectively out of the circuit. This is the setting for flat high-frequency response. When the arm is rotated to the end connected to R_1 , the higher frequencies are bypassed around the attenuating network R_1 and R_2 and fed directly to the grid of the tube. This produces the maximum treble boost. As shown in the curves of Fig. 4, the high transition frequency is about 3000 cycles at full treble boost. This transition frequency can be

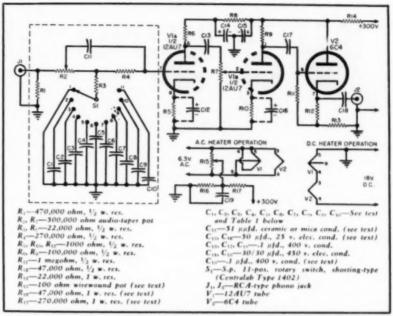


Fig. 3. Schematic of control and amplifier. Section in dotted portion can be added to an existing amplifier, if desired, or built in conjunction with amplifier diagrammed.

raised, if desired, by using a smaller condenser in place of the 51 μ pfd. specified for C_{tt} , or lowered by using a larger value.

In order to provide a good signalto-noise ratio with a minimum of distortion, the tone control circuits are
connected to the grid of the first tube
of the amplifier and the gain control
is placed between the first and second
stages. As the input impedance of the
amplifier is not less than about 150,000 ohms at any frequency, irrespective of the tone control settings, it
may be fed from either a triode amplifier or cathode-follower stage of a
tuner or phono preamp.

The input signal level should not be greater than about 1 volt. If the tuner or phono preamp used furnishes an output greater than this, a gain control should be used on the input source to reduce its output to the proper value. For minimum distortion, the input level should not be greater than necessary to provide sufficient output to drive the power amplifier used in


SW. POS.	CAPACITY (µid.)	TRANSITION FREQ.
1	Short	Flat
2	.2	36
3	.15	48
4	.1	73
5	830.	106
	.05	145
7	.035*	207
	.022	330
	.018	400
10	.015	480
11	.01	725
".035 µid. µid. in paral	made up of .03 lel.	μfd. and .005

Table 1. Values of C, through $C_{\rm in}$ and the resultant transition frequencies. The switch positions correspond to those shown in Fig. 3 and the resulting curves shown in Fig. 4.

the system to full volume. As the over-all gain of this amplifier is about 12 db, a 1-volt input will furnish 4 volts output.

The use of a cathode follower in the output stage provides an output impedance of about 650 ohms so that a hundred feet or so of shielded cable can be connected between this amplifier and the power amplifier of the (Continued on page 88)

Fig. 4. The response curves of the improved bass-boost control. See Table 1.

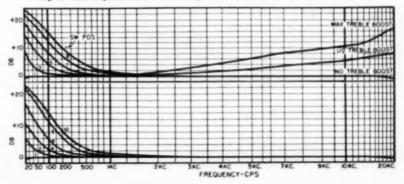

1954 TV RECEIVER SPECIFICATIONS

Continuation of the list of mechanical and electrical specifications on new TV sets for service technicians. See next issue for additional listings.

					TUBI	28			VIDEO I.F. FREQ. (MC.)	H.V.4 (KV.)	U.H.F. PRO-	POWER (WATTS)	SPECIAL FEA- TURES
MFR.	CHASSIS	TUNER	I.F1.	VIDEOZ	AUDIO	SWEEP1	P.S.	CRT	FREQ. (MC.)	(RV.)	PRO- VISION	(WATTS)	TURES
	KCB78	6BQ7 6X8	eCB6 eCF6 eCF6	6CL6 12AU7	6ALS 6AU6 6AU6 6AV6 6K6GT	6EQ6GT, 6K6GT 6SN7GT, 6SN7GT 6W4GT, 12AU7	1B3G T SU4G SY3GT	17CP4 17QP4	45.75	16	11	215	5
RCA	KC883	6BQ7 6X8	6CB6 6CF6 6CF6	6X8° 12AU7 12AU7*	6ALS 6AU6 6AU6 6AU6 6AV6	6AX4GT, 6EQ6GT 6K6GT, 6SN7GT 6SN7GT, 6X8° 12AU7°	5U4G	21AP4 21EP4A 21ZP4A	45.75	18	11	215	5, 10
	KCS84	6BQ7 6X8	6CB6 6CF6 6CF6	6X8* 12AU7 12AU7*	6ALS 6AU6 6AU6 6AV6 6K6GT	6AU4GT, 6CD6G 6K6GT, 6SN7GT 6BN7GT, 6X8* 12AU7*	1B3GT 5U4G 5Y3GT	24CP4A	45.75	18	11	245	5, 8, 1
RADIO	C210P &	6BQ7A 6J6	eche eche eche	6AL6 6AU6 6CL6 6CL6	EALS EAUE EAUE 12AU7	6AL5, 6CB6 6CD6, 6S4 6SN7, 68N7 6W4, 12AT7 12AU7	1B3 8U4G 5Y3	24CP4A 27EP4 27RP4	42	18	Strips or 11	365	Designs for cus tom ir stalla-
	2118	6BZ7 6U8	6CB6 6CB6 6CB6	CK706 29G8	6AL5 6AU6 6AV6 25C5	6ALS, 6BE6 684, 12AU7 12AU7	1B3 6AX4 25BQ6	21YP4	41	18	11	175	2, 3
TEON	21711	6BZ7 12AT7	6CB6 6CB6 6CB6	6AL5 25C5	6AL5 6AU6 6AV6 25C5	6ALS, 6BE6 6S4, 12AU7 12AU7	1B3 6AX4 25BQ6	21YP4	20	18		175	2, 3
RAYTHEON	24T2	6BZ7 6U8	6CB6 6CB6 6CB6	6AH6V 6AU6 CR706	6AL5 6AU6 6AV6 50C5	6ALS, 6BE6 6BF6, 6BF6 6B4, 12AU7	1B3 5Y3 12AX4 25CD6	24DP4	41	18	11	265	2, 3
	24Т3	6BQ7A 12AT7	6CB6 6CB6 6CB6	6AH6V 6ALS 6AU6	6AU6 6AV6 80CS	6ALS, 6AV6 6BE6, 6BF6 6S4, 12AU7	1B3 5Y3 12AX4 26CD6	24DP4	20	18		265	2, 3
SENTINEL	X 19	6BQ7A or 6BZ7 6J6	6CB6 6CB6	1N60 6CL6	6ALS 6AU6 6SN7° 6W6	6BQ6, 6SN7* 6SN7, 6SN7 6W4, 12BH7	1B3 5U4	17HP4A 21FP4A 21YP4A		15	11 or Strips	225	5, 10
	X21	6BQ7A or 6BZ7 6J6	6CB6 6CB6 6CB6	1N60 6CL6	6ALS 6AU6 6SN7* 6W6	6BL7, 6CD6 6SN7, 6SN7 6SN7*, 6V3 6V3, 12BH7	1B3 5U4 5U4	24CP4A 24TP4A 27EP4		18	Strips	250	10

^{1.} Video i.f. tubes only. 2. Includes detector and a.g.o. 3. Includes sync section and a.f.o. 4. CRT 2nd anode voltage. 5. Removable safety glass. 6. Local-fringe a.g.o. adjustment. 7. High-fidelity sound. 8. Aluminized picture tube. 9. TV-radio-phono combination. 10. Built-in antenna. 11. 82-channel tuner. 12. Adjustable dial light. "Part of tube is used in another section.

Fig. 1. The appearance of unmodulated r.f. interference as caused by oscillator radiation.



TVI TROUBLESHOOTING

By CARL J. QUIRK

Allen B. DuMont Laboratories

Author, "A Handbook of Television
Interference"

N the first two articles of this series, we laid the groundwork for successful interference investigations. In this article, we will discuss specific interferences, their causes and suggested cures.

Fig. 1 illustrates interference belonging to the unmodulated classification. Further, adjusting the finetuning control could indicate whether this interference was tunable or untunable. Let us direct our attention to cases of the untunable-unmodulated type first.

Oscillator radiation. Of the many sources of unmodulated-untunable interferences, without a doubt the most prevalent source is that of oscillator radiation into other TV sets. This problem is caused primarily by TV sets using an i.f. in the 21-mc. range. The oscillator of the offending receiver radiates a signal whose frequency is approximately 21 mc. plus the frequency of the sound carrier of the received signal. The radiated signal thus falls into a higher channel. The intensity of the interference will, of course, depend upon the radiated signal strength and beat frequency. The closer the interfering signal is to the video carrier of the interfered-with signal, the greater will be its effect. Table 1 shows the possibilities of this interference.

Interference due to oscillator 2nd harmonic radiation will occur primarily in locations where the sets are close together or connected together in some manner; for example, in a dealer's store, or in an apartment house where the sets are back-to-back with only the wall of the adjoining apartment separating the two receivers. In such cases, if a master distribution system is in use, it is not enough that the sets be isolated electrically through the use of suitable isolation pads. It is also important that there be adequate physical separation. This is essential since a great deal of the radiation takes place from the chassis proper.

This type of interference is one of the most difficult to eliminate successfully. One of the reasons and, without

Part 3. Methods of eliminating TVI due to local oscillator radiation and video i.f. harmonics.

a doubt the most important one, is that the interference occurs "on-channel;" i.e., it enters the gate through which the desired signal enters. Any attempts to eliminate the interference by traps at the front end of the set usually will have a noticeable effect on the picture.

The author was successful in eliminating this interference in one particular case by the use of a seriestuned trap to ground in the last i.f. stage, as shown in Fig. 2. To eliminate the interference, which incidentally occurred on channel 13, the trap was tuned into the passband until the interference disappeared. Since this cut a "slot" into the i.f. passband, it might be suspected that the effect would be quite noticeable in the picture. This was not the case though, and the picture seemed unaffected. However, if the set was tuned to another station which had a test pattern on, the notch was plainly visible in the vertical wedge of the test pattern due to the absence of modulation for the width of approximately 500 kc. Unfortunately, such a cure has definite disadvantages, one of which is evident when the owner of the offending set changes the tuning and thus pulls the interference out of the trap.

This particular type of cure will work best when the offending set is not of the intercarrier type. In such a case, the point of tuning is fixed and, except for oscillator drift, the interference should stay in the trap.

At present, most manufacturers are using an i.f. of 41.25 mc. for sound and 45.75 mc. for video. Since the oscillator frequencies used for this i.f. do not fall into any channel, the problem of oscillator interference is minimized. There is, however, a possibility that harmonics of the oscillator, when operating on certain low channels, will fall into certain high channels. For example, for channel 2, the oscillator signal is 101 mc. Its second harmonic of 202 mc. may interfere with the video carrier of channel 11 (199.25 mc.) to produce a beat of 2.75 mc.

There are several things which can be done to minimize oscillator radiation interference:

(Continued on page 102)

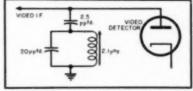


Fig. 2. Trap used in the output of the video i.f. strip to eliminate i.f. due to an interfering oscillator signal.

Table 1. List of the possibilities of interference due to oscillator radiation. The local oscillator of one receiver radiates a signal which mixes with the video carrier of the television signal of another receiver set to a higher channel producing a beat frequency which appears on the CRT as vertical or stant lines or bars.

OFFENDING SET TUNED TO			OFFENDED		
Channel	Video Carrier	Local Oscillator	Channel	Video Carrier	BEAT
2	55.25 mc.	81 mc.	5	77.25 mc.	3.75 mc.
3	61.25 mc.	87 mc.	6	83.25 mc.	3.75 mc.
4	67.25 mc.	93 mc.			
5	77.25 mc.	103 mc.			
6	83.25 mc.	109 mc.			
7	175.25 mc.	201 mc.	11	199.25 mc.	1.75 mc.
8	181.25 mc.	207 mc.	12	205.25 mc.	1.75 mc.
9	187.25 mc.	213 mc.	13	211.25 mc.	1.75 mc.



DAVID FIDELMAN Author, "Guide to Audio Reproduction"

How to repair audio systems and check newly constructed audio components by using standard service techniques.

THE high-fidelity reproduction of sound is rapidly becoming one of the major fields of electronics. At one time, those interested in this field were a relatively small group of technicians and engineers who built most of their own equipment, and those high-fidelity enthusiasts who could afford to own custom built equipment. Most of the service and construction was done by technicians who specialized in the setup and installation of custom audio systems.

At the present time, however, the general public has become interested in high-fidelity reproduction and the major radio manufacturers are beginning to produce large quantities of high-fidelity audio equipment for general sale to the public. With the increasing sales of such equipment, there is an increasing amount of service and system setup by the radio and TV service technician who is not an audio specialist.

However, some of the techniques required in the service, construction, and installation of audio equipment are different from those used in standard radio and television servicing. It will be necessary for the service technician to become familiar with these new techniques and to learn how to apply those he is already using.

The basic setup for any type of audio measurement is shown in Fig. 1. A known input signal is applied to the input of the system and the resulting output is measured across the load impedance. Each different unit requires the correct type of input signal and the output must be measured by the proper type of measuring instrument. In audio systems, the various quantities which it may at times be necessary to measure are: (a) audio frequency electrical signals; (b) characteristics of recordings such as

discs and magnetic tapes; and (c) characteristics of transducers such as microphones, pickups, and loudspeak-

The actual testing and troubleshooting process can be separated into two basic procedures-first, to evaluate the performance of the system or unit and determine whether there is some failure or decrease in quality; second, to locate the actual failure. It is generally possible to listen to the overall performance of a sound reproducing system by ear and rapidly determine in a very rough way whether it seems to be operating properly. However, quantitative measurements and the location of any failure in the system can only be done with the proper test instruments. These include:

A variable-frequency sine-wave oscillator

An audio-frequency vacuum tube voltmeter

An oscilloscope

A standard test record

A calibrated microphone

These are the basic instruments needed for testing sound reproducing systems and should be a part of the equipment of every service technician.

Fig. 2 shows a typical test equipment setup for checking the over-all performance of a sound reproducing system. An electrical signal, either from the signal generator or from a test record played on the record player, is fed into the amplifier (through a matching impedance in the case of a signal generator). The sound output is measured by a microphone fed to a v.t.v.m. For this purpose the characteristics of the microphone must be accurately known.

Signal Tracing

The best method of determining where a failure has occurred is by use

of the signal-tracing technique. The same basic method is used in locating and correcting both system failures and failures in a single unit of a system. A system failure must first be localized to a particular unit, then more intensive servicing locates the particular component failure in the unit, so that it may be corrected.

The procedure used in signal tracing to locate a system failure may be

summarized as follows:

1. A single-frequency sine wave (a frequency of 1000 cps is suitable) of the proper voltage is applied to the input of the system or unit and the output terminated in the correct load resistance or in the loudspeaker. The output impedance of the signal generator should match the input impedance of the unit (a matching network may be used).

An oscilloscope or a vacuum tube voltmeter is used to observe the signal at progressive points in the system, starting from the input and progress-

ing to the output.

3. If the system or unit is not operating properly, then at some point in the circuit the signal may either disappear entirely between two successive test points, or one unit may not have the correct gain or output level, or the distortion may become excessive, or any of a number of other difficulties may be encountered depending upon the exact nature of the circuit failure.

In this manner, any failure or improper operation in a complete sound reproducing system can be localized to the individual unit at fault. It is then necessary to locate the specific

failure in this unit.

The unit should first be visually inspected to detect any obvious failures. Then, with power off, the resistance from "B+" to ground should be measured to indicate any direct breakdown. After the visual check and the measurement of resistance from "B+ to ground, the unit should then be turned on and the power supply voltages measured. If the plate or the heater voltages are not correct, then the failure should be looked for in the power supply or in those sections of the circuit which could cause unnatural loading conditions due to component failure.

If the power supply voltages are correct (or any break-downs have been corrected), all the tubes warm up when heater voltages are applied, and if the equipment is still not operating properly, the signal-tracing technique should be used to locate the failure in the unit. The procedure is approximately the same as for the complete system: Apply a single-frequency sinewave signal of the proper voltage to the input of the unit through the correct impedance and use an oscilloscope or a vacuum tube voltmeter to observe the signal, starting at the input and progressing to the output. At some point in the circuit, the improper operation will be found. When an incorrect signal is located in the plate circuit of a specific tube, or in the grid circuit to which it is coupled, the following tube in the circuit should be removed from its socket to eliminate any effects reflected into its grid circuit. If removing this tube corrects the difficulty, then the trouble is probably an open connection in the plate circuit causing the grid to conduct as a diode and heavily loading the preceding plate circuit. Otherwise the error is in the circuit between the two points where the improper operation shows itself.

Once the difficulty is localized in this manner, inspect the circuit visually, then with an ohmmeter and a voltmeter to find the circuit failure.

Testing New Constructions

With chassis and circuits that have been custom-assembled and wired, it is necessary to troubleshoot and check all of the work that has been performed to locate any errors that may have been made and to insure that they are corrected. The use of the proper troubleshooting procedures can greatly simplify and reduce the amount of work and effort involved, and prevent possible damage to the equipment. Basically, the same procedure should be used when new constructions of any type of equipment are turned on for the first time:

 Check the entire circuit against the schematic and wiring diagrams to eliminate obvious errors. A continuity check with an ohmmeter will also disclose possible errors before the equipment is turned on.

Connect the ohmmeter between "B+" and ground; it should show a very high resistance if the circuit is wired correctly.

Remove the rectifiers from their sockets before power is turned on, so that the a.c. and heater circuits can be checked without the application of plate voltage.

4. If all the tube heaters light up and the tubes become warm, and no wiring errors show up, the rectifiers should then be plugged into their sockets to obtain plate voltage.

5. Connect a resistor across the input of the unit under test, equal to the output impedance of the preceding unit in the complete system. Connect the correct load resistance to its output. Then, with no signal applied to the input, there should be no output signal across the load resistor.

If there is an output voltage with no input signal, then the circuit is not operating properly. The specific circuit wiring error can often be located just by observing and classifying this output signal.

If there is excessive hum, there may be a wiring error in the heater circuit, or in the plate voltage filtering, or there may be an open grid circuit.

In amplifiers designed without negative feedback, the presence of oscillation in the output may be due to improper wiring and component layout which causes a large amount of capacitive coupling between high-level and low-level parts of a high-gain circuit.

In amplifiers where negative feedback is taken from the secondary winding of the output transformer back to an earlier stage, the presence of oscillation may mean that the feedback connection has been made to the wrong side of the secondary. Reversing the connections should remove the oscillation by correcting the phase of the feedback from positive to negative.

In some feedback power amplifiers, there may be a high-frequency oscillation which is not eliminated by reversing the connections to the output transformer secondary. This oscillation is due to high-frequency phase shift in the circuit or transformer, which causes the feedback to become positive instead of negative at high frequencies. It is generally eliminated by connecting a small condenser in series with a high resistance to ground in one of the high-impedance plate circuits within the feedback loop.

A very low-frequency oscillation (at frequencies as low as a fraction of a

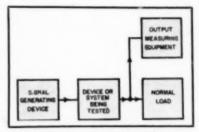


Fig. 1. Basic setup for testing audio gear.


cycle-per-second), known as "motorboating," may exist in the amplifier due to positive feedback through the power supply at low frequencies. The cure for this is to increase the amount of plate decoupling in the low-level stages.

After this initial procedure has been followed, an audio signal should then be applied to the input of the unit. The resulting output signal will indicate whether the remaining wiring in the signal circuit is correct. If the proper output signal is obtained when the appropriate input signal is applied, then the unit is operating properly and may be used in the system. If the proper output signal is not obtained, then the difficulty can best be located by the use of the signal-tracing technique.

Record Changers, etc.

It is generally simpler to troubleshoot and service the electronic components and sections of the system than the electromechanical components. These units are usually completely assembled at the factory, and only minor repairs and adjustments can be made without seriously affecting their operation and performance. However, it is not usually necessary (Continued on page 116)

Fig. 2. Over-all test of sound reproducing system. The electrical input from a signal generator and the sound output measured by a calibrated zaicrophone and vacuum tube voltmeter are used. Care must be taken to avoid acoustical resonances in the room. The characteristics of the test microphone must be accurately known.

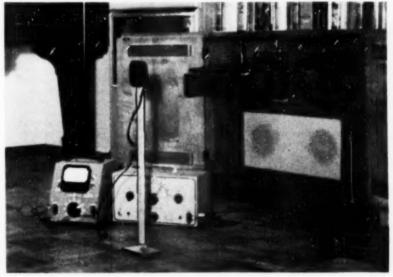



By BERT WHYTE

HE music lover who lives in the City of New York is a very lucky person. Few places in the world can offer such quantity and quality of musical events-operas, choral works, symphony concerts, chamber recitals. All these and more are available to the New Yorker. If the music lover is a hi-fi fan, New York is seventh heaven. Live concerts on high quality FM are common, along with recorded music programs from some of this country's finest FM stations. If our hi-fi fan wants to hear a new piece of equipment, he has dozens of hi-fi distributors who will cater to his de-When records are to be purchased, he can whet his musical appetites in famous record stores, where the "Golden Rule" is not silence, but "thirty percent off list." I could go on and on. It's no wonder many people envy the luck of the New Yorker.

There is little chance of anyone becoming bored with the musical life of New York. Take for instance this nifty idea I came across not long ago. I was in N.Y. with a few friends, fairly late in the evening. We had just come from a recording session and everyone was hungry and thirsty. Now if there is one thing New York is more amply endowed with than anything else it's eating places. After the usual suggestions that we eat, "in the restaurant," or "the cute little place on 48th," someone in the crowd insisted that we go to the Prince George Hotel. He said we would find something really unique in their restaurant. With no disrespect intended, the Prince George Hotel would never have entered our minds as a place to eat. It's sort of out of the main stream of activities, on the lower part of Madison Avenue. The hotel has seen better days and is now what you might call "genteel." It is neither high class nor is it shabby or seedy. More out of curiosity than anything else we decided to go. As we entered the dining room, a very large and handsome room in the old tradition, I looked to the right and what I saw nearly floored me! There was a sort of counter about 12 feet in length at that end of the room. Behind this counter was a very attractive young brunette presiding over a microphone, a professional Fairchild transcription table and turret arm, and several high power amplifiers! In three display racks in front of the counter were the familiar bright jackets of classical LP records. In the wall behind the counter was a large screen or grille which concealed four 15-inch woofers, four tweeters, and associated networks in a large theater-type baffle. There could be no doubt! It was a hi-fi system, by Gad! After we were seated I noticed what looked like a menu on the table. And so it was, except that it was a musical menu. On this were listed selections ranging from Bartok's "Miraculous Mandarin" to the "Nutcracker Suite." You checked off what you would like to hear and the waiter conveyed this to the young lady in charge, and presto!, believe it or not, up comes your selection and it is played at a good room-filling level! No background music here. I looked around to see if there would be squawks about the high volume from some of the other patrons. Far from this, they were listening raptly. The system was very good and everything was well balanced. After the initial shock wore off, I decided to find out how long this sort of thing had been going on. The young lady was most helpful and introduced me to Mr. John Andrews, head of a firm called "Music of Distinction." The principal activity of this company is wired music, but in this instance, this was the initial effort with a high-fidelity installation, not intended for background music use. The evening I was there marked the third week since its inception. And what was the public's reaction? Shock at first, of course, but it was not long before the room became known to the hi-fi bugs and it was smoother sailing from then on. Most record companies cooperate with the venture and all the latest releases can be heard. Yes, people still talk while the selections are being played, but it is the people who are subdued, not the music. I think you will agree this is indeed something unique and something which might well be introduced in other cities. After enduring the miserable audio and corny music on background systems for so long, this was a treat. Yessir! New Yorkers are lucky people. They have everything in music. But you can't tell me there aren't plenty of other towns capable of supporting a high-fidelity eating emporium. P.S. The food was good too!

WAGNER LOHENGRIN

Chorus and orchestra of the Bayreuth Festival 1953 conducted by Joseph Keilberth. Lohengrin-Wolfgang Windgassen; Elsa-Eleanor Steber; Ortrud-Astrid Varnay; Telramund-Hermann Uhde; King Henry-Josef Greindl; Herald-Hans Braun. London LLA-16. RIAA curve. Price \$29.75.

This is the third version of "Lohengrin" to appear on LP and by all odds the best. The fact of primary importance is, of course, the authenticity of the performance. Since this "Lohengrin" was recorded at an actual concert of the 1953 Bayreuth Festival, there can be no question on this point. Naturally, mere authenticity in itself is not a guarantee of a good performance. So it is a happy thing to report that this is a good performance, and the recording has much to recommend itself over the competing versions. One thing you must accept from the start. This is a typical "actual concert" recording with all that this implies. Coughing, creaking of music stands and risers, shuffling of feet, all manner of extraneous noises are heard in quantity. Either you feel that these "noises" lend an "on hand atmosphere" to the recording (as I do) or they annoy you. It must be said that although there is a large quantity of noise, most of it is at such a level that it does not intrude upon the score.

The cast is well chosen. Eleanor Steber is in magnificent voice and her "Elsa" is a brilliant portrayal. Certainly this is one of Miss Steber's most effective roles. Astrid Varnay is perfect as Ortrud, a role in which she is familiar to most opera-goers. "Lohengrin" in this recording, Wolfgang Windgassen, is unknown to me. His performance indicates he is thoroughly familiar with the demands of the role. While he has a strong, robust voice, there was evidence of straining at times and at other times his tone was somewhat nasal. In spite of these minor shortcomings his is the best "Lohengrin" of the three available recordings. Mr. Windgassen lends an air of delicacy, a sensitive restraint that is refreshing in contrast to the usual German heavy-handedness. The other soloists are competent but not outstanding. Choral work is good and the famous "Wedding March" is well done.

Sound on this recording is generally good, but quite variable. Some parts are very clean and wide range, other parts sound constricted and compressed. String tone is good with some edginess, brasses come through best of all and percussion is weighty but at

(Continued on page 107)



Tape and wire recording are not as "modern" as many would like to think. The technique is almost sixty-six years old!

man has been intrigued with the sound of his own voice—and frustrated by his inability to reproduce it. History reports that as early as the 3rd Century B.C., Heron of Alexandria attempted to devise a machine that could talk or make animal sounds. However, it wasn't until the year 1791 A.D. that a "talking machine" was invented which could actually speak short sentences. These were man's early efforts to create or generate sound.

An amateur scientist in the year 1857

described an invention which he named the "Phonautograph." It was an ingenious device which traced a visible pattern of the sound of the human voice. It is almost frightening to think of the dazzling possibility that apparently had completely escaped the amateur scientist, the possibility of simply reversing the process and getting back the original sound which he had recorded. But, man was not to be easily deprived of this scientific advancement and within a few years of 1857 a number of people suggested the principle of the phonograph. One of them, l'Abbé Lenoir, even used the name "Phonograph" in a technical paper in 1877, the year Edison built his machine. Thus man, after so many thousands of years of anxiety, had discovered one mechanical means of recording and reproducing sounds and intelligence. This, as we know, was only the beginning.

In 1888 the magazine Electric World published an article by Oberlin Smith in which he suggested the use of a permanent-magnet recording technique. He proposed that a cord or silk thread be impregnated with steel dust or short clippings of fine steel wire. He also suggested, but thought impractical, a length of steel wire for magnetic recordings. Unfortunately, Mr. Smith never actually built a magnetic recording machine.

In the latter half of the 19th Century any boy who was interested in electricity considered telephone work to be the highest goal of attainment in an ambitious life. All young scientists dreamed of achieving their bit of success in that field. One such young man was Valdemar Poulsen, an unsuccess-

ful medical student in Denmark. The ambitious young Poulsen decided to leave medicine and turn to other pastures. In 1893, when he was 24, he obtained an appointment as a trouble-shooter for the Copenhagen Telephone Communication.

We will probably never know how Poulsen got his ideas for practical magnetic recording, but his ideas were quite unique and completely original. Many great inventions are challenged every year and the court records are filled with histories of litigations, claims and counter-claims. But no one other than Valdemar Poulsen has ever claimed to have invented the "Telegraphone," as his magnetic recording machine, the forerunner of present day tape recorders, was named in his original patent application in Denmark in 1898.


The "Telegraphone" won the Grand Prix in the 1900 Paris Exposition. It created a sensation. People came from everywhere to see it. Technical journals and contemporary newspapers were filled with stories, mentions, and references to it.

In the United States Poulsen was awarded patent number 661,619, dated November 13, 1900. Poulsen used a steel wire, 1/100th of an inch in diameter, drawn rapidly past magnetic cores surrounded by coils through which sound currents were passed. When the wire was again passed through similar magnetic cores, voltages were generated in their windings corresponding to the original currents. It worked extremely well, when judged by the standards then prevailing. However, frequency response was quite restricted and noise was high and dynamic recording range limited to approximately 20 decibels. According to reports of that day, everyone who heard it was enchanted by the naturalness of the sound reproduction! The "Telegraphone" operated with earphones, but everyone assumed that this difficulty would be overcome shortly. Actually it was not overcome until the development of electronic amplifiers, about 25 years later.

On the commercial side, Mr. Poulsen came to America seeking investment capital. In 1903 the American Telegraphone Company was formed with a capital stock of \$5,000,000 at a par value of \$10.00 a share. The company's objective was to manufacture "Telegraphones" for use as dictating machines and telephone recorders. The machine was capable of 1/2 hour recording time, with the steel wire moving at the extraordinarily high velocity of 7 ft. per second. Compared with early mechanical dictating machines, the longer playing time, the relatively low distortion, and the fact that the wire could be used over and over again made strong "selling" points.

It was terribly unfortunate for the company and its investors that certain of the operating features became strong "unselling" points. The speed at which the wire traveled in recording was just about as fast as was practical at that time, making it impossible to speed up the rewind time. This meant that before playing back a reel of magnetic wire which contained dictation, one had to wait. What was worse, threading a "Telegraphone" was much more involved than the simple procedure of placing a cylinder on a mechanical dictating machine. Eventually the

(Continued on page 124)

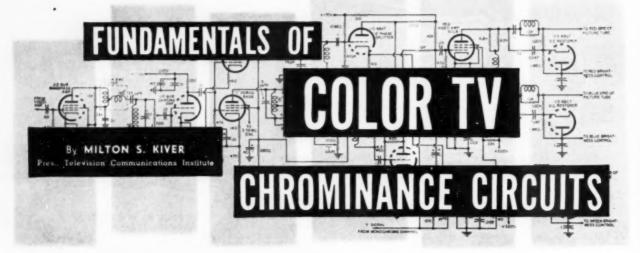

Part 5. Analysis of the chrominance circuits of three typical color TV receivers using the 3-gun color tube.

N the previous article we followed the full video signal (containing both black-and-white and color components) from the antenna to the video second detector. After detection, we had the 0 to 4 mc. black-and-white signal plus the color information. The latter was present as sidebands of the 3.58-mc. color subcarrier which meant that the color signal would require additional detection (or demodulation) before we could use it for application to the color picture tube. Thus, detection in a color receiver is a two-step process. First we remove the carrier which brought the full signal to the receiver. Then we must remove the color subcarrier so that the color video frequencies which it possesses may become available. It is important to keep this distinction in mind.

The black-and-white portion of the full signal is amplified by one or two video stages and then transferred to the matrix. While this is happening, the color subcarrier and its sidebands are diverted to the chrominance section of the receiver. See Fig. 1. This

section is concerned only with the color portion of the signal and it consists basically of a bandpass amplifier, the I and Q demodulators, and I and Q amplifiers and phase splitters. The output of the system is fed to the matrix network where, in combination with the monochrome or Y signal, we reobtain red, green, and blue voltages which are then applied to the proper control grids of the tri-gun color tube.


The complete circuit of the chrominance section of a television receiver is shown in Fig. 2. The incoming signal, which contains both chrominance and luminance components, is applied to the grid of the bandpass amplifier. This tube will permit the signals to pass at all times except during the horizontal retrace period (including the color burst) when the tube is keyed to cut-off by a negative voltage pulse obtained from a winding on the horizontal output transformer. The pulse is applied to the screen grid of the bandpass amplifier through a .01 µfd. condenser. The tube is keyed out during the color burst interval in order to avoid unbalance in the color background due to the d.c. restorers clamping on the color burst rather than on the tips of the sync pulses.

The control grid of the bandpass amplifier also operates in conjunction with a color killer stage. This latter stage (not shown in the diagram) biases the bandpass amplifier to cut-off when no color signal is being received. However, when a color signal is active, the color killer stage removes its bias and the bandpass amplifier is able to function normally. In this way we avoid having spurious signals pass through the color system when it is inactive and produce random colors on the screen.

A filter in the plate circuit of the bandpass amplifier has a bandwidth of approximately 2.4 to 5.0 mc. See Fig. 3. This enables the circuit to pass only that portion of the total signal containing the color information. The rest of the signal, containing only monochrome or luminance voltage, is sharply attenuated.

A chroma control terminates the filter and with it the set viewer can adjust the depth of saturation of the colors in the picture. The need for such adjustment may arise because of the level of the surrounding light in the room, because of the personal prefer-

Fig. 1. Block diagram of the chrominance section of a color television receiver. The exact circuitry varies from set to set.

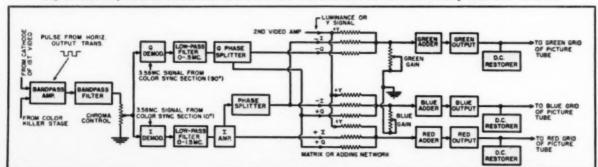

ence of the viewer, or because of variations in the color circuits of the receiver. Whatever the reason, the control is not a particularly critical one and it may be varied over a considerable range without overly distorting the picture as far as its tonal values are concerned.

From the chroma control, the signal is fed in equal measure to the control grids of the I and Q demodulators. At the same time both tubes receive, at their suppressor grids, a 3.58-mc. signal. The latter represents the missing color subcarrier and is needed in the demodulator to properly reproduce the original I and Q color video signals. The 3.58-mc. signal which the I demodulator tube receives is 90° out-of-phase with the 3.58-mc. voltage applied to the Q demodulator. This is required since the I and Q sidebands themselves are 90° out-of-phase with each other.

The detected Q signal appears at the plate of $V_{\rm ma}$ and is passed through a 0 to .5-mc. filter before being applied to a Q phase splitter. The latter stage then supplies negative (at its cathode) and positive (at its plate) Q signals necessary for the matrixing network into which the signals are fed.

The 3.58-mc. color subcarrier signal is not required beyond the demodulator and it is shunted away from the grid of the phase splitter by the series-resonant trap L_{20} , C_{210} .

In the I channel, the detected I signal is passed through a 0 to 1.5-mc. filter and then through an I amplifier and an I phase inverter before being applied to the same matrixing network. Positive I signals for the network are obtained at the plate of the I amplifier; negative I signals appear at the plate of the following phase inverter.

A .5 microsecond delay is designed into the I system and its purpose is to slow down all I signals so that they keep in step with the corresponding Q signals. The time it takes a signal to pass through a system is found to be inversely proportional to the bandpass of that system. That is, the narrower the bandpass, the longer it takes for signal passage. In a color receiver, the Q channel has the narrowest bandpass (0-.5 mc.) and its signals suffer the greatest amount of delay. The bandpass of the I channel extends from 0-1.5 mc. and so its signals are not slowed down as much as the O signal. Finally, the Y or monochrome channel has the widest bandpass (0-3.2 mc.) and its signals are delayed the least in

To insure that the I, Q, and Y signals arrive at the matrix at the same instant, it is necessary to artificially increase the delay time of the Y and I signals to that of the Q signal. In the Y channel, this is done by inserting a 1.0 microsecond delay line. In the I channel, the additional delay required is on the order of .5 microsecond. While no special delay line is employed in the I circuit of Fig. 2, the over-all characteristics of the system shown have been so fashioned that this added delay is actually present in distributed

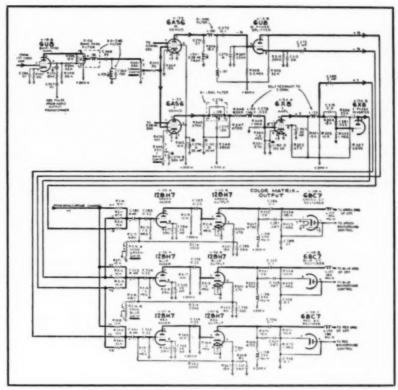


Fig. 2. Schematic diagram of the chrominance circuits of an RCA color TV receiver.

form. That is, each section of the circuitry contributes some share toward the delay and by the time the signal has arrived at the matrixing network, it has been moved back in step with the Q signal.

Note that the I channel has one amplifier stage more than the Q channel. This is due to the narrower bandpass of the Q channel. A narrower bandpass permits us to use higher load resist-

Editon's Note: Part 1 of this series, which appeared in the March, 1954 issue, explained color mixing and its application in color TV. Part 2, appearing in the April issue, described the NTSC color signal. The block diagram of a typical color TV receiver was described in the May issue. The June article in this series described the tuner, sound, and some of the video circuits of a color receiver. In view of the many requests received in this color to the video circuits of a color receiver.

the video circuits of a color receiver.

In view of the many requests received,
RADIO & TELEVISION NEWS will publish
this series in reprint form. The first three
parts are in a single unit (50 cents), the
balance will be reprinted in individual
parts at 20 cents each. For quantities of
50 or more, write for quotations. Address
your inquiries to RADIO & TELEVISION
NEWS Reprint Editor, 366 Madison Ave.,
N. Y. 17, N. Y.

ances, with a corresponding increase in gain. The difference in gain of the two demodulators is on the order of almost 7 to 1. For a 2-volt peak-to-peak signal input, the peak-to-peak value of the signal at the plate of the Q demodulator is 20 volts, while at the plate of the I demodulator it is only 3 volts.

The Matrix Section

The matrix or mixing section is the place where the I, Q, and Y signals

combine to reproduce the original red, green, and blue signal voltages. There are a variety of mixing networks possible, but the most economical and straightforward is the resistive network. See Figs. 2 and 4. From the NTSC specifications, the I and Q signals have the following composition:

I = -.27 (B-Y) + .74 (R-Y)Q = .41 (B-Y) + .48 (R-Y)

These represent two equations and if we solve them simultaneously for B-Y and R-Y we obtain:

B-Y = 1.72Q - 1.11Ior B = Y + 1.72Q - 1.11Iand R-Y = .62Q + .96Ior R = Y + .62Q + .96I

Now, what do these equations tell us? They reveal that if we take 1 voit of signal from the Y channel, and 1.72 volts of positive Q voltage from the Q channel, and 1.11 volts of negative I voltage from the I channel, we obtain 1 volt of blue signal. Of course, we are not restricted to voltages this small; we may use much larger voltages, as long as we maintain the same relative relationship between the I, Q, and Y voltages taken from these three channels feeding into the matrix network.

The red signal is obtained by using different proportions (and polarities) of the Y, I, and Q voltages than were used for blue. This is indicated by the last equation and the red signal is then dealt with separately.

Still missing is a green voltage and this can be obtained from still another equation which is also derivable from the NTSC specifications. That is:

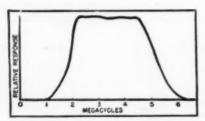


Fig. 3. Response of the bandpass filter in the plate circuit of the bandpass amplifier of the circuit in Fig. 2.

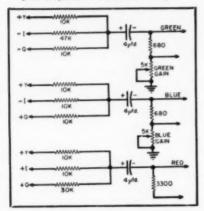


Fig. 4. The matrix network for combining the Y. I. and Q signals in the proper proportions to give red. green. and blue signals in circuit of Fig. 2.

(G-Y) = -.51 (R-Y) - .19 (B-Y) and from this, by a little mathematical manipulation.

$$G - Y = -0.64Q - 0.28I$$

or

$$G = Y - .64Q - .28I$$

Hence, within the same matrix, we can obtain the desired green signal by combining 1 volt of Y signal with .64 volt of negative Q signal and .28 volt of negative I signal.

The foregoing equations make it evident why a resistive matrix network can work and also why positive and negative I and Q voltages are required,

whereas from the Y channel only a single positive signal is needed.

Let us return now to Fig. 2 and briefly check the red, green, and blue amplifiers to make certain that the voltages they receive at least conform in polarity to the voltages indicated in these equations.

The green amplifier (or "adder" as it is labeled on the diagram) receives a Y voltage, a negative I voltage, and a negative Q voltage. The circuit, of course, is so designed that these signals are present in the ratio of 1 to 28 to .64.

The blue amplifier receives a Y voltage, a negative I voltage, and a positive Q voltage. Finally, the red amplifier receives a Y voltage, a positive I voltage, and a positive Q voltage.

Each of these voltages is passed through two video voltage amplifiers and then applied to its respective control grid in the tri-gun picture tube. Bandpass of each system is on the order of 3.2 mc. Over-all gain controls for the green and blue channels are provided to permit the gains of these sections to be adjusted relative to the red channel. In the initial tri-gun picture tubes that were made, the efficiency of the red phosphor was lower than the efficiencies of the green and blue phosphors. To compensate for this, more drive was required at the red control grid, or what is the same thing, less drive for the green and blue grids. Adjustment of the two gain controls served to satisfy this condition. A d.c. restorer is included in each path to bring each color signal to the proper level before it is applied to the picture tube

The chrominance channel of another color television receiver is shown in Fig. 5. The complete signal is brought to the grid of the bandpass amplifier from the master contrast control. The tube admits all of the signal except the color burst because during this interval it is keyed off by a negative pulse applied to the screen grid.

In the output circuit of the bandpass amplifier there is a 2.1 to 4.2 mc. band-

pass filter terminating in a 500-ohm chroma control ("color intensity control"). As before, the chroma control governs the amount of color signal reaching the rest of the chrominance section and hence it regulates the intensity or saturation of the colors viewed on the picture tube screen. The color signal receives an additional stage of amplification beyond the chroma control and then it is fed in equal measure to both the I and Q demodulators.


The demodulators in this system are also the recipients of two additional voltages. One voltage, in the form of a negative biasing voltage, is obtained from a color killer tube. When a color signal is being received, this bias voltage drops to zero and both demodulators conduct. On the other hand, when no color signal (and hence, no color burst) is present, the negative voltage from the color killer tube is high enough to cut both demodulators off. The over-all effect, then, is the same in this system as in the previous one, although the approach is slightly different.


The second voltage applied to the I and Q demodulators is provided by a 3.58-mc. generating section. This is the missing color subcarrier and is applied in equal measure but with a 90° phase difference to each demodulator. The tubes then mix this signal with the incoming color sidebands to provide the detected I and Q color signals at the output.

In the *I* channel, there is a 0-1.5 mc. low-pass filter, an amplifier and a phase splitter. Also, sufficient delay is incorporated in this circuit to force the *I* signal components to keep in step with the *Q* signal components. Positive and negative *I* signal voltages are available at the plate and cathode terminals, respectively, of the phase splitter for use in the matrix network.

The Q channel is somewhat less extensive, containing only a phase splitter and a 0-.5 mc. low-pass filter. The output from this section, too, is fed to (Continued on page 75)

Fig. 5. Schematic diagram of a chrominance section with a chroma amplifier stage.

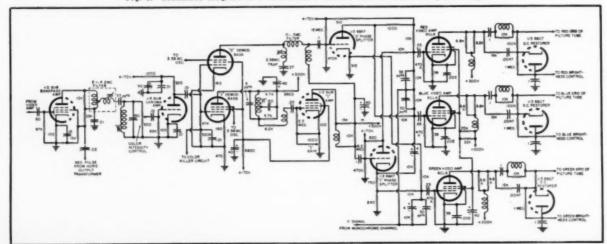

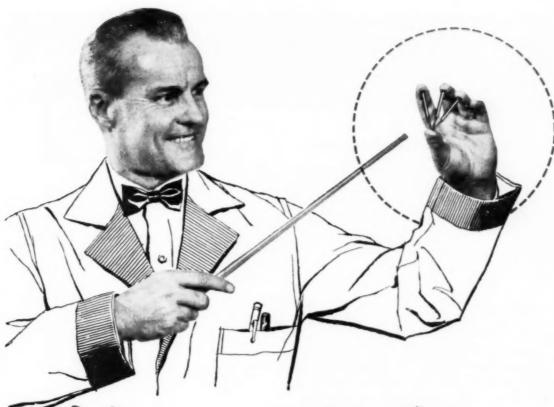

When you get to the core...

DELCO RADIO MAKES ITS OWN OF POWDERED IRON FOR HIGH-QUALITY PERMEABILITY-TUNED COILS!



FINAL TEST ON IRON CORE ASSEMBLIES AT DELCO RADIO. Here, all iron core assemblies are carefully checked for permeability and separated into very narrow tolerance permeability groups. To insure quality performance, Delco Radio exercises rigid control over the components used for both original equipment and service parts in its auto radios.

For example, the powdered-iron cores of Delco Radio's RF, IF, or tuning coil assemblies are made to exacting specifications at the Delco Radio plant. Powdered iron is treated with a binding agent and then compressed into shape by a special machine. Skilled craftsmen attach the connector, and the head end of the core is notched for the tuning tool blade. The core is now ready to be inspected and sent to the tuner department.

This careful manufacturing results in greater customer satisfaction—always. Delco Radio service parts, made by the world's largest manufacturer of auto radios, are available through your UMS Delco Electronic Parts Distributors.

DELCO RADIO

DIVISION, GENERAL MOTORS CORPORATION, KOKOMO, INDIANA

DISTRIBUTED BY ELECTRONICS WHOLESALERS EVERYWHERE

A GENERAL MOTORS PRODUCT

International SHORT-WAVE

Compiled by KENNETH R. BOORD

HE Oslo Students Radio Club, University of Blinderen, Blinderen, Oslo, Norway, uses 7.210, 11.850. The two transmitters are SBR400:2 type and tubes are S.F.R.P. 500 in push-pull. Input of the final amplifiers is 800 watts. Plans to use half-wave horizontal dipole on 7.210 and halfwave vertical on 11.850. Has no towers, but has antennas atop the Physical Institute of Oslo University, a building about 90 feet high. Has no directional antenna system. Transmitters and studios are at Blinderen, a suburb 5 miles north of Oslo's center. The station has no interval signal, but at the beginning and end of transmissions a recording of a Scandinavian student song (by women's choir) is played. Announces in English once or twice during each transmission, "This is the Oslo Student Radio Station." Plans have been made to build better antennas. Began broadcasting Aug. 24, 1950. Verifies listeners' reports by card, letter; would prefer reports in English, French, German, or a Scandinavian language. Transmissions are bi-annual and take place only Aug. 30-Sept. 7 inclusive at 1705-1735 (sometimes 1715-1745). Next transmission will be August-September of this year. Transmissions are always in connection with Students Week, and programs are mostly glimpses of student life in Oslo. The participants, like the technicians, are all active students. (URDXC) Be on the lookout for this one on 7.210, 11.850, Aug. 30-Sept. 7, 1954, around 1705-1745; otherwise, you may have to wait two years for another chance to log and/or verify it!

Radio Club Notes

Spain—Luis Diez Alonso (EA-1-12-U), Santander, Spain, advises that the second International Technical Conference of Radio Amateurs will be held in Santander, Aug. 16-22. The conference has been organized by the Spanish Union of Radio Amateurs under the sponsorship of the Mendenez Pelayo International University, Santander. The first such event was held in 1952.

USA-The Newark News Radio Club has chosen these officers for the coming year-Irving R. Potts, president; Walter L. Townley, treasurer; Albert J. Sauerbier, executive secretary; Benjamin Feinstein, assistant executive secretary; G. Dudley Clarke, Canadian vice-president, and Charles E. McCormick, Norman L. Maguire, Roger Legge, Abe Cohen, Charles S. Sutton, Donald Hill, Robert W. Gorsuch, Eugene S. Allen, Charles P. Atherton, William N. Roemer, Ben Adams, Jr., Robert W. Botzum, vice-presidents. The club recently held its 26th Anniversary Dinner at Eatontown, N. J.

Around the World

Anglo-Egyptian Sudan—Radio Omdurman now uses new 4.975, 7.5 kw., and 6.437, 700 watts; no change in schedule; has no crystal control which may account for varying frequencies reported (to around 4.995A at times). (Scheiner, N. J.)

Angola—Radio Diamang, 9.340, Dundo, noted 1305 with popular musicals, vocals in English by man; at 1316 identified in Portuguese and continued with piano music; wiped out 1328A by

CWQRM. (Pearce, England) Luanda, 11.862, noted 1400-1730 when closes with "A Portuguesa." (Rowell, Minn.)

Austria—Lately, Radio Oesterreich, Vienna, has been using 9.490A at times instead of 9.665 around 0300-0400 and other times. Noted some days on 9.490A around 1200. (Pearce, England)

Azores—Ponta Delgada has been noted by Pearce, England, and Niblack, Ind., on new 11.925A at 1500-1600, but since this was compiled may have gone on summer schedule of 1400-1500.

Balearic Islands—Radio Menorca, 7.405 tuned 0925 with classical music and songs, man and woman announcers in Spanish, went off with Spanish National Anthem 1000; also tuned 1455 when was good level with light musicals. (Pearce, England)

Belgian Congo—OTM, 6.295, Leopoldville, noted 1830 with relay from ORU, Brussels, to 1846, followed by announcement for Radio Congo Belge, then left air. (Ferguson, N. C.) Noted with news in French, Flemish 0005-0020. (Morris, O.)

Belgium—ORU4, 15.335, Brussels, noted from 1200 in French, Dutch, excellent level. (Morris, O.; Miller, Ga.) ORU has made seasonal change from 9.767 to 11.850 for broadcast to North America 1900-2200, still relayed by OTC, Belgian Congo, 9.655. (Foster, III.)

Bruzil—ZYK3, Recife, signs off in English after Spanish program around 2120 on 11.825A; has news in Portuguese just prior to closedown. (Bulmur, Brt. Columbia) Lately, Radio Record, PRB22, Sao Paulo, has been using 11.960A instead of 9.505. (Saylor, Va.; ISWC, London) Sao Paulo, 15.135, noted 1830. (Rowell, Minn.) Radio Tamoio, 9.610, noted strong level 2000 in Portuguese. (Foster, Ill.) PSL heard on measured 7.940 in Portuguese session 1730-1800 closedown. (Ferguson, N. C.)

British Honduras—ZIK2, 3.300, Belize, noted 2130-2230 closedown with songs and announcements in English. (Reidler, Pa.; Dexter, Iowa) Some days heard as late at 2353 closedown.

(Continued on page 93)

Short-wave listeners will have an opportunity August 30-September 7 to try to log the Oalo Students Radio Club. University of Blinderen. Blinderen. Oslo. Norway. around 1705-1745 EST on 7.210 and 11.50. Broadcasts are made only bi-annually during the observance of "Students Week." It is considered a very choice contact.



(Note: Unless otherwise indicated, all time is expressed in American EST: add 5 hours for GCT. "News" refers to newscasts in the English language. In order to avoid confusion, the 24 hour clock has been used in designating the times of broadcasts. The hours from midnight until moon are shown as 0000 to 1290 while from 1 p.m. to midnight are shown as 1300 to 2400.)

The symbol "V" following a listed frequency indicates "varying." The station may operate either above or below the frequency given. "A" means frequency is approximate.



"He says he's heading for WALTER ASHE where the "Surprise" Trade-Ins come from"

AMATEUR GEAR



TRANS-CITER Not \$177.00



NEW JOHNSON VIKING RANGER TRANSMITTER-EXCITER KIT. 75 watts input on CW, 65 watts on phone. Bandswitching 160 through 10 maters. Selfcontained VFO, modulator and power supply. TVI suppressed. Less tubes. Model 240-161. Net \$179.30



HALLICRAFTERS SX-71 Less speaker. Net \$249.95 Matching speaker. Net \$19.95 Most economy-minded folks will make a beeline for a bargain. And there's no better bargain anywhere than the money saving kind made possible by our "Surprise" Trade-In Allowance on your used test and communication equipment. Get your trade-in deal working today! Wire, write, phone or use the handy coupon below.

TEST EQUIPMENT-

The Perfect Pair for FM-AM-TV Servicing

PRECISION APPARATUS Multi-Band Signal and Marker Generator. 88-240 MC range. Model E-200C. Net \$76.93






PRECISION APPARATUS Wide Range Sweep Signal Generator. 2 to 480 MC range. Model E-400. Net \$136.95

All prices f. o. b. St. Louis . Phone CHestnut 1-1125

Walter Ashe
RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.

	8-7-54
WALTER ASHE RADIO COMPANY	
1125 Pine Street, St. Louis 1, Missouri	
Rush "Surprise" Trade-In Offer on my	
for	elecal)
(show make and model number of new equipment de	isked)
Rush copy of latest Catalog.	
Name	
Address	

Send for your copy today

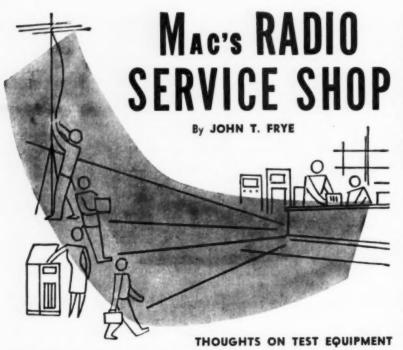

MAC had come down to his service shop this warm July evening to try out some new test records and a test tape he had just received. While he was busy running the signal-tonoise checking portion of the test tape through the recorder, he heard the front door open and bang shut.

"Ha!" came the accusing voice of Barney, his assistant, as the youth strode through the door of the service department. "You trying to put something over on me? What's the idea of sneaking down here after hours? What're you holding out on me?"

"Now calm yourself, Buster, before you melt a connection," Mac said soothingly. "It just happened these records and tapes came in late this afternoon after you had gone home, and I was eager to try them out at a time when I would not be interrupted—I hoped," he added pointedly.

"You could have let me know," Barney grumbled. "I saw a weather forecast for heavy thunderstorms for tonight, and I came down to be sure I had pulled the master bench switch. Gosh," he broke off, as his eye caught sight of a stack of red, yellow, green, and blue, 5- and 7-inch plastic reels, on two of which were wound rolls of green and blue plastic tape, "are those the test tapes?"

"Nope. Those are just some of the new colored reels and tapes recently put on the market. I'm going to try and work out a color-code scheme for filing our recordings that will let us know at a glance if a particular reel of tape is important not-to-be-erased material, is recorded from the microphone or by direct pickup, or if it contains blank tape, etc. Since we have five colors of reels, including the transparent, and three colors of tape, count-

ing the conventional brown, the possibilities are considerable, and I want to work out a system that is simple and easy to remember but that will allow us to file our tapes under many color-keyed listings.

"The test tape is on this five-inch reel," he said. "It and those test records over there are the ones we read about in that article in the May issue of RADIO & TELEVISION NEWS as being released by the Dubbings Company."

"Say, you're really becoming pretty loopy about this tape business, aren't you?" Barney asked guizzically.

"Couldn't you change 'loopy' to 'interested'?" Mac asked. "T'll confess I'm greatly intrigued by the possibilities of tape recording, especially now that it is possible to record light images and other information on tape as well as sound. I keep thinking that possibly there is something here that will solve a problem that is beginning to be a big one."

"What's your problem?" Barney wanted to know.

"It's not just my problem; it's the growing problem of every service technician. In brief, it seems to me that the test equipment situation is getting somewhat out of hand. We've reached the point where our service instruments are more expensive, more complicated, more subject to trouble, and harder to learn to use than the apparatus upon which we work. If things keep on at the present rate, it does not take too great a stretch of the imagination to picture a time soon when the technician will be so busy studying and selecting new service equipment, learning how to use it, and keeping it in repair that he will not have any time left over at all for doing service work."

Barney grinned broadly at this pic-

ture. "Guess it is not too far-fetched at that," he conceded. "The other day I counted up a total of sixty some tubes that are in use in just our test equipment. Sixty tubes and their associated circuits represent a lot of room for trouble. Much of that equipment, too, must or should be constantly checked to be certain it is operating as it ought to. As a 'ferinstance,' we do not depend upon the calibration of the sweep generator but use our marker generator to indicate exact frequencies; then we do not rely on the accuracy of the marker generator but check it against a crystal oscillator; and finally, we do not take the crystal oscillator frequency for granted but check it against WWV. Sounds kind of wacky, doesn't it?"

"Sure does," Mac agreed, "and that's only one example. The increasing number of articles we see in service magazines on how to check, how to maintain, and how to use the many, many service instruments considered essential for present-day radio and TV servicing is a key to how serious this state of affairs is becoming. You've got to keep in mind that all thought and energy expended on service instruments is so much lost motion as far as direct addition to your income is concerned. When you are studying and working on service instruments, you could be working on a radio or TV set and being paid for doing so."

"But if you really know your service instruments and if you keep them in good shape, you can do more and faster service work," Barney argued.

"I'm not disputing that," Mac explained; "but what I am trying to say is that anything that takes your attention away from the essential job of repairing sets cuts into your income. Service technicians are constantly being told they should become better businessmen, which is another way of saying they should evaluate all their procedures strictly according to whether or not these activities in-crease their net income. Up to a point, time and money spent on service equipment will still yield an increased income in spite of the fact that the money is subtracted and the time is diverted from the service business proper. Eventually, though, the law of diminishing returns whittles down this increase until it no longer exists. I'm thinking that point is not too far

"What can be done about it?"

"Candidly, I'm not sure anything can; but I've some ideas I'd like to see tried. Manufacturers could help a lot if they would prepare service instructions with an eye to the equipment found on a typical service bench rather than the instruments on hand in their own engineering laboratories. I don't mean they should try to write up this service data so that everything can be done with a v.o.m.; but at the same time I feel that service instructions calling for special high-gain, broadband oscilloscopes, sound and video

(Continued on page 103)



Right for You and Your Customers

Because of excellent drift characteristics and extremely accurate taper curves, Mallory Midgetrols give your customers the set performance they want—long and trouble-free. Mallory Midgetrols are engineered for precision performance in both TV and radio sets despite variations in temperature and humidity.

Because of simplified design and construction, Mallory Midgetrols are easy to install quickly. Round, tubular shafts can be cut fast, accurately... are easily adapted for split-knurl, flatted, or set screw type knobs. And you can attach AC switches without control disassembly.

Because from every angle—quality, price, performance—Mallory Midgetrols are right for you... and your customers. Use them always.

Look at ALL 3 Features of this Mallory Control "Deal"

(1) With the special Mallory Control Kit you get a selection of controls and switches that give coverage of more than 50 radio and TV set models. (2) The Controls are selected on the basis of set popularity in your area. (3) You get FREE a metal storage cabinet when you buy this deal.

Ask your Mallory Distributor or write P. O.
Box 1558, Indianapolis, Indiana.



MALLORY

CAPACITORS . CONTROLS . VIBRATORS . SWITCHES . RESISTORS RECTIFIERS . POWER SUPPLIES . CONVERTERS . MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA



ARTSNY STORY

THE Associated Radio Servicemen of New York, Inc. (ARSNY) was founded in 1947 primarily to fight a bill in-troduced into the New York City Council calling for the licensing of radio service technicians. The first hectic meetings of the group provided a membership of approximately threehundred technicians. An organization was formed and immediately requested and received free radio time to answer the charges of incompetence and fraud hurled at the legitimate radio service technicians by public figures. ARSNY was so effective in combating this bad publicity that the bill was shelved, and the hard-working legitimate service technicians in New York City received recognition. After this initial success. the membership realized that they had created a potent organization for promoting their mutual welfare, and they decided to embark on a permanent program of mutual aid. This included an apprenticeship program whereby students worked with ARSNY members to receive practical experience so as to assure a steady supply of competent service technicians. Also, frequent lectures on servicing were arranged and business-building methods were discussed

The introduction of commercial television brought many new people into the trade and increased the demands upon the technician's knowledge. What had been a more or less stable business suddenly expanded to huge proportions. The rapid sale of a high-priced commodity, serviceable by a limited number of available technicians, offered a tremendous profit potential to those in the field. To meet this challenge, the association (now ARTSNY) organized regular technical lectures to help train its members in TV circuitry and fast methods of servicing. But, the needs of the membership became more and more complicated as business grew and the individual members found it necessary to specialize in either the business or technical aspects of servicing. To solve the problem of how to serve each member more effectively. ARTSNY divided its total membership into two chapters-a business chapter and a technical chapter.

Each of these chapters is headed by a chairman who is also a vice-president of ARTSNY. Each chapter has its own roster of officers and holds its own meetings at the common clubhouse. The business chapter holds meetings the second and fourth Thursdays of each month, at which time there are talks on business methods, advertising, licensing, and other topics of interest to the men who operate their own service businesses. The technical chapter, which meets on the first and third

Thursdays of each month, presents technical lectures by field service engineers of TV receiver manufacturers and other well-known speakers. The attendance at these meetings is limited to active technicians but, of course, many service shop operators also attend the technical meetings since they, too, are service technicians, and vice versa.

In addition to the preceding program, ARTSNY sponsors a TV clinic at its clubhouse. Here, at its workbench every Wednesday evening, members bring in their problem chassis (those sets which have proven particularly difficult to service), and in the common give-and-take with other technicians, under the supervision of a field service engineer, these sets are serviced, and valuable training is obtained by all concerned.

At the present stage of the organization, ARTSNY has about five-hundred members, approximately one-half of whom own their own businesses. To become a member, a technician must have at least four years of full-time practical experience in the maintenance and repair of radio and television equipment, as well as pass a practical and theoretical examination on servicing. Also, all members must subscribe to the code of ethics of ARTSNY.

Recently, the National Broadcasting Company began a publicity program to acquaint the people of New York City with the advantages of using legitimate service technicians for maintaining their radios and television sets. To this end, WNBC, the radio outlet and WNBT, the television station, are presenting spot announcements valued at approximately \$60,000 a month, informing their listeners and viewers of the existence of ARTSNY, and the advantages to be gained by using ARTSNY members. During these announcements, a telephone number is given for ARTSNY and, at the clubhouse, a full-time paid employee handles all calls for service and routes each request to the ARTSNY member closest to the potential customer. The association also publishes a monthly bulletin, "ARTSNY News."

Realizing that a good public relations program will go far toward obtaining acceptance of its services by the public, ARTSNY has sponsored many helpful causes. One is a program to repair, at no charge, defective TV sets donated by the public for hospitals and institutions. The association also has a grievance committee to expedite complaints by customers against service technicians. All complaints are investigated and, if fraud is suspected, ARTSNY assists in pressing charges.

-30-

RADIO & TELEVISION NEWS



Buyers are getting wiser. The quality of their TV reception is your responsibility ... and they'll hold you to it! For your protection, sell and install WALSCO, the finest antennas

ever built for VHF and UHF.

WALSCO IMPERIAL CONICAL (all-channel VHF)

Featuring the new, exclusive "Barrier Disc" Insulator to prevent shorts and maintain lasting high gain performance anywhere. Designed for color as well as black and white. Not affected by dirt, moisture, salt ... will not rust. Stainless steel hardware prevents corrosion losses permanently. Pre-assembled . . . guaranteed 3 years! Single Bay . . . only \$9.95 List. Also available in Dual and 4 Bay Stacks.

WALSCO CORNER REFLECTOR (UHF)

No other UHF antenna so effectively combines all three . . . (1) extra high gain: (2) all-channel reception; (3) sharp vertical and horizontal directivity. Features the hollow, unbreakable X-77 Insulator . . silicone treated to shed dirt and moisture . . . not affected by extreme heat, cold or wind. Single Bay ... \$10.95 List. Also available in 2 and 4 Bay Stacks.

TRODIES EDRPORATION

3602 Crenshaw Boulevard, Los Angeles 36, California


Branch: 315 West Walton, Chicago, Illinois

Overseas Distributor: Ad Auriema, Inc., 89 Broad St., New York 4, N.Y. Canadian Factory Distributor: Atlas Radio Corp., Ltd., 560 King St. West, Toronto 2-8.



you're on easy street with PHOTOFACT

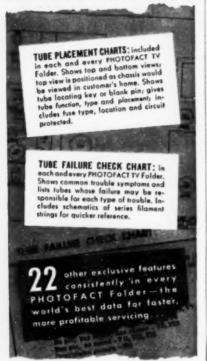TUBE PLACEMENT and TUBE FAILURE CHECK CHARTS



NOW! GET THE PROOF FOR YOURSELF!

FREE

We'll send you a Free Photofact TV Folder just ask us for it!

Learn for yourself how PHOTOFACT pays for itself by earning bigger profits for you! We'll send you the proof—a FREE specimen PHOTOFACT TV Folder that shows all the features found consistently and exclusively ONLY in PHOTOFACT. Send for your FREE specimen TV Folder now. Examine it. Compare it. You'll see why PHOTOFACT belongs in your shop! And you'll want to ask your parts distributor about the pay-as-you-carn-plan. Only \$25 down brings you the entire PHOTOFACT Library. Write for FREE specimen TV Folder—learn now how to earn more!

HOWARD W. SAMS & CO., INC. 2203 E. 46th St., Indianapolis 5, Ind.

HOWARD W. SAMS & CO., INC.

SAVE THAT RECTIFIER

By JOHN P. FATH

Don't throw away those 27 ½ volt 35Z5GT's! They can be used in this low-voltage a.c.-d.c. power supply.

A LOW-VOLTAGE a.c.-d.c. power supply is a very useful piece of equipment to have around the shack whether you're a radio and TV technician, home experimenter, or a ham. Despite the ever-faithful "junk box" which all shacks possess there is always the cost of the rectifier tube to take a small nip out of the wallet. If you should choose a rectifier which requires a series heater dropping resistor—you then have another addition to the initial cost. Should you choose the 117-volt heater type you can expect an early replacement since these tubes are notorious for their heater burnout problems. Why buy a rectifier for these power supplies when in all likelihood you've been throwing away perfectly good rectifiers? Use "27½" Z5GT rectifiers in your supply.

rectifiers in your supply.

It is well known that the major cause of rectifier failure in a.e.-d.c. radios using the 35Z5GT is a burnout of the pilot lamp section of the heater. A quick look at a tube manual will show that approximately four-fifths of the heater is still good and will heat the eathode sufficiently for completely satisfactory

service.

The heater is divided into the panel lamp section, which is rated at 7½ volts with no panel lamp shunting it, and the main section rated at 27½ volts (35 volts minus 7½ volts). It is an easy task then to build a half-wave power supply using a series-dropping resistor to obtain the required 27½ volts at 0.15 ampere. The writer has employed such an arrangement in an "intercom" unit using a 50L6GT and a 12SQ7GT in series with the "27½" Z5GT and a 160-ohm line cord. The unit has been in service for seven years now and has never had a tube replacement.

After saving four of these "lame" 35Z5GT tubes it becomes unnecessary to obtain a series current-limiting resistor because it is a simple matter to wire the tube heaters in series to obtain full use of the line voltage and also to gain the advantages of bridge rectification. It

is possible to obtain the full current capability of the 35Z5GT in these circuits, i.e., 100 milliamperes. The fact that the cathode is not up to design temperature is of no consequence as the copious supply and zero cost will completely overshadow the replacement problem.

problem.


The circuit of Fig. 1 shows a bridge rectifier which provides either positive or negative voltage with respect to ground by the simple expedient of connecting the "minus" terminal to the ground post for the former polarity or connecting the "plus" terminal to the ground post for the latter polarity. The circuit can be "dressed up" by adding a 117-volt pilot lamp, a fuse, and a "plate" switch, as indicated by the dotted lines. Note that the "plate" switch is on the load side of the power supply instead of directly in the plate lead of the rectifiers. This is recommended because of the large value of the input condenser. The instantaneous impedance of the filter system is zero ohms at the instant that the power is applied to the plates (assuming the cathodes are already up to operating temperature) causing excessive current to flow through the rectifiers and seriously damaging the cathodes. By placing this switch in the load side of the power supply we overcome this problem since the filter condensers are fully charged at all times. Without the "plate" switch, the aforementioned condition never obtains as the cathodes come up to temperature so slowly that the rectifier internal resistance limits this "surge" current to low values until the condensers are fully charged and the cathodes are up to temperature.

temperature.

When operating the power supply with one side of the output grounded it is important to remember that the chassis can be operating at or near line potential through the rectifiers and therefore constitutes a safety hazard unless a line-isolating transformer is employed by the operator.

-30-

Fig. 1. Schematic of bridge rectifier using "lame" 35Z5GT rectifiers. See text.

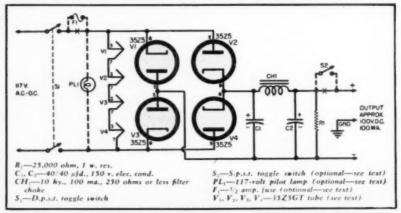




RECEIVERS, etc.

- Save by ordering direct from
- 2 All high quality standard brand components
- 3 increased knowledge through actual construction
- Sound engineering insures excellent performance.
- Kit construction is fascinating and enjoyable.

Heathkit MODEL 0-9 OSCILLOSCOPE KIT

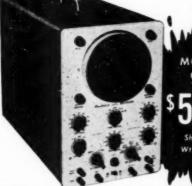

MODEL 0.0

New features unbeard of in a kit oscilloscope have been added to the already popular Heathkit series. All top quality components are used including a brand new RCA 5UP1 CRT. Ten other first line tubes complete the lineup. Voltage regulation provides a rock steady pattern regardless of normal line voltage variations. A built-in blanking amplifier eliminates the retrace line entirely. Other important advantages are a phasing control, Z axis input, direct connections to the deflection plates, I volt peak-to-peak calibration voltage and a calibrated grid screen.

Wiring is simplified by the use of the harness technique which also results in a neat professional appearance. Extremely wide vertical bandwidth allows accurate reproduction of even a 509 KC Square wave. Excellent focusing characteristics are made possible by the use of the new RCA 5UP1 CRT and a spot shape control. One of the most versatile of test instruments, the Heathkit 0-9 Oscilloscope will be invaluable in the gadio and TV service shop, as a work project in schools and for all types of circuit investigation work in the laboratory. Its new features make Model 0-9 comparable in every way to many commercially built oscilloscopes selling for as much as \$400. Don't pass up this opportunity to add a really fine instrument to your service or experimental lab.

Heathkit VOLTAGE CALIBRATOR KIT

The use of a Voltage Calibrator will greatly increase oscilloscope usefulness. Provides a convenient method of making peak to peak voltage measurements by establishing a relationship between the unknown wave shape and the Voltage Calibrator. Voltage ranges .01–100 volts peak to peak. The Voltage Calibrator features direct reading scales and a regulated power supply system.



\$7750

Shipping Wt. 4 lbs.

Heathkit ELECTRONIC SWITCH KIT

The Heathkit Electronic Switch Kit The Heathkit Electronic Switch Kit will further extend acope usefulness by permitting simultaneous observation of two individually controlled traces. Continuously variable switching rates 10 cps to 2,000 cps in three ranges. Will also serve as a square wave generator over the range of switching frequencies.

MODEL

5-2

5-3

50

Shipping Wr. 11 lbs.





Heathkit VACUUM TUBE VOLTMETER

The beautiful new 1953 Heathkit Model V-6 VTVM, the world's most popular kit The beautiful new 1953 Heathkit Model V-6 VTVM, the world's most popular kit instrument, now offers many outstanding new features in addition to retaining all of the refinements developed and proven through the production of over 70,000 VTVM kits. The Heathkit VTVM now features extended voltage ranges with 59% greater coverage on the DC range. New 1½ volt low scale provides well over 2½ inches of scale length per volt permitting faster measurements with greater accuracy. AC and DC ranges are $0-1.5 \div 1-5 \div 0-150 \div 500-1500$ volts (1,000 volts maximum on AC). Ohmmeter ranges are X1, X10, X100, X1,000, X10K, X100K X10K meg. Measures .1 ohm to 1,000 megohms. Other features are db scale, center scale zero adjust and polarity reversal switch. High 11 megohm input resistance virtually eliminates circuit loading.

The low anti-inflation price of this tremendously popular kit includes all tubes, necessary constructional material, test leads and the construction manual.





Heathkit AC VACUUM TUBE VOLTMETER KIT

MODEL AV-2 \$2950

Shipping Wt. 5 lbs. A new amplifier type AC VTVM that makes possible those sentitive measurements so essential in laboratory or audio work. Ten voltage ranges covering from .01 KMS full scale to 390 volts RMS full scale. Input impedance I megohm with frequency response 20-50,000 cycles. Ten DB ranges from —52 to +52 DB. Four diodes in meter bridge circuit for maximum linearity.



Heathkit HANDITESTER KIT

MODEL M-1 \$1450 Shipping

Wt. 3 lbs.

The ever popular Handitester is now supplied with a Simpson 400 microampere meter movement. Provides AC and DC voltage ranges 0-10-30-300-1,000-5,000 volts. Ohmmeter ranges 0-3,000 and 0-300,000 ohms. DC current measurements 0-10 and 0-100 milliamperes. A completely self contained portable instrument.

HEATH COMPANY • Benton Harbor 15, Mich.

HEATHKITS for the ENGINEER

Heathkit VISUAL AURAL SIGNAL TRACER KIT



MODEL T-3 S

Shipping

Designed especially for service applications in AM-SW-FM-TV repair work. If and audio two channel input. More than adequate sensitivity—new noise locator circuit—calibrated wattmeter—substitution speaker—visual signal indication. Can be used with scope and VTVM, checks phono cartridges, phono mechanisms, microphones, tuners, etc. Let the Heathkit Visual Aural Signal Tracer help you.

Heathkit CONDENSER CHECKER KIT

An instrument designed solely for its particular job. Not a "sideline" or a multiple function instrument. Measures value and quality of unknown condensers and resistors. Capacity range .00001 mfd to 1.000 mfd. Resistance range 100 ohms to 5 megohms. Sensitive electron beam indicator—five polarizing test voltages—safety spring retails and the same range and sensitive. An amazingly accurate instrument at this low price.



\$1950 Shipping

Heathkit RESISTANCE SUBSTITUTION

MODEL RS-1

Choice of 36 switch selected resistance values 15 ohms to 10 megohms. All stand-ard RTMA 1 watt 0% resistors. Buy those lab and service applications.

BOX KIT

Ship. Wt. \$550

NEW Heathkit 20,000 OHMS PER VOLT

MULTIMETER KIT

Here is the solution to all service problems requiring a portable measuring device of high accuracy, 20,000 ohms/volt sensitivity on DC and 5000 ohms/volt on AC. Full scale voltage ranges of 1.5, 5, 50, 150, 500, 1500 and 5000. DC current ranges of 150 microamperes; 15, 150 and 500 milliamperes; and 15 amperes. Resistances are measured from .2 ohms to 20 megohms in 3 ranges and decibels from -10 to +65 db.

Model MM-1 uses standard commercially available batteries and is not affected by strong RF fields as encountered in and near transmitting equipment. 1% precision resistors on a very easily wired ring type range switch and a highly

accurate Simpson 50 microampere meter fully qualifies the Heathkit Multi-meter for close tolerance laboratory and service work. The meter movement is placed in a recessed position for maximum non-glare readability. The kit includes the attractive black bakelite cabinet, 2 color meter scales,

Ship. Wt. 6 lbs. test leads, batteries and all other necessary components. Overall cabinet size is 51/2



MODEL MM-1 \$2650

wide x 4" deep x 735" high,

Heathkit SIGNAL GENERATOR KIT



Ship. Wt. 8 lbs.

The standard service instru-ment for align-ment work. .1 IC Callyst from 160 KC to 110

Calibrated harmonics up to C. Internal (400 CPS) and 220 MC external modulation. Pre-calibrat ed coils for all 5 bands. Good sta-bility and accuracy. All test lead-

Heathkit GRID DIP METER KIT

One hand operation. pre-wound coils cover 2—250 MC. Controlle sensitivity.
as an oscil-lator or an

absorption Extra low frequency coils avail-

MODEL GD-1B

\$1950 Ship. Wt. 4 lbs.

Heathkit TUBE CHECKER KIT



MODEL TC-2 \$2950

Portable Model TC-2P at \$34.50, Wt, 14 lbs. No. 91-8 Cab-inet only at \$7.50, Wt, 7 lbs. No. 355 TV Picture Tube Adapt-er at \$4.50, Wt, 1 lb.

Shipping Wt. 12 lbs.

Heathkit LABORATORY GENERATOR KIT



MODEL LG-1

Ship. Wr.

A professional laboratory instrument designed for extreme accuracy in frequency and output level. Colpits oscillator operates in 5 ranges from 159 KC to 30 MC. Panel meter calibrated in output voltage and percent of modulation. Output in excess of 1 volts. Features complete shielding of oscillator, buffer and attenuator sections; regulated power supply and 50 hm output cable. Comparable instruments priced many times higher than the cost of this new kit.

Heathkit LABORATORY REGULATED POWER SUPPLY KIT



A regulated variable 160-450 volt DC output power supply for the lab or servi-ice shop. Accurate voltage and current measurements with large Simpson meter. AC supply 6.3 volts at 4 amperes—standby switch eliminates warmup time. Low hum content—5 tube time. Ship. Wt. 20 lbs.





Measure output power levels directly with the Heathkit Audio Wattmeter. Flat response to frequencies from 10 CPS to 250 KC. Full scale ranges of 5 MW, 50 MW, 500 MW, 5 W and 30 W. Db calimodel.

MODEL +48. Uses non-inductive AW-1 built-in load resistors providing impedances of 4, 8, 16 and 600 ohms. Meter bridge uses 4 germanium diodes.

Ship. Wr. \$2950

HEATH COMPANY · Benton Harbor 15, Mich.

SERVICEMAN · AMATEUR · STUDENT

Heathkit MPEDANCE BRIDGE KIT



MODEL 18-2 \$5950 Modern design with built-in 1 KC gen-erator for AC meas-urements. A choice of the Wheatstone, Maxwell, Hay or capacitance com-parison bridges for

parson bridges for measuring resist-ance, capacitance, induc-tance, dissipation factor and storage factor. ½ % resistors and precision mica condensers provide maxi-mum accuracy. Completely. mum accuracy, Completely AC operated.

Ship. Wt. 15 lbs. Heathkit DECADE

RESISTANCE KIT MODEL DR-1 \$1950

> Ship, Wt. 4 lbs.

Individual switch selection of twenty 1% precision resistors in 1 ohm steps from 1 to 99,999 ohms. Sturdy ceramic wafer switches featuring silver plated contacts and smooth, positive detent action.



MODEL QM-1 \$4450 Ship. Wr. 14 lbs.

Heathkit COMMUNICATIONS RECEIVER KIT Full coverage from 550 KC to 35 MC on 4 bands, with good sensitivity and selectivity. Features ele-trical bandspread, BFO.



MODEL AR-2 Ship. Wt. \$2550

METER KIT

A typical Heathkit invasion of the laboratory instrument field. Here is the first successful low priced Q meter ever offered in kit form. Oscillator supplies RF in the range of 150 KC to 18 mc. Reads Q directly on calibrated meter scales. Measures Q of condensers, RF resistance and distributed capacity of coils. Calibrate capacity or with

Heathkit

Heathkit AUDIO OSCILLATOR KIT

MODEL AO-1

Ship, Wr. 11 lbs.

eatures sine or square

or square
wave coverage from
20-20,000 cycles in 3
ranges. Variable 10 volt output level
at 600 ohms impedance. Thermistor
controlled linearity-precision multiplier resistors—distortion less than
6%. An outstanding instrument value
at this amazing low price.

trical bandspread, BFO, headphone jack, slide rule dial with ham band identification, RF gain control, noise limiter and phone - stand by - CW switch. Top quality, high gain components used throughout. Pre-wound coils in a shielded turret assembly and a transformer operated power supply assure trouble-free performance.

Cabinet available sena-Cabinet available separately. No. 91-10. Shipping wt. 5 lbs. Price \$4.50.

Heathkit AMATEUR TRANSMITTER KIT

Power input up to 35 watts on 80, 40, 20, 15, 11 and 10 meters. Can be crystal or VFO excited. Complete with modulator input socket and VFO power output provisions. Other desirable features are good shielding, AC line filter, key click filter, standby switch and a 52 ohm coaxial output. Model AT-1 is AC operated and is suitable as an exciter for a higher powered rig. Complete with full instructions for construction and use.



MODEL AT-1

\$2950 Ship. Wt. 16 lbs

Heathkit DECADE CONDENSER KIT

brate capacitor range of 40 mmf to 450 mmf with vernier ±3 mmf. All measurements made at the oper-ating frequency. Switch selected 1% mmf. to 0.111 mfd. in steps of 100 mmf.

MODEL DC-1 \$1650

hipping Wt. 4 lbs.

Heathkit AUDIO GENERATOR KIT

A new extended range 18 cycles -1 megacycle audio instrument at a re-markably low markably low price. Five con-tinuously vari-able output ran-ges - 600 ohm out-put impedance— low distortion figure, less than 4% from 100 cps through audible range.



MODEL AG-8 \$2950

Ship. Wt. 11 lbs



BATTERY

ELIMINATOR KIT

Heathkit BAR GENERATOR KIT

Small, compact and easy to use, Model RG-1 supplies hori-zontal or vertical bars for TV linearity adjustments. Output cable clips directly to the TV receiver antenna terminals.

Ship. Wt. \$1450

WRITE FOR Free CATALOG

New 40 page 1954 Cat-alog lists all kits, specifications, schematics and latest price infor-

Heathkit

TELEVISION SWEEP

GENERATOR KIT



MODEL TS-3

Ship. Wt. 18 lbs.

Simplify your TV alignment jobs with the new Heathkit TS-3. Full coverage on fundamentals from 4 MC to 220 MC at an output of well over 100,000 microvolts... Automatic blanking and wide range A triple marker system ranges

from 19 MC to 180 MC using a Colpitts oscillator plus the 4.5 MC crystal controlled oscillator for check points (crystal

furnished). Provisions are also made for using an external marker Featured is the new sweep system, using an *INCREDUCTOR con-trollable inductor, Sweep width is variable from 0 to 12 MC at the lower RF frequencies and increases to 0-50 MC at the highest . . . Oth advantages are power supply regulation, constant RF output level, independent marker and RF output control circuits, low impedance output and properly terminated output cables. The construction manual is complete in all detail and with a reasonable amoun care, Model TS-3 will serve faithfully for many years to com-

*Trademark, C.G.S. Laboratories, Stamford, Connecticut



Ship. Wr. \$3150

MODEL BE-4

HEATH COMPANY • Benton Harbor 15, Mich.

Heathkit FM TUNER KIT

MODEL FM-2

\$2250

MODEL BR-2

\$1750

Shipping Wt. 9 lbs.

Sensitive transformer operated 8 tube circuit. Frequency cov-erage 88-108 mc. Pre-assem-bled and tuned "front end." Vernier tuning with slide rule type dial.

NEW Heathful

BROADCAST BAND RECEIVER KIT

NEW HEATHKIT WILLIAMSON TYPE AMPLIFIER KIT The ideal amplifier for custom high fidelity audio installations. Tops in performance, value and flexibility of operation. Either Altec Lansing Peerfess or Acrosound output transformers available. Frequency response ±1 db 10 CPS to 100 KC, negligible hum and noise levels and pienty of reserve power for complete listening pleasure. First Williamson Type Amplifier supplied with matching preamplifier.

Heathkit ECONOMY 6 WATT AMPLIFIER KIT

MODEL A-7B

\$1550 Ship. Wt. 10 lbs.

Dual in puts—
separate base and treble tone controls—output impedances of 4, 8, and 15 ohms. Performance far beyond that normally expected for the price.

A-7C: Includes preamplifier for low level input devices.

Price \$17,50

Heathkit HIGH FIDELITY 20 WATT AMPLIFIER KIT

MODEL A-98

\$3550 Shippin



\$6950 \$6950 Acronound and Power 54975 weight 30 only......

(Less Cabinet) Ship. Wt.

> Heathkit LOW PRICED Stagle UNIT

> > AMPLIFIER KIT MODEL W-4M \$3975

W-3 Amplifier Kit (Includes Main Amplifier with Acrosound

W-3M Amplifier Kit (Includes

PRICES OF VARIOUS COMBINATIONS: W-2 Amplifier Kit (Includes Main Amplifier with Peerless

Ship. Wt. 28 lbs.

The famous Heathkit Williamson Type Amplifier is now available in a single chassis. Includes power supply and power amplifor. En joy the same high quality reproduction at less cost by eliminating the second chassis, connecting cables, etc. Size 15 ½ "wide—7" high—9" deep. Model W-4 includes W-4M and preamplifier WA-P2. Shipping weight 35 lbs. Price \$59,50.

HEATHKIT HIGH FIDELITY PREAMPLIFIER KIT

MODEL WA-P2 \$1975 20000 Ship. Wt. 7 lbs.

Complete compensation for LP, NARTB, AES and early 78 recording characteristics. An ideal control unit for the custom Hi-Fi system. 5 individually controlled inputs, 4 turnover and roll-off switch positions, 3 twin triode tubes, cathode follower output, monitored recorder output, shock mounted tube chassis and proper shielding. All condensers are of the molded plastic type. Critical input circuits feature low noise deposited carbon resistors. Use it with any conventional high fidelity amplifier.

Outstanding features of the Heathkit 20 Watt Amplifier include a frequency response of ±1 db from 20 CPS to 20 KC, less than 1% harmonic distortion at rated output, separate (boost and cut) hass and treble tone controls, 4 selected input jacks, hum balancing control and output impedances of 4, 8, 16 and 500 ohms. Flexibility is emphasized in the input circuits with builtied, in preamplifier and proper equalization.

Complete receiver with chassis mounted 514° PM Speaker and new rod type antenna. Covera the full broadcast band (550 KC-1690 KC) with excellent sensitivity and selectivity. Operates as a receiver, tuner or a phono amplifer. High gain miniature tubes and 1F transformers. Easy tuning with direct planetary drive.

Cabinet available separately, Fort No. 91-9. Ship. wt. 5 sam Banders Price 54,50.

HEATH COMPANY Benton Harbor 15, Mich.

	MAIL YOUR ORDER	OR	DER	BL	ANK	
	MAIL YOUR ONE TODAY TO THE HEATH COMPANY BENTON HARBOR IS, MICHIGAN	From				SHIP VIA Parcel Post Express Freight Best Way
QUANTITY		ITEM	(P)	LEASE PRINT) _	MODEL NO.	PRICE
						1

Enclosed find () check () money order for Please ship C.O.D. () postage enclosed for

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

ON PARCEL POST ORDERS insure postage for weight shown

pounds.

ORDERS FROM CANADA and APO's must include full remittance.

Basic Color TV

(Continued from page 62)

appropriate points in the matrix network.

The remainder of the chrominance channel consists of three individual 6CL6 amplifiers, one for each of the three color signals, and three d.c. restorers. Action here is similar to that existing at the same point in the previous system and additional explanation is not required.

There are many ways of handling the color signals and the chrominance circuits of one manufacturer would differ in some respect from those of his competitors. Figs. 2 and 5 illustrate two possible approaches. Still another is shown in Fig. 6 and it contains several interesting features. The color signal is received from the first video amplifier by a bandpass amplifier. The chroma control is contained in the cathode of this stage and as much signal as desired is tapped off here and transferred to a second bandpass amplifier via a 1N34 crystal. The purpose of the germanium crystal is closely linked to the negative triggering pulses which are fed into the circuit via R1 and L. The negative pulses appear during the horizontal retrace interval when the color burst is passing through the circuit. The arrival of the pulse prevents the 1N34 from conducting since the pulse amplitude is greater than that of the color burst coming from V_1 and, consequently, the color burst is effectively prevented from continuing farther into the chrominance section. At all other times, the signal polarity is such that the 1N34 conducts and so whatever voltage is present across the chroma control reaches the grid of V_2 . This, then, is the way this circuit removes the color burst from the chrominance channel.

The bandpass of V_1 and V_2 extends from 2.1 mc. to 4.8 mc. and the signals within this range are amplified and then transferred to a 6J6 cathode fol-

lower (V_3) .


The next recipients of the color signal are the I and Q demodulators. The signal is fed in equal measure to grid No. 1 of both 6AS6's. At the same time, grid No. 3 of each tube receives a 3.58-mc. subcarrier voltage. The peak-to-peak value of this signal is on the order of 18 volts and the only difference between the 3.58-mc. voltages is a 90° phase difference.

In the I section, the demodulator is followed by an amplifier and then a phase splitter. The latter tube makes positive and negative I voltages available to the matrix. Bandpass of the I

section is 1.3 mc.

In the companion Q section, the demodulator is followed by a single phase splitter which provides positive and

Fig. 6. Chrominance circuit containing a manual color killer switch and a 1N34 crystal circuit for eliminating the color burst signal from the chrominance channel.

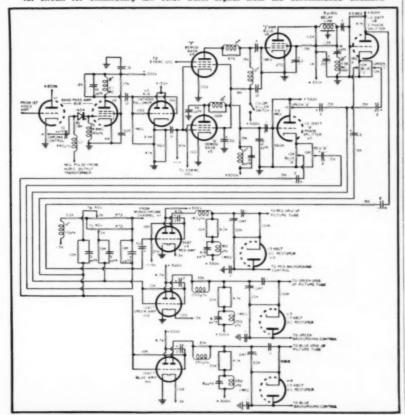



NEW INVENTION OUTMODES ALL PRESENT ANTENNAS!

53 CLAIMS GRANTED IN 5 U.S. PATENTS ON NEW REVOLUTIONARY ANTENNA INVENTION!



* GUARANTEED TO POSITIVELY OUTPERFORM ALL OTHER ANTENNAS (with or without rotor motors) on ALL UHF, and ALL VHF stations 2 thru 83 from ALL directions.

★ GUARANTEED to positively give you the CLEAREST, SHARPEST, most PERFECT GHOST-FREE pictures possible in both COLOR and

22222222

MONEY BACK GUARANTEED TO RECEIVE ALL CHANNELS 2-83 FROM ALL DIRECTIONS AND POSITIVELY OUTPERFORM ALL OTHER ANTENNAS WITH OR WITHOUT A ROTORMOTOR 5 ೮೮೦೮೮೮೮೮೮

UPTO 10 TIMES MORE POWER-FUL THAN ALL PRESENT CONVENTIONAL ANTENNAS!

New, revolutionary antenna, while being up to 10 times more powerful than conventional antennas, is still able to receive all television and FM stations from all directions without a rotor motor of any kind. The electronic prientation switch used with a new type transmission line developed specifically for this extra powerful antenna now makes it possible to clearly receive stations heretofore considered out of range. It is now possible to put up just one antenna, use just one transmission line, pay for just one installation and receive the finest possible reception from the stations in and coming to your area regardless of their direction.

ONCE AND FOR ALL SOLVE YOUR ANTENNA PROBLEM

47-39 49th STREET, WOODSIDE 77, N. Y.

EXETER 2-1336

CORONA RADIO KITS EASY TO BUILD . EDUCATIONAL EXCELLENT RECEPTION Broadcast Superhet

CORONA RADIO & TV CO.

TV TRADE-IN SETS

Philco • Emerson • GE • Admiral • Motorola • Tele-King • Others 10"-\$17; 12" to 17"-\$20 up

WASHTEK SERVICE CO.
Besten Road, Brenx, N. Y. DA 3-9281



negative Q signal voltages for the matrix. The bandpass of this section extends to .5 mc. in accordance with the nature of the received signal. It is interesting to note that should the bandpass of this channel be broadened above .5 mc., color infidelity would occur because of the presence of some higher frequency I signals in the Q channel. When the bandpass is limited to .5 mc., these "spurious" I signals are attenuated below the point of visibility and do no damage. But if the cut-off were extended, they would reach the picture tube and cause color "distortion."

There are several features worthy of special mention in the I and Q stages of Fig. 6. The "B+" voltage for the screen grids of V, and V, may be cut off by a manual switch called the "color killer" switch. When a blackand-white broadcast is being received, this switch is turned to the off position, disabling both demodulators and preventing any spurious signals from passing through the color section. For a color broadcast, the switch is turned back on again. This is a simple (and economical) form of color killer circuit. However, it does possess the disadvantage of requiring the set user to know when a color transmission is being received, otherwise all he will get will be black-and-white pictures. In the two previous systems, the color killer network functioned automatically; when a color signal was received, the killer voltage was automatically removed and a color picture appeared on the screen.

Another feature of Fig. 6 worth noting is the use of an actual delay line in the I section. In the other systems, the delay was distributed throughout the I system.

The voltages which the I and Q phase splitters apply to the matrix are nearly all individually adjustable. In this respect it is of interest to note the names applied to these controls. In the I phase splitter, there is a "Green I" and a "Blue I" adjustment. The "Green I" control is so named because the voltage from this point goes to the green amplifier stage and variation of this voltage would affect the hue of the green seen on the screen. The same type of reasoning applies to the "Blue I" adjustment since the voltage from this control goes to the blue amplifier stage. Three similar controls are employed in the Q phase splitter.

Finally, there are two adjustments near the point where the brightness signal enters the matrix. These are labeled as Y_n and Y_a adjustments and they control the amount of Y signal fed into the blue and green amplifier stages via the matrix. Definite relationships exist among the I, Q, and Y voltages and these relationships must be carefully observed if the proper hue, brightness, and saturation are to be obtained on the screen. By making a number of controls available, the service technician can make whatever compensating adjustments may be required to achieve the proper color (To be continued) rendition.

RADIO & TELEVISION NEWS



Here is your guarantee

If you fail to pass your Commercial L completing our course, we guarantee training without additional cost of an successfully obtain your Commercial you first sit for this examination with completing your course.

YOUR FCC

have had any practical ex-ce—Amateur, Army, Navy, repair, or experimenting.

TELLS HOW -

OUR AMAZINGLY EFFECTIVE JOB-FINDING SERVICE HELPS CIRE STUDENTS GET BET-TER JOBS. HERE ARE JUST A FEW RECENT EXAMPLES OF JOB-FINDING RESULTS:

GETS CIVIL SERVICE JOB

"Thanks to your course I obtained my 2nd phone license, and am now employed by Civil Service at Great Lakes Naval Training Station as an Equipment Specialist." Kenneth R. Leiser, Fair Oaks, Mtd. Del., McHenry, III.

GETS STATE POLICE JOB

"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police." Edwin Healy, 264 E. 3rd St., London, Ky.

GETS BROADCAST JOB

"I wish to thank your Job-Finding Service for the help in securing for me the position of transmitter operator here at WCAE, in Pittsburgh."
Water Koschik, 1442 Ridge Ave., N. Braddock, Pa.

GETS AIRLINES JOB

"Due to your Job-Finding Service, I have been getting many offers from all over the country, and I have taken a job with Capital Airlines in Chicago, as a Radio Mechanic."

Harry Clare, 4537 S. Drexel Blvd., Chicago, III.

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME IN SPARE TIME:

Name and Address	Lie	ense	Lessons
Lee Worthy, 2210/2 Wilshire St., Bakersfield, Cal			**
	4mg	rnone	16
Clifford E. Vogt, Box 1016, Dania, Fla	1st	Phone	20
Francis X. Foerch, 38 Beucler Pl., Bergenfield, N. J.	1st	Phone	38
S/Sqt. Ben H. Davis. 317 North Roosevelt, Lebanon, III	150	Phone	28
Albert Schooll.	2-4	Phone	22

CARL E. SMITH, E.E. Consulting Engineer, President

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Desk RN-66, 4900 Euclid Bldg., Cleveland 3, Ohio

TELLS HOW -

EMPLOYERS MAKE JOB OFFERS LIKE THESE TO OUR GRADUATES EVERY MONTH!

Engineering

Letter from nationally-known Airlines, "We would also appreciate if you would place the follow-ing additional advertisement in your building— Wanted—Superintendent of Communications— Salary 466.6 ber month."

Letter from nationally known sirplane manufac-turer. We need men with electronic training or experience in radar maintenance to perform oper-sional check-out of radar and other electronics at line salety. amounting to \$329.33 per month.

Letter from nationally-known Airlines, "We are contemplating placing . . an Airline Ground Radio Engineer." Starting salary \$385 per month.

FE C LICERSE

These are just a few of the examples of the job offers that come to our office periodically. Some licensed radioman filled each of these jobs; it might have been you!

Ours is the only home study course which supplies FCC-type examinations with all lessons and final tests.

FRE

INCLUDED IN OUR

TRAINING AND

COACHING

Your FCC Ticket is required by most employers as proof of your technical ability.

MAIL COUPON NOW!

INFORMATION

Cleveland Institute of Radio Electronics Desk RN-66—4900 Euclid Bldg., Cleveland 3, Ohio (Address to Book No. to avoid delay)

I want to know how I can get my FCC Ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC License and the amazing new booklet, "Money-Making FCC License information."

Be sure to tell me about your Television Engineering Course. Address

City .

CANNON Sub-Miniature PLUGS



For Your Miniaturization Program!

Sove space... sove weight... rugged. 1000's of usest Pressed steel shells. Heavily gold-plated copper-alloy 5-amp. contacts give untarnishing high surface conductivity and corrosion resistance. Take #20 solder-tipped wires. Polarization means. Saltspray resistant shells. Flashover 1700v dc.



Receptacles Hermetically-sealed

Round steel shells. Pin receptacles have fused vitreous insulators to give true hermetic seal. Adaptable to box-or panelmounting. Pin or socket plugs have resili-ent moisture-sealing insulators, gold-plated contacts. Bayonet latch. Cord connectors have resilient sleeves. Contacts 5-amp. Flashover 1700v dc.

Write for Cannon Sub-Miniature Bulletins . . . TODAY! Refer to Dept. 145

CANNON ELECTRIC COMPANY, 3209 Humboldt St., Los Angeles 31, Calif. Representatives and Cannon distributors in all principal cities.



GANNON ELECTRIC

The Curve That Conforms

(Continued from page 49)

of equalization is the occasional recording in which the manufacturer cannot adhere to the standard curve. Why? Simply because the acoustics of certain concert halls and the use of certain repertoire does not sound good with the standard curve. This is one of the major reasons why a flexible preamp is still a necessity.

It would be nice if all the LP records now in existence could be recut with the new curve. Given this and a pre-equalized ceramic cartridge of high enough quality, you could dispense with preamps altogether and have "super" systems with undreamed of signal-tonoise ratios. Perhaps this great day will come sooner than we think. In the meantime, it appears that despite RIAA standardization, we will have You may problems of equalization. have caught the term "recut with the new curve" a few sentences ago. As you probably know, the life of a master-mother-stamper is most uncertain. Accidents happen and plates are ruined. Stampers wear out after so many pressings. The procedure when this happens is to get out the tape of the original and cut another master.

The question has probably occurred to you by now (especially in regard to older recordings made prior to the RIAA curve) "Is the new curve used in recutting and how do I identify it?" The answer to this is still further reason for holding on to that preamp of yours. In other words, you will have no way of knowing whether an old recording has been recut with the new RIAA curve, or is still the original curve. There is no escaping the fact that we still must have provision for equalizing the older discs in our libraries as well as sufficient flexibility to equalize those new discs which do not seem to conform to the RIAA standard. Naturally, everyone should be glad that this new RIAA curve seems certain of universal adoption. There is no question that it will make life easier for the harrassed audiophile. It is not, however, the panacea for all of the problems involved in reproducing recordings correctly. You would be ill advised to think otherwise.

Another important question. should you do if you are planning to build or buy a new preamp? The answer depends on whether or not you have a collection of records or are starting from scratch to build a record library. If you are buying a preamp it will make no difference. Manufacturers will continue to put out preamps incorporating all of the equalization curves. There are too many old records in circulation to warrant changing over to the new curve exclusively.

If you are building your own preamp and have no records on hand, by all means concentrate on the RIAA curve. Your editors will continue to publish, at least for some time, preamplifiers incorporating all of the old curves. In those cases where the RIAA curve is the only one desired, automatically eliminate circuitry for the other curves. This should simplify the over-all preamp construction.

Now, let's hear from the industry

about the new curve:

Albert Pulley (Chief Engineer, RCA Victor)-"Of course the new curve is identical with our 'Orthophonic' which we have been using for some time now." (Incidentally, Mr. Pulley pointed out that Victor records marked "New Orthophonic" on their jackets are not merely cut with the new curve, but are so designated because of all the other factors such as microphoning, etc., which is part of the "New Orthophonic" process). All other new Victor records are cut with the new RIAA curve whether or not they state "Orthophonic" on the jackets. Mr. Pulley also asserted that all replacements and even the "Treasury" series would be cut with the RIAA curve whenever possible.

William Bachman (Chief Recording Engineer, Columbia)-"We are using the new RIAA curve in all new Columbia recordings. All replacements will be cut with the RIAA curve whenever

possible.

C. Robert Fine (Chief Engineer, Mercury Records)-Mr. Fine indicated that Mercury would go along with the industry in using the RIAA curve in all new releases.

Remy van Wyck Farkas (Director of Artists and Repertoire, London)-"We have been using the RIAA curve for some months now. Our entire catalogue will be recut with the RIAA curve as soon as stocks of the records with the older curve become depleted."

Capitol has been using the RIAA curve for some time now. Decca and MGM will use the new curve in future releases. All of the smaller companies whose output is pressed by Columbia and Victor will use the new curve. Notable exception to the almost solid swing to the RIAA curve is Westminster. Dr. Kurt List stated that for the time being Westminster would use the old NAB curve. Dr. List did not elaborate as to why this should be, but you can be sure Westminster has a valid reason, and we predict that they will hop on the RIAA bandwagon before too long.

Well, that's it! With the adoption of this new curve, the record industry has taken a significant step forward in the direction of standardization. It is to be hoped that this is but the forerunner of more such action in the -30future.

INTERNATIONAL CONTACTS

CC has again reminded amateurs that "radio communications between amateurs of different countries shall be forbidden if the Administration of one of the countries concerned has notified that it objects to such radio-communica-

Cambodia, Indonesia, Iran, Korea, Laos, Thailand, and Vietnam are the countries involved in the ban. -30-

Compare! Save!..on RAD-TEL TUBES SERVICE . . . OVER 300 TYPES IN

INDIVIDUALLY GU BOXED

1E7

IV



YOKE

1.95 No. 7-55° YOKE 99+ Lots of 3

Granco "Star" UHF CONVERTER

22.45

Philco TV BOOSTER



STANDARD BOOSTER, COMPLETE, \$5.95

VARIABLE CONDENSERS

Gang AM and FM ontains 2 separate or AM and 2 for adder condensers, iched slug tuned ections I with the stringer is shaft. 89, 79c Garig AM 3 Garos FM No. 10 89c 79c

padders and 79c 69c

No. 12 89c 79c

No. 96--Famous Standard Coil



Cascode Tuner

-\$34.50

ANODE CAPS, 19c ed. Lots of 10



No. 132 - Cathode Ray Tube Rejuvenator

Fits all makes of picture tules. Completely automatic. East install, no tools needed.
A.C. parallel circuits.
Old Picture Tubes Are !
Useful. List price—\$5.95.

1.39

New Parts At Old Fashioned SAVINGS! All



1.95 \$1.85 ea.





I kit of 50 assorted ceramic discs, biplates, tubular condensers. All condensers popular sizes, used in T.V. and F.M. sets. A MUST kit.

List price—\$10.00

Lots 1.89 ea.



Army-Navy **HEADSETS**

dividually boxed.

2.95 2.83 ea.

No. 44-10-INCH

2.15 ez.



69c ea. DOUBLE FLYBACK TTR-172

5 3.60 --

Type 7A5 Price Type 6AU6 Type .38 OA4 .68 6AV5GT .83 7A6 69 14A4 69 14A5 OB₂ .81 6AV6 40 7A7 .69 OC3 72 6AX4CT .65 7A8 .68 14A7 63 OD3 7AD7 14AF7 .70 6B4 OZ4M 6BA6 49 7AF7 .55 .53 1486 63 6BA7 **7B4** 1488 .63 .45 1A7GT .47 6BC5 7B5 1407 .79 1AX2 .62 6BD5 786 .69 14F6 **787** 7C4 1B3GT .73 6BD6 45 .49 14F7 88 .43 6BE6 .51 14F7 .65 705 .69 14H7 6BF5 706 1417 1G6 6BF6 .59 .30 114 7E5 .59 14N7 30 6BG6G 1.25 1H5GT .49 **6BH6** .53 7E6 .30 14R7 79 1L4 46 6B16 .49 7E7 59 1457 89 1LA4 7F7 59 6BK5 .80 79 14W7 30 7G7 1LA6 .69 .89 14X7 6BK7 .80 69 ILC5 14Y7 6BL7GT 7H7 .59 62 .83 .79 19BG6 1.39 **6BN6** .59 7K7 1LD5 .59 .69 19T8 6BQ6CT .98 .69 .59 ILE3 7L7 59 19V8 .79 6BQ7 .90 7N7 .69 1LG5 .69 6BZ7 .90 24A 39 **707** 7R7 .66 25AV5GT .83 **1LH4** .69 6C4 40 25BQ6GT ILN5 .59 .89 .98 6C5 .39 INSCT 757 .79 .67 25L6GT .51 606 1P5GT .57 7V7 .89 25W4GT 6CB6 .54 105GT 7X6 7X7 .54 25Z5 6CD6 1.11 .66 .62 6D6 185 25Z6 49 **7**Y4 .69 26 154 6E5 .48 45 155 .51 6F5GT 7Z4 .59 39 39 **1T4** .58 12A4 .60 32L7 89 6F6 .59 104 12A6 54 6C6 42 105 .50 12A8GT .61 35B5 .52 6H6CT .37 43 6JSGT .43 12AL5 35C5 .51 1X2A 12A0 .63 616 .52 35L6CT .51 .41 12AT6 .47 .54 .59 .43 35W4 2A3 .30 617 2W3 12AT7 .38 6K5 35Y4 35Z3 2X2 .49 12AU6 6K6CT .45 3A4 45 6K7 .44 12AU7 .60 3E5 46 6L6 .64 12AV6 .39 35**Z**5**G**T 3LF4 .73 69 6L7M .68 12AV7 39 3Q4 3Q5GT 48 **6N7M** .63 12AX4 67 42 42 .49 6Q7 6R7 12AX7 .63 55 .45 45 354 .69 .99 44 .58 12AY7 45Z3 3V4 12AZ7 .59 45Z5 49 654 .48 **5U4G** .55 657M 12B4 50A5 .55 5W4GT 6S8GT 12BA6 .49 50B5 .52 5Y3GT .37 6SA7GT .55 12BA7 .60 50C5 .51 .45 6SD7GT 50L6CT 5Z3 41 12BD6 45 .61 6A6 51 .51 6SESCIT 46 12BE6 50Y6 49 6A7 .69 6SG7GT 50Y7 .50 12BF6 6AB4 .44 6SH7GT 49 12BH7 49 .63 6AC5 .69 6SI7GT 41 12BY7 .65 49 6AC7M .86 6SK7GT .53 12BZ7 .65 57 58 .90 6AF4 6SL7GT 48 12C8M 34 58 60 6AG5 56 70L7 97 6SN7CT .59 12H6 56 6AG7M .99 .63 49 6SQ7GT 12SC7M .46 6AH4 .57 1215 6SR7GT 42 76 44 6AH6 6SS7GT 42 49 .57 6Aj5 65 6T4 99 12K8 59 78 47 6AK5 6AK6 .55 59 **6T8** .80 12Q7 80 43 1258GT 83V **6US** .57 62 68 6ALS .42 12SA7GT .65 84/6Z4 606 46 6AQ5 .50 .78 12SF5 50 **6U8** 59 85 6AQ6 6AQ7 125G7 .37 6V6GT .50 117L7 99 .70 6W4GT 12SJ7M .67 117P7 99 6AR5 .45 6W6GT .57 12SK7GT .63 117Z3 .37 6ASS 12SL7GT .50 6X4 .37 .57 117Z6 69 .52 6AS6 .69 6X5CT .75 12SN7GT 807 99 6AT6 .41 125Q7GT .56 6X8 866A 1.39 6AU4CT .68 6Y6C .48 Hi-Po

Price

Price

Price



6AU5GT

115 Coit St. Integrity Is Our Chief Asset Irvington 11, N. J.

TERMS: A 25% deposit must accompany all corders—balance C.O.D. All shipments F.O.B. Irvington warehouse. ORDERS UNDER \$10—11.00 HARDLING CHARGE. Subject to prior sale.

PLEASE: Send full remittance . . . allow for postage and save C.O.D. charges! We refund all unused money!

.82 7A4

Phone: Essex 5-2947

12V6GT

Tubes in Bold Type Cover 90% of Bemand

46

#567 1.39

NO INTEREST!! Buy on our radically new

Plan Payment

NO CARRYING



00 614" x 915" x 415"

Superior's new Model 670-A

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms CAPACITY: .001 to 1 Mfd. I to 50 Mfd. (Quality test for elec-


REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries DECIBELS: -4 to +18 +14 to +38 +34 to +58

ADDED FEATURE:

The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

The Model 670-A comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions.

Superior's new Model TV-11

 

Tests all tubes including 4, 5, 6, 7, Octal, Lockin, Peanut, Bantam, Hearing Aid, Thyratron, Miniatures, Novals, Sub-Miniatures, Novals, Sub-Miniatures, Proximity fuse types, etc.

Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-II as any of the pins may be placed in the neutral position when necessary.

when necessary.

The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible

to damage a tube by inserting it in the wrong socket.

socket.
Free-moving built-in roll chart provides com-plete data for all tubes.
Newly designed Line Voltage Control compen-sates for variation of any Line Voltage between 105 Volts and 130 Volts.

NOISE IEST: Phono-jack on front panel for plug-ging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

The model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

EXTRA SERVICE—The Model TV-II may be used as an extremely sensitive Condenser Leakage Checker. A relaxation type oscil-

lator incorporated in this model will detect leakages even when the frequency is one per minute.



AN AC OPERATED Superior's New Model 660-A

PROVIDES COMPLETE COVERAGE for AM-FM & TV Alignment

SPECIFICATIONS:

TUBES USED:

SPECIFICATIONS:

Generates Radio Frequencies from 100 Kilecycles to 80 Megacycles on fundamentals and from 60 Megacycles to 220 Megacycles on powerful harmonics. Accuracy and Stability are assured by the use of permeability trimmed Hi-Q coils. 6 R.F. available separately or medulated by the internal audio oscillator. — Built in 400 cycle sine wave audio oscillator used to medulate the R.F. signal also available separately for audic testing of receivers, amplifiers, hard of hearing aids, etc. 6 R.F. Oscillator Circuit: A

high transcenductance heptode is used as an R.F. escillator, mixer and amplificahigh transconductance hoptode is used as an R.F. ceciliator, mixer and amplifier. Medulation is effected by electron coupling in the mixer section thus isolating the osciliator freem load changes and affording high stability. * A.F. Oscillator Circuit; A high transconductance hoptode connected as a high-mu tride is used as an audio escillator in a High-C Colpitt Circuit. The output (over 1 Volt) is mearly pure sine wave. * Attenuator: A step ladder type of attenuator in use.

THE MODEL 660-A COMES COMPLETE WITH COAXIAL CABLE, TEST LEAD AND INSTRUCTIONS.

MOSS ELECTRONIC DISTRIBUTING CO., INC. Dept. B-104, 3849 Tenth Ave., New York 34, N.Y.

Please send me the units checked. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

Name																					
F	Name	 0.70			*	*		*	*		. ×	*	*	×		8		9	0.11	* /	_

1-6BE6 as R.F. Oscillator,

I-6BE6 as Audio Oscillator I-6H6 as Power Rectifier

mixer and amplifier

Address														

0		Total Price \$28.40
	\$7.40 down payme menthly for 6 m	nt. Balance 33.50
п	MODEL TV-11	Total Price \$47.50

U	\$11.50 down payment. Balance \$6.00 menthly for 6 menths
0	MODEL 660-A Total Price \$42.95 \$12.95 down payment. Balance \$6.00

	monthly for a months.					
	0	I enclose \$ as down payment				
CityState	0	Ship C.O.D. for the down payment.				

NO INTEREST!! Buy on our radically new

Payment Plan

NO CARRYING CHARGES!!



Superior's New Model 770-A

The FIRST Pocket-Sized

NEW "FULL VIEW"

71% MORE SCALE AREA!!

Yes, although our new FULL-VIEW D'Arsonval type meter occupies exactly the same space used by the older standard 2/7." Meters, it provides 71%, more scale area. As a result, all calibrations are printed in large easy-to-read type and for the first time it is now possible to obtain measurements. instead of approximations on a popular priced pocket-sized V.O.M.

Features

* Compact—measures 3½" x 5½" x 2½"

* Uses "Full View" 2½ accurate, 850 Microampere D-Arsonval type meter

* Housed in round-cornered, molded case

* Beautiful black at thad possible.

moided case

Beautiful black etched panel.
Depressed letters filled with
permanent white, insures
long-life even with constant

Specifications

THE MODEL 770-A COMES COMPLETE WITH SELF-CONTAINED

BATTERIES, TEST LEADS AND ALL OPERATING INSTRUCTIONS. ONLY



Superior's New Model 70 UTILITY TESTER

FOR REPAIRING ALL **ELECTRICAL APPLIANCES · MOTORS · AUTOS**

As an electrical trouble shooter the Model 70:

- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakages, etc.
 - · Will measure current consumption while the appliance under test is in operation.
 - Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.
 - Leakage detecting circuit will indicate continuity from zero ohms to 5 megohms (5,000,000 ohms).
 - Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.

As an Automotive Tester the Model 70 will test:

- . Both & Volt and 12 Volt Storage Batteries . Generators . Starters . Distributors . Ignition Coils . Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers • Directional Signal Systems • All Lamps and Bulbs • Fuses • Heating Systems
- Horns Also will locate poor grounds, breaks in wiring, poor connections, etc.

Handsome round-cornered mold-Handsome round-cornered mold-ed bakelite case, 3½, "x5½," x 2½,". Complete with all test leads. Also included is a 64 page book giving detailed in-structions for testing all elec-trical appliances, submotive equipment, etc.

SUPERIOR'S NEW MODEL TV-40

. TUBE T

A complete picture tube tester for little more than the price "make-shift" adapter!! of a

The Model TV-40 is at piete! Self-contained, in EASY TO USE:

Tests all magnetically deflected * tubes . . . in the set . . . out of the set . . . in the carton!! SPECIFICATIONS:

- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale. . Tests for inter-elument shorts and leakages up to 5 megohms.

· Tests for open elements.

olf A.C. outlet, then attach tester socket to tube base (ion trap need Model TV-40 C.R.T. Tube Tester comes absolutely complete—nothing else to buy. Housed in round cornered, molded bakelite not be on tube). Throw switch up for quality test . . . read direct on Good-Bad scale. Throw switch down for all leakage tests. case. Only



MOSS ELECTRONIC DISTRIBUTING CO., INC. 3849 Tenth Ave., New York 34, N. Y. Dept. 8-104,

Please send me the units checked. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become interellabely due and payable.

Name.....

City......Zone...State.....

Balance \$4.00 O Model TV-40 Total Price \$18.85 \$3.85 down payment, Balance \$4.00 monthly for 3 months.

C Ship C.O.D. for the down payment.

UHF TRANSMITTER-RECEIVER



plete with R.F. and tubes. With Len

ARC-5/R-28 2-METER RECEIVER

Here is the 2-meter superhet you have been looking for! Absolutely one of the BEST available today! Tunes from 100 to 158 Mes. in four crystal channels. (Easily converted to continuous tuning.) Tube lineary is as follows. 7174.—H.F., 7174.—Miser, 2-12847.—let and 2nd L.F. 16,9 Mes. \$19.95

AN-75 PORTABLE ANTENNA-With Base

For portable or vehicular operation. Used as a portable, antenna is clamped to radio bousing. On vehicles, it is clamped under hood or to other sup-port. Collapsed length is 12 inches. \$1.95 Extends to 84 inches. Flexible New. \$1.95

SCR-183 TRANSMITTER RECEIVER. Complete with 12 V. dynamotor and tubes. 40, 80 meter. F.H. for mobile. New with service manual. \$24.50

TG-10 CODE KEYER

Self-Contained Automatic unit for code practice sig-nals from an inked type recording. Complete with 7 tubes and electric eye: Audio freq, output of 800 CPS. Size: 11 x 24 x 18%"—119-220 VAC 50 cy.— 78 BPM motor can be used for a turntable—Power unit can be used for a P.A. system.—Wt. \$22.50 65 lbs. Brand New



C.A.P.

Freq. range 100-150 MC. With

modulation section and speech amplifier. Less tubes & crystals, with conversion dope. \$9.95 Used, good condition. (See Nov/58 CQ.)

ARB NAVY RECEIVER

105 to 9050 KC. Four Bands, Calibrated Dial, LF Ship-BC-86 & 40 Meter—complete with Tubes and Dynamotor, For 24 Volt operation; easily converted to 110 V—12 or 6 Volt. Size: 84° x 74° x 154°. Excellent cond. \$29.50 With schematic

With schematic
DU-1. DIRECTION FINDER LOOP AMPLIFIER for ARB receiver, With tubes and loop.
Excellent condition. With schematic...\$19.95



ID6/APN4

BEST HEADSET & MIKE BUYS

H-16U HEADSET.	
HS-18 HEADSET.	New 2.48
HS-23 HEADSET	. High imp. New 4.95
HS-30 HEADSET	. Featherweight type, Low
imp. NEW	
HS-33 HEADSET	. Low imp. New 5.50
HS-38 HEADSET	. USED, excel, cond 1.49
NEW	3.50
RS-38 MIKE. N	EW . \$4.98 Excel 2.75

T9-MODULATION TRANSFORMER, For BC-610 Tratsmitter, Pri. 16,000 ohms cT: sec. 8,330 ohms @ 250 ma, Fully shielded steel case, New. \$34.50



Sound Powered Handset TS-10

Uses no batteries or ex-ternal power source. Ideal for TV installation work, s, connecting outbuildings,

farms, construction projects, connecting extensions, etc., includes 5 ft. cord. NEW. Each.

FREE HAM FLYER!

Featuring Loads of Special Values SEND FOR YOUR COPY TODAY!

All shpts. F.O.B. whse. Calif, residents add sales tax, 25% deposit required. Specify shipping instructions and ADD SHIPPING COSTS TO EACH ORDER. All items subject to prior sale and change of price with-such salings.

ARROW SALES INC

The products described in this column are for your convenience in keeping up-to-date on the new equipment being offered by manufacturers. For more com-plete information on any of these products, write direct to the company involved.

SERVICE INSTRUMENT

The Hickok Electrical Instrument Company, 10524 Dupont Avenue, Cleveland 8, Ohio, is now offering a new multi-range electronic volt-ohm-



meter which is designed to speed radio and TV servicing.

The Model 225 is designed around a 9" internal pivot meter and features extra long scales to minimize reading errors and permit the unit to be used at practical working distances.

The new unit matches other instruments in the company's line and is housed in a blue hammertex steel case 16" wide, 13" high, and 7" deep. Complete specifications are available from the company on request.

EQUIPMENT ENCLOSURES

Elgin Metalformers Corporation, 906 N. Liberty St., Elgin, Illinois is now offering a new instrument cabinet which comes in a baked-on, two-tone, smooth enamel finish.

The top, bottom, back, and both end panels are quickly removable with a screwdriver, allowing complete access to the interior. The new "Emcor" cabinets can be stacked vertically or horizontally and locked together with "Speed Nuts" and a screwdriver. The unit accommodates chassis with a 8%" x 19" front panel and a depth of 15". Chassis guide supports are adjustable to chassis of any width up to

BASIC PRINTED CIRCUITS

Tri-Dex Company, P. O. Box 1207, Lindsay, California is now offering a line of standard printed circuit boards for experimental and laboratory development applications.

Six compact standard "Tri-Dexes" provide for most tube and basic circuits. A seventh unit is universal for filtered power supplies. Each unit is mounted directly on a tube socket and provides clearly marked, preconnected eyelets for all resistors and condensers

for each basic circuit. Any suitable resistors and condensers may be used. Each stage may be quickly assembled as a compact unit and shielded with the aluminum plate provided.

Each "Tri-Dex" is supplied complete with instructions, shield, and mounting hardware.

"DUOVOLT" GENEMOTOR

Carter Motor Co., 2641 N. Maplewood Avenue, Chicago 47, Illinois has announced the availability of a dualvoltage genemotor that will operate on either 6 or 12 volts.

"Duovolt" powered mobile radio equipment may be transferred from one car to another, irrespective of battery voltage, without impairment of transmitting and receiving quality, without replacement of the genemotor, and without modification of the wiring hookup.

The new unit incorporates two separate 6-volt input windings, each having its own field. Six or 12-volt operation is obtained simply by connecting the four input leads in parallel or in series.


For complete information, mechanical and electrical specifications, write Dept. 7 of the company.

I.F. TRANSFORMER

Aladdin Radio Industries, Inc., Nashville, Tenn. is in production on a unique 43 mc. i.f. transformer with a tuning range of 25 to 90 mc.

Tradenamed the "Ulti-Mite." the new transformer features a new tuning principle that eliminates the conventional powdered iron core. Molded nylon studs provide smooth tuning that is not affected by vibration.

All adjustments are made from the

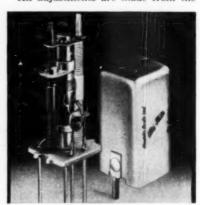

top, only the terminals are exposed through the special molded base. The base is a heat-resistant polyester resin which is stable and not affected by

heat. The "Ulti-Mite" can be dipsoldered with printed circuits as well as adapted to conventional strips. All units, interstage or diode, are housed in %" square aluminum cans with either spade bolt or solder lug mount-

COMPONENT BRIDGE

Cornell - Dubilier Electric Corp., South Plainfield, N. J. has introduced a condenser-resistor bridge, the BF-60, which measures the important charac-



teristics of virtually all types of condensers and resistors and determines their quality.

The new instrument detects opens, shorts, and intermittents: the capacity between wires and shieldings: transformer windings; wires in cables and makes possible the measurements of insulation resistance of paper, mica, and ceramic dielectric condensers.

For full details on this new portable bridge, write E. J. Maginot, sales promotion manager of the company.

FOUNDATION CHASSIS

A series of five new foundation chassis, suitable for amplifiers, transmitters, power supplies, and other electronic applications has been introduced by Insuline Corporation of America, Manchester, N. H.

The units feature perforated covers that provide both ventilation and protection for parts mounted inside. Made of heavy steel, the chassis and covers are finished in marine gray ripple enamel. Detachable side handles are included.

The chassis depth is three inches. Over-all dimensions of the five models are: No. 3965—5½" x 10" x 9"; No. 3966—8" x 12" x 9"; No. 3967—7" x 17" x 9"; No. 3968—10" x 14" x 9"; and No. 3969—10" x 17" x 9". Special sizes are available on a custom basis.

HIGH-VOLTAGE CONDENSERS

Centralab, 900 E. Keefe Ave., Milwaukee 1, Wisconsin is now offering a new line of precision high-voltage condensers which have been designed to eliminate the twisting off or breakage

The condensers are available in 500 μμfd., 20,000 volt sizes. Heavy 8-32 threads on both the terminal and condenser lock the terminal tightly and precisely into the "Hi-Vo-Kap." Internal corona is prevented by seating the terminal at the bottom of the condenser tap, thus avoiding any air gap.

The new attachable terminal condensers are available singly or in packs of five. Write Department E10 for copies of bulletins 28-2 and 42-201. covering these units.

TRANSISTOR KIT

Precise Development Corp., Oceanside, Long Island, N. Y. is marketing a transistor kit, the Model T1.

The new kit includes all equipment, transistors, transformers, coils, etc., necessary to permit the purchaser to acquire basic transistor knowledge through actual experimental and practical use of audio one-stage amplifiers through transformer-coupled amplifiers and special circuits.

A simple instruction book covers the physics of transistors and shows the applications.

TEST SOCKET ADAPTER

Pomona Electronics Co., 524 W. Fifth Ave., Pomona, California has introduced three new service aids to the electronics field.

The new units consist of 7- and 9-pin miniature test socket adapters and an 8-pin octal test socket adapter. They may be used for making measurements of voltage, resistance, audio, and video from the top of the chassis while the set is in operation.

The adapters are inserted between the tube base and its socket. This completes the circuit and makes all



RADIO and TV Manuals

Your complete source for all needed RAD10 and TV diagrams and servicing data. Nost amazing values. Still sold at pre-Korean prices. Only \$2 to \$3 per volume. Every Basile manual contains large schematics, all needed alignment facts, parts li-ts, voltage values, trimmers, dial stringling, and sorvice the schematics, all needed alignment parts Hi-ts, voltage values, trimme stringing, and service hints. Ex-volume is a practical treatise on s a full year's sets, with giant blu-wavefours, hints, alignment and chasts, production changes. See Each TV

Supreme Publications

Sold by all Leading Parts Jobbers

New TELEVISION COURSE

Amazing Bargain. Complete. Only \$3

NEW PRACTICAL COURSE

Here is your complete training in television servicing. Amazing value at only \$3, complete. These new lessons cover every fact, adjustment and repair of all types and makes of TV receivers. Giant in size, mammoth in sope, just like other correspondence courses selling for over \$150.00. Gur amazing offer permits you to obtain the course complete for only \$3.

COMPLETE TV TRAINING

New, casy-to-follow, well illustrated lessons on circuits, picture faults, adjustments, short cuts, about UHF, alignment, antenna problems, troubleshooting, service hints, how to use test equipment. Many large practical sections prepared by leading manufacturers. Just published. Send trail coupon today and use the complete Television Servicing Course at our risk

COVERS EVERYTHING IN TV

Let these course lessons take non into TV nervicing the easy way. The very first lesson of this sensational course tells how to do simple repairs. You can start earning money immediately. Second beson tells you what is wrong, by just looking at the picture—ne instruments used. Lesson 4 has 32 large, 8½ x 11° pages and 28 large illustrations on antenna installations and improvements. Another 12 lessons deal with trouble-shooting, alignment, UTP converters, test equipment, picture analysis, and all types of new circuits.

AMAZING BARGAIN VALUE

With this new course you will find your-elf doing TV repairs in minutes — Instantly nding faults. Most amazing bargain. Ex-mine this course for 16 days. Look nee-tic material, read a few lessors, apply one of the hints. Then decide to keep the secons at the bargain cost of £3 (full price), a return the material.

NO-RISK TRIAL ORDER COUPON

: SUPREME PUBLICATIONS, 1760 Balsam Rd., F	, Highlan	d Pork, IL
--	-----------	------------

Radio Diagram Manuals |

- 1953 Radio Manual, \$2.50

- 1948 5 1947 5 1946 2 1942 5 1942 5
- 1941 0 1940 8 1939 8

- Rush today TV manuals checked ☑ below and Radio manuals at left. Satisfaction guaranteed.

 ☐ New Television Servicing Course, complete.....\$3.
- - 1948 TV, 53. ☐ 1947 TV & FM, only \$2. ☐ I am enclosing \$ Send postpaid.

Send C.O.D. I am enclosing \$ deposit.

| 1926-1938 Manual, 92.50 | Master INDEX only 256 | Address:

Must - Often - Norded

1954

Television

Don't read this ad if you are looking for cheap tubes. But if you want GOOD TUBES at reasonable prices, this is for YOU. ES & PARTS ALL TUBES are guaranteed for one year . . . individually boxed. 89c | \$AHS - 6AHS - 6AHS - 6AHS - 79 | \$AHS - 79 | \$AQS - 179 | \$AQS - 170 | \$A Very BEST BRANDS available for immediate delivery. 79c 12Av7 12Av6 12Av7 12Av6 12Ax7 79c 12Ax7 29 12Ax7 149 128A8 1.19 128A8 1.19 128A8 1.49 68H6 2.95 68J6 .89 68K7 1.19 68L7 690 68Q6G 79 68Q6G7 59c 58 179 179 6A05 680 6806 1.19 6L5G 35 6875 79 6806 1.19 6L5G 35 6875 39 290 290 290 290 225 305 206 307 290 307 304 59c 5 U4G. 1.19 5W4GT SY3GT SELENIUM 79c 6A/ 55 6A6 69c 6AC96T 59 6AC96T 59 6AF4 6AG9 RECTIFIERS 65 mit...5 .69 75 mit... .79 79¢ 12A7 .89 12A8 .89 12AH7 .89 12AH7 .89 12AL5 89¢ 12AT7 29c SAGE TUBE KITS MISCELLANEOUS BUYS I. F. TRANSFORMER-486 He....29c PILOT LIGHTS. Tyre No. 47 10 for 39c; 100 for \$2.93 374, 174, 185, \$2.19 The equivalent of 40 dipoles All Four Tubes for ...

187... 1US, 354, 183,
AC-DC Pertable Kit. VOLUME CONTROLS FOR SWITCH.

2" shaft, \$ meg, \$\frac{1}{2}\$ meg, \$\frac{1}{2}\$ SUARANTEE \$15.95 304, 174 1RS, 188, List Value \$8.00. Tube \$1.98 meg 2-e
SINGLE ION TRAPS. 58
DOUBLE ION TRAPS. 99. 29c
OUTPUT TRANSFORMER. 99. 29c
For SGLS. 29c: for 8V8. 39c
S-foot LINE CORD U. 10 for 81.7
TV INTERLOCK CORDS. 99. 49c \$2.49 This is a BIG ANTENNA. Reflectors 9 feet long. Corrical elements over 10 feet long. Solid rugged wind proof constructure. \$22.94 5085, 128A6, 128E6, \$2.59 5 Tubes for \$2.59 501.66T. 35250T. 125076T. 125076T. 125076T. 5 Tubes for \$3.39 Value \$7.50. 4-Tube \$1.98 Grade Super Directionic **REGENCY RC-53** CONICAL TV ANTENNA 10 Element conical throughout. Only rugged \$3.95 **AX-548 ULTRA-FRINGE AREA** TV ANTENNA SYSTEM Double bay array, with stacking bars . . \$7.25 Double bay array, with barness and stacking bars 4 Bay array, with harness and stacking bars igned to give the finest reception in ultra-pe areas where signals arrive from more than nule direction. a single direction.

All channels for ULTRA-FRINGE AREAS

4-BAY SUPER DIRECTRONIC

4-BAY SUPER DIRECTRONIC All channel UHF Conver-483g" aluminum elements
Complete with all harnesses; 6-position beam selector; 139° of "AIR-COME" TRI-TUBE LINE.
High gain superior to any standard broad-band
antenna, with greater gain on low-band channels.
Balanced construction for equal distribution ter. Much more gain than THE DAVIS strips, and fits \$14.96 SUPER-VISION weight.
No motors or electric power. Clearest signal is obtained electronically. ALL-CHANNEL ANTENNA List price \$100.00 ALLIANCE #U83 Dealer's net Guaranteed to Please in Every TV 2055 **Automatic Tenna-Rotor** the Fastery. Dealer Net 1954 Model Complete with twin lead, mast, mount and everything you need for deluxe installation \$27.54 Simply set pointer at desired di-rection. Antenna turns there and stops automatically. No drifting. List....\$49.95. CONICAL Thrust Scaring Stacket :: TBS2. Prevents buckling and bonding of the mast. BRAND NEW TV PICTURE TUBES Complete his contains everything you need for professions installation. For all argument good receptions as a large of the contains a second profession of the contains a seco TV ANTENNA List. . \$4.95 Dealer net. . \$2.97 PICTURE TUBE BRIGHTENERS They will protong the life of your old picture tubes many, many 300 OHM TWIN LEAD

All Tubes Have	Baylight Type Dark "A"	or "B" Faces
SIZE PRICE	SIZE PRICE	SIZE PRICE
7JP4 17.98	10.05	30CP4 AF AF
88P4 18.95	19.95	25.95
108P48 12.95	101.04 33.34	20484 27.42
12/P4 4E OF	16884	21484 38 10
121.040 13.93	19.95	21.004
12UP48 17.40		31694 20.00
	14WP4A 22.20	25.0004
18.40	16YP4A A4-40	219004
	20.95	34.95
14074 19.90	178P4A ZU.33	21794
14HP4 10.00	17094 21.40	212P4 29.95
15AP4A 20.50	17024 24.90	24AP4 42.95
16AEPA 20.30	17494 34.90	82.50
164544	171.04 30.95	24074 02.30
20.BU	17794 24.90	27EP4 78.50
10EP48 20.20	100040	27GP4
102744 20.20	26.80	79.95
100740 77 71	1201-12 FAIR	22804
16JP4A	Intras	21000
THESE ARE	15 MONTH	ATRPS
THESE AME	QUARANTEE O	M ALL TYPES

PICTURE TURES

1,000 ft. 13.95 20 Ga., 80 Mil, 100 ft. 1.80 1,000 ft. 1.80 UNF TUBULAR 300 OHM LINE

All Channel Foam Line, 100 ft. for \$6.05. 30 ft. for \$3.05

TV MASTS and HARDWARE

Four Conductor Rotor Coble Clear or Brown, Very Special, 1,000 ft.

.... \$34.50

100 n. \$1.95

3239 West North Avenue, Chicago 47, Illinois

GUARANTEE ON ALL TYPES SEND 25% DEPOSIT AND WE WILL SHIP FROM STOCK IMMEDIATELY

WE GIVE YOU FULL \$3.00 CRED-IT WITHIN ONE YEAR TOWARDS THE PURCHASE OF ANY NEW PICTURE TURE.

21" TV CONVERSION KIT COMPLETE WITH CABINET AND NEW TUBE

15 Month Guarantee New you can make that conversion. This table model cabinet eliminates your bettle neck. Supplied complete with 21° pic-ture tube, 70 degree yoke, gold mask and safety plate, fly back transformer and width coll, very easy to install and all for

TY CONVERSION VITE

	IA	CON	AE	ĸ	210	N	V	ı	J.	3			
ALL N		Easily in degree y	statte	4 0	NTH onsistin	to of	rest	an	@¥	ta	ube.	7	0
	1 20-	Conversion Conversion	Kit.	80	above,	09/10/20	iete		* *		925	1.9	15
17	21"	Conversion Conversion	St.	*	above,	eamp	lete	* *	* *		71	÷	H

Twin load int.

Mast Int.

Ten foot mast. Scambes, expanded end, sturyly \$2.39

s. m. pussass Mast, heavy gauge 114 diam, with interlocking end, \$10 we extless begeber for a tenfoctor.

\$1.25

Auth section.

\$1.25

\$1.25

\$1.25

\$1.25

\$1.2 LL shipments F.O.B. Chicago. ORDERS LESS THAN \$5.00—\$1.00 SERVICE These prices supersede all previously advertised prices, subject to change TERMS: 25% DEPOSIT with order, balance C.O.D. CHARGE. CABLE ADDRESS: CONTULAB. PREMIER TV RADIO SUPPLY, division of CONTINENTAL CORPORATION

FILTER CONDENSERS

FP Type or Tubular

with	Leads-F	resh
8 mfd. 8 mfd. 10-19 20-20 30-30 40-40 60-40 80-40 10 mfd. 20-20 30-30 40-40 40-40 40-40 40-40 50-40 80-40 40-40 40-40 50-40 80 80-40 80 80-40 80 80-40 80 80-40 80 80 80 80 80 80 80 80 80 80 80 80 80	480V.	.35
8-8	450V.	.45
10-	450V.	.39
10:10	450V.	.45
20-	450V.	.45
20-20	450V.	.49
30-	.450V.	.49
30-30	450V.	.59
40	450V.	.49
40-40	450V.	
60-40	4504	.00
80	450V	6.9
60.40	450V	1.29
10 mfd	SOV	19
20.	SOV.	.19
25-	SOV.	.19
50-	sov.	.25
100-	50V.	.29
20 mfd.	150V.	.38
20-20	150V.	.45
30	150V.	.45
30-30	150V.	.49
40	150V.	.49
40-20	150V.	.49
40-40	150V.	.49
50-30	150V.	.49

RESISTOR KITS

Insulated Ug. 1 and 2-watt assertment of most used values, I.R.C. Ohmite, Stack-pole, Speer.

100 fer. \$2.95

MOLDED TUBULAR BY-PASS CONDENSERS

.005	- 6							
	. 83	 ÷	'n	'n	٠		×	
	. 82							
.05	. 12							
1	. 25	 ×	×			*	×	*

WELLER Solder Guns

NEW DUAL HEAT 2 Lights No Shadow 9-440—180— 100 Watts...\$10.95 0-550—275— 200 Watts...11.95 SINGLE HEAT

5-400-135 Watts. \$8.95 9-500-250 Watts. \$9.95



Transformer TV Horizontal output, univer-sal replacement 14,500 V. \$2.49 00



70 degree cosine yoke with 4 leads and network



Write for ser free CATALOG

ARmitage 6-5550

P. M. SPEAKERS

32" COAXIAL PM SPEAKERS. High Fidel-lty with Crossover filter attached. 20 watts; 40-19,000 cps. response; 8 ohm Voice-coit...ea, \$12.95

15" COANIAL SPEAK-ER. 20-17,500 cps. 25 watts.

SPEAKER ... \$10.95

... \$19.95

connections readily accessible without removing the chassis from the cabinet or turning the set upside down.

RESISTANCE SOLDERING

Vermaline Products Company, P.O. Box 222, Hawthorne, N. J. has developed a new resistance-type soldering unit, the Model 10.

Designed especially for production soldering of printed circuits, germanium diodes, and transistors, the unit is equipped with an adjustable heat control which prevents scorching of printed circuit plates. It is rated from 25 to 1000 watts.

A data sheet giving complete specifications on the Model 10 is available on request.

CARTRIDGE SELENIUMS

A new range of cartridge-type selenium rectifiers has been added to the 'Seletron" selenium rectifier line by Radio Receptor Co., Inc., 251 W. 19th St., New York 11, N. Y.

Included in the group are hermetically sealed glass-encased units, phenolic-encased half-wave axial lead units, and phenolic-encased bridge type and unmounted cells for special assembly

A six-page data bulletin, No. 178, has been issued on these new units. It contains complete characteristics, reference curves, circuits, etc.

450-470 MC. GEAR

General Electric Company, Syracuse, N. Y. has announced production of new radio transmitter-receiver combination units for operation at recently authorized frequencies between 450 and 470

Designed for police and fire departments, taxicabs, and some industrial applications, the mobile models will function from either 6 or 12 volt batteries with no adjustments necessary



to revert from one to the other. Nominal output of mobile units is 20 watts. All station units have 40 watts output and are rated for continuous duty.

U.H.F. STANDOFFS

Television Hardware Mfg. Co., 919 Taylor Ave., Rockford, Ill. is now offering a completely new line of TV standoffs designed especially for u.h.f.

According to the company, the design permits their use with all kinds of lead-in line with particular emphasis on the newer hollow-core types. The "E-Z" standoffs are said to minimize the transmission loss from the antenna to the receiver. A new polyethylene insulator securely holds the lead-in

BUY DIRECT . . . and SAVE!

'PRE-FAB'

High Fidelity TUNERS and TUNER KITS introducing the LATEST DESIGN

LINS CHROMATIC T



CHECK THESE OUTSTANDING FEATURES

- 412" tuning meter. Each tuner calibrated in microvolts for direct reading of signal
- strength.

 Not a kit. Completely wired, ready to use with FM antenno and amplifier.

 Sensitivity 3 microvolts with 20 DB of
- quieting.

 A.F.C. with disabling switch.

 New, compact, low design. Only 5½" high.

 Matches latest bookshelf amplifiers.

 Yellage regulator tube for added stability.

 Newly designed front-end using 88Q7 tube.

- rsigned front-end using 68Q7 tube.
 ultaneous audio output—high and
- law impedance.

 Ultra wide range response, 20 to 25,000

TUNERS

- cycles.

 Distortion less than 34 of 1%. Hum 50 D8
- below pragram.

 Beautiful golden brown metal cabinet completely enclosing tuner.

 514"x19" relay rack panel integral part of
- - Twelve tubes.

Tone compensated valume control.
 Plus many other smaller features which make this tuner the hottest item since high fidelity!

Overall size: 19" W. x 51/4" H. x 81/2" D. Shipping weight: 15 lbs.

RE-FAB KITS COLLINS ALSO AVAILABLE




with AFC \$58.50



FM/AM Tuner Kit

50 with AFC *81

ifier . . .

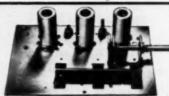

FMF-3 Tuning Unit 21/2 lbs

AM-4 Tuning Unit Shipping weight: 2½ lbs.

For Users of Collins Tuners:

Receive \$5.00 credit toward the new FMF-3A front end! Mail us your old front end with \$13.75 and we will send you the new, improved FMF-3A with AFC or, remit the full amount of \$18.75 and when we receive your old unit in return a check will be mailed you for \$5.00.

Collins Audio Products Co. is in no way | offiliated with Collins Radio Co.

To: Collins Audio Products Co. Inc. P.O. Box 368, Westfield, N. J. Dept. RN7 Tel. WEstfield 2-4390

| Chromatic Tuner | FM Tuner Kit with AFC ☐ IF-6 Amplifier

FM/AM To with AFC FMF-3 Tun. Unit AM-4 Tuning Unit with AFC

Address City State Amount for Kit \$

See weights, add shipping cost \$....

WHEN YOU THINK OF TUNERS, THINK OF COLLINS AUDIO PRODUCTS

wish

AFC

*18.75

ner Kil

RON 1

GUARANTEED! . . . LOWEST PRICES EVER!

All tubes individually boxed . . . unconditionally guaranteed for one year.

TYPE PRICE (TYPE PRICE	TYPE PRICE	TYPE PRICE I	TYPE PRICE
OF445	6Q740	68K778	6UB	1287 40
1A787 53	6A8443	68L7GT78	6V380	125A7GT45
	6AC765	68N690		125K7GT45
		SEGSGT 83	6W4G7 43	125L7GT60
1H351 51				
11.651	SANAGT			
11.651	6A/596		6X437	125Q7GT38
1LC649	6AK596	68Z795	6X5GT38	198G6G . 1.48
INSGT51	6ALS43	60441	6X8 80	197871
18551	6AQS48	6C8651	7FB	258Q6GT82
15543	GARS48	6CD6G 1.63	7N749	25L6GT41
17451	GAT637	6CU698	12ALS43	25W4GT 43
104	GAUSGT 60	6F642	12AT637	252559
19543	6AU643	6F5GT44	12AT771	2526GT36
1×265	GAVSGT 60	646 80	12AU643	358548
1×2	6AV637	6AF4 1.02	12AU7SR	35C548
2A735	GAX4GT60	6J5GT49	12AV642	35L60741
	GAXSGT60	6/661		
			1207407 00	
3050761			12AX7 61	
354 48				35250733
374, .48	68C548	65441	12AZ765	50A549
5U4G43	60E646	9980199	128472	508548
8V4G49	987548	65A7GT49	128A646	50C548
SY3GY30	68F648	65K7GT45	128A758	SOLEGTSO
574G40 57342	68G6G 1.18	65L7GT60	128E646 128Y765	Type 8040
52342	68H651	65N7GT60	128Y765	117Z333
6A840	681691	65Q7GT38	128H761	117L7GT . 1.20
6K740	68KS75	67871	1282763	11726GT68

FREE \$7.20 list value Bonus Box of three 65N7 tubes and 25 assorted resistors with each order of \$25 or more.

GIFT OFFER One 68666 tube will be shipped FREE with any order accompanying this ad.

We now have a complete line of special purpose and transmitting tubes in stock.

Write for quotations on your requirements-Dept. T.

We guarantee your orders to be shipped the same day they are received!

Minimum order \$10.00. 25% deposit on C.O.D. orders save parcel post charges. Orders accompanied with full remittance will be shipped prepaid anywhere in continental U.S.A. All orders subject to prior sale.

Send for Free complete tube listing

	SPE	CI	AL	!
while they la	2	9c	each	10 for \$2.50
Type 1A4P 1C6 1C7Q 1D5GP	Type 187GT 1F4 1H4G 2A7	Type 19 1629 22 33	Type 34 35 35/51 36	Type 37 39/44 46 49

These specials are new, famous make, in-dividually boxed. Order new.

TELTRON ELECTRIC COMPA

428 Harrison Ave., Dept. RN7, Harrison, N. J.

Phone HUmboldt 4-9848

ENJOY 3 COLOR TELEVISION FILTER SCREEN NOW

Changes dull eye-straining black and white pic high property of the picture of th

Zingo Products, Johnstown 19, New York



\$2.95 EACH OR 2 FOR \$5.00!

shone Company Upright Tel-lete with cords, in tested ed condition with 50 ft, of tape, inter-communication f tape, inter-communication Tape and wire offer for this Complete line of telephones, dial, magneto, inter-communication, etc. Write for free list. All shipments F.O.B.

TELEPHONE ENGINEERING CO.

Acrosound Ultra-Linear

TRANSFORMERS

for the ultimate in High Fidelity amplification

TO-300 for Ultra-Linear circuits with KT-66's, 807's, etc. \$24.75 TO-310 for Ultra-Linear operation 18.75 net

TO-330 for push pull parallel Ultra-Linear circuits 39.75 net TO-350 for Ultra-Linear 100 watt amplifiers with 6146 tubes Prices slightly higher in West

It takes more than a tapped output transformer to make an Ultra-Linear amplifier. It takes the exclusive patented Acrosound Ultra-Linear transformer designed for this application and crafted to the most rigorous specifications. Whether you build your own, convert an existing amplifier, assemble a kit, or buy a manufactured amplifier you can have genuine Acrosound Ultra-Linear circuitry, the finest available. Full transformer data and high fidelity circuits are available on request.

ACRO PRODUCTS CO., 369 Shurs Lane, Phila. 28, Pa.

without the need for metal encircling the wire. The insulator swings into position and locks into the metal bail through a unique hinging action. No pliers or special tools are required for installation.

NEW EXCITER

Central Electronics, Inc. 1247 W. Belmont Ave., Chicago 13, Ill. is offering a new exciter which has been tradenamed "Multiphase" Model 10B. The unit incorporates a new carrier



control which is adjustable from zero to full output, making it unnecessary to disturb the carrier null adjustments. It also contains a new a.f. input circuit for two tone tests or phone-patch input.

Peak output is 10 watts. Multi-band operation is provided from 10 to 160 meters using plug-in coils. It has voicecontrolled break-in on single sideband, AM, and PM. Switchable single sideband, with or without carrier is provided. Suppression of unwanted sideband is 40 db or better.

VOLTAGE STANDARD

Sorensen & Co., 375 Fairfield Ave., Stamford, Conn. has developed a new tubeless a.c. voltage standard which is designed for calibrating meters and oscilloscopes

The Model VRS-AC10 uses no tubes, is small in size and weight, and is extremely stable. Three ranges, 1 mv. to 100 mv.; 100 mv. to 1 v.; 1 v. to 10 v., are available at an accuracy of ± .25%. Output loading is 1 megohm or higher and the output may be shorted without damaging the instrument.

NEW PROBE LINE

Electronic Instrument Co., Inc., 84 Withers Street, Brooklyn 11, N. Y. is offering five new Eico instrument probes, three for scopes and two for vt.v.m.'s.

The Model PD is for TV waveform tracing in low-Z or low-frequency circuits. The Model PLC is for TV waveform tracing in high-Z, high-frequency, or wideband circuits. The Model PSD demodulator probe increases scope usefulness so it can be used as a waveform tracer, gain analyzer, and alignment indicator in all TV, radio, r.f. and i.f. stages. The two v.t.v.m. models are the PTP-11 or 25 and the PRF-11 or 25. The first unit permits reading of peak-to-peak voltages directly on the d.c. scales while the second unit is for r.f. measurements up to 250 mc. -30-



BOOKS for Servicement Amateurs

Servicemen **Experimenters**

RADIO . T.V. . AUDIO . ELECTRONICS

200. HOW TO USE SIGNAL AND SWEEP GENERATORS. By J. Richard Johnson. A practical handbook for the service technician, the radio amateur and the experimenter. Emphasis is on how to use the equipment, not on why it works. Lavishly illustrated, it gives test uses and discusses problems and their solutions in using this equipment.

228. TELEVISION SERVICING. By Walter H. Buchsbaum. This gives clear simple instructions on the installation and maintenance of every type of TV receiver . . . shows you how to locate and repair every conceivable trouble a TV set can have . . . offers the latest information on the design and construction of TV receivers. It also devotes an entire, new chapter to color television, showing exactly how color TV receivers differ from black-and-white receivers. \$5.95

229. TECHNIQUES OF TELEVISION PRODUCTION. By Rudy Bretz. This is a comprehensive handbook for the studio engineer and technician, covering all of the equipment and materials used in producing television programs. It deals with the television cameraman, cameras, and camera handling; TV lenses; cutting; switching equipment; technical limitations and the production problems involved; graphic materials; projection equipment; mirrors and prisms; composite shots and the illusion of space; special effects with graphic materials; studio effects; electronic effects; television scenery, make-up, and lighting; audio problems in TV; and remote pickups. 464 pages. \$10.00

230. THE RADIO MANUAL, Fourth Edition. By George E. Sterling and Robert B. Monroe. No other single volume now available covers the entire field of radio so thoroughly-from elementary electrical and radio theory to the most advanced applications in AM, FM, and Television Broadcasting, Marine Radio, and Marine Navigational Aids, Emergency Services, State, Federal and International Laws. 820 pages.

232. RADIO TROUBLE SHOOTING GUIDEBOOK, vol. 1. By John F. Rider and J. R. Johnson. A troubleshooting guidebook that covers AM, FM, troubleshooting, undesired signals, weak signals, distortion, noise, dead receivers. 140 pages. 5½ x 8½. Paper bound.

205. HOW TO TROUBLESHOOT A TV RECEIVER. By J. Richard Johnson. A step by step guide for newcomers. \$1.80

206. UHF TELEVISION ANTEN-NAS AND CONVERTERS. By A. Lytel. Latest information on all types, covers latest UHF instal-lation techniques. \$1.00



TV TROUBLESHOOTING AND REPAIR GUIDE BOOK, vol. 2. By Robert G. Middleton. A gold mine of valuable TV service information. Troublemine of valuable TV service information. Trouble-shooting front end; Servicing the Video I-F strips; Faults in video amplifiers; Trouble analysis in sound I-F and detector systems; Practical pointers in audio amplifier servicing; Trouble in horizontal circuits. 160 pages. 8½ x 11. Paper covered. Price 53.30

234. THE RADIO AMATEUR'S HANDBOOK. Compiled by the American Radio Relay League staff. 800 pages, including catalog section. Price \$3.00

235. THE SATURDAY REVIEW HOME BOOK OF RECORDED MUSIC AND SOUND REPRODUCTION. By Edward Tainall Canby, C. G. Burke, and Irring Kolodin. Here is complete, specific information on how to get the most out of improved equipment, how to choose among the wealth of new recordings offered, and how to get the ultimate in listening pleasure out of your collection. \$4.50

HEARING AIDS, THEIR USE, CARE, AND REPAIR. By M. Mandl. Provides information needed by users, prospective purchasers, dealers and servicemen. 90 illus. 158 pages.

208. MODERN OSCILLOSCOPES AND THEIR USES. By Jacob H. Ruiter, Jr., 360 pages, 370 illus. \$6.00

211. INDUSTRIAL ELECTRONICS: An Introduction to Modern Industrial Electronic Practice. By Dr. R. Kretsman. \$5.50

224. RADIO DATA CHARTS. By R. T. Beatty. Charts required in the design of radio receivers cover such items as frequency, wavelength, inductance, capacity, frequency, self-inductance, r.f. coil windings, reactance of coils or condensers, transformer design, choke and transformer design. The only equipment necessary to utilize any of the nomograms is a straightedge.

New!

4th Edition



frequency modulation to the repairing of televial sets and the explanation of an actual troub

224. TELEVISION AND FM RECEIVER SERVICING. By Milton S. Kiver. New, third edition of this famous definitive text. Explanatory material is offered freely so that the student or novice technician may derive maximum benefit from this text. Eighteen chapters cover antennas, TV receiver installation, TV test equipment, r.l. stages, video i.f. and detector stages, video amplifiers, and a.g.c. systems, CR picture tubes, servicing intercarrier receivers, using TV test patterns, deflection systems, etc. Service technicians who have come to depend on Kiver as reference will welcome this new volume.

34.20

227. TELEVISION REPAIR MAN'S TUBE LOCA-TION GUIDE. By William Prior, Jr. Almost every known make of set including over 4000 models are covered with tube location diagrams. Put it in your service kit, in your shop, in the home. Only \$1.00 221. HiGH FIDELITY SIMPLIFIED, 4th Ed. By Harold D. Weiler. A non-technical explanation of hi-fi techniques and the necessary components which constitute a hi-fi system. Covers the latest tape recorders and the newest types of enclosures and speaker systems. 208 plates. 52.50 222. HOME MUSIC SYSTEMS. By Edward T. Canby. How to assemble parts at greatest savings. \$4.00

223. HIGH FIDELITY HANDSOOK. By Greene, Radcliffe and Schaeff. A virtual encyclopedia of step by step instructions, hundreds of diagrams that make it easy, inexpensive to select, install, assemble, and enjoy your own HI-FI system for records, tape, FM, AM, TV. Expert guidance in layman's language. \$4.50

new!

214. A GUIDE TO AUDIO REPRODUCTION. By David Fidelman. An A to Z explanation of
the reproduction of sound. Discuses all phases of systems and
requirements plus design, construction, assembly, and testing
of systems and components. Explains in detail the circuitry of
preamptifiers and amplifiers;
complete discussion of phono cartridges, tuners,
microphones, loudspeakers and enclosures. For the
radio and TV service technician, engineer and esperimenter. Companion volume to Weller's High
Emplified. 250 pages.

Fidelity Simplined. 250 pages.

217. HIGH FIDELITY TECHNIQUES. By John H.
Newitt. For the engineer, home builder of audio
gear, service technician, studio personnel and professionals in the audio field. 12 chapts. in easy to
sead language.

37.50

RECORDING AND REPRODUCTION OF 216. RECORDING AND REPRODUCTION OF SOUND, 2nd Ed. By Oliver Read. A complete presentation of the entire subject of sound. Discusses modern theory and methods used in the recording and reproduction of sound, based upon years of experience and research. Includes charts and Appendix. 810 pages.

237. INTRODUCTION TO COLOR TELEVISION. By M. Kaufman and H. Thomas. Discusses color wavelengths and frequencies; primary colors and circuits used in a color TV receiver and gives complete explanations as to their operation—setting up and adjustment procedure.

22. MONTAN INTERNICE AUTO.

up and adjustment procedure. 32.10
238. HOW TO INSTALL AND SERVICE AUTO
RADIOS. By Jack Darr. This book for service
technicians discusses installation problems and special servicing requirements of the automobile
radio. It gives information on antenna installations for the car, vibrator testing, noise suppression, and it furnishes a complete list of tools, spare
parts, and other equipment needed to do auto
radio repairing and servicing. 51.90

239. HOW TO LOCATE AND ELIMINATE RADIO AND TV INTERFERENCE. By Fred D. Rowe. Both radio and television interference are discussed; why they occur and their solutions. \$1.88

FOR THE YOUNG READER

FOR THE YOUNG READER

231. ALL ABOUT RADIO AND TELEVISION.

By Jack Gould, Radio and Tolevision Editor,
The New York Times. The how and why of
radio and television are explained clearly and
directly in simple language and with over 100
illustrations and diagrams. It shows how a
picture is changed into electricity, how to
build a foxhole radio, why we have networks,
how to communicate with the moon by radar.
160 pages. 6½ x 9½.

\$1.95

When You Want a Book

Your Radio & TV News Book Service will attempt to procure any book in this field for you. Just send title, author and price. NOW ----

BARIO & TELEVISION NEWS BOOK SERVICE BOOK BY	MAI	L IMIS CO	OFOR		1
RADIO & TELEVISION NEWS BOOK SERVICE, Dept. R7				Dept. R7	

201 East 57th Street, New York 22, N. Y. I enclose \$... . . for which please ship postpaid books circled or indicated below. If not satisfied I can return them within 5 days for refund.

200 205 206 208 211 216 217 218 221 222 223 224 227 228 229 230 231 232 233 234 235 236 237 238 239

Any book not listed..... \$..... \$.....

Address

ALL ORDERS SHIPPED POSTPAID. Sorry, no COD's. Add 3% sales tax with orders for N. Y. C. delivery; add 25¢ per title for delivery outside U.S.A., except for APO's.

July, 1954

TUBES 40% TO 70% TUBES ODS/ VR150 .85 .69 .49 .49 .09 1.18 .39 1.19 .70 .70 1.25 .75 1.45 .49 .75 1.45 .49 .75 .54 .54 1L4 2B22 2C26 2C26A 2D21 2X2 3B22 3D6 5R4GY 6AK5W 6AK5W 6AL5 6AQ5 6AS6 6BA6 6BE6 6BE6 6BQ6 6C4 6D4 6H6 6J4 .50 215A 2.50 221A .50 316A 4.25 388A SCOTCH BRAND SOUND RECORDING TAPE feet (List F

SPECIAL \$2.99 SCR-274N COMMAND ARC-5 EXCELLENT RECEIVERS USED TRANSMITTERS \$8.95 12.95 ADDITIONAL EQUIPMENT BC. 456 Modulator BC. 450 Control Box (3 Receiver) BC. 451 Control Box (Transmitter) BC. 442 Relay Unit (ANT) Florible Shafting with gear to fit 1.95 1.29 1.79

1200

Single Transmitter Rack Single Transmitter Rack DM-33 Dynamotor for Command Set BC-221 Frequency Meter \$139.50 stal and tubes

MODULATED TYPE
MODULATED TYPE with ACLIPPITED TYPE WITH ACLIPITED TYPE WITH ACLIPPITED TO BRAND \$199.50 ited quantity of BRAND NEW MODULATEL REQ. METERS so Frequency Motors are factory treated, frequency alignment and GUARANTEED. \$210.00 checked

HEADSETS high impedance, BRAND with ear pads.

ow impedance, BRAND NEW ear pads, cord and Pl.54

MICROPHONE SUPER-SALE MIKE-magnetic type consisting of t MC-253, Cord CO-287, Plug PL-179 Jack JK-26
7-45 MikE Carbon Lip Mike
7-17 MikE Carbon - HRAND NEW
7-13 MANOSET - BRAND NEW
7-12 - Western Electric Carbon Hand Mike with
Cord & PL-68 Plug. BRAND NEW 3.95 4

TAKE YOUR PICK FROM THESE BARGAINS! (TALS for the BC-458 Command Transmit-, plug-in type, 6200 KC, BRAND NEW... \$1.95 dete art of COILS for BC-458 Command

....... SAVEL SAVEL SAVEL **SCR-522 RECEIVERS**

tess oscillator assembly, frequency chifter and tubes. Contains all Cails, Yransformers, Resistors, Condensers and other SPECIAL! 2 for \$10.00

****************** MINIMUM ORDER \$2.00

Immediate delivery—send 25 % deposit on C.O.D. orders. If sending full remittance, allow for postage and save C.O.D. charges. All shipments F.O.B., N.Y.C. warehouse. (N.Y.C. residents add sales

PLATT ELECTRONICS CORP. Dept. A. 489 Broome St., N. Y. 13, N. Y. PHONES: WO 4-0827 and WO 4-0828

A Bass-Boost Control

(Continued from page 53)

system without appreciable loss of high-frequency response. If this amplifier is to be mounted within one or two feet of the power amplifier, the cathode follower, V_2 , can be omitted from the circuit. The output could then be taken from C_{17} , resulting in fewer parts and a smaller amplifier

The bass-boost control consists of a Centralab type 1402, which is an 11position, single-section, shorting-type switch, small enough to fit into a twoinch-deep chassis. A shorting-type switch is necessary in order to prevent clicks when the control is turned. The original screws were removed from the switch and two 6-32 round-head machine screws, two inches long, substituted for them. Two one-inch spacers were used to mount a Cinch-Jones type 2004 4-point terminal strip on the rear of the switch. The condensers were then mounted between the switch terminals and the terminal strip which is connected to ground.

This bass and treble boost control can be added to the input of an existing amplifier if desired, instead of building the complete amplifier shown here. The parts included within the dotted lines should be wired into the amplifier in the same manner as shown in the circuit of Fig. 3. If the treble boost control is not required, R2 can be changed to a 470,000-ohm, 1/2 watt resistor and R_s and C_0 eliminated from the circuit. The grid of the tube in that case, should be connected to the junction of R_2 and R_3 .

As the control introduces a loss of 23 db at 1000 cycles, this much additional voltage gain must be available if it is incorporated into an existing amplifier. If this gain is not available then it is advisable to build the complete amplifier shown in Fig. 3.

Fig. 1 shows the underside of the amplifier as built by the author. As a 5" x 7" x 2" chassis could be easily fitted into the cabinet used, there was no need to make the amplifier compact. The treble-boost control, R_3 , is mounted in the center of the front drop of the chassis, and the volume control, R_1 , is mounted to the right. The placement of the other parts can be readily determined from the photograph.

In the installation for which this amplifier was built, 18 volts of d.c. was available for heater supply, so the heaters of the 12AU7 and the 6C4 were connected in series. The use of d.c. made it possible to eliminate cathode bypass condensers C_{12} and C_{16} and to run unshielded leads in the chassis. The polarity of the heater supply is not important and either side can be connected to ground. If the heaters are to be operated on a.c., it will be advisable to include C_{12} and C10 in the circuit and to shield the leads from the input jack, J_1 , to R_2 and those from R_2 to R_4 , in order to reduce

hum to a minimum. The heaters, of course, should be connected in parallel.

R13 acts as a hum-balancing pot when a.c. is used. If the 6.3-volt winding of the transformer in the supply to be used with this amplifier is connected to ground or to a bias voltage, this connection must be removed to prevent R_{13} from being shorted out. R_{14} and R: make up a voltage divider across the 300-volt supply to furnish a 45-volt positive bias on the heaters. C_{10} is a bypass condenser to keep the heaters at ground potential at audio frequencies.

A 5" x 7" bottom plate should be used to complete the shielding of the chassis

The plate power requirements are 6 milliamperes at 300 volts. This can be obtained from the supply for the power amplifier and should be well filtered.

Although the conventional bassboost control is simpler in design, this improved unit, by its performance, amply compensates the builder for the few additional parts required.

P.A. Rentals

(Continued from page 51)

number of years. Race tracks, football and baseball stadiums, and other seasonal operations are often customers for this rental-purchase plan.

Periodic disposal of equipment at substantial price reductions benefits both you and your customers. This way you may keep your rental equipment up-to-date and your customer gets good equipment at wholesale or below wholesale prices. In many cases you will be able to give a "new equipment" guarantee, otherwise the units can be sold "as is."

You may wish to bolster your commercial sound equipment with a line of high-fidelity audio products for home installation. A nearby interior decorator and cabinetmaker may wish to join you in a venture to design, build, and install high-fidelity equipment. Servicing such equipment can be a very profitable venture especially in metropolitan areas where hi-fi is booming.

On the assumption that it is better to work with your competitor rather than against him, you might find it mutually advantageous to lend (or rent at low cost) equipment to each other on jobs that are so large that either of you don't have enough equipment individually to handle the job. Or, on certain occasions, a joint venture may be profitable. Under these circumstances it is best to have only one of you make the agreement and arrangements with the customer as he may lose confidence in you if he feels you need help and it is easier for him to deal with only one agency.

There are so many facets to this world of sound that you will undoubtedly run across many angles that may transform what originally was a sideline into a full-fledged and booming business. -30-

JI

BI

Pioneer Amateur Station

(Continued from page 34)

what this spark sounded like on the air is hard to describe. It was generated by gas explosion and fluid flow return, and it sounded just like that. The nearest thing today is a loose wire in a pole transformer. It defies any other comparison. But we were on the air with "power."

The summer of 1912 found us in Philadelphia one day listening to a receiver with a galena (lead sulphite) crystal detector, and we got a piece to try. It worked better than the old electrolytic detector, but "setting" the "catwhisker" on a sensitive spot was a job until we learned to judge the degree of sensitivity from the pickup of a buzzer spark.

In the fall of 1912, with the messy acid of the electrolytic detector removed from the picture, the receiver was built into a cabinet. The detector and condenser switch was placed on the top and the slider operated by pulling out a knob on the end of the cabinet. This cabinet receiver survived the years, and is shown in Fig. 4. The circuit is identical with that shown in Fig. 1 with the galena crystal substituted for the electrolytic detector.

A natural question at this point is, what distance did this equipment cover? The battery-operated coil first used was of course local, not over 10 miles range, and when the power line was connected the distance was extended to occasional contacts up to 150 miles. The receiver brought in many stations up and down the coast from Boston to Key West, and many inland stations of the day. Its range depended on atmospheric conditions, as is the case with today's receivers. At night, stations all around the Great Lakes were clearly heard in West Chester.

Another question often asked: "What frequency (wavelength) did you use?" The most accurate answer is "Don't know." The only thing we had to go by

JED MANUFACTURING CO. BROOKLYN 4. NEW YORK

was the publication, from time to time, of technical articles stating that a coil and condenser of given dimensions would give you 200 meters or 300, as the case might be. No such thing as a wavemeter (frequency meter) or standard frequency signal existed outside of government bureaus and a few of the larger laboratories. With these given coils (helix) and condensers, all an amateur could do to tune his transmitter was to insert a flashlight bulb in the antenna lead, and keep moving clips on the helix until the bulb was lighted to maximum brilliancy. That, in the early days, became your working frequency. Naturally much interference with commercial services and the Navy resulted.

Much was written in the early 1920's when spark was ruled off the air about its broad tuning, and this referred to well constructed commercial transmitters as well as home-built jobs like ours. Within five miles of our direct-coupled spark, any reception below 500 meters was purely accidental.

In 1916 the author took the examination, got a license, and the call "3BV" was assigned. At the same time a "loose coupler" or receiving transformer was purchased, together with a Murdock .001 µfd. variable condenser, a Turney "Crystaoli" detector and a pair of C. Brandes "Navy" model headphones. Fig. 5 shows this new apparatus, our first factory-made gear, and the old receiver as set up at the time (1916). The new receiving apparatus was a marked improvement over the old single slide tuner, the individual tuning of the antenna and detector circuits nearly doubled the signal strength. Also the secondary of the loose coupler would slide out of the primary, sharpening the tuning. The Murdock variable condenser was shunted across the secondary of the loose coupler and gave the final touch to the close tuning of any station heard.

The really novel feature of this losse-coupled receiver was the "Crystaoli" detector. A galena crystal was mounted inside one end of the hub of a



Only from famous COYNE do you get this modern up-to-the-minute TV Home Training. Easy to follow Step-by-Step instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Personal guidance by Coyne Staff. So practical you can quickly EARN MONEY IN A TV-RADIO SALES AND SERVICE BUSINESS—part time or full time. Not only FINEST TRAINING but COSTS MUCH LESS—pay only for training—No costly extras.

SEND COUPON for DETAILS PREE SEND COUPON BELOW for Picture Folder and full details including EASY PAYMENT PLAN. NO COST OR OBLI-GATION—NO SALESMAN WILL CALL



3 For UHF-VIIF open wire

B. W. COOKE, Pros. COYNE FOUNDE

A TECHNICAL TRADE INSTITUTE CHARTERED NOT FOR PROFIT 500 S. Paulina Bopt. 84-HTS Chicago 12, Illinois

B. W. COC COYNE EI 500 S. Paul Send FRI vision-Radi	LECT lina S EE Pi	RIC it.,	Chic Chic e Fol	SCHO ago L der an	i, III., D d details	of your	
Name					******		
Address							****
City.					St	ate	



2 For VIIF flat twin leads



1) For all UHF or VHF tubular twin leads



Turn your experience into a big, new, better-paying career!

Day by day industrial plants are adding more electronic devices—for sorting, counting, checking, almost any control job you can name. Cash in on industry's great need for men who can keep these devices in top working order. Make more money, feel more secure, doing work that is second nature to you. With what you already know about electronics you have a long head start in a field just beginning to boom. GET INTO IT RIGHT NOW with the help of just beginning to boom. NOW with the help of

PRACTICAL INDUSTRIAL **ELECTRONICS LIBRARY**



Here's the practical kind of information t

How to keep the plant's tronic equipment

performing as it should How to locate and cor-rect tube and circuit rect tube and circuit troubles quickly and easily

easily

How to install, service, and maintain even brand new equipment without being stumped by new circuits

No long sessions on math theory! Instead you t: Clear explanations how tubes and tube-erated circuits work in operated circuits work in motor controls, welding controls, heat controls, etc. A complete manual that covers all mainte-nance procedures. A hand-book of 433 industrial electronic circuits with each fully described. Trou-hieshouting charts tested bleshooting charts, tested working methods, step-by-step directions—every-thing you need to start right now is here.

Contains Chute's Electronics in

Industry Miller's Maintenance Manual of Electronic Control Markus & Zeluff's

Handbook of Indus-trial Electronics Cir-

cuits
enney & Fahnestock's
Electron Tubes in Industry cuits He

Shows facts

Now to operate the vacuum tube voltmeter

How to correct ignitor mistire

How to maintain light sources for photoelectric contro

How to protect cir-

How tubes serve in conveyor synchron and hundreds more

FREE TRIAL-EASY TERMS

	W-HIII B RTN-7, 3			NYC 36			
for 10 will se paid.	days' exa nd \$2.56, (A saving) Otherwi	then \$ of \$3.5	n on ap 4,00 a r	proval, nonth i the re	In 1 intii i gular	day 122,50 price	s I
Name							1.61
Addres							
City			Zert	ie	State.		
	ed by					N-7	

small rubber disc, the opposite end of the hub being closed with a metal plug. The space between was partially filled with metal filings. This detector was "set" by slowly revolving the disc in its clips while the spark from a low frequency buzzer "cohered" the filings when a sensitive spot was found. This was by far the best crystal detector up to that time, and because of its shockproof mounting, often stayed in adjustment for a week or more.

The station remained more or less like the photograph of Fig. 5 until closed down for World War I in 1917. The author went to sea in radio during that affair and in September 1919 opened up 3BV again. This station (Fig. 6) is the same loose-coupled, "Crystaoli" detector receiver used before the War. We had worked large sparks during the War and learned something about them. A Murdock oscillation transformer was purchased and a rotary spark gap made. However we still had d.c. power, so had to continue the use of the electrolytic interrupter and spark coil. A Roller-Smith hot-wire ammeter was added to measure antenna current.

Now we were really "in business" with over 3 amperes of antenna current, the transmitter inductively coupled to the antenna, and sharp as a razor on 200 meters. We got little benefit from the rotary spark gap as the modulation of the interrupter came through and the resultant note sounded like a buzz saw striking a nail in a log. Fig. 7 shows this transmitting apparatus, now mounted in a display case, in much better detail than the general station picture.

By June 1922 the station had been completely rebuilt as far as receivers go: the vacuum-tube detector and amplifier connected through switches to a honeycomb coil receiver for long-wave. and a variometer inductively-tuned receiver for amateur and broadcast, had replaced the old loose-coupled receiver. The same old spark had been placed on the floor at the end of the table. All of the apparatus shown in Fig. 8 was home-made and was described in detail in various early issues of Radio News in 1921 and 1922.

At the beginning of 1923, the real active days of the 3BV spark ended. Shortly after the picture (Fig. 8) was taken, a.c. power became available and a 1 kw. transformer was installed. With the rotary gap it produced a wonderful musical note on the air, but by this time the need for earning a living brought the writer to Savannah, Ga. as radio supervisor of the U.S. Shipping Board. After a year or so, the YL became the OW (we were plainspoken in those days), and we started up in Savannah as 4EO-4ZD-4XX.

The first Savannah station (Fig. 9) was on the air late in 1923, first as 4EO and then as 4ZD and combined with the 4XX commercial experimental station license. This station was a 100watt Hartley oscillator c.w. transmitter on the new short-wave (high frequency) bands. Plate supply was 1200 volts d.c. from motor generators. The receiver was a honeycomb coil affair with one stage of r.f., and was written up in the July and October 1924 issues of Radio News. The transmitter was housed in the cabinet supporting the loudspeaker, the receiver in the center of the large cabinet with a Grebe detector, and two-stage audio amplifier in the right compartment.

The "X" license in those days was granted for serious experiments with short-wave (high frequency) transmissions. Generally, any wave below the 200 meter point was allowed, and most of the stations at the time gravitated to wavelengths between 75 and 110 meters. The basic reason for this selection was that available parts were not capable of withstanding the higher frequencies. Condensers, for example, of "good" quality, just burned up. We worked a lot of foreign countries and had many good U.S. contacts as well.

Late in 1924 found the family moving into their own house in Savannah where there was plenty of space for a radio room, so the station shown in

Fig. 10 was set up.

The transmitter was a rebuilt version of the previously-mentioned 100watt Hartley, remodeled to get down to 20 meters. With more room, better parts, and ventilation it worked much better. To describe the station, Fig. 10, let us start with the transmitter on the right end of the table, next comes an old Navy CM 294 receiver for low-frequency work, next a short-wave regenerative receiver, and on the left end of the table is the large panel of a 10tube superheterodyne receiver made from a BCL failure of the early days. Plug-in coils gave a range from 20 to 800 meters, with one stage of r.f. ahead of the first detector. The circuit of this receiver is shown in Fig. 12. This receiver was the result of toying with the idea that Armstrong's superheterodyne would someday be the ultimate in all receiver fields. It cost a small fortune to develop this from a complete failure. Little or nothing had been published about what the big companies were doing with superhets, although it was a well-known fact that they were working on them. In this case results, then and now, have more than justified the time and money spent on this receiver

In 1927 a move from Savannah to the North was necessitated by our getting involved in radio compass work through the superhet development. Most of the next few years were spent traveling, so that there was no more time for amateur radio. We had a try at manufacturing quartz crystals in the early days in Savannah, and got into the design of modern transmitters using crystal control in their oscillators. We had to face it, amateur radio was over for us.

What had been accomplished with all this expenditure of time and money? We were established in radio compass work as a result of the superhet, and magazine articles had paid for most of the things they described. What was

accomplished technically in the way of advancement can be partially measured by a comparison of Fig. 11 and Fig. 12 as far as receivers go. Transmitters advanced from plain open untuned sparks to excellent c.w. and phone units. Possibly the most important of all, as a group, amateurs proved that the band below 200 meters, assigned to them originally because it was believed of no value to commercial or military services, was in fact the most valuable band in the spectrum. -30-

PIONEER "BROADCAST"

By CHARLES G. COOKE Life Member, V.W.O.A.

HERE is the story of what was probably the first instance of music being broadcast by wireless.

It was in the spring of 1906 and the "USS Illinois" to which I was attached as wireless operator had just returned with the Atlantic fleet from winter maneuvers in the Carribean to Hampton Roads, Virginia.

I was on wireless watch using an electrolytic detector when I heard a spark changing its pitch to play what was clearly the first line of "Home Sweet Home".

Amazed and curious, I began a round of visitations to the wireless offices of the other ships in the fleet.

Finally, I found on the "USS Missouri" an ingenious operator with an 80 volt d.c. generator feeding a large spark coil primary through a mercury-turbine interrupter driven by a small motor, the speed of which was governed by a sliding rheostat which had been cali-brated C. D. E. F. G. A. B. and C. Thus it was only necessary to push

the rheostat slider to the desired note, wait for the speed to stabilize, and push down the key

You should remember, however, that in those days there were no wireless traffic controls, no interference, and the

sky was the limit on jabber.

-30-

SOMETHING NEW IN ELECTRONICS

to be announced

in August

RADIO & TELEVISION NEWS

POPULAR ELECTRONICS

POPULAR ELECTRONICS

POPULAR ELECTRONICS

watch for August

RADIO & TELEVISION NEWS



SINGLE SIDE BAND LE. FORMERS

APC Capacity tuned interstage 1.F. Transformer peaked at 1625 KC. Litz wire wound on powdered iron core with allow MRA Coupling Condenser excellent for Crystal or Mechanical filter for single side band. All N.W.

FLUORESCENT FLOODLIGHT

RADIOSONDE UNITS

Type AN/AMQ-1. Used by weather stations. Unit is ent into air on balloon to transmit information on emperature, moesture, and harometric pressure to the ground. All New. \$4.94 Ea.

304 TL TUBES

High Power Triode. Bulk Packed. All Checked. Special \$3.95 Ea.

-	ì	Thouse	ands!	CRY!	TALS	Thou	sands
7	•	FT-24) mental	Freq.	th Harr	listed	below	Funda in KC
370	390	410	430	449	469	486	508
372	392	412	432	451	470	488	810
374	394	414	434	453	471	490	512
376	396	416	436	454	473	492	554
378	398	418	438	456	475	494	9.14
380	399	420	440	458	477	496	514
382	400	422	442	460	479	458	820
384	402	424	444	462	480	802	
386	404	426	445	464	482	504	
388	406	428	447	466	484	506	
Each	Freque	ncy				. 6 For	\$1.0
500	KC						1.21

SOUND POWER HANDSETS

All new...... Per Pair \$18.95

FIELD TELEPHONES

HEAD SETS

TRIPODS

BC 375 TUNING UNITS

TU-26 (200-500 KC), TU-7 (4500-6200 KC), TU-8 (6200-7700 KC), TU-9 (7700-19000 KC), All with Vernier Dials, and Many useful parts Low Priced @ \$1.30 to.

POLE CLIMBERS AND BELTS

elephone Type Climbers with Leather Leg Straps. sed, Excellent Cond. Pair \$2.95 Ea. aftery Tool Belts, Leather, to use with pole climbers. sed. Excellent Cond. \$3.50 Ea.

SELSYN MOTORS

Type 5F synero Motors, used in pairs for remote fining or remote position indicators, 115 V., 60 Cy. operation, size 31.5 Biam, x 514 long.

SPECIAL A.C. MOTORS

40 Horse Power Bodine Sync. Motor, 1800 R.P.M. perstes on 110 V. 60 Cy. Has 2 shafts and fan per dange mount. Uses 5 Mrd. Camettor for starting-sed for Fan. or small Grinder, Buffer or Hobby work. If in excellent condition. sector \$7.95

MIDGET SELSYNS

ype operates from 6-12 Voits 60 Cycle. Use as both the control of the control of



PROP PITCH MOTORS

CRYSTALS

		601	S. S. W.	MATERIAL PROPERTY.	B.C - 2	œ,		. 3	Marc I	mţ	,			
1690	2050	2280	2467	2711	2900				3540	Т	38.70	_	4050	П
1705	2075	2295	2478	2725	3000				35.75		3885		4055	
1720	2082	2300	2491	2732	3010				3655		3890		4065	
1738	2090	2315	2500	2745	3023				3665		3895		4085	
1746	2105	2326	2510	2764	3027	5			3695		3905		4090	
1770	2106	2335	2514	2775	3055				3702	5	3920		4150	
1790	2131	2340	2527	2776	3077	5			3705		3925		4175	
1810	2155	2355	2540	2807	3095				3730		3935		4177	5
1830	2175	2360	2586	2816	3117				3765		3940		4210	
1850	2195	2375	2587	2831	3149				3769		3950		4215	
1870	2202	2390	2599	2851	3161				3770		3965		4240	
1890	2215	2395	2605	2863	3190		3317		3775		3985		4305	
1910	2220	2415	2625	2894	3201		3345		3790		1995		4325	
1930	2235	2422	2643	2895	3227	5	3365		3792	5	4012	5	4345	
1970	2240	2435	2665	2899	3270		3395		3807	5	4015		4380	
1990	2255	2440	2670				3412		3825		4020		4440	
2010	2258	2446		2926				5	3830		4030		4745	
2030	2275	2466	2710	2960	3311		3462		3855		4035			

PRICE 85e Ea. 8 For \$4.50, SHIP BAND FREQUENCIES 2142, 2174, 2638, 2570 Ea.

12 VOLT DYNAMOTOR

Pack, Complete New Unit liter and Relay Base. Continue in MA output or intermittent are all NEW in

RM-29 FIELD PHONES

note control unit for Transmitter or Receiver sums.

Les used in the property of the control of \$1.50, tery as field telephones. Enclosed in a metal case i with a canvas carrying lung. Ideal for House to age or Intercom. All NEW less handsets of \$8.05.

PE 104 VIBRATOR POWER SUPPLY of BC-054 Transformer, Input, 60 R 12V.D.C., tput, 6, 14 and 84 U.D.C. Pos. 1.4, 6, 12 and v.D.C. Neg.

12 or 24 VOLT VIERATOR INVESTER

o for Montile Harto, Trues, alone, in NVERTER, t. 60. Cycle is desired. Can be used on 12 Votts or. Onut, 110 V, 60 cycle, 240 wat manifest the in enclosed separate wherever for each limit take. In enclosed separate wherever for each limit take.

HEAVY DUTY 12 VOLT SATTERIES
Thor-32 VOLT 23 AMP. HOUR Battery. Use for Trucks. Boats, Bus. Mottle Radio. All New 29.98 Ea.
Willard or Prestolite 12 VOLT, 68 AMP. HOUR Battery. Use for planes, cars or Mothle Radio with Spill-proof Caps. All New, Bry Charged.

RADIO DIRECTION FINDER Receiver, Frequency Range 100 m. Sense and ds. Has Loops mounted on top with Sense and Circuits, Less power supply, In Enc. Cond.

MICA CAPACITORS

POUR PIG. A	UPRIGHT MOUR	IIIMO2
MFD Ea. 1000 V. 1 \$1.00 07 .95 .062 .90 05 .85	MFD. Ea. 2500 V. .025 2.28 .00075 1.50 .0006 1.50 .0008 1.25	MFD 80 00006 95 00005 95 8000 V. 004 3 50 002 3 28
1800 V. .078 1.25 .05 1.10 .039 1.10 .03 1.00	3888 V. 008 1.80 004 1.80 004 1.50 003 1.80 002 1.80	0015 3 25 001 3 25 0008 3 25 00075 2 75 0005 2 75 00045 2 35 0004 2 35
.03 . 2.25 .01 . 2.00 .006 . 1.50 .005 . 1.50 .003 . 1.25 .0027 5 1.25 .00125 . 1.25 .00125 . 1.00	3000 V. 000628 1.38 0005 1.25 0004 1.28 00025 1.25 00025 1.25 00008 1.00 00008 1.00 00008 1.00	.00009 1 50 7800 V. .0005 3.93 8000 V. 01. 8.95 0006 4.50 0005 4.50

FIG. B SCREW TERMINAL 1200 V. ... 2500 V.

.05	8.001	022	.83		
.04	.83	.02	.85		.50
.02	.75	.01	.75		.25
		001	.65	.003 1	25
600 V.		.008	.80	.002 1	00
01	.65		1.00.00	.0018 1	.00
047	7.5	1250 V.		.00063	.90
.0375	2.5	0.3	.95	.0004	.90
.02	.73	.025	83	.0005	.90
.0005	.45	.01	.80	.0004	.65
.00015	.35	.006.,,,,,	.60	.00025	.85
.00009	.35	.004	.00	00018	.85
1000 V.		2000 V.		.00005	.78
.01	.75	.0004	.75	3000 V.	

of one of the control of the control

	ARMY AMMUNITION CANS	milita	MIT CON	Steady Sput cent mount cred Heavy	with carry Duty Ext	with m	e. and 26	racket a feet
ll parts of buff or p	Type M-3 50 Cal. Cans 12" Long x 6" Wide x 712" Deep. Type M-1 Cans 1612" Long x 312" All aluminum with Leather Handle and Hinged Top with hasp Use for all your tools. O.D. Color, clean them \$1.50	2 3XB 10 1	MFD. MFD. MFD. MFD. MFD. MFD.	ALL D.C.	FIXED yranel C YOLTAGE 79 95 95 95 95 1	BATIN I MFD. 2 MFD. 8 MFD. 0 MFD.	1000 V. 1000 V. 1000 V. 1000 V. 1000 V.	1.28 3.95 4.98 1.50
,	PROP PITCH MOTORS for your Beam Antenna: 20 Vott to 32 folt. A.C. or D.C. Motor: It's RPM Gear, all brand New Ug H.P. as above. \$36.95 &a.	7 8 8 8 10 15 20	MFD. MFD. MFD. MFD. MFD.	600 V 1 600 V 1 600 V 2 600 V 2 600 V 2 600 V 2	95 95 25 25 95	MFD. MFD. MFD.	1500 V 2000 V 2000 V 2000 V 3000 V	1.95 1.95 3.50 3.95

Orders Promptly Filled, F.O.B., San Francisco ... All California Orders Add 3% Sales Tax ... Be not age stamps. 20% Bep. on all C.O.D. orders. All Items subject to prior sale and prices subject to change solice. On purchases under \$5.00 send full amount.

STANDARD SURPLUS

1230 Market St., San Francisco 3, Cal. Telephone HEmlock 1-3106



Installing Color Tubes (Continued from page 48)

convergence voltage shape control can be adjusted.

9. The vertical dynamic convergence adjustments affect the horizontal and d.e. convergence settings and vice versa. Again it will be necessary to spend some time and care in making all adjustments and subsequent touch ups. The author had to start all over twice during his first convergence adjustment problem, but after some practice the convergence procedure now takes only about 10 minutes.

10. As a final check, vary the d.c. convergence control slightly and see if it improves convergence at the edges. If it does, some improvement in the dynamic convergence setting is needed. When d.c. adjustments show no such improvement, the dynamic convergence controls are properly set.

In the large screen, 19-inch shadowmask picture tubes, the convergence adjustment is somewhat different since magnetic rather than electrostatic convergence is used. Between the purity coil and deflection yoke a set of three electromagnetic assemblies are located as shown in Fig. 3. In place of the three positioning magnets a single permanent magnet assembly is used which has major control over the blue electron gun. To adjust convergence in this system it is again helpful to use a dot pattern. Proceed as in the case of the 15-inch tubes up to the d.c. convergence adjustment, then follow the steps given


1. Set all dynamic convergence controls to minimum and adjust the red and green d.c. convergence potentiometers to give yellow dots in the center of the screen.

Adjust the blue d.c. convergence control and positioning magnet to obtain white dots in the center.

 Adjust vertical and horizontal dynamic convergence controls for equal color triangles along the vertical and horizontal axes.

4. Readjust the three d.c. convergence controls for uniform white dots. Slight touch ups of the dynamic convergence controls may be required. Because the convergence forces are magnetic, the a.c. through the convergence coils will look like the voltage wave-

Fig. 9. Dot pattern when the d.c. convergence voltage is too high. Here, the blue dot is on top with the red to the left and the green to the right below.

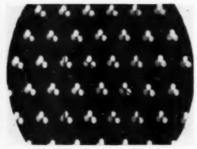

form in Fig. 6. The voltage across the coils will look somewhat like a sawtooth. Another feature of the 19-inch tube convergence adjustment is the reduced interdependence between the different controls. This makes for simpler and faster convergence adjustment.

Before looking at color pictures, the brightness and screen controls must be set properly. First, with no picture on the screen, turn the brightness control to maximum and adjust the red, green, and blue screen controls (see Fig. 5) to obtain a medium gray screen appearance. This should be approximately the brightness of an almost dark monochrome raster such as appears when no signal is received on a monochrome receiver. Balance out the three colors until a neutral gray shade is achieved. Now tune in a monochrome picture and set the contrast control for good white highlights. Adjust the blue and green background controls until the white is a true white and contains no dominant color. Next, turn the brightness control down until the white highlight is medium gray and touch up the green and blue background controls until this is again a neutral shade. The correct adjustment of these controls is achieved when the brightness control variation does not produce a change in hue, but only in brightness.

Color Adjustment

The great moment has arrived and we are ready for the first color pictures. In Fig. 5, separate red, green, and blue gain controls are indicated. Many manufacturers do not advise touch ups of these controls without special test signals or test equipment. Usually these controls are set carefully at the factory and do not need further adjustment.

Tune in a color telecast just like any other TV signal. Adjust the chromaticity control slowly until the colors appear vivid enough. Too little chromaticity will result in pastel shades or pale colors instead of rich saturated colors, while too much chromaticity will result in dark flesh tones. If it appears as if a red, green, and blue rainbow moves over the picture, the color sync section is out of synchronization. If flesh tones appear purple and red appears blue, the color sync phase is wrong. These adjustments are usually on the chassis or under a panel together with other secondary controls.

If it appears that the various colors are wrong, that red is too purple, yellow too orange, etc., this should never be compensated for with the screen, background, or brightness controls. Such a defect is best adjusted with a color test signal of known colors, such as can be obtained from a color bar generator or else from a station test pattern. Then the red, green, and blue gains can be set, the *I* and *Q* channels adjusted, and the entire matrixing unit can be serviced.

The customer should be carefully instructed in the use of the operating controls and warned against adjusting the secondary controls under the hinged front panel of the set and on the side or back of the chassis. —30—

International Short-Wave

(Continued from page 64)

(Ferguson, N. C.) Noted parallel over 4.950 to after 2215. (Miller, Ga.)

British New Guinea-VLT6, 6.130, Port Moresby, fair around 0330 with news, weather reports. (Kapp, Calif.)

Bulgaria-Sofia, 7.671, noted for a few days parallel over new 7.215 channel, but has returned to 7.255 where has news 1500-1515, 1615-1645; also says has news 1715-1730. (Pearce, England) Excellent 2000-2030 to North America on 9.700. (Rubin, Mich.) And 1730-1800 on same channel.

Cape Verde Islands-CR4AA, 7.398A, noted opening 1500 with band selections, closing 1700A with "A Portuguesa." (Pearce, England)

Ceylon-Radio Ceylon, 9.52, noted closing 1228. (Pearce, England) Is fair level on this channel some days from 2030 opening, but usually has QRM from Copenhagen, same frequency. (Saylor, Va.) Is now on 11.770 at 2030-2330. (Sanderson, Australia)

Chile-CE766, 7.66 Santiago, tuned 0045 when had music and comedy program in Spanish. (NNRC) CE1180, 11.998A, noted some days 1800-2100, fair volume in Minn. (Rowell)

China-Radio Peking. 11.65A, has news again 0930, also 0400; not audible every day; 11.96, 15.06A are used for English 2200-2228A sign-off. (Balbi, Calif.)

Colombia-HJFW, 5.020, noted 2215-2300, all-Spanish. (Reidler, Pa.) HJEF, Cali, noted on 4.76A to 2330 close-down. (Powers, O.) HJFU, 4.797A, Armenia, caught signing off 2310.

Cuba-COCQ, measured 9.670, Havana, noted 0755 with identification in Spanish, then religious service in that language. (Ferguson, N. C.)

Cuprus - ZJM6, 6.790, Limassol, Sharq-al-Adna, noted with news in (Morris, Arabic 2300-2315 fade-out. O.) The 11.72A outlet heard 2345 with news in Arabic, then music. (Sanderson, Australia)

Denmark-OZF3, 6.060, Copenhagen, noted 1510 relaying Home Service in Danish: 1600 news in Danish, off 1617 after call. (Pearce, England) Heard some days on 15.165 at 0900-1000, English 0950. (Butcher, Mass.)

Dominican Republic-HI2T, 9.735A, has good signal in Spanish 2015-2130. (Rubin, Mich.) HI4T, 5.970, good level around 1730. (Stanley, Conn.)

Egypt-Cairo tuned 0735 on 15.315, Arabic; 0800 had time pips, call in English, "Egypt Calling Her Friends in India," Egyptian and Indian songs, 0830 news; at 0900 began Urdu for Pakistan; at 1030 noted Arabic session parallel over 7.035, 12.030, and with different program near 9.745A; noted over 12.030, 7.055 as late as 1812. (Pearce, England) Measured on 12.029 recently. (Ferguson, N. C.)

El Salvador-YSS, 9.55A, noted with nice musical program 2230; slight QRM. (Winch, Calif.)

England-BBC noted opening on

ANY ONE OF THESE

HI-FIDELITY RECORDINGS

150 to 15,000 Cycles}

BEETHOVE

"Egmont" and "Coriolanus" Overtures



ZET 🖭 BACH Concerto No. 3

"Carmen" Suite

HERE is an amazing offer to lovers of fine music!
Yours FREE—any one of these magnificent recordings—brilliantly performed by the celebrated Netherlands Philharmonic Orchestra, under the baton of the distinguished British conductor Walter Goehr. These recordings, pressed from the purest "Vinylite" Plastic, represent the last word in HIGH FIDELITY reproduction. Each has remarkable beauty of tone and virtual absence of surface noise. Yet you may have any one of them FREE! OR—you may have ALL THREE records for ONLY \$1.

We make this amazing offer to introduce you to the superb new Musical Masterpiece Society record-ings. Each month you will receive notice of the two recordings selected by the Society. You may accept these records at our special price of LESS THAN ONE THIRD the usual retail price. Or you may reject any monthly selection either before or after you receive it.

There are no "strings" attached to this generous offer, and you are not obliged to buy any records

at all! So rush coupon to: The Musical Master-piece Society, Inc., Dept. 477, 250 W. 57th St., New York 19, N. Y.

Dept.		7.	25	0	W		5					eid	*	٧.	ie	16.			
Ples		sel	nd	me	0 0	he	-	iig	gh	-ti	de	lit	y	L.	P.	F	1141	ors	đ
NOTE:	H :	con	t h	Sve	0.0	he	ch	and for	l (N	E	res	CAN	d.	50	dis	B.D.	RI	u
Plea month reject. And I satisfie	y ne	ele not des	Hy Hy	8	te of	e re	ac ac ac at	Est th ord	ay In In	En And	interior	h	e.if	th ma	iy IRS	Si Ben	cet	ety of one	y' si ke
Plea months reject. And I	y ne I i may d.	not not she sm	ify ctic no reti	e con	of tol	e re	e acte	th treel	n In te fo	po po	onto	h ch	e d' I	th ma o e	ig iy ini	Sic Ben Ben Ben	e i cet pe	ety of ore	or district
Plea monthly reject. And I satisfie	y ne t i may d.	ele not dec sm	ify of in no refu	e con	te of other	ere lgr ay	e acte	in the second	n te	to be	interest	th chi	e di il	th ma o e	is co	Sic Berry Be	eci cer pl	ety ot ote	or the second

Save More Dough

e as used in t 224A Oscillos

POWER TRANSFORMER amp. Fil. FB for -79¢ plus 35c for

CERAMIC CONDENSERS
Kit of 100 asstd. Brand new, standard brands. \$10 value.

APS 13 Complete 420 MC Radiophone

\$3.95

\$14.95 VALUE RF sections, con-

DC-34 & DC-35 CRYSTALS Spacing 34"

Each 89c

CRYSTALS FT 241-A Holders L₂" Pin SPC. Marked 54th or freq. from 370 to 540 inclusive. \$4.75 postpaid

500KC Crystals 51.39 ca. 5 KC 51.39 ea.
Ship BAND FREQUENCIES 2142, 2174, 2658, 1000 KC Crystals or 200
267052.49 ea. KC Crystals ... \$3.49 ea.

rite for FREE Surplus Catalog. Thousands of items not listed. If you don't see it, write. If shipments F.O.B. warehouse, Minimum order \$3.00.

Harjo Sales Co.

GET INTO ONE OF THESE GREATER OPPORTUNITY FIELDS OLDEST, BEST EQUIPPED SCHOOL OF ITS KIND IN U. S.

Prepare for your future NOW. Get prac-tical training in TELEVISION — RADIO — ELECTRICITY—ELECTRONICS—all vital in Industry. Prepare now for a better job that also offers areal future in the years ahead. Learn on real equipment at Coyne—no advanced education or previous experience needed.

Approved for Veterans—finance plan—en-roll now, pay most of tutton later. Part time en-ployment service while training if needed. FREE BOOK Clip coupon for Hig Free Hlustrate of the China Coupon for Hig Free Hlustrate

NE " CAL TRADE INSTITUTE CHARTERES

500 S. Paulina St., Chicago, Dept. 84-85H

-	TECHNOLIA - IETEANDEM - MANIE - MELL	
ı	B. W. COOKE, Pres. COYNE ELECTRICAL School	
1	500 S. Paulina St., Chicago 12 Send FREE BOOK and det ☐ RADIO-TELEVISION	tails on:
1	NAME	
	ADDRESS	

CITY.....STATE..

Build Your Own Interior -Styled Cabinets



presenting the

paul klipsch-designed REBEL IV . . .




Now you can build your own Klipsch Corner Horn En-closure and save money identical money identical
in acoustic design
to assembled units
and easily put together with a minimum of tools.
Priced for the home-builder unfinished birch

\$36.00" Net for 12" \$42.00° Net for 15"

BASS REFLEX and EQUIPMENT CABINETS

eal housing for hi-fi compo-nts removable panels ske future changes easier, subspeaker cabinet acoustically-sioned for either 12" or 15" eaker.

Compartment 20 N., 2114" W. (inside

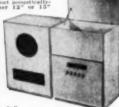

All kits include *k" white pine plywood cut to size, baffle precut for 12" or 15" speaker. Saran Plastic Acoustic lotth, Kind Acoustic Insulation, Assembly and finishing instructions,

No. 80 ...\$27.00* (Equipment Kit)

No. 8112 . \$18.00* (12" speaker)

No. 8115 .\$18.00* (15" speaker)

CORNER FOLDED HORN ENCLOSURES

of bass heretofore only possible through the

No. 61 (12" speaker) ..\$19.95* No. 43 (15" speaker) ..\$23.95*



rices higher West and South.

Write for free catalog and nearest distributor

G & H WOOD PRODUCTS COMPANY 75 NORTH 11th STREET BROOKLYN 11, N. Y.

3.975 in English for Europe 1315. (Pearce, England)

Ethiopia-Radio Addis Ababa, ETAA, 15.054AV, still has English news 1315 on Sat. only; other days has music at that time. (Pearce, England, others)

France-Paris recently has been noted opening 1000 on 7.055A with same program as in progress on 6.200; heard with English Service 1500-1600 on 6.045, 9.620A. (Pearce, England) More recently, I've noted this at good level over 11.700A. (Boord) Parallel on 9.625A. (Bellington, N. Y.)

Heard opening 0030 on 9.55; English talk 0045; QRM'd 0100-0130 sign-off.

(Balbi, Calif.)

French Equatorial Africa - Lately, Brazzaville has been using 9.625A instead of 9.440 for portions of its broadcasts; if not found on 9.440, try 9.625A. (Pearce, England, others) Radio A.E.F., Brazzaville, noted on 9.965 at 1400 with news in French, 1415 with songs. (Pearce)

French Guiana - Radio Cayenne, 6.233A, noted 1735 with popular musicals, wiped out 1800 by QRM. (Pearce, England) Heard opening 1730 in French, bad CWQRM. (Scheiner, N. J.)

French West Africa-Dakar's 9.562 channel still noted with English 1715-1730 closedown Mon., Wed., Fri., Sat.; Portuguese then Tue., Thur. (Murphy, N. Y.; Butcher, Mass., others)

Germany - RIAS, 6.005A, Berlin, noted at fair level 2030-2300 when QRM took over; news in German 2100, 2200. (Saylor, Va.) Summer schedules of Overseas' Service, Cologne, are 0530-0830, 11.795, 15.275; 0930-1230, 1300-1600, 1700-2000, 11.795, 7.290; 2030-2330 (to North America), 6.075, 7.290.

Gold Coast - ZOY, 4.915, Accra, noted in Britain with news 1215, clos-

ing 1300. (ISWL)

Greece-FBS, 7.420, Athens, strong with music 1010 tune-in, had QRM from Moscow; songs at tune-in 0115. (Pearce, England) Radio Athens, 9.607, heard with news 1245, fair level in N. Y. (Chatfield) VOA's "Truthship," The Courier, noted on 6.015 at 1945-2045 sign-off. (Butcher, Mass.)

Guadeloupe-FG8HA, 6.066A, Basse-Terre, heard through terrific QRM 1815 when identified in French and

had French music. (NNRC)

Haiti-4VCP, "La Voix du Nord." is now on 6.200, audible after 1815 when Paris-Inter leaves channel; announces as on 6.198. After a sojourn on 6.301, 4VWA, "Radio Citadelle," Cap Haitien, is back on 6.157, noted with news in French 1800. ("La Radio Mondiale," France) Latest channels announced by 4VEH, Cap Haitien, are 9.656 "mornings" and 9.675 "evenings": has new identification signal consisting of 10 notes on organ, repeated for about 5 minutes before sign-on. (Saylor, Va.) Radio Commerce, 6.090A, good from 1900 in French. (Dexter, Ia.) 4VRW, 10.074A, has English session 2130 Thur. (Pearce, Ill.)

Holland-English is now radiated from Radio Nederland weekdays only 1045-1125 to South Asia, Africa, 17.775, 15.425, 15.22, 6.025; 1645-1725 to Europe, North America, 11.73, 9.59, 6.025;

POWER TRANSFORMERS

Comb. Transformers 115V/50-60 cps. Input Comb. Transformers 115V 50-60 cps. Input CT-479 7000V 018A (2 X Ind. V. Test) 2.5V 5A 17.800 V. Test) 2.5V 5A 17.800 V. Test (2 X Ind. V. Test) 2.5V 5A 17.800 V. Test (2 X Ind. V. Test) 2.5V 5A 20.0520V 5000M 6. 3V 3A 6.3V 17.800 V. Test (2 X S V 3A 20 V

MOBILES! C.D. MEN! CAP!! PE-101 DYNAMOTOR-Converts Easily to Supply Unit Delivering 12 VOLT INPUT OR 6 V INPUT
610 V @ 150 MA OR 300 V @ 90 MA
325 V @ 125 MA 160 V @ 110 MA
BRAND NEW WITH CONVERSION DATA
53.75
Send check or M.O. Shipping charges C O.D.

DYNAMOTORS

VOLTS	AMPS	VOLTS	AMPS	PRICE
14	6.2	330	170	56.75
28	7	5.60	250	3.95
28	3.25	375	150	7.50
27	1.78	285		3.95
12	9.4	275	110	8.95
		500		
28	10	300	.260	6.95
-		150	010	
		14.5	8.	
28	19	1000	350	22.50
14	2.8			12.95
13.5	12.2		300	
		BBV	1C	12.50
18	3.2	450	.06	4.49
12	2.3	250	0.9	6.95
cellent		* Repla		PE 94.
	VOLTS 14 28 28 27 12 28	VOLTS AMPS 14 6.2 28 7 28 3.25 27 1.75 12 9.4 28 30 28 10 28 10 28 12 28 3.25 14 2.8 13.5 12.2 18 3.2 12 3.25 12 3.25 13 3.25 14 2.8 15 3.2 16 3.2 17 3.2 18 3.2	VOLTS AMPS VOLTS 14 6.2 33.0 28 7 540 28 3.25 378 28 1 7 275 28 10 300 1150 28 10 14 28 28 10 14 28 28 10 300 14 2.8 230 14 2.8 240 15 3.2 8849 18 3.2 8849 18 3.2 8849	VOLTS AMPS VCLTS AMPS 14 6 2 330 170 28 7 25 375 250 27 175 28 775 250 28 1 25 375 250 27 175 28 775 100 28 30 300 260 28 30 300 260 28 10 100 350 14 2 8 220 08 13.5 12 2 320 08 18 32 450 05 12 2 350 05

PE-218-H: Input: 25 28 vdc. 92 amp. Output: i1Sv. 350/500 cy 1500 volt-amperes. NEW ... \$37.50 PE-208: Input: 28 vdc. 36 amps. Output: 80 v 800 cy. 500 volt-amps. Dim: 13"x5½"x10½". \$22.50

COMMUNICATIONS EQUIPMENT CO.

PUT YOUR OSCILLOSCOPE TO WORK!



Modera Oscilloscopes and Their Uses e most widely used book of its kind!

326 pages 370 pictures Price \$6.00 Dust off that oscilloscope of yours! Put it to work fully on the dozens of jobs it can do better than any other instrument. Ha nd le jobs TWICE AS FAST, better and lots more profitably! This hig book, MODERN OSCILLOSCOPES AND THERE USES shows you how

in a way you can real-ly understand. Clearly and

in a way you can real-ly understand. Clearly and simply, it explains exactly where and how to use your 'scope on all types of AM, FM and TV service. Iron trouble-shooting to set re-aligning and everything in between. No fancy theory, You quickly learn how to make connections; how to adjust circuit components; how to set the controls; and how to set the controls; and how to analyze patterns fast and right! Practice from it 10 days — at our risk! See for yourself how much this clear, easy instruction can mean!

RINEHART & CO., Inc., Dept. RN-74
232 Modison Ave., New York 16, N. Y.
Send MOBERN OSCILLOSCOPES AND THERE
USES for 10-day FREE EXAMINATION. It I decide
to keep book, I will then send you 80 00 plus a few
cents postage in full payment. If bod. I will fedure

Name

City, Zone, State

Of Tride U.S.A -Cash with order only. Price \$6.50. Money back if book is returned in 10 days.

2130-2210 to North America, Australia, New Zealand, 9.59, 6.025.

Hong-Kong-ZBW3, 9.525, still has BBC news relay 0600. (Sanderson, Australia)

Hungary-Budapest's 6.248A channel noted 1720-2230, part of time relays Moscow's North American Service (English); has CWQRM. (Reidler Pa.) Noted with English 1500-1530 on 6.248A, 7.220; says also has English 1700-1730 on these channels, (Pearce, England)

India-Mysore is currently scheduled 2030-2145, 4.800, 0300-0400, 6.065, 0700-1200, 4.800. Srinagar is scheduled 2130-2330, 4.860, 0200-0330, 6.110, 0730-1145, 3.277. (Scheiner, N. J.)

Indo-China-Radio Hirondelle, "La Voix d l'Union Forces Française de Indo-Chine du Nord," 7.408, Hanoi, tuned 1035 when had dance music records; call in French 1051, then news headlines in French; closed 1100A with "La Marseillaise"; also noted from around 1730 and with news in French 1800. Radio France-Asie, Saigon, heard still on 11.83 with English-French session 0900-1100. (Pearce, England) Noted over 15.420 at 0500 with news, then good musical session.

Iran-Radio Teheran is back on 15.100 for summer, noted with call in Arabic 1330, news in German 1445. (Pearce, England) Heard with French 1500 over 15.100 parallel 3.785, 6.155. ("La Radio Mondiale," France) Should have English 1515 and close 1530A.

Iraq-Radio Baghdad. 11.700A, noted 1330 with vocal Arabic music, 1400 news in Arabic, 1415 call in English, but QRM was bad then and was jammed; should have English session 1415-1500 closedown. (Pearce, England) Heard with news in Arabic 2345, then Western music, (Sanderson, Australia)

Israel-When this was compiled, Tel Aviv, 9.010A, still had English ("Voice of Zion") session 1615-1700 closedown, but by now may be on summer time, in which case this may be one hour earlier (1515-1600). (Pearce, England, others) Heard well 1655. (Leake)

Italy-Rome's 11.905A outlet noted with news 1615, news in French 1630. (Bulmur, Brt. Columbia) The Sun. 1240-1250 period on radio subjects noted strong on 11.810, 7.290, said also on 15.400. (Pearce, England) Heard with Spanish session 2130-2150 on 6.213A. (Stark, Texas)

Japan-AFRS, 6.08, Far East Network, Tokyo, has replaced 11.815 outlet, fair signal 0400; JKL, 4.86, is parallel. (Balbi, Calif.) Radio Japan has been sending out monitoring report blanks to selected listeners. (Anglado, Miss.) Often tests over JOA3, 9.695, JOB4, 11.780, at 2300-2400 with Japanese vocal recordings, usually has no announcements, makes adjustments, stations go on-and-off, usually only parts of recordings are played; opens 2400 to North America. (Morgan, Calif.)

Kenya Colony-Nairobi, 4.855, noted 1430 with orchestral recordings. (Pearce, England)

NEW ITEMS

* RECORDER FOR CODE TAPES

BC.791—Recorder and Ampliner of Code Signals directly from a Radio Receiver or local sending on %; Paper Tape with ink writing stylus. Tape can be played have 2,117976T Tubes. 115 Voit 60 eyele operation. No Tubes, Tape, or Tape Puller included. Tape Puller from TG-10 or TG-34 can be used.

PRICES-NEW: \$7.95 - USED: \$4.95

* PRACTICE CODE TAPES

Co.e Training and Practice Inked Paper Tages on 16 MM 400 ft. Reels for telegraph and radio operation. 15 Reels to a Set. in wood case—for use with TG.34A and TG.10 Keyers. and TG-10 Keyers.
Complete SET—Price..... \$12.95

SEPARATE TAPES for following lessons:

Tape #11-Traffic Tape #8-Code Groups
Tape #12-Traffic Tape #2-Receiving Each on 16 MM Reel, in metal container: \$1.25 Ea.

TG-34A KEYER: 119 or 230 V. © 50 to b0 cycle—KEYER TG.31A is an automatic unit for reproduction audible code practice signals previously recorded in ink on paper lape. By use of the self contained speaker, the unit will provide code practice signals to one or more persons or provide a keying oscillator for use with a hand key. The unit is compact, in purtable carrying case, complete with tubes, 10°, 2° 1.3 hare speaking manual. Size: 18°, 10°, 2° 1.3 hare speaking manual. Size: 18°, 10°, 2° 1.5 hare speaking manual.

BRAND NEW: \$24.95 . USED: \$14.95

TG-10 KEYER: Same function as TG-31A, only larger, using 2(687-2/616-2/681/--1/5046 Tules and 1/923 Photo Cell. Housed in standard Metal Cabinet, can be removed for 19" rack mtg. Size: 11" H x 24" W x 181½" D.

PRICES-NEW: \$29.95 - USED: \$19.95

BLOWERS-115 VAC 60 CYCLE



DUAL TYPE: 100 CFM. 4 take: 2" Dis. Each Side. plete Size: 8" x 6". Orde 1C880

COMPACT TYPE: 108 CFM hotor built inside squirrel cape. to built inside squirrel cape. Type: 108 cfm No. 2C067 M x 8½ M x 8½ M x 8½ D D. Order No. 2C067 FLANGE TYPE: 140 CFM, 3½" intake: 2½" Dis-Complete size: 7½" W x 7½" H x 6¾" D. Order No. 10007

FLANGE TWIN: 275 CFM, 4½" intake; 3½" x 3" Dis Complete size: 11½" W x 8½" H x 8-1/16" D. Order No. 2069

TRANSFORMERS-110 V. 60 CYCLE PRI.:

*** TAM STORMERS*** THU Y, 60 CYCLE PRI.; 5 Valt CT-25A = 10,000 V, Ins. OPEN FRAME = 6.5 X 1.4 Amp. 1.25 24 V, I Amp. 1.24 V, ½ Amp. 1.50 6, 24, or 30 V, 8 A, 5. Sec. Two 12 V, 4 A. Winding—Gives 12 V, 8 A, 6. CT 24 V, 4 Amp. CONSTANT VOLTAGE TRANSFORMER-IIS V. 60 Cycle 80 VA. Sola # 30726

SOUND POWERED HEAD AND CHEST SET



TELEPHONE WIRE FOR THE ABOVE

COMBAT TYPE-2 Cond. Twisted, Rubber Covered Medium Weight, W-130...... @ to per Ft. FIELD WIRE-2 Cond. Twisted, Weather- \$4.75 proof, Heavy Duty, W-110-525 Ft, Roll.

ANTENNA EQUIPMENT

MAST BASES-INSULATED: MP-22 BASE — (Illustrated) Ins. spring action: direction of bracket can be raised or lowered easily.

MP-132 BASE-I" heavy coil spring: 2" Ins. Overall length: 11/2". Weight: 234 lbs. \$3.05

MP-S-33 BASE—Insulated type with heavy coil spring and 5" dia. Inc. Requires 2" hole for mounting. Weight: 9 lib. MP-48 BASE-Insulated type oil spring. Requires 12 mou with heavy coil spring.

MP-37 BASE—Insulated type with heavy coil spring
7" dia. insulator; requires 1%" bele for mounting
Weight; appres 10 by

MAST SECTIONS FOR ABOVE BASES:

Larger Diameter Section: MS-54

ARC-5 COMMAND FOUIPMENT:

R-25 ARC-5	Rec. 1.5 to 3 MC.	No Tubes	Used:	\$14.95
R-26 ARC-5	Rec. 3 to 6 MC.	No Tubes	Used:	7.85
R-27 ARC-5	Rec. 6 to 9 MC.	No Tubes	Used:	6.95
R-28 ARC-5	Rec. 100 to 156 M	C. No Tubes	Used:	12.95
T-20 ARC-5	Trans. 4 to 5.3 8	IC	New:	16.85
	Trans. 7 to 9 MC			

274-N COMMAND EQUIPMENT:

BC-454 Rec. 3 to 6 MC	£ 19.195
BC-455 Rec. 6 to 9 MC	9.95
BC-458 Trans, 5.3 to 7 MC	58.165
BC-459 Trans. 7 to 9 MC	10.95
FT-225 Mtg. F/BC-456 Used: 50c New:	.95
FT-220 3 Rec. Rack Used: \$1.50 New:	2.50
FT-221 3 Rec. Shock Used: .50c New:	.95
BC-450 3 Rec. Cont. Box Used: \$1.50 New:	2.00
BC-451 Trans, Cont. Box. Used: \$1.00 New:	1.50
PLUG-Male for rear of Rec. or Trans	.05
DM-32 Dynamir F Rec. 24V. Used: 32 95. New:	6.95
DM-31 Dynamir F Modulator & Trans. Used:	2.95

Coaxial Cable & Connectors



CD-1071 CORD—With PL-259 Plugs each end, Re-movable Vinylite covering over Plugs, 50 ohm reax 2 F1. long. Prices: Spé Each—Or in Lots of 18 @ Spé Each.

PL-259—Plug ea. end & 32"—RG-54 U—S8 ohm Site UG-21/U—Plug ea. end & 32"—RG-11/U—75 ohm And UG-22 U—with 4" Coaxial Cable.

RG.6. U (SPECIAL) 51.5 chm. Same size as RG.6. U, Prices I to 100 ft @ Sc per ft.—100 to 500 ft. @ 7 to per ft.—500 to 1000 ft. or 7¢ per ft.—1000 ft. Rolls (or more) or 6 kgc per ft.

DYNAMOTORS

PE-101 DYNAMOTOR—6 or 12 Volt. (Reprints of original CQ conversion articles—Oct. 4 Dec. "52 issues—furnished.) This is the Dynamotor the Hams have been talking about! Easily adapted to supply 625 V. © 150 MA. and 325 V. 125 MA. © 12 Volto—7 306 V. 30 MA. and 160 V. 110 MA.

8.94	PU	T	OUTPU	T:	STOCK	PRIC	ES:
V	LT	8:	VOLTS:	MA.	Nia.	USED:	NEW:
1.4	VD	C	230	90	DM-21	\$6.05	
1.8			330	150	BD-87	6.95	\$8,95
1.4			250	50	DM-25	6.95	8.95
14			1000	350	BD-77	14.95	29,95
28			210	125	DY-22	7.95	
12	or	24	500	50	USA 0515		4.95
12	ac	24	275	110	USA 0516		4.95
6	10	12	500	160:	PE-103	29.95	39.95
12			230	90	PE-133	6.95	8.95

Address Dept. RN · Minimum Order \$5.00 · Prices F.O.B., Lima, O. · 25% Deposit on C.O.D. Orders

RADIO SA 132 SOUTH MAIN ST. LIMA, OHIO

Something NEW in Electronics to be Announced in August Issue



Free!


Get More Service Calls with EICO DECALS

For Store Windows & Cars. Write EICO Brooklyn II, N.Y. Dept.RD-7

LEARN TV SERVICING

Dept. 8-74.

WESTERN TELEVISION INSTITUTE

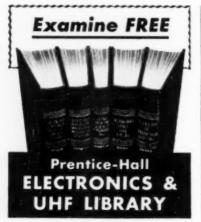

Edited by W. L. EVERITT

Pay Easy Installments If You Keep Set

Turn to this new, up-to-date Library with complete confidence, for dependable facts on any phase of modern electronic theory and practice. These volumes, by outstanding authorities, give you thorough guidance—clearly written, logically arranged, profusely illustrated.

Electronic Fundamentals and Applications By Prof. John D. Ryder, Univ. of Illinois

Complete, logical, easy-to-follow treatment of (a) physical principles underlying electron tubes, (b) the characteristics of vacuum tubes, (c) all basic tube streams. Includes: Electron Ballictics. Cathode-Ray turn tubes, but the streams of the complete streams of the c

Electromagnetic Waves and Radiating Systems

By Prof. Edward C. Jordan, Univ. of Illinois Covers entire field of electromagnetic engineering, heludes propagation as well as radiation and transnission. Full treatment of UHF transmission lines, wave guides, antennas, slot antennas, radiation and diffraction, ground-wave and sky-wave propagation.

Ultra High Frequency Engineering By Thomas L. Martin, Univ. of Arizona

Theory and technique of ALL the new fields of electronic engineering: Radar, Televinetring, Electronic computing, Farsimir, Television, Blind landing systems, Pulse-time modulation, Ionosphere measurements . . and the others.

Networks, Lines and Fields By Prof. John D. Ryder, Univ. of Illinois

By Prof. John D. Ryder, Univ. of Illinois.

Network transformation and theorems, Resonance, Impedance transformation and coupled circuits. Filter, General transmission line. High-Frequency line, Iransmission of the electromagnetic field. Radiation, Transmission and reflection of plane waves at boundaries, Guided waves between parallel planes. Wave

Elements of Television Systems By George E. Anner, Univ. of Illinois

Complete hasic theory, plus current practice, covering: Closed TV Systems. Commercial Telecasting Systems. Color TV Systems Gives clear exposition of all phases of picture transmission, including the new technique of dot interlace.

SEND NO MONEY-EXAMINE FREE

Just mail coupon below to get complete 5-Volume Set on 10 DAYS FREE TRIAL. If not completely satisfactory, return in ten days and owe nothing. Or keep the set and pay only \$5.35 down and \$8 a month for five months until full price of \$15.35 is paid. Decide for yourself—without risk or obligation—just mail coupon to examine Library ten days free.

PRENTICE-HALL, Inc., Dept. M-RTN-754 Englewood Cliffs, New Jersey
Send me the Prentice-Hall ELECTHONICS & UUR I IBRABY 5. Volumes: for ten days, free examination, If fully satisfied in fer days I will send you \$3.55 plus few couls postage and then \$8 a month for five return the Library in ten days and owe nothing,
Name
Address
City and State

Malaya BFEBS, 15.435, Singapore, strong 1115-1145 relaying BBC; before closing 1150, gave schedule for India 0800-0900, 15.435, 0915-1030, 11.820, 1030-1130, 15.435, 11.820; for Burma 11.955, 7.120, 0815-0900, 0800-0815 7.120, 0915-1130, 9.690, 7.120; had "Radio Newsreel" from BBC 0900, then program in Burmese on 11.955. (Pearce, England) Heard on 11.820 at strong level 0715-0900 sign-off in English, relaying BBC, announced 15,435 in parallel; also announced new channel of 7.955 with different program in English 0800. (Miller, Ga.)

Radio Malaya, 7.200, Singapore, noted 0630 with news. (Sanderson, Australia) Kuala Lumpur, 6.025, heard 0915 with talk in English. Forces Broadcasting Service, 5.010, noted with native music, woman announcer, bad QRM, 0830. (Morgan, Calif.)

Monaco—Radio Monte Carlo, 7.349, noted in English 1735-1800A closedown some days. (Stanley, Conn.)

Mozambique—Radio Clube de Mocambique, Lourenco Marques, has negotiations under way for the purchase of another 10 kw. short-wave transmitter and a 50 kw. medium-wave transmitter. (Scheiner, N. J.)

Nepal—Scheiner, N. J., has received word from officials of Radio Nepal. Kathmandu, that the station has never tested on 9.856 as reported by overseas sources; the new m.w. 250-watt transmitter likely will be used by August, but the new 5-kw. s.w. outlet will probably not come into use before next year. Is scheduled on 7.100, 250 watts, 2200-2350, 0250-0420, 0630-0720 with programs in Nepali, Newari, Hindi, English (latter 2340-2345, 0650-0655).

New Zealand — Summer schedules direct from Radio New Zealand read to Australia 1300-1545, ZL18, 9.52; 1600-2345, ZL19, 11.83; 0000-close, ZL18, 9.52. To Pacific Islands, 1330-1545, ZL2, 9.54; 1600-2345, ZL3, 11.78, 0000-close, ZL2, 9.54; closedown currently is 0545 weekdays, 0620 Sat., 0500 Sun.

Nigeria—Radio Nigeria, 4.800, Lagos, noted 1515 with African vocal music; 1430 had short story in African dialect. (Pearce, England) A Nigerian outlet is noted on 4.890A with English program of music 1500-1715. (Peddle, Newfoundland)

Norway—Oslo's 15.175 outlet heard at good level Sun. 1100 with religious program, at 1200 with "Norway This Week" (English). (Jones, N.C., others)

Outer Mongolia—Ulan-Bator-Choto, 6.250A, noted 0953 with man in Eastern language; 1000 gave call, had slow news in Eastern language, probably Mongolian; off 1022 with anthem. (Pearce, England)

Pakistan — Radio Pakistan, 7.010, noted with news 1015-1030; at 0515-0530 on 17.770 with "Radio Reel" in English; with news 0730 on 17.71. (Pearce, England) Heard on 7.150A with news 0730; on 11.726 at 2115 with news. (Sanderson, Australia)

Paraguay—ZPA1, noted on 5.95A at 1830, fair level in Spanish. (Chatfield, N. Y.) Moved from 6.275. (Stark, Texas)

Peru—OAX4V, 5.89, Lima, noted in Spanish, fair level 2000. (Chatfield, N. Y.) Lima's 9.562A outlet heard 2350-2400 when closed at strong level. (Deuring, Alberta)

Philippines—DZH9, 11.855, Manila, noted with news 1300, then religious program in Indonesian to 1330, followed by Japanese; identified in English 1330, 1400. (Bulmur, Brt. Columbia) DZH7, 9.73, noted 0700, news 0715. (Waltz, Washington) DZH5, 9.690, Manila, is sometimes good level

NEW TV STATIONS ON THE AIR

(As of June 25, 1954)

The following new stations bring the lists published in previous issues up to date.

STATE, CITY	STATION	CHANNEL	FREQUENCY RANGE (IN MC.)	WAVELENGTH (IN FT.)	POWER*
Colorado					
Grand Junction	KFXJ-TV	5	76-82	12.74	1.45
Oklahoma					
Ada	KTEN-TV	10	192-198	5.08	252
Enid	KGEO-TV	5	76-82	12.74	100
Texas					
Beaumont	KBMT-TV	31	572-578	1.72	18.6
Territories					
San Juan, P.R.	WAPA-TV	4	66-72	14.61	56
San Juan, P.R.		2	54-60	17.8	100
Mexican Border					
duares	XEJ-TV	5	76-82	12.74	.5

KITO-TV, channel 18, San Bernardino, California: WTAC-TV, channel 16, Flint, Michigan; KACY, channel 14, Festus-St. Louis, Missouri; XELD-TV, channel 7, Matamoras, Mexico; CMTV, channel 11, Havana, Cuba, have gone off the air. WKLO-TV, channel 21, Louis-ville, Kentucky; and WFPG-TV, channel 46, Atlantic City, New Jersey, have been temporarily suspended.

Station WAAB-TV was listed incorrectly in the May table; it should have been:

Massachusetts
Worcester WAAB-TV 20 506-512 1.94 74

The frequency of the video carrier = 1.25 + channel lower freq. limit. Total number of TV stations now on the air in U.S.: 383 (131 of which are u.h.f.).

*From Station CP application.

in Japan around 0500; DZH2, 9.640, Manila, noted 0645-0730 in Spanish, then with English identification. (Japanese Short Wave Club)

Poland-Warsaw has English for North America 0600-0630, 9.570; 0715-1945-2015, 11.740; 1715-1745, 2315-2345, 0030-0100, 6.025. (ISWC London) Good on 11.745 at 0715-0815. (Pearce, Ill.)

Portugal-CSB51, 12.875, noted with native music 1730. (NNRC) Emissora Nacional, Lisbon, uses 11.96A at 0945-1200; opens 1200 on 9.795; noted on 11.915A at 1000; (Pearce, England) Rowell, Minn., notes CSA27 now on 9.746A at 1900-2100 at good volume in Portuguese to North America.

Portuguese Guinea - CQM, 5.839, Bissau, heard 1645 with popular recordings, announcements in Portu-

guese. (NNRC)

Roumania - Bucharest noted with English 1430-1500, audible on 6.143A, 6.210, 9.252A, 9.570, 12.032 (latter QRM'd by Cairo's 12.030A channel). (Pearce, England) Has folk music 1100 on 9.570, announced in English, French, German. (ISWC, London) Heard with English 2200-2225A, news 2220, on 9.57 parallel 6.143A, nice level. (Saylor, Va.) And 2330 on 9.57. (Sanderson, Australia, others)

Sao Tome—CR5SB, 17.677, noted Sun. from 0700 to 0740 fade-out. Should close 0800. (Ferguson, N. C.)

Sarawak-Malmo DX-aren, Sweden, says, "Radio Sarawak will begin its radio service soon, but only with a weekly program produced by Sarawak Broadcasting in Iban for the Sarawak Rangers in Malaya; the program is recorded in Kuchen and flown to Singapore for reproduction over the Forces Broadcasting Service transmitter on 5.010; will be radiated on Friday evenings (Friday mornings EST)."

Saudi Arabia-Revised schedules of Djeddah are 2300-2355, 3.990, 6.100, 6.175, 7.120, 9.650; 0700-0730, 1045-1135, 1215-1315, 3.990, 11.640, 11.750, 11.850, 11.950, for Arabic; Urdu 0800-0840 on 11.950 only as is Indonesian 0900-0940. (Scheiner, N. J.)

South Korea-Pusan, 7.935, heard 0600 with man in Korean, fair strength but with QRM. (Morgan, Calif.; San-

derson, Australia)

Spain-Valladolid, 7.006, noted opening with marches 1402. Radio Mediterraneo, Valencia, near 6.995, noted 1350 with Spanish news and sports results, call 1400, good signal. (Pearce, England) After trying 9.585 for some time, Radio Nacional de Espana, Madrid, is back on measured 9.356 (announces 9.363) with English 1515, 1800, 2215A. (Ferguson, N. C.; Shundberg, Ill.; others)

Spanish Morocco - A short-wave transmitter of 1 kw. on 6.067 soon will relay m.w. programs of Radio Dersa, 904 kc., Teutan, 5 kw., with Spanish 0700-0900, 1100-1300, 1500-1900; Arabic 0900-1100, 1300-1500. (Scheiner,

Sweden-Radio Sweden, 9.535, is strong in Utah 2200-2330 or later. (Woltjen) Heard opening in English for Eastern North America 0700 on

HARVEY Always Has It

STEWART-WARNER

PORTAFONE

Model 73 Citizens 2-Way Radio

A lightweight, self-contained radio receiver and transmitter. Has a trans-mitting and receiving range from several hundred yards to several miles, depending upon terrain. Any U. S. citizen over 18 years of age can easily secure a license for this approved equipment. No technical knowledge

ortafone weighs only 28 ounces and fortaine weighs only 28 ounces and fits comfortably into the hand, Power can be obtained from several supplies. The Partafone Handy Battery Pack is for portable use. The Central Station Power Pack is for use where 115 volt AC is available. The Partafone Citizens Radia Power Pack is for use with automobile storage hatteries.

Pertatane Model 73, per pair, including antennas and carrying cases (less \$199.50 batteries or power pack)

Add Fed. Excise Tax 7.00 andy Battery Pack Central Station Power Pack Citizens Radio Power Pack (specify 6 or 12 volts)

TV SPECIAL!

each \$490 Same as used in the RCA 630TS and 8TS30 television chassis. Has 21.25 oc sound, and 25.2 mc video outputs, Ideal for servicemen, experi-menters, etc.

lete with 3-616 tubes

HI-FI SPECIAL Brand New . . . In Factory-Sealed Cartons

WESTERN ELECTRIC 755-A



8-inch PM High Fidelity Speakers

Reproduces entire audible frequency range with wide angle high frequency distribution. This famous speaker is offered at a fraction of its original price.

WHILE THEY LAST.



SPEAKER **ENCLOSURE**

Rookshelf Model S-R-U

An ideal enclosure for the 8-inch Western Electric 735-A. Small enough to be inconspicuously mounted on a bookcase shelf. Reproduces amazingly clean bass fundamental. Dimensions: 11" high x 10" deep x 23½" long.

\$24.50 Model 5-8-U for 8" speakers

SONAR SONAFONE

Portable and Marine Radiophone Model M4W



Compact, A-channel, 2-way radio telephone. Has built-in antenna, speaker, and re-chargeable batteries. Weights under 20 lbs. Transmitter range: 5 to 50 miles. Cevers Coast Guard, telephone and two ship-to-ship channels.
Complete (less crystals)
Fed. Tax 6.62 \$198.50

Battery Charger

TIONAL NC-98 RECEIVER

\$149.95

and built-in Power Supply (less speaker)



in matching cabinet_\$11.00

Anywhere in the world order by mail direct from Harvey. Enclase estimated shipping charge.

Excess will be refunded. NOTE: Prices Net, F.O.B., N.Y.C. Subject to change without notice. Generous Trade-In Allowances On Your Present Equipment.

RADIO COMPANY, INC.,

103 W. 43rd St., New-York 36 - JU 2-1500

RECEIVING

THREE TOP BRANDS ONLY! AT TREMENDOUS SAVINGS OVER REGULAR WHOLESALE

OTHER TUBES AVAILABLE AT SAME LOW, LOW PRICES


Latest Code Dates . Boxed . Fully RTMA Guaranteed 12AU7 .85 12BA6 .73 12BA6 .78 12SA7 .80 12SK7 .77 12SQ7 .67 35W4 .49 35Z5 .51 50L6 .75 .62 6AKS 1.30 .95 6ALS .63 1.06 6AQS .76 .63 6AU6 .67 .48 6AV6 .60 .80 68A6 .71 68Q7 1.42 68Z7 1.52 6CB6 .76 6J6 .92 616 6K6 .63 6AV6 .60 6K6 .65 125K .80 68A6 .71 65N7 .85 125Q 1.25 68C6 1.98 6V6GT .75 35W .83 68K7 1.28 6W4 .75 35K 1.40 68Q6 1.42 12AT7 1.05 50L6

Send for FREE catalog of additional tubes and parts

Brand New Pix Tubes Full One Year Guarantee

STUART ELECTRONICS DISTRIBUTORS

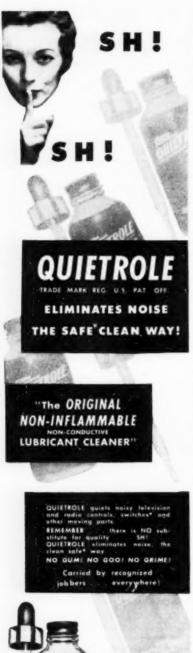149-09 Union Turnpike Flushing 67, N. Y. OLympia 8-3553, 4352 Dept.—8-7 Minimum Order \$19.00 OLympia 8-3551, 4352
TERM\$: 25% Check or Money Order, Balance C.O.D., F.O.B. New York. Satisfaction Guaranteed or money back in 10 days.





Spartanburg, South Carolina

11.705 (moved from 15.155 for summer); and on 9.620 to U.S.-Canada 1900-2145, moved from 6.065. (Saylor,

Switzerland-United Nations Radio, Geneva, HBQ, 6.675, noted opening 1315 daily except Sat., Sun.; Eng. 1330 Mon., Wed., Fri., French Tue., Thur. International Red Cross Committee, Geneva, tested recently on 7.210 at 0100, 1700, and at other times in various languages including English. (Pearce, England) During summer, Berne is using only 6.165, 7.210, 9.535 to North America 2030-2300. (Foster, Ill., others)

Taiwan-H. P. Tsong, acting general manager for Broadcasting Corporation of China (Taiwan), has sent Scheiner, N. J., these complete schedules for stations operated by the Corporation—"Voice of Free China," Taipeh. 2200-0100 to America, mainland China, Korea, Japan, South Sea Islands, Southeast Asia, BED3, 15.235, BED6, 11.736 (50 kw.), (English 2205-2230, 2335-0000); 0530-1200 for mainland China, Japan, Korea, South Sea Islands, Southeast Asia, BED6, 11.736 (50 kw.), BED7, 7.130 (20 kw.) from 0800; 1400-1600 for Europe and Near East (English 1420-1445), BED4, 11.920 (20 kw.). Armed Forces Radio Station, BEC22, Taipeh, 7.000, 1.5 kw., Chinese; BED24, Kachsiung, 11.350, 1.5 kw., Chinese; BEC26, Tso-Ying, 10.300, 1.5 kw., Chinese for local area and Chinese mainland, all at 1730-1030. Broadcasting Corporation of (Home Service), Taipeh, BED29, 6.095, 3.5 kw., Chinese 1730-1030. "The Voice of Justice." Taipeh, in Chinese, BEC36, 7.300, 3 kw., 1700-1230. The Japanese Short Wave Club says BED29, 6.095, has English daily except Sat. 1800-1850 parallel m.w. 860 kc., announces "This is the Taiwan Broadcasting Station in Taipeh." Morgan, Calif., notes BED32, 9.785A, at 0320 with woman in Chinese.

Tangier-VOA's relay of Radio Maroc. Rabat, 15.205, noted opening 0730, woman in English, man in French and Arabic; then had Arabic vocal music; 0800 news in Arabic; closed 0930. (Pearce, England, others) "Radio Voice of International Evangelism, Tangiers," near 7.305, heard opening in English and Spanish 1500, closed 1600: says on air 0800-0900 Sun., 1500-1600 weekdays. (Pearce, England) Heard in N. Y. closing 1604A, weak level. (Bellington) The Danish commercial station, Danmarks Reklame Radio. Tangier, has been heard again in Britain on 7,300A at 1615. (Radio

Sweden)

Thailand-Heard in Australia with news in Thai 1900 on HSK7, 11.910A. (Sanderson)

Turkey-By this time, Radio Ankara should be using 15.160 instead of 7.285, parallel 9.465, for English to Western Europe-Britain 1600-1645. Technical University of Istanbul, 7.030, tuned 1435 when had classical music; off 1502 with orchestral selection. TAV, 17.825, noted opening to Southeast Asia 0830, off 0915. (Pearce, England) TAT, 9.515, still good to North

America in English 1815-1900, (Strong,

Md., others)

Uganda-Radio Kampala is scheduled 1000-1230 on 5.026. (ISWC, London) Is now using 500 watts, to be increased to 11 kw. later this year. USI (Indonesia)-YDF6, 9.710, Djakarta, noted with recorded popular

tunes, woman in English, 0630-0700, then with Chinese-language session in beam to Australia-New Zealand-Philippines. (Bulmur, Brt. Columbia) Has news 0615, good level in Va. (Saylor) Excellent in English 0930-1030. (Kapp, Calif.) Heard over YDF8, 9.865, 1330 with call in Dutch, popular musicals; 1400-1500 in English; parallel on

11.785A. (Pearce, England)

USSR—Noted with English 1400-1630 on 9.74, 9.595, both good level. (Balbi, Calif.) Heard on measured 9.736 in English 1500, closed 1557. (Ferguson, N. C.) Heard on 7.215A at 1800 with news at strong level. (Winthrop, N. Y.) Noted on 9.735A with English for Europe at 1432 tune-in. (Bellington, N. Y.) Home Service heard on 11.840A at 2200-2400. (Bulmur, Brt. Columbia; Morgan, Calif., others)

Yugoslavia - Radio Belgrade noted with news 1339-1345, 1745-1800 on 7.200, 6.100. (Pearce, England)

Press Time Flashes

The NNRC reports that a low-powered station will be opened in the 6mc. band sometime during the year on Tarawa in the Gilbert and Ellice Islands group; the information came to Legge, N. Y., from C. W. Adams, Chief Wireless Officer, Betio, Tarawa Island, who operates amateur station VR1A in the 20-m. ham band.

Radio Athens sent schedule of 0215-0630, 0700-0800, 1000-1100, 1130-1145, 1200-1300, 1330-1430, all on 9.607; 0830-0945 on 6.177. TAZ, Izmir, Turkey, listed for 6.600, noted nearer 6.525 recently 1145 with Western popular music; at 1200 relayed news in Turkish from long-wave TAR, Ankara. (Pearce,

England)

WRUL officials say that recently added goodwill broadcasts have received high commendation from listeners in North America, Latin America, Europe, and Asia; listener response has increased to such an extent that some of the public service programssuch as news reports and stock market reports-have attracted new sponsors, station officials advise.

New schedule for Radiodiffusion National Khmere, Phnom Penh, Kingdom of Cambodia (Indo-China) received direct from station officials lists 6.090, 10 kw. (has increased power), at 1900-2000, 0000-0200, 0600-0915. (Scheiner, N. J.) By this time Israel's new 50 kw. (Israeli Post Office) transmitter should be in use by Tel Aviv. Radio Sweden's summer schedule is 0600-0645, 15.155; 0700-0745, 0800-0845, 0900-1045, 1100-1145, 11.705; 1200-1245, 1300-1400, 15.155; 1800-2100, 9.535; 1800-1845, 11.705; 1900-2145, 9.620; 2200-2245, 2300-2345, 0000-0045, 11.705; 0100-0200, 15.155; European Service 1500-1700, 6.095; "Sweden Call-

GREATEST TUBE BUYS

Every Tube GUARANTEED 6 Months

BRANDED—BULK PACKED IN ORIGINAL MFR'S NESTED CARTONS OR INDIVIDUALLY BOXED

EVERY TUBE METER & CHASSIS TESTED FOR TOP QUALITY

-	0Z4 .49 1U5 .38 6BG6G 1.10 6SR7 .49 7Y4 .40 19T8 .61 1A4P .35 1X2A .65 6BH6 .45 6T8 .57 7Z4 .45 22 .35 1A5 .30 2A5 .39 6BJ6 .46 6U7 .49 12A6 .39 25AV5 1.05 1A7GT .45 2A7 .35 6BL7GT .65 6U8 .59 12A7 .98 25BQ6GT .75 1B3GT .65 2X2 .39 6BN6 .88 6V3 1.04 12AT6 .31 25L6GT .40 1C5GT .39 3LF4 .71 6BQ6GT .69 6V6GT .38 12AT7 .57 25Z6GGT .37 1C7G .35 3Q4 .48 6BQ7 .88 6W4GT .41 12AU6 .34 32L7GT .39 1D7G .35 3Q5GT .48 6C4 .31 6W6GT .41 12AU7 .59 33 .29 1E7GT .35 3V4 .46 6C5GT .41 6X4 .35 12AV7 .60 34 .29				
OA4G \$.50		6BF5 \$.69	65Q7GT \$.37	7X6 \$.57	19BG6G \$1.15
	1U538	6BG6G . 1.10	6SR7 49	7Y4	19T8 61
1A4P35	1X2A65	6BH645	6T8 57	7Z4 45	22 35
1A5	2A5 39	6BJ646	6U7 49	12A639	25AV5 1.05
1A7GT45	2A735	6BL7GT .65			
183GT65	2X2	6BN688	6V3 1.04	12AT631	25L6GT .40
1C5GT39		6BQ6GT .69			
1C7G35	30448				
1D7G35					
1E7GT35	35446				
1F4		6C649			
			767 43		
					30.44 35
					47 75
					49 32
			767 80		
1LG575	6AQ7GT69				
		6SA7 59	7J730	125R749	50L6GT59
1LH475	6AS562	65A7GT .61	7K7 80	12Z3 39	117Z339
1LN575	6AT6	65C7 81	7L780	14A753	117Z6GT .70
1N5GT61	6AU636	6SF5GT58	7N7 57	14AF763	9003 1.10
1Q5GT39	6AV5GT79	65G759	7Q7 57	14B645	801A 35
1R4 81	6AV636	6SH765	7R759	14C580	803 2.95
1R546	6BA633	65J754	757 85	140765	814 3.50
15440	6BA757	6SK7GT .39	7V7 87	14E665	836 7.95
155	6BC546	65L7GT .49	7W794	19 35	866A 1.45
1T4	6BE637	6SN7GT .46			


Minimum Order: \$10.00. Terms: 25% with order balance C.O.D. Please include postage. All prices subject to change without notice. F. O. B. New York City. Mail Order Division:

TRANSAMERICA ELECTRONICS CORP.

115 Liberty Street New York 6, N. Y.



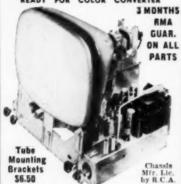1954 INTERCARRIER 630FA-3 WITH TONE CONTROL & FRONT FOCUS READY FOR COLOR CONVERTER



most powerful fringe area Here is the assis on the market today . . . the one V engineers and servicemen are buying r themselves. Clear, sharp, exceptional ception up to 200 miles.

THE ONLY CHASSIS WITH 10 WATT PUSH-PULL HI-FI AUDIO SYSTEM AT

Fed. Tax included

495 Less C.R. Yube and Brackets

Complete with Two Speakers—12" Hi-Fi Waofer and Tweeter With UHF 83 Channel Converter—\$211.90

Detailed Service Manual & Schematic-\$1 Write for FREE Descriptive Folder

COMBINATION SAVING!

TV PICTURE

630 FA-2A Chassis 21" Picture Tube Mah. Consolette Cabinet • Mah. Consolette Cabinet 244 Fed. Tax Incl. With mask, glass, tube mtg brackets FOR THE 1 UNITS

Techmaster 513995 Techmaster 2430-9 Chassis. 24" Rect. 5214

This Month

TUBE SALE enderd Brands. Factory New Guar. 1 year. \$32.95 \$34.95

- Tube Round r 6 Mus : \$79.95 24" Tube Rect. \$39.95 27" Tube Rect. \$79.95
- Guar. 6 months Hing and Steeve for 24" Round \$ 7.50 UHF Tuner...\$18.95

16" and 17" 20" and 21" 24"

TV GOLD

PLASTIC MASKS

CABINET BUY ut for 630 FA-24

tube mount. \$49.95

WEBSTER CHANGER

hassis. With mean, gleas t tube mount. \$49.95 ing brackets. \$49.95 in Flond ...\$59.95 brush. \$24.95 FREE cabinet brochure Mrs. surplus. \$24.95

We Won't Be Beat on Hi-Fi Equip.

REGAL FM-AM RECEIVER



no output. Sep-de bass and treble controls. Built FM-AM antenna. With 12" Ih-Fi wher \$5 additional

Also complete line of Tuners, Amplifiers, Speakers, Phono Pick-Ups and Cartridges and Changers

Fisher Pitot
Garrad RCA
Gen't Electric University
Grommes VM
Jensen Webster
Pickering Wharfedale Send us your requirements Full, illustrated catalog available,

pandise brand new, factory fresh, guaranteed, mone orders filled upon receipt of certified money order for \$25 as deposit on TY chas-, on other items. Balance C.O.B. F.O.B.

AIREX RADIO CORP.

SHOLVROOM: 171 Washington St., N. Y. 7 Cortlandt 7-5218

ing DX-ers" is Fri. 1045, 1730, Sat. 0215 on 6.065. Station officials of Radio Belize, Brt. Honduras, have informed Gay, Calif., that the 6.100 outlet is now operating 1300-1500, 1900-2200 daily.

Radio France-Asie, Saigon, Indo-China (Vietnam), has been lately on 9.625A instead of 9.75A with English 1100 for Europe; closes 1127A with "La Marseillaise." "Voice of Vietnam." Saigon, is weak now on 6.17, and the 9.625 outlet has QRM from XEBT, Mexico, during 0930-1000 English news session. (Balbi, Calif.)

Summer schedules of Radio Japan are 0000-0100, 15.135, 11.780; 0200-0300, 15.135, 11.780; 1800-1900, 15.135, 11.780; 0400-0500, 15.135, 11.780; 0530-0730, 11.705, 9.675; 0900-1000, 15.235, 11.705: 0745-0845, 11.705, 15.235; 1000-1100, 11.705, 15.235; 1115-1215, 11.705, 15.235; 1230-1330, 11.705, 9.675; 1400-1500, 11.705, 9.675. (Cisler, Calif.; Hakansson, Sweden, others)

Acknowledgment

Thanks for the fine reports, fellows! Keep them coming to Kenneth R. Boord, 948 Stewartstown Road, Morgantown, West Virginia, U.S.A. K.R.B.

Spot Radio News

(Continued from page 20)

As to the actual techniques available, the consultant went on, they include card, coin, line, air-code, cash and credit systems, and in a variety of combinations.

In his opinion subscription TV will be quite a project. "To develop this new-and enormous-market will be no penny-ante proposition," he emphasized. "It will call for a lot of technological know-how; a vast amount of production and sales engineering; ample production facilities; a lot of merchandising skill, courage and imagination and finally a barrel of risk money."

FOR THE FIRST TIME since the freeze lift in July, 1952, no station grants were issued during an entire week; the last week in April. A number of factors were responsible; fewer applicants, complexity of hearings now under way and the confusing ultra-high picture.

Before the lull and a week after, business picked up and several new approvals were issued. A listing of the new grants appears at the bottom of

THE INVENTOR of the remarkable radar-mapping device, known as the plan-position indicator or PPI, Dr. Robert M. Page, associate director for electronics at the Washington, D. C. depot of NRL, has finally received official recognition. He has been awarded patent 2,677,127.

PPI gives a radar operator a complete picture of the area searched or swept by his set on a CRT. During the war, the device enabled gunners and bombers to hit unseen targets, detect enemy ships and aircraft, and navigate ships under unfavorable weather conditions. Today, this device aids in landing airplanes at fog-shrouded airports, assists in the navigation of commercial liners and smaller craft, and also helps meteorologists to forecast and track hurricanes.

Everyone is grateful indeed to this eminent scientist for his brilliant invention, which has played so vital a role in the affairs of the military and our daily lives.....L.W.

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of constructive permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

STATE	CITY	CALL	CHANNEL	FREQUENCY (mc.)	POWER*
California	San Jose	3.13 5.17 1.11	11	198-204	178
Kansas	Wichita	KAKE-TV	10	192-198	316
Kentucky	Lexington	WLEX-TV	18	494-500	171
Michigan	Marquette		6	88-94	24.5
Missouri	St. Louis	KWK-TV	4	66-72	100
New York	Buffalo		2	54-60	100
North Carolina	Fayetteville	WFLB-TV	18	494-500	94
**	Gastonia	WNSC-TV	48	674-680	14.4
Oklahoma	Muskogee	KTVX-TV	8	180-186	316
Washington	Seattle		20	506-512	200

NEW CALL LETTER ASSIGNMENTS

Alabama	Selma	WSLA	8	180-186
Arkansas	El Dorado	KRBB	10	192-198
California	El Centro	KPIC-TV	16	482-488
Idaho	Nampa	KTVI	6	82-88
Kansas	Great Bend	KCKT	2	54-60
New York	Buffalo	WGRB	2	54-60
**	Carthage	WCNY-TV	7	174-180
South Carolina	Florence	WBTW	8	180-186
South Dakota	Rapid City	KTLV	7	174-180
Texas	Houston	KTLJ	13	210-216
Vicainia	Newport News	WACH-TV	33	584-590

*ERP = (effective radiated power, kw.) be announced

.. = Call letters to





. Statoscales FEICO SCOPE PROBES

SCOPE DEMODULATOR PROBE KIT \$3.75 WIRED \$5.75

LOW CAPACITY PROBE WIRED \$5.75 KIT \$3.75

DIRECT PROBE KIT \$2.75

SCOPE PROBES Kit ... \$9.95 Wired \$14.95 WIRED \$3.95

SPECIAL

ALL 3

VTVM PROBES

VTVM RF PROBES KIT \$3.75 WIRED \$4.95

PEAK-TO-PEAK PROBES KIT \$4.95 WIRED \$6.95



See these amazing probe values at your jobber today. Write now for FREE catalog RP 7. Read EICO'S other ads in this issue—turn to Advertisers Index!



"TV MANUFACTURERS' RECEIVER TROUBLE CURES" edited by Milton S. Snitzer. Published by John F. Rider Publisher, Inc., New York. 109 pages. Price \$1.80. Paper bound.

This is the fifth in this publisher's current series of handbooks for service technicians.

The new volume covers receivers manufactured by Sparton, Stewart-Warner, Stromberg-Carlson, Sylvania, Tele-King, Trad TV, Transvision, Travler, Wells-Gardner, Western Auto ("Truetone"), Westinghouse, and

Like the previous volumes in this series, the pertinent information is presented completely but concisely and remedial procedures are described in detail.

"THE MAGIC OF ELECTRONICS" by Edward J. Bukstein. Published by Frederick Ungar Publishing Co., New York. 251 pages. Price \$3.95.

This book is a "survey" of the entire field of electronics, presented in the form of brief, non-technical essays, Since the scope of this work is so vast the treatment is, of necessity, abbreviated.

The author, a frequent contributor to this magazine, discusses such topics as the electron tube, industrial process and control operations, electronic medical devices, detectors and counters, safety and communications equipment, industrial television. Geiger and scintillation counters, the transistor and its applications, test equipment, and other units of similar type in widespread use.

For the layman whose interest in electronics has been stimulated by newspaper stories and articles in popular magazines, this book will go a long way towards satisfying his curiosity as to what makes electronics "tick."

"AUTOMATIC RECORD CHANGER SERVICE MANUAL" by Sams Staff. Published by Howard W. Sams & Co., Inc., Indianapolis. Price \$3.00. Vol 5. Paper bound.

This is the fifth volume in the current Sams series covering not only record changers but multi-speed changers, and tape recorders. This volume covers equipment made during 1952-53.

Products of Admiral. Ampex. Brush. Collaro, Crescent, DuKane, Ekotape, Knight, Magnecord, Masco, Pentron, Revere, Tape Master, V-M. Webster-Chicago, and Wilcox-Gay are included.

As was the case with the previous releases in this series, data on each unit includes a photograph, general information, an "exploded" view, operating instructions, parts list, and service data.

A cumulative index covering all five volumes is also included to facilitate locating material about the unit on the shop bench. Service technicians will

STAL PICKUP CARTRIDGES

cartridges you are most likely to encounter in your service work!



Lowest investment for broadest coverage! The RK-54 is beyond all doubt the most practical Replacement Kit on the market! Proof? Simply this-you get the broadest coverage at the lowest investmentonly \$22.55 list! Think of it - 3 Crystal Cartridges replace 192 of those specific Cartridges most likely to be in need of replacement! Two of the Cartridges consistently have been "best sellers" in the Shure line-as established by actual sales to Servicemen! The Cartridges are: Model W22AB, 3-Speed, 2-Needle Cartridge-Model W26B, All-Purpose, Single-Needle Cartridge-Model W78, 78 RPM, Dual-Volt, Dual-Weight Cartridge, Model W78 is the new, versatile Cartridge that replaces 149 other Cartridges. This Cartridge alone will become a sensation overnight! Order a Replacement Kit from your Distributor today-once you have worked with this practical kit you will find that these three Cartridges are dependable replacements-will make your service work faster, easier and more profitable!



TRANSPARENT PLASTIC BOX IS FREE! This Handy Box is 5" long, 31/2" wide, 11/4" deep.





FAMOUS BC-645 i Transmitter-Receiver

BRAND NEW! CLUDED. This swell ris original factory carton. BRAND 'Version Diagram in the swell ris originally cost over \$1000— song! You get it all, in original factory carton. BRAND

yours for practically a song! You get it original factory carton, BRAND \$29

NEW, complete with 17 tubes, \$29

Steps were supply.

Shg. wt. 25 lbs.

PE-101C DYNAMOTOR for BC-645, has 12-24V input (eggy to convert for 6V Battery operation, instructions included).....only \$4.85 UHF ANTENNA ASSEMBLY. \$2.45 CONVERSION BOOKLET. Instructions \$2.50

HEADSETS	Excellent	BRAND
MS-23 high impedance	\$2.25	\$4.45
HS-33 low impedance	1.79	5.45
NS-30 low imp (featherwt)	1.49	2.22
H-16 / U high imp (2 units)		7.95
CB-307A cords, with PLSS plug		
and JK26 lack, R' form		0.0

	MICROPHONE BARGA		
T-44	Mike	Brand New	81.19
T-45	Navy Lip Mike	Brand New	\$1.49
T-17	Carbon Hand Mike	Brand New	\$7.95
T-30	Carbon Throat Mike	Brand New	8 .69
T-24	Single Button Carbon Mike	Brand New	83.95

SCR-274N COMMAND and ARC-5 EQUIPMENT All Complete With Tubes—Prices Slashed!

Type 8C-453 Revr. 190-550 Kr	USED	USED \$34.50	HEW B44.50	-
8C-454 Revr. 3-6 Mc.		11.25		
RC-455 Revr. 6-9 Mc.		10.95	21.95	
RC-456 Modulator		2.75		
BC-457 Kmtr. 4-9.3 Mc.		16.50	3.75	
BC-458 Xmtr. 5.3-7 Mc.		9.75		
8C-459 Xmtr. 7-9.1 Mc.	12.99	14.25	23.50	
8C-696 Xmtr. 3-4 Mc		29.95		
BC-450 3-Revr. Control I		1.49	1.98	
BC-451 Kmtr. Control B		1.28	1.49	
3-Receiver Back		1.79	2.95	
2-Transmitter Back		1.59	3.25	
Single Transmitter Rack			3.25	

ARC-5/T-23 Transmtr, with crystals, \$39.50 tubes, circuit diagram. Brand New \$39.50

ARC-5 MARINE RECEIVER-TRANSMITTER Combination Transmitter and Receiver, complete with tubes. NEW!

BEACON RCVR BC-1206-C

\$12.95

GOULD 6-VOLT STORAGE BATTERY AND NEW. 15 Amp. \$6.95

GOULD 4-VOLT LEAD STORAGE BATTERY



	-	DYN	AMO	TOR	5 -	-
Type		funt	Out		Euc.	Brand
DM-32A	28V	I.IA.	250V	.058.	84.00	87 50
DM-33A	28V	3 A.	576V	.16A.	1.95	3.49
DM-40	14V	3.4A.	172V	.138A.		3.95
DM-28	28V		224V	OTA.	2.25	4.99
PE-73	28V	20A.	1000V	.350A.	9.50	12.50

25% Doposit with order Balance

Radio Supply Co. Dept. N-7 ., New York 7, N. Y., CO 7-4605 Branch: 16 W. Kinzie St., Chicago, III.

find that such volumes on their reference shelves will expedite their service jobs and save both time and money.

"AN INTRODUCTION TO RADIO AND TELEVISION" by D. C. Phillips, J. M. Grogan & E. H. Ryan. Published by The Ronald Press Co., New York. 407 pages. Price \$5.00.

This is a practical manual for those interested in the programming end of radio and television. It is a "how-todo-it" book covering announcing, acting, programming, directing, writing, and newscasting.

Since this text is the work of three men of varied experience in actual telecasting and broadcasting operations, the book is meaty and down-to-

"BEGINNING TELEVISION PRODUC TION" by Melvin R. White. Published by Burgess Publishing Co., Minneapolis. 103 pages. Price \$2.50.

This is a workbook for students of speech, drama, and radio and is designed to be used in colleges and schools where radio and TV courses are offered.

It covers such topics as the problems of black and white TV, production personnel, studio and equipment, lighting for TV, TV sets and properties, etc.

Instructors in TV production should find this manual of assistance in setting up a well-balanced course. -30-

TVI Troubleshooting

(Continued from page 55)

- 1. Remove the antenna of the offended set as far as possible from other antennas.
- 2. Remove the transmission line of the offended set away from other transmission lines.
- 3. In cases where the interference is so strong that it causes the picture to go negative, the use of an attenuator pad in the antenna input will decrease this effect noticeably. The Centralab printed circuit H-type pads are quite useful for this purpose. In fact, such a pad might also be used even if the TVI is not causing overload but is quite severe. In any case, it would be wise to try several values of attenuation before settling on one.
- 4. Avoid placing TV sets close to one another. Investigate the possibility in apartment houses of an offending set being back-to-back, through an apartment wall, with the set with the TVI.

Video i.f. harmonics. Interference from this source is tunable and unmodulated. Cures usually take the form of chokes in the "B+" and heater leads that go back to the tuner, correcting the lead dress, filtering of the detector output and, in some cases, of the video amplifier output. In the event that the leads to the CRT are very long, it is advisable to place a choke in series with the lead that carries the video signal to the CRT. This choke should be located below the chassis, and should be resonant at the frequency of the harmonic that is giving the trouble.

Intercarrier sets do not suffer as much from the effects of these harmonics because it is possible to tune away from the beat and still get satisfactory reception. For split-channel sets, the simplest and most positive cure is to change the i.f. alignment so that the harmonic will either fall out of the band altogether, or else will be so far away from the carrier that it will cause no trouble. Field experience has proven this to be the most satisfactory method of eliminating the beat once and for all.

High channel interfering with low channel. In most cases, the interference is due to the video carrier of the high channel TV station. The video carrier mixes with the second harmonic of the oscillator (set for the low channel) to produce a signal in the i.f. range. If the signal is strong enough, the actual interfering video signal will sweep back and forth across the desired signal. However, in most cases, a diagonal line pattern will re-

The basic problem involved is to attenuate the video signal that is producing the interference. Probably the simplest way to do this is to use a stub. One end of the stub, which is nothing more than a length of 300-ohm transmission line, is connected in parallel with the transmission line at the input to the receiver: the other end is left open. The stub should be electrically equivalent to a quarter-wavelength of the frequency that it is desired to attenuate. This results in a short circuit across the antenna input at the frequency of the interfering signal. Table 2 presents the approximate lengths for each undesired signal. These lengths are slightly longer than normally required to allow these stubs to be cut with a pair of diagonal cutters while watching the picture for the most effective elimination of the interference. (To be continued)

Table 2. The video carriers of the high channels shown here may mix with the second harmonic of the low-channel oscillator frequency to produce an interfering i.f. The correct stub connected to the receiver input, as described in the text, will correct this condition. The last line gives a TVI possibility for a 40 mc. i.f. set.

INTERFERED CHANNEL			APPROXIMATE STUB LENGTH
2	9	187.25 mc.	20 inches
3	11	199.25 mc.	18 inches
4	13	211.25 mc.	16 inches
5	8	181.25 mc.	22 inches
6	10	193.25 mc.	19 inches
4	8	181.25 mc.	22 inches

Mac's Service Shop

(Continued from page 66)

crystal markers for every channel, etc., is pretty well wasted on the average technician. Far too much of this manufacturer-prepared service information sounds as though it were written to impress a competitor's engineering staff rather than to aid the technician."

"Maybe we ought to have some kind of standardization of service instru-

ments," Barney suggested.

"That would be a good idea if it could be worked out. For example, if various service instrument manufacturers and set manufacturers could get together and decide what instruments are essential for modern service work and what minimum specifications for those instruments should be, that would be an excellent first step. Then service instructions could be prepared around these standardized instruments. Furthermore, a technician buying a piece of test equipment would only need to com-pare the specifications of the instrument being considered with the standard specifications to know whether or not he could rely on it to do the job.

"He does not know that now, I was reading a couple of months back where an experimenter checked six different commercial sweep generators and found only one make had sufficiently good linearity, flat response, and adequate sweep to warrant its use without making allowance for errors and that one cost over four hundred dollars! In using the other five, the technician had first to identify the shortcomings of the particular instrument and then to take these peculiarities into account in observing every trace produced with it. That's like trying to hunt with a rifle that shoots several degrees to the left of where the sights point. You may be able to do it, after a fashion, but it'll not be easy.'

"What's all that to do with test tapes?" Barney demanded.

"Keep your shirt on; I'm coming to that," Mac retorted. "I keep thinking that what is really needed in TV service is a signal generator that will produce a real honest-to-gosh TV signal in the same way our AM signal generator produces an actual radio signal. Now that a complete television program can be recorded in black and white or color on a single tape, I believe we are in striking distance of this ideal. First we shall need a couple of oscillators representing video and audio carriers whose frequencies can be adjusted to the carrier frequencies of any channel. Then the video oscillator will be AM modulated with the picture information on the tape and the audio oscillator will be FM modulated with the tape's audio track. The output of the oscillators will be combined. controlled, and fed to the antenna terminals of the TV set being tested.

"The picture information on the tape can contain any type of information

Pay Only 10% Cash Down 18 Months to Pay on Major Equipment



LEO I. MEYERSON

Now it is easier than ever to buy from WRL. Pay as little as 10% down and the balance in 18 months. No red tape — we handle our own financing. We will give you a generous trade-in allowance on your present equipment. We have over 600 reconditioned used items — with new factory guarantee. Send for free list, You will profit most when you deal with WRL — THE WORLD'S MOST PERSONALIZED RADIO SUPPLY HOUSE and THE WORLD'S LARGEST DISTRIBUTOR OF AMATEUR RADIO TRANSMITTING EQUIPMENT.

HALLICRAFTERS 5-40B \$119.95 HALLICRAFTERS SX-71 \$249.95



\$954 Per Month (12 months)

\$12.00 CASH DOWN

Communication receiver with built in speaker covering 540-Kc to 44 Mc in four bands. One RF stage, 2 IF stages.



\$1363 PER (18 Months)

\$25.

Double Conversion sharp selectivity, plus built-in NBFM at moderate cost. 11 tubes plus voltage regulator and rectifier. Low down payment.

HALLICRAFTERS RECEIVERS AVAILABLE FOR IMMEDIATE SHIPMENT MODEL \$10.90 \$199.95 \$3.97 \$ 5.00 \$ 49.95 5-76 \$20.00 S-38C \$7.95 \$10.00 \$ 99.95 5X-62 \$19.07 \$35.00 \$349.95 \$249.95 S-72 Port \$8.74 \$109.95 \$13.62 \$25.00 \$9.54 \$12.00 \$119.95 HT-20XMTR \$24.50 \$44.95 \$449.50



FREE 1954 CATALOG

Get your BIG NEW 1954 WRL CATALOG, offering the greatest selection of radio and television equipment, parts and supplies for the Novice, Experimenters, Hams and Professionals.



WORLD RADIO LABORATORIES R. y
\$415-27 W. Broadway
Council Bittist, Iowa
Please send me:

3' x 4' U.5. Redie WRL XMTR Info
Map 25c Sk.71 Info
New Cotolog S-408 Info
Used Equipment List NEW LOG BOOK 25c

City

City

SPEAKER RECONING

Complete line Cones, Spiders, Rings and Voice Coils, Custom Built Voice Coils, Low prices, Write for Parts List and Reconing information.

WESTERN ELECTRONICS CO.
3164 West Culfax Denver 4, Co

BARGAIN
HUNTING?
SERVICEMEN!
Write for SENSATIONAL CATALOG
HENSHAW RADIO SUPPLY

GET INTO ELECTRONICS



You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Hegin Jan, March, June, Sept. Campus life, Write for catalog.

VALPARAISO TECHNICAL INSTITUTE Dept. RD Valparaise, Indiana

SPECIAL ALE MONTH

WESTON MODEL 301-3" Round Bakelite Case, 10:00 ohms per volt (0:1 Ma) 0:50 Volt DC scale. Multiplier removes easily... \$4.95 ea.

PLATE TRANSFORMER BARGAIN

by Chicago Trans. Co. 3000-0-306 Bi-Ma. Primary 115V., 60 Cy. Type apped to reduce Voltage to 2500 V. BOXED IN ORIGINAL CASES. E AT

paranteed. This is your

WESTON METERS

G-136 VAC Mectiner type	37.72
0-100 V.B.C. (1000 phms /v)	5.95
0-10 Volts BC (1000 ohms/v) "	5.95
O-1 Ma (KV Scale)	5.95
0-50 Ma Oc	5.95 .
0-150 Ma DC	5.95
0-1.5 Mills DC	5.95
0-1.5 Mills DC. 0-200 Microamps (Spec. Scale) Medit F31	7.95
0-1 Ma (0-100 Scale)	6.95

PANEL METERS OV'T SURPLUS. G.E., WESTINGHOUSE, WESTERN ELECTRIC, SIMPSON, ETC. 009' SURIN ELECTRIC, SIMPSON, STC.

3" METERS

100-0-100 Microamps 5.95
0-80 Microamps 5.95
0-400 Microamps 5.95
0-200 Microamps 5.95
0-200 Milliamp 4.90
0-200 Milliamp 4.90 2" METERS 100-0-100 Microamp \$5.05

MANY OTHER METERS IN STOCK, PLEASE WRITE YOUR REQUIREMENTS.

WESTON FREQUENCY METER
Model 814. 350 to 450 cycles, 100 to 125
Volts. Regular Price \$100.00. \$3995 EA. Our Price. Brand New

	OII	CON	DEN	ISERS	
4	MED-SOOVEC	8 .95	- 6	MFD-2000VDC	54.95 g
0	MFD-600VDC	1.50	10	MFD-2000VDC	6.95
2	MFD-1000VDC	.95	1.2	MFD-2000VDC	7.95
3	MFD-1000VDC	1.25	3	MFD-2500VDC	3.95
5	MFD-LOGGVDC	1.95	- 2	MFD-2500VDC	5.95
2	MFD-1000VDC	2.98	2	MFD-3000VDC	4.95
5	MFD-1000VDC	3.50	- 2	MFD-4000VDC	1.50
3	MFD-1500VDC	2.65	- 19	MFD-4000VDC	2.75
8	MFD-1500VDC	2.85	. 8		2.75
6	MFD-1500VDC	2.95	15	MFD-5000VDC	49.50
0	MFD-1500VDC	3.75	. 1	MFD-7500VDC	1.78
5	MFD-1500VDC	4.50	3	MFD BOOOVDC	24.95
2	MFD-2000VDC	2.25	1	MFD-20KV	49.95
3	MFD-2000VDC	2.95	.00	025 MFD-25KV	5.50
4	MFD-2000VDC	3.95	24	MFD-240VAC	4.95

G. E. RELAY CONTROL

Contains a sigma midget 8,000 ohm, relay (trips at less than 2 MA), high impedance choke, bi-metal strip, neon pilot and many useful parts. The sensitive relay alone is worth much more than the total tow price of ...\$1.25

WIRE WOUND RESISTOR KITS

assorted 10 Watt

WIRE WOUND RESISTORS

so order w					mpp. y		***	
to Watts. 20 Watts. 25 Watts. 30 Watts. 100 Watts.	From From From 1	Ohm Ohm Ohm	to to	50K 100K	Ohms Ohms Ohms	Ea. Ea.		.15 .20 .30 .40

EIMAC VACUUM

EIMAC VACUUM
CONDENSERS
12 MMF 32KVDC.31.95
00 MMF 32KVDC.32.95
250 VA.....933.69

READ 'N' SAVE BARGAINS

2" NATIONAL "S" Meter, 0-1 Ma movement.	
calibrated in DB	2.98
Non-ind resistors, 250, 100 watt	.85
6 Henry 100 ma chokes	.85
Heinemann ckt brkr, 5.8 amp. 110 V	.98
Var. ceramic trimmer 7 to 45 mmf	.25
Eric 500 mmf coramicons	.50
15V AC relay SPST 15 Amp contacts	1.75
220V AU relay SPST 15 Amp contacts	1.75
.01 mmf, 1000 VDC Micas \$ for	.95
.0004 2500 VDC Micas	98
.04 600 V Micas 5 for	9.9
100,000 ohm. 100 Watt resist	45
	1 25
Fit. Transf. 115V, 60 cy Sec. 10V @ 1.75 Amp	1.23
Fil. Trans 115V, 60 cy Sec. 6.3V @ 7A	4.00

Min. Order \$3.00-25% with Order-F.O.B. New York, PEAK ELECTRONICS CO.

66 West Broadway, New York 7, N. Y.

Phone WOrth 2-5439

needed for testing. In fact, just a standard test pattern would provide a wealth of information; but other portions of the tape could produce patterns such as are normally obtained from a cross-hatch generator, a dot generator, or a color bar generator. Picture information could be entirely removed and just the sync signals observed. The output of the generator could be attenuated from a maximum to a strength such as would represent the weakest fringe-area reception.'

"You don't think that kind of an instrument would be cheap, do you?"

"No. but I'm sure it would replace several other instruments now used whose total price would more than equal its cost. Still more important, a technician using such an instrument could determine in a few minutes more information about the condition of a receiver under test than he would be likely to learn in several hours of probing with conventional test equipment. I'm not saying we ought to have cheaper equipment. My argument is that we should have fewer and better instruments that will tell us more in less time. The way it is now, all the manufacturers seem to be trying to do is to load us down with more and more test equipment. As it is, we've had to put sideboards on our service bench to accommodate this equipment, and the end is not in sight."

"Somebody is always spoiling things," Barney complained. "I was just planning on setting up in business as a test equipment technician, and I had already worked out a fine business motto: 'Brainy Barney, the Serviceman's Serviceman.' "

W.I.M.U. HAMFEST

THE annual W.L.M.U. hamfest will be held at Big Springs, Idaho on August 7, and 8 with hams from Wyoming,

Idaho, Montana, and Utah attending. Write W7NVR, Opal H. Clayton, Route 2, Idaho Falls, Idaho for full details on this affair. -30-

TV Signal Survey


(Continued from page 43)

the signals have been found to be going directly skyward! In addition, the answers to deep slots, strong lobes, noding effect, and many of the other problems of reception are easily ascertained.

Irregularities of terrain in particular and surrounding areas create special problems in reception, and weather also has an important effect. Moisture laden clouds tend to bend waves and cause ghosts. Distorted pictures, interference, and weak signals are often caused by such varied things as defective fluorescent lamps, power line noise, auto ignition, welding machines, and aircraft engines. The type of antenna, its height and position are of the utmost importance, depending upon location of the set. Sometimes moving an antenna only six inches on the roof gives almost 100% improvement in performance. Weeks of flying over an area, testing signal strength and patterns of TV stations-measuring radiation in both vertical and horizontal planes-produced data leading to the development of improved antennas specially designed for the area. Findings are reported in full to the TV stations, jobbers, dealers, and technicians in the territory as a preliminary to marketing the antenna.

The station is able to effectively analyze the performance of its radiating system and programs accordinglysaving the considerable time it would have taken the station to accomplish the same results. Jobbers have a certain knowledge of what to merchandise in areas surveyed, dealers can get maximum results from their efforts, and set owners are more satisfied with their TV reception-all because a couple of fellows wanted to get enough information to build a much better antenna. -30-

A three-day color TV symposium for service technicians, held recently in Philadelphia. included a talk on color TV test equipment by J. R. Popkin-Clurman, president of Telechrome, Inc., shown below. The symposium was sponsored by the Council of Radio & Television Service Associations, a group of service associations from New Jersey. New York, and Pennsylvania, in cooperation with local parts distributors and manufacturers. The color TV lectures, coordinated by Lewis Winner, were attended by service technicians from many cities. This will be an annual CRTSA affair.

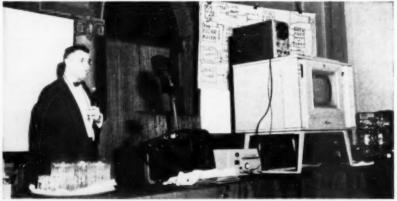

An Editorial

(Continued from page 31)

eral special tubes made their appearance and these were quickly purchased and tried out by hams in an effort to enhance the performance of their receivers. The tendency to purchase parts instead of making them at home really took hold during this year.

In 1921 amateurs, in cooperation with the Government, were giving daily market reports to farmers, newspapers, and local telephone exchanges. On April 15, 1921, the Bureau of Markets, United States Department of Agriculture, sponsored an extended system of disseminating news of marketing conditions by means of amateur radio.

On September 3, 1921, the Radio Exposition was held in Chicago. Approximately 2000 delegates attended the convention held under the auspices of the American Radio Relay League, marking the first national convention of the association. Some 300 sectional clubs affiliated with the League represented more than 6500 amateur wireless stations. Plans were perfected at the convention for trans-Atlantic wireless tests to take place in December.

In 1922 a warning was given to amateurs using wavelengths in excess of those authorized in their licenses which had resulted in much unnecessary interference. Following tentative reports of the Department of Commerce on radio telephony, waves were allocated according to class of service. The Amateur Committee accepted the recommendation that the band for amateurs be 150 to 275 meters and that the limits be fixed by law under the Department of Commerce. On December 8, 1921, the first amateur overseas transmission took place and later Dr. Lee de Forest gave his first demonstration of the "talking movie" with perfect synchronization. With or without accompanying pictures, he could photograph sounds, vocal or instrumental, on an ordinary moving picture film and from the same standard film reproduce the photographed sounds. 1922 was also the year that Edwin H. Armstrong developed the famous Armstrong regenerative receiver. He was also one of the designers and constructors of station 1BCG which was heard in Scotland.

This interest in radio was demonstrated by the applications for amateur transmitting stations of which there were 16,467 on September 1, 1922. On June 30, 1921, there were only 10,809 amateurs authorized to send radio communications, an increase of 5658 during that short period.

Fighting hard to demonstrate the real mettle of the radio amateur, Mr. Louis Bastain of New Orleans, Louisiana, 5HB, during the American Legion Convention, sent two complete messages to another radio amateur, 7SC, at Seattle, Washington, some 2200 miles distant. Bastain's home-made transmitting set, although rated at

779999999999999999

You are FRONT ROW

CENTER ... with FAIRCHILD'S High Compliance Diamond Cartridge

Now-you hear for yourself-new brilliance in recorded sound reproduction made possible by the Fairchild Series 215. This remarkable high-compliance cartridge brings amazing life-like quality to the most delicate nuances of recorded sound and eliminates completely listening fatigue caused by tracking distortion. Compare. You'll select Fairchild professional quality

at only \$37.50

with FAIRCHILD's Plug-in Type **Transcription Arm**

Only by eliminating the adverse effects of arm resonance can records sound their best. Fairchild's new transcription arm allows the cartridge alone to lift all of the tone color from high-fidelity recordings. Dual pivoting plus a precision engineered offset provide continuous midgroeve tracking. And an automatic built-in arm rest safeguards the stylus. Any standard cartridge slides into the Series 280.

Professional quality at \$29,50



Imagine - tailoring your high fidelity system to your listening room characteristics. The exclusive Balanced-Bar feature makes this possible. An initial adjustment matches your speaker system to your room acoustics when the Balanced-Bar is in an unbroken horizontal position. Yet there's full professional flexibility of control for the unusual record. Complete record compensation and gain con trols plus an exciting new listening level adaptor. Four dual-triode tubes and a built-in power supply. Just as important, decorator styling keyed to today's living.

Net to users ... \$ 98.50



SEE YOUR AUDIO DEALER or for free folder write RECORDING : EIGHT AVENUE & 154th STREET, WHITESTONE, L. I., N. Y.

THE REAL PRESE

50% DISCOUNT on UHF Converters and ANTENNAS

Our Area is saturated with these items and we have large stocks left. Send for list of TV Bergains

Sample Items

Regency RC600 Converter (Reg. \$49.95)

Bow Tie Antenna & Reflector (Reg. \$3.95) \$1.75

Many Other Bargains H & H ELECTRONIC SUPPLY, INC.

MORE JOBS than graduates

Demand for our engineer-ing graduates exceeds supply. Effective placement. Study in this world tam college established 1884. Quarters start Sep Jan., Match, June. Approved for Korean Vets.

Electronic Engineers

Bach. Sci. degree in 27 months

mplete Radio Eng. courses . . . TV, UHF and
I. Also Mech., Civil, Elec., Chem., Aero, and
Im. Eng.: Bus. Adm., Acet. Small classes. Wellaipped labs. Modest costs. Prep. courses. Write
Ican McCarthy, Director of Admissions
for Catalog and Campus View Book.





• Wire Recorders

- AmplifiersSoldering Iron
- Radios
 Dictating Machines
- Turntables
 Small Electric
 Drill

SIZE: 4"x5"x6"

Travelectric SUPER

\$3795

Model 6-71160, 60 Cycle, 60-75 Wells

FULLY GUARANTEED

See your Jobber or Dealer

Terado COMPANY
1058 RAYMOND AVENUE
ST. PAUL 14, MINNESOTA

In Canada Write: Atlas Radio Corp., Ltd. 560 King St. West, Taronto 28, Ont. Export Sales Division: Scheel International, Inc. 4237 N. Lincoln Ave., Chicago 18, III. U.S.A. Cable Address—Harsheef only 20 watts, reached out to every state of the Union and Canada.

A new world's record was established for daylight transmission by using a Beverage antenna. This transmission took place on October 28, 1922 and spanned the distance of 2800 miles from Honolulu to Seattle. The station was operated by Thomas Marshall, 6ZY.

Amateur station licenses increased from 10,809 to 15,504 between June 30, 1921 and June 30, 1922. The total on December 1, 1922 showed 16,888. The increase in amateur interest was gratifying to the Government and it recognized the fact that these young men constituted a reserve of trained operators, some of whom had already contributed to the radio art. They had learned during World War I that many amateurs were found to be superior to the average commercial operator in resourcefulness, technical knowledge, and operating efficiency.

The ARRL, December, 1922, made plans to attempt two-way trans-Atlantic amateur radio communications. In all, 316 amateurs succeeded in spanning the Atlantic. The highest honor for amateur radio, the Hoover cup of the ARRL, was awarded in 1923 to Fred B. Ostman, 20M. This cup, awarded annually, was given to the best all-around amateur radio station.

The year 1923 found Donald H. Mix, 1TS, chosen as wireless operator to accompany Dr. MacMillan on his famous polar expedition and to transmit from the ship "Bowdoin" a story once a week on his arctic adventure. Later the same year, Jack Barnsley, 9BP, Prince Rupert, B. C., communicated with the "S. S. Bowdoin" then in the Arctic.

In September, 1924 the Government extended radio channels for amateurs. General and restricted amateur station licenses were issued permitting the use of the wavelengths between 75 and 80 meters; 40 and 43 meters; 20 and 22 meters; and 4 to 5 meters for pure c.w. telegraphy 24 hours a day. This was great news for the ham and the field of experimenting was thrown wide open. Shortly thereafter the 13,000 miles separating London and New Zealand were bridged successfully for the first time when two British amateurs exchanged radio messages using low powered home-made apparatus. Other events of equal importance followed immediately thereafter, opening up further possibilities for the amateur.

1925 was the year when the French experimenter, Pierre LaFond, F8CN, experimented with resistance-coupled amplifiers which have now become commonplace. A combination transmitter and receiver called the "Uni-Set" was described in the March, 1925 issue of Radio News by H. M. Towne, 1ADG. The use of short waves and wire interconnection of stations was developed at a rapid pace in 1925. Short waves had finally found their place in commercial and amateur transoceanic communications and transmission of rebroadcasting, both at home and to places across the seas. The "Regenerative Neutrodyne" also made its appearance that year and John L. Reinartz, 1QP — 1XAM — wrote an interesting article telling how amateurs were exploring the short waves below 40 meters.

Yes, 1925 was a banner year for the ham. The Government, realizing the potential possibilities of the ham, was giving more leeway and cooperation with short-wave experiments already under way and special schedules of transmissions were formulated. Shortwave tests had proven very successful over long distances and the Government, at that time, had planned to equip Naval District Communication Centers with small high-frequency receiving sets for practical and training purposes. They had a definite interest in developing amateurs into prospective Naval Reserve radio operators.

The Signal School at Ft. Monmouth, New Jersey (1924) recommended that a system be organized so that radio amateurs of the United States could join an Army amateur radio system (AARS) and a board of officers was ordered to get together with officials of the ARRL to work out a plan of organization and operation. This was approved by the War Department on September 28, 1925 and with this official blessing the newly created AARS went to work. Some 300 amateurs were included in the initial membership but its growth thereafter was slow. Although the plan aroused much enthusiasm among radio amateurs who were willing to do their part, the lack of funds and personnel prevented the Signal Corps from giving proper attention to the organization. Soon many lost interest in the AARS and resigned. Something more timely, something more within the dream of the average amateur, was needed to make the AARS click. This vital something was introduced when a revised plan was put into effect on January 1, 1929. It emphasized as its prime objective full cooperation with the American Red Cross

On May 17, 1926 George W. Linn. Jr., 2CJE, established radio communications between the Byrd North Pole Expedition and the Navy Department at Washington, D. C.

Down in Australia, in the year 1927, amateur radio played an important part in maintaining communications during the severe cyclone and flood which cut off all telegraph service. In this emergency the authorities fell back on the assistance of amateur radio. Licensed amateurs, working on short waves, were invaluable in maintaining communications during the disastrous New England flood of 1927. They were also contributing, during that period, to the progress of civilization by keeping exploring expeditions in touch with their home bases. In that year, Col. Clair Foster, 6HM, succeeded in working South Africa and China on the same day, thus completing his coveted record of all continents on the same tube-a common 201A and dry batteries. Contacts were made on 38.2 meters; except for communication with an English amateur on 20.2 meters.

During the period from 1927 to 1941 the ultra-high frequencies were developed largely through the efforts of the amateur. Public address systems, facsimile, amateur television, sound-onfilm recording, tape recording, and many other new developments were being worked on in many a basement shop.

The late '20's and the '30's were years of continuous development and experimenting with new circuits, improved vacuum tubes, a.c. power supplies, and scanning-disc television.

When the United States entered World War II thousands of amateurs were eager to serve with the Signal Corps and other branches as radio operators, technicians, etc., and on the home front thousands more joined up with industry to produce the finest military communications equipment almost overnight.

Dr. Lee de Forest, in 1941, wrote of "Color in Television" and described the CBS tests of Peter Goldmark, The difference between the Farnsworth dissector tube and the RCA Iconoscope were explained. Alfred Ghirardi and John F. Rider were monthly columnists in Radio News. ASCAP and BMI were quarreling over the air. The sale of phono-radios increased tremendously. The term "high-fidelity" was used frequently by this magazine as far back as 1941. FCC stepped in to stop ham contacts with foreign stations. Radio News scooped the press with its article, "British Radio Combats Blitz."

The Japs struck at Pearl Harbor while the January, 1942 National Defense Issue was on our presses. This special and well-timed review of military communications was the forerunner of four historical "firsts" for a technical magazine. These issues became essential reference for all military communications and are still in demand. Throughout the war RADIO News reported extensively on radio developments and its editors were active with the Radio Intelligence Division of FCC and the Foreign Broadcast monitoring stations—reporting techniques employed and results achieved in combating clandestine radio.

Following World War II we were privileged to witness the Atom Bomb Tests at Bikini and to publish our exclusive reports on communications at "Operation Crossroads." There follows the impact of television, microwaves, color TV, and interest in hi-fi.

When Radio & Television News made its debut in July, 1919, radio was still in its swaddling clothes of spark coils and oatmeal box receivers. To cover all of the highlights of the past 35 years is not possible in one article and we have touched only a few. The growth of our industry still continues and we welcome many new readers each month. The success of any publication is a measure of reader and advertiser loyalty. To both we say thanks—and to pledge ourselves to a continued effort on your behalf. —30—

Certified Record Revue

(Continued from page 58)

times muddy. It's easy to tell that you're in a large hall, as acoustic perspective here is almost over-reverberant. Soloists sound far away, until you hear the orchestra and then you realize the balance is correct. I heard a distinct "wow" or two in the recording. This is probably due to the curse of much European recording; electric voltage fluctuation which affects tape speed adversely. Is this "Lohengrin' worth the outlay of nearly thirty dollars? I would say yes. In spite of its faults, the virtues are many. While this version may not earn the appellation "definitive," it is close enough to it to warrant your interest. Now that there are three versions of this opera, it will likely be a long time before another edition becomes available. If you've held off buying "Lohengrin" until now, take a listen to this version. As far as I'm concerned, the combination of better over-all sound and the authenticity of the Bayreuth performance makes this the preferred recording. The recording conformed to the new RIAA curve with a slight boost in the bass and a slight cut in the treble. Surfaces were moderately quiet. An excellent English-German libretto is furnished.

TCHAIKOVSKY

THE NUTCRACKER
Minneapolis Symphony Orchestra conducted by Antal Dorati. Mercury "Olympian" OL-2-101, Old AES curve. Price \$11.90.

Before you sigh and say in disgust, "What's this, another Nuteracker Suite?," take a good look at the title in this heading. For this is not the Suite from the "Nutcracker," this is the first complete recording of the "Nuteracker Ballet." And what a delightful treat it is to hear. One wonders what dictated the selection of the familiar music in the Suite, and the deletion of much music that is infinitely more interesting. Taken as a whole, with all of the well known music of the Suite in its proper sequence, this is an utterly new listening experience. Why a score so rich and colorful has not been committed to LP before is a mystery. At any rate, it's ours now to enjoy and Mercury has given the project its most deluxe treatment. The album is two heavy wooden covers bound by a linen-like material in peppermint candy striping and a fancy red cord holds the illustrated pages of the "program notes" in place. On the front cover and throughout the pages which tell the story of the "Nutcracker," are some of the most charming and delightful line drawings of the various characters in the ballet. The album came "factory sealed" in cellophane, certainly a step in the right direction.

The recording itself is magnificent. Antal Dorati's conducting is obviously a labor of love and each section of the



RIDER BOOKS FOR JULY

TV FIELD SERVICE MAN-UAL, VOL. 2

Edited by Harold Alsberg

The finest practical data for in-the-home servicing. Tube layouts; picture tube adjustments; rear and front controls; tube complement; tuner and horizontal oscillator adjustments; key voltages; tuner dial stringing; trouble symptoms; chart with tubes and parts to check; series filament wiring. Book lies flat, spiral binding. Covers 1947 through 1953. Volume 2 covers: Bendix, Capehart, CBS Columbia, Crosley, DuMont.

Approx. 160 $(51/2 \times 81/2")$ pages, illus. Soft cover.

Yolume 1 (Issued in May) Covers: Admiral, Affiliated Retailers (Artone), Aimcee (AMC), Air King, Air Marshall, Allied Purchasing, Andrea, Arvin and Automatic.

128 (5½ x 8½") pages. Soft Cover. Volume 1 Only \$2.10

2. HOW TO SERVICE TAPE RECORDERS

Everything you need to know about what is inside a tape recorder—operation of the recording head, types of electronic circuits, kinds of drive mechanisms used, trouble shooting—and how to service the many types of tape recorders with practical examples. Also discusses requirements for a tape recorder repair shop. Soft cover.

SPECIALIZED AUTO RADIO MANUALS

Cover 5 years production (1950 thru 1954) of factory installed car radios. Identical data from other sources is just not available! Contains: Parts List, Schematics, Tube Layout, Voltages, Trimmer Location, Chassis Views, Chassis Pictures, Dial stringing and complete installation and removal information.

3. INDEPENDENT CAR MANUFACTURERS

Covers-Kaiser-Frazer, Henry-J, Stude-baker, Nash, Hudson, Packard, Willys.

VOL. I-A (Released in May) Ford . . . Lincoln . . . Mercury

VOL. 2-A (Release in June)

Buick . . . Cadillac . . . Oldsmobile

VOL. 3-A (Release in June)
Chevrolet, Pontiac, GMC Trucks,
Chevrolet Trucks

Each Volume 81/2 x 11 ... Soft Cover Write for complete 32-page

NEW RIDER CATALOG

Buy these books now from your jobber, bookstore—if not available from these sources, write to:



ballet is meticulously detailed, each musical fragment polished and burnished, until it becomes a scintillant gem of perfection. Dorati is, of course, a ballet conductor of note, and his previous recordings in this field have been well received, as have his transcription of Strauss' "Graduation Ball" and other ballet scores. In the more familiar sections of the "Nutcracker," his tempo is faster than most but seems justified in the light of the ballet taken as a whole.

Soundwise, the recording is fantastic. Certainly this score lends itself to hi-fi treatment and Mercury's engineers have gone whole hog on this one. Super clean, edgeless strings, bright brilliant brass, woodwinds which really soar and some incredible percussion. You'll hear thunderous tympani rolls here, and in the section which is prelude to the "Battle with the Mouse King" a combination of bass drum and cymbal clash which is positively awesome. WHAM!! If your system is a good one with a big speaker, this will rock your walls. At the start of the battle, a toy soldier calls out "Who goes there?", and fires his rifle. The score actually calls for a pistol shot here and if you are not expecting it, you'll really jump! Boy, if this doesn't test your system's transient response, nothing ever will. The battle itself is replete with tympani, triangles, cymbals and just about anything else you would care to mention. Throughout the ballet the reproduction is startling, and it's not hard to predict that this recording will find much use as a demonstration piece. I also predict Mercury will sell carloads of this one. It has every quality to make it a sure winner. A delightful and listenable score, fabulous sound, great conducting, smart packaging. Unreservedly recommended to you. The AES curve was adequate with controls flat. Quiet surfaces.

MONTEVERDI VESPERS OF 1610

The London Singers, Ensemble Orchestral de L'Oiseau Lyre conducted by Anthony Lewis. Margaret Ritchie, soprano; Elsie Morrison, soprano; William Herbert, tenor; Richard Lewis tenor; Bruce Boyce, baritone; Geraint Jones, organist. London "Editionz de L'Oiseau Lyre" OL-50021/2. RIAA curve. Price \$11.90.

Another of the initial releases in the "Editions de L'Oiseau Lyre," and one of the best musically and soundwise. I had a particular interest in this recording since I was fortunate enough to have made a binaural recording of the American premiere of the work conducted by Leopold Stokowski. Which makes for an interesting comparison.

As with most of the first releases of "L'Oiseau Lyre," the musicianship was of very high order in this recording. Of the soloists involved, Americans are most familiar with the work of Margaret Ritchie and Richard Lewis. Both are in their usual good voice here and their performances are entirely convincing. The other soloists

have less luster, but are nonetheless competent. Choral work, especially important in this piece, is very good indeed, with some of the best ensemble singing I have heard from Europe. If you are not familiar with this work and the title sounds a little formidable, don't let that scare you away. Here you will find a lovely, altogether ingratiating score, beautifully balanced between soft, tender, most lyrical passages, and rousing, exciting masses of sound as full chorus, orchestra, and organ join forces. The closing sections of the "Magnificat" are especially thrilling.

Mr. Lewis is an astute conductor and has full command of his considerable forces. Soundwise, the recording is good, but not distinguished. An occasional "fuzziness" was annoying and strings were edgy at times. Brass came through best of all and percussion, while muddy in sections, was adequate to the demands of the score. Excellent balance was maintained between orchestral and vocal elements, and spacious acoustics helped matters considerably. When you hear a work like this, and you happen to have a binaural version of the same work. the case for binaural sound is certainly valid. In the binaural recording, the choral work and the big climaxes took on a quality altogether different from the discs. In the disc, there was the almost inescapable choral "blur." On the binaural tape the chorus is completely distinct and articulate, the delineation of all elements very obvious. The directivity and depth of the binaural reproduction lends a perspective of uncanny reality. Well, who knows? It may not be too long before wonderful works like this are available in binaural editions. In the meantime, this recording is as good an exposition of this work as you're likely to get, and certainly worthy of your interest. The recording uses the new RIAA curve, but sounds better to me with a little treble cut and a little bass boost.

BRAHMS

CONCERTO #1 IN D MINOR FOR PIANO AND ORCHESTRA

Rudolph Serkin, pianist with Cleveland Orchestra conducted by George Szell. Columbia ML4829. Old NARTB curve. Price \$5.95.

Wilhelm Backhaus, pianist with The Vienna Philharmonic Orchestra conducted by Karl Bohm. London ffrr LL-911. RIAA curve. Price \$5.95.

What does one do about two recordings like this? In other words, when faced with such formidable talent on both discs, how do you decide who wins the potted palm? Serkin and Szell have come up with a version of this concerto that for brilliance and sheer musicianship is hard to beat. The gifted Serkin essays the work at a tempo much faster than the score would seem to indicate and receives support from Szell in this contention. Backhaus, one of the "piano giants" of our time, takes his Brahms at a more leisurely pace. His is the more

constrained, more deliberate reading and, for that matter, closer to Brahms' intentions. Bohm and the Vienna Philharmonic are in splendid rapport with Mr. Backhaus. In matter of sound, the Cleveland disc has a closer, dry type of sound and the Serkin tone is more percussive than Backhaus. The Vienna Philharmonic has a more spacious acoustic perspective and the Backhaus piano more smoothly liquid, than percussive. I think each version must stand on its own merits. If you want a reading more to the classic mold, then the London may be your choice. If on the other hand you want your Brahms with more dash and fire, the Columbia disc is for you. It's strictly a matter of taste here. Both discs conformed perfectly to their respective curves. Quiet surfaces.

BARTOK

PIANO CONCERTO #3

PROKOFIEV
PIANO CONCERTO #3

Leonard Pennario, pianist with The St. Louis Symphony Orchestra conducted by Vladimir Golschmann. Capitol FDS,

P8253. RIAA curve. Price \$5.95. This arrived too late to compare with the London disc of these works last month. Pennario is a young pianist with a terrific technique. His performance is the most dazzling yet recorded. While his tempo may be regarded by some as too fast, it lends a certain life, a spontaneity to these works, in keeping with their musical content. I still think Mr. Katchen on the London disc is the more polished performer, but there is much to be said for Pennario's exuberance. Soundwise, it's a toss-up. The Bartok is better sounding here than on the London disc and the Prokofiev sounds better on the London than on this Capitol disc. Both are very close to each other. Piano tone is more percussive in this version than the *London*, recording generally is "close-up" with good string tone, excellent brass and percussion. Mr. Golschmann lends sympathetic support to Mr. Pennario, and the orchestra sounds much better in this disc than in its previous efforts for Capitol. The RIAA curve (Continued on page 110)

NEW SUPER POST TOWERS FOR TELEVISION ANTENNAS IN FRINGE AREAS

Available in Heights

from 33 ft. to 100 ft. TOWERS OF STRENGTH

TO LAST A LIFETIME

Self-supporting tower built up of galvanized steel sections. No guy wires necessary. Easy to erect. Safe and resistant to high wind. Available in heights 33 ft., 47 ft., 60 ft., 73 ft., 87 ft., and 100 ft., with bases in proportion.

FRINGE AREA TV BUYERS MUST HAVE SPECIALLY BUILT TOWERS FOR CLEAR RECEPTION

Tower and the TV set go hand in hand as a package sale to rural TV buyers. Provides an extra sale and profit to dealers. An excellent fast selling accessory for jobbers and dealers.

TERRITORIES OPEN FOR JOBBER DEALER FRANCHISE

Write for complete structural details, packing, prices, discounts, and territorial assignment.

MANUFACTURED BY

AERMOTOR CO.

Dept. 6107, 2500 Roosevelt Road, Chicage 8, Illinois
BUILDERS OF STEEL TOWERS SINCE 1888

Each | Type

TINDENT RADIO & TV TUBES GUARANTEED ONE FULL YEAR

Each | Type



WINDSOR "WONDER-BEAM" 3-WAY TV ANTENNA



For Average Areas, Fringe Areas, and UHF, Adjustable arms, and new electronic wonder-switch for optimum performance with any TV

Thousands of Service Organizations and Dealers send us REPEAT orders month after month—they KNOW you can DEPEND on the WINDSOR promiss of PEAK PERFORMANCE: Every tube we ship is first carefully tested in our labs, right in a radio or TV set, under actual operating conditions. Each WINDSOR tube is aftractively packaged in the famous WINDSOR carton that has gained consumer acceptance throughout Americal VI-and SELL—WINDSOR TUBES, with CONFIDENCES.

Each | Type

Н	6A8GT68	6BE651	6Q7GT35	7A5	7R7
1	6AB4	6BF566	6R7	7A6	787
И	6AC5GT82	6BF6	684	7A758	7V7
	6AC790	6BG6G 1.47	6S8GT75	7A8	7W7
1	6AF4 1.10	6BH663	6SA7GT57	7AD7 1.05	7X6
	6AG559	6B1653	68C7	7AF763	7Y4
	6AH4	6BK576	6SD755	7AG765	724
1	6AH689	6BK797	6SF5GT	7AH765	12A6
1	6AK5 1.05	68L7GT94	6SG755	7A1770	12AL5
ı	6AL3	6BN698	68M7GT52	784	12AT6
1	6AN8	6BQ6GT98	6817GT52	785	12AT7
1	6AQ551	6BQ7	68K7GT55	786	12AU6
1	6AQ6	6BY5G85	6SL7GT68	787	12AU7
1	6AQ7	6BZ7 1.09	6SN7GT59	7C4 1.05	12AV6
1	6AR542	6C4	68Q7GT	705	12AV7
_]	5A8555	6C5GT60	6T8	7C650	12AX4
٦	6AS7G 4.50	6CR658	6U4GT60	7C7	12AX7
1	5AT642	6CD6G 2.04	6U5	7E5	12AY7 2.
1	6AU5GT85	6D663	6U8	7E6	1284
1	6AU647	6E5	6V3 1.09	7E7	128A6
ı	5AV585	6F5GT54	6V6GT .51	7F7	12BA7
ı	5AV641	6H6GT55	6W4GT50	7FB	12BD6
ı	6AX4	6J5GT44	eweer63	7G785	12BE6
ı	5B8G93	816 218	6X4	7H7	128M7
ı	5BA6	617 ,70	6X8	71785	12BY7
ı	6BA7	6K6GT45	6X5GT36	7K7	1215GT
1	6BC558	6K7	6Y6G	7L7	128A7GT
1	5805GT98	6L6G88	6ZY5	7N7	IZSH7GT
ı	5BD654	6L6GA88	7A4 XXL57	79762	I I2SK7GT

FREE! WINDSOR TUBE CADDY

Most practical service-aid ever designed for Radio & TV repairmen! Now offered RDEE with every purchase of \$150,00 or accumulated purchases totalling \$160.00 within 99 days, (You well Caldy credit memo with each nurchase.)

- Carries approximately 125 tubes including meters and coils
 1654" Long, 8": "Wide, 1354" High, Weighs only 9 lbs.
 Ruggedly constructed with heavy leatherette covering, strong
- S14.95

mindent ELECTRONIC TUBE CO.

2412-N NOSTRAND AVENUE, BROOKLYN 18, N. Y.



h	Type	Each ;	1.0	
П	128L7GT	.67	124	A /
ı	128N7GT	.59	7.00	1
П	128Q7GT	.46		
ı	12V6	.51		-
1	14A7	.58	4,	4
1	14AF7	.68		
1	14B6	.50		
1	14C5	.85	Type	Each
П	1407	.70	2526GT	,46
ı	14E6	.70	35A5	.55
	14E7	.85	35B5	.53
d	14F7	.69	35C5	.53
П	14F8	.99	35L6GT	.52
ı	1417	.85	35W4	.33
ı	14917	.75	35Y4	.48
ı	1407	.62	3523	.48
ı	14R7	.85	35Z5GT	.33
	1487	.80	50A5	.55
И	19BG6G	1.53	50B5	.52
H	1978	.87	50C5	.52
ı	25AV5	.85	50L6GT	.52
	25BQ6GT .	.98	50X6	.55
ř.	25L6GT	.53	117Z3	.43
ŀ	25W4GT	.53	117Z6GT	.75

WINDSOR "BROW-LITE"




Leave Both Hands Free To Work! World's most useful flaste

World's most useful flash light! Ideal for Radio & TV Repairmen. Uses at an dar d penlite batteries and hith. Won't but.

tandard enlite bateries and aib. Won't interfere with gl ides above them over the outplete with

omplete with \$4.95

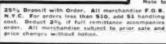Write for Additional Tube Types and Prices. We also stock Special Purpose and Transmitting Tubes at Similar Savings. Dept. N-2.



with experience in the fields of Systems Engineering Communication Information Theory Circuit Engineers Development Electromechanical **Development** Equipment Engineering

THE OPENINGS

Advancements in the fields of wave propagation, translation of information, communication theory, circuit techniques and equipment miniaturization have created a number of new openings for qualified engineers in the Hughes Advanced Electronics Laboratory,

AREAS OF WORK

Assurance is required that relocation of applicant will not cause disruption of an urgent military project. The communication group is concerned with the design and development of unique radio communication systems and with exploiting new radio communication techniques. Specialists in propagation phenomena, antenna systems, network theory, magnetic recording, wide-band amplification, and intricate electromechanical devices are active in this program.

Hughes

DEVELOPMENT

LABORATORIES

and Engineering
Staff
CULVER CITY,
108 ANGELES
COUNTY,
CALIFORNIA

Scientific

was adequate with controls set flat. Surfaces not as quiet as is usual with Capitol discs.

MOZART SYMPHONY #41 (JUPITER) SYMPHONY #35 (HAFFNER)

Pittsburgh Symphony Orchestra conducted by William Steinberg. Capitol

FDS, P8242. RIAA curve. Price \$5.95. Both of these works have been recorded many times previously, but never in this particular coupling. Mr. Steinberg has chosen a rather slow tempo for the "Jupiter," which however, he uses to good advantage in creating some splendid sonorities with the ever-improving Pittsburgh Symphony. His deliberateness is fortunately never heavy-handed which saves this particular performance from the downright "stodginess" typical of this treatment with other conductors. Steinberg's reading of the "Haffner" is something else again. Here is all glitter and brilliance. This is the lighthearted Mozart at his sparkling best. As to preferences, I still like Sir Thomas Beecham's version of the "Jupiter," but in the "Haffner," Steinberg takes his hat off to no one.

From the sound standpoint, both symphonies receive the best recording yet afforded them. String tone is very clean, woodwinds are exceptionally bright. All other elements are sharply in focus. Good spacious acoustics help to maintain the illusion of liveness. A little treble roll-off helped

the RIAA curve to my ear.

RUSSIAN PROGRAM
Philadelphia Orchestra conducted by
Eugene Ormandy. Columbia ML4856.
Old NARTB curve. Price \$5.95.

An attractive potpourri of works by Rimsky-Korsakov and Tchaikovsky. While all of them have been recorded before, none (with the exception of the "Capriccio Espagnol") has ever been afforded such a virtuoso performance and such excellent sound. More or less frankly intended as display pieces for the Philadelphia Orchestra, the results are magnificent. The Philadelphia is truly an incredible instrument. The luster of its strings, the brilliance of the first desk men, is a revelation to the ear. Of the Rimsky-Korsakov works, the "Dance of the Tumblers" is the most effective and exciting. The well known "Flight of the Bumble Bee" is taken in stride by the orchestra and the "Capriccio Espagnol" is well performed, although I still prefer the sound of the Paray-Detroit Symphony version on Mercury. In the "Capriccio Italien" of Tchaikovsky, the orchestra turns in a stunning reading under the baton of the perceptive Mr. Ormandy and even out-guns the reading of the redoubtable Sir Thomas Beecham. Plenty of fire and fury here. The "Andante Cantabile" from Tchaikovsky's "Quartet #1" is a pleasant little interlude from the bing and bang of the other works on the disc. Throughout, the recording is very clean and well balanced. Notable percussion and brass sounds. A

premier disc from all aspects. NARTB curve was just right with controls set flat. Quiet surfaces in my copy.

SCARLATTI

THE PASSION ACCORDING TO ST.

Choir of St. Thomas' Episcopal Church, New Haven, Conn., members of Yale University Orchestra conducted by Howard Boatwright. Blake Stern—Evangelist; David Laurant—Jesus; James Borden—Pilate; G. George—organist. Overtone LP1. Old NARTB curve. Price \$5.95.

Another worthy effort from that venturesome small company, Overtone records. This is not only a first performance on LP it is, as far as anybody knows, the first performance since the days of Scarlatti! The reason for its neglect is preoccupation with the "Passions" of Bach and Schutz, although that can't be the entire story. Certainly it should not have been neglected from a musical standpoint, for this is a remarkable documentation of Christ's Passion. In contradistinction to the "Passions" of other composers. Scarlatti used the complete text of the Passion. This is unusual, as is his use of the orchestra in a work that is purely liturgical. Whatever his reasons, the result is to our musical enrichment. Blake Stern, who has been heard in the "St. John Passion" of Bach on the Victor label, is as effective and telling here as he was in that performance. His traversal of difficult phrasings and intonations is a miracle of fluency. The other soloists are excellent singers and carry off their roles with ease. The Choir was evidently thoroughly trained for this event and it has a solid, satisfying sound.

The reproduction of a work as complex as this is always a problem, which has been met successfully on this disc. There is a minimum of choral "blasting" or blur, and the whole is cleanly articulate. If you are a lover of the baroque in music, you'll like this splendid work. I liked a little bass boost in conjunction with the NARTB curve. Good surfaces.

McDONALD (HARL) SUITE FROM CHILDHOOD CAPLET

THE MASK OF THE RED DEATH Ann Mason Stockton, harpist with The Concert Arts Orchestra conducted by Felix Slatkin. Capitol FDS, P8255. RIAA curve. Price \$5.95. Two attractive "first time on LP"

Two attractive "first time on LP" selections make up the music on this disc. "The Mask of the Red Death" is a modern work scored for string orchestra and harp. It is as eerie as its name, being frankly programmatic. The story is taken from the work by Edgar Allen Poe, and it certainly is a grisly tale. The harp plays a very important role in this work, being used in abstract form and descriptively as well. The harp realistically tolls the midnight hour like an old clock, and the string orchestra uses all sorts of devices like harmonics and mutes, and odd bowing techniques to convey

the eerie terror of the work. In this composition you will hear some wonderful string playing and some of the best reproduction of strings on record.

The "Suite From Childhood" is a very engaging work with fragments of nursery tunes running all through The composer engages in clever transposition of these nursery themes. but they are not grotesquely distorted and the themes are easily recognizable. The harp is again of major import in this work and is used most effectively. The work is, in general, very colorful and gay, and while "modern" in structure, is easy to assimilate. Miss Mason is a superb harpist and in this recording you will hear some really outstanding reproduction of the harp. The over-all level of sound quality is the best to come from Capitol thus far. The RIAA curve was adequate, with controls set flat, and surfaces were quiet.

MOZART

CONCERTO #23 FOR PIANO AND ORCHESTRA CONCERTO #24 FOR PIANO AND ODCHESTRA

Clifford Curzon, pianist with The London Symphony Orchestra conducted by Josef Krips, London ffrr LL-918, RIAA curve.

Price \$5.95. Among the most popular of Mozart's piano concerti are the two recorded on this London disc. Their popularity is well deserved as they are certainly among the most "tuneful" music Mozart ever wrote. As with nearly all the standard repertoire on LP, these concerti have been recorded many times before. So, we come to the old question; is this new version superior to what has appeared previously? The answer is a decided There may be those who pre-"ves." fer the old Lili Krauss recordings, or those of Schnabel. I'll admit they were my favorites up to now. Curzon is one of today's better pianists and it would be a real crank who could find major faults with his reading of these concerti. Dynamics, phrasing, articulation, he is masterful in all of these. His tempi come closer to Krauss' than anybody else's reading, and Madame Krauss was always known to hew the straight and narrow in matter of tempo. A master craftsman, Curzon handles the concerti with a light touch throughout and brings a sort of liquid grace to these lovely works. Krips is an old hand with Mozart and his accompaniment is complementary to Mr. Curzon. A good balance between piano and orchestra is maintained.

The sound is by far the best on records, with bright, clean-toned piano, and smooth strings. About the only thing I could quibble with is that the action of the piano, the thumping of the hammers, could be heard at times. This is most unusual for *London*, as they are usually very careful about such things. The RIAA curve needed an assist in the bass end to sound right to my ears. Surface slightly ticky.

—30—





PALLEY SUPPLY CO. 2263 E. VERNON AVE. / DEPT. TV-3
Los Angeles SB, California



MODEL 27-Z TESTER



RADIO CONTROL

eiver. Passes \$2.95

CAN CONTAINING 4 CLARE TYPE K \$2.95

10-0-0-0-K! TURN A KNOB on the shaft of all motor-like device and one or more of the sam 827.50 EACH. But we \$1795

FILTER-CAPACITOR STEALS! Ea. 19c, 10 for \$1.49 @ con VDC, oil filled.

\$45.00 HI-FI HEADSET AT \$7.95

24-HOUR TIME CLOCK SWITCH

90% DISCOUNT! With \$4.95

TRANSFORMER. TRANSFORMER. 115 V. Su es GA. for above solenoid & many SELENIUM RECVIFIER. 30 VAC Wave. For above transformer & M

12 V. RECEIVER DYNAMOTOR

GENERATOR-ALTERNATOR SPECIAL

200 AMP 24 V. GENERATOR

arine-aircraft-tarin-etc. Heavy Duty 24-30 charcing-weiding-etc. Heavy Duty 24-30 4400-8000 RPM. G.E. type 2CM-8182 Air Pli. Excellent condition. A \$47.50 \$9.95

12 V. DYNAMOTOR



2" rd.; e-1 mm \$3.95 Sec. a Secus \$3.95

G. L. ELECTRONICS, INC.

SCHEMATICS - CONVERSIONS FOR SURPLUS GEAR

NEW LIST! MANY ADDITIONS! stamped, self addressed envelope for C. Add 25c for chart explaining AN ociature.

BOX 1220 GOODHEART BEVERLY HILLS, CAL

RADIO-TV Service Industry News

AS REPORTED BY THE TELEVISION TECHNICIANS LECTURE BUREAU

AS WE MOVE into the normal luil in the electronics servicing business during the summer months, it seems quite evident that the months ahead will witness the largest mortality rate in service businesses the industry has experienced to date. A combination of factors that included the light Winter and early Spring, the leveling off of industrial activity and the tremendous interest in do-it-yourself programs brought about an earlier - than - usual decline in consumer interest in service. And, oddly enough, a large number of men chose this particular period to launch new service businesses!

Three or four years ago the heaviest mortality in the business of television servicing was among the larger shops. This was brought about by over-expansion, failure to conserve contract income to carry the businesses through light months, and general mismanagement. The large organizations that managed to weather this period of business attrition were given a breathing spell of good business during the last Presidential campaign and they were able to adjust the operating patterns of their organizations to the "hill and valley" characteristics of television servicing.

Most of the multi-manned organizations have added air conditioner installation and service (which reaches its peak during the season when TV service volume is at its lowest point); major appliance servicing; traffic appliance servicing; auto radio servicing; and 2-way communications systems maintenance to level off their service volume.

An important thing the large service organizations learned the hard way was that service must be sold. They found out that it was impossible to maintain an adequate, dependable volume of business without a consistent. professionally-prepared service sales promotional program. So in those organizations, business promotion is of equal importance to technical competence. You can't cash in on the latter unless you are able to sell it profitably.

So now it's the one-man shop that gets hurt the most when the volume of service business drops off. Since he seldom is able to build an adequate cash reserve when business is good and time doesn't allow him to accomplish the flexibility that is possible in multimanned organizations, he is apt to get into serious financial difficulties when business is down for several months in

Industry Jitters

The television industry finds itself in a bad spot with color TV still bogged down in the laboratories while the industry stumbles along producing and selling monochrome receivers at no profit to anyone. Just how long this situation will exist is still anyone's guess. Some industry factors feel that color sets will not be produced in volume until a simpler tube that will produce a picture comparable in size to the present twenty-one inch monochrome tubes, is developed.

RCA's program of producing and aggressively promoting their current set with the 15" tube is an attempt to duplicate, on a smaller scale, the spectacular merchandising success they achieved back in 1946 when they went all out on black-and-white TV. Should this happen; should the public accept and buy the present RCA color receivers at the price of one-thousand dollars and over-buy RCA's currently planned production, the industry would be up to its ears in color set production before the end of the year.

However, even the maximum possible production of color TV receivers during the last half of this year would provide little, if any, business to the independent servicing industry. For the protection of their brand names, TV set manufacturers will have to supervise the placement of the installation and service work on their color receivers until all of the bugs have been taken out of production-line sets. This means, simply, that independent service shop operators should not look to color TV to add to their business volume for quite some time.

Everyone had hoped that the rapid expansion of TV through the addition of hundreds of u.h.f. stations would provide a product and service market that would tide the industry through to the time that color would be available in volume and at prices the average set



. Built-in spotlight.

· Lifetime tip.

Soldering heat in 2½ seconds.

30 \$5.96

FREE!

EXTRA SPECIAL! 16 RP4 PICTURE TUBE \$16.49

Write Dept. RN-7 for New BARGAIN BULLETIN

STEVE-EL Electronics Corp. New York 7, N. 1

74 MAGNEMITE in Action Around the World!



son recording deep in Africa's Gold Coast. · American Museum expedition in ra . Dwight Cooks interviews for CBS all over

Wherever you go, whether it be to the North Pole or the bottom of an African dia-mond mine, it's not too far for the Magnemite, truly portable tape recorder, whose versatility and unfailing dependability has gained global popularity for itself.

You'll never grow tired carrying a Magnemite, since these units weigh as little as 15 lbs. com-plete with batteries. Letterhead size, this mighty little handful meets NARTB standards and will easily satisfy your most critical recording needs. For the whole MAGNEMITE story write to Dept. RT

AMPLIFIER CORP. of AMERICA 398 Broadway, N. Y. 13, N. Y.

owner could afford to pay. But it is not working out that way. Ultra-high-frequency telecasting is bogging down badly and interest in building new u.h.f. stations is fast waning.

Space does not permit a discussion of the factors involved in the general failure of u.h.f. to take hold nor of the several plans put forward to keep it from going the way of FM. However, nothing spectacular will be accomplished that will add materially to the volume of service business in the months ahead.

Jobber Sales to Public

The tightening market for service is bringing many of the adverse factors that affect the business of servicing into sharp focus. Second only to the evils of inadequate pricing of service labor, the bugaboo of service that is most often the subject of letters from our readers is that of the indiscriminate sale of replacement parts, tubes, and accessories by parts distributors.

The big question that has been posed by dozens of service business operators who have written your editor is this-"Are parts distributors 'jobbers' or 'retailers'?" There is no denying the fact that the availability of dealer net price lists to the public generally presents a very serious problem to every service businessman in his relations with his customers when he honestly presents itemized lists of parts and tubes used in repairing a TV or radio set.

Although over-the-counter selling of replacement parts and tubes indiscriminately to everyone who walks into a distributor's store is felt most seriously by service operators in metropolitan areas, the condition has been rapidly fanning out into all areas as many parts jobbers press for the last penny of business they can squeeze out of the areas where they operate. It is not a healthy condition for the industry itself for it could bring about an acceptance of dealer net prices as actual retail prices which, in turn, would eventually force a change in the entire pattern of parts and tube distribution.

In a "do-it-yourself" book recently published to encourage the average set owner to repair his own TV set, the author devotes one chapter to advising the reader how to save money on the cost of tubes and parts by buying them from any one of the numerous radio jobbers or wholesalers who are anxious to sell him. The writer of this book tells his readers that tube list prices are meaningless and explains how tube bargains are made possible by set manufacturers dumping surplus tubes with parts distributors at less than manufacturers' cost.

It is extremely doubtful whether one person out of ten-thousand set owners who might read this book could successfully service his own set from the instructions it gives. Yet every set owner who might read it would long remember that "list prices are meaningless" and be influenced by the inference that only a sucker pays list prices for tubes and parts used in repairing TV or radio sets.




It brings you up to date on the latest developments in America's most complete line of volume controls, switches, capacitors, Printed Electronic Circuits*, and steatite insulators.

Got your free copy

Tear out the coupon in the Centralab

> announcement on page 21

0-3454 113

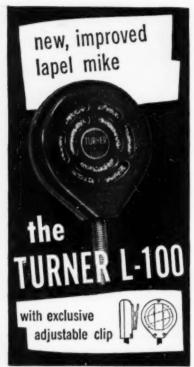

The handiest, low-cost lapel mike on the market. Highest quality Bimorph moisture-sealed crystal gives excellent voice reproduction. A tough alligator clip really holds — it's rubber padded, can't tear your clothing. And the clip is adjustable — you can clip on the Turner L-100 from any angle and the mike stays straight up, cord hangs straight down. Unit is 2-in. diam., weighs 1 oz. less cable. Response, 50-10,000 c.p.s.; level, -52 db. Available without clip, and with ceramic interior. Ceramic interior specifications — response, 80-9,000 c.p.s.; level, -61 db. Model L-100 (with clip and 20-ft. coble) List Price: \$12.50

Model 100 (without clip and with 7-ft, cable)
List Price: \$ 8.00
Medel L-100C (same as L-100 but with ceramic interior) ___List Price: \$12.50
Medel 100C (same as Model 100 but with ceramic interior) List Price: \$ 8.00



THE TURNER COMPANY

900 17th St. N.E. Cedar Rapids, Iowa

MAIL THIS COUPON TODAY

for complete information

I want Turner	all the L-100	facts	on	the	new
Name.					
Addres	ss				
City					
State .			-		

Experienced service operators know from experience that it is unwise to list in complete detail the parts, tubes, and accessories used in making a set repair. Many a service technician has had an embarrassing time in trying to explain to a customer why he charged two dollars for a tube when the customer knows he can get it for less at a distributor or from a mail-order

Fortunately, in many areas parts distributors sell only to bona fide service shop operators. Where this is done, service accounts have been classified and service shops given means of identification which entitle them to buy at dealer net prices.

Unfortunately, the problems involved in channeling the distribution of replacement tubes, parts, and supplies so that only legitimate service businesses would be able to buy at dealer net prices are very complex. The electronics manufacturing industry is, in itself, a highly diversified and complicated industry and within its framework are many elements that use tubes and components in far greater volume than the retail servicing industry. Then, too, there are large segments not connected with service who, in the aggregate, buy substantial quantities of the products used in service but are not directly concerned with set servicing.

Consider, for a moment, the needs of radio hams, hobbyists, and experimenters. Amateur radio enthusiasts were tinkering with wireless long before we had commercial radio broadcasting. They have been constantly in the forefront of electronic developments and much of the industry's progress can be traced to experiments by amateurs at their own expense. The network of amateurs that blankets the country is one of the country's most effective-and from a tax standpoint, inexpensive-defense organizations and invaluable when disaster strikes anywhere. No one would deny the radio amateur the right to purchase the equipment, tubes, supplies, and parts he needs to pursue his hobby at the best possible price.

Then there are thousands of electronic hobbyists and experimenters who are as avidly enthusiastic about their avocation as are the model railroaders, woodworkers, auto enthusiasts, and model plane builders. They are also confirmed shoppers in getting the material they need at the lowest possible price. The confirmed hi-fi enthusiast falls into this category and, of course, if he can't buy hi-fi equipment locally at dealer net prices, he will order from a mail-order concern. And in this connection, it should be pointed out that if the present mail order sales structure were not in existence there would be manufacturers who would be producing and selling hi-fi units to the general public by mail.

In total, it is estimated that there are possibly a half million electronically-interested people sufficiently conversant with circuitry and components who would seek out sources of supply



Multi-Drawers are handy allsteel storage cabinets perfect
for storing easily-lost small parts like condensors, small tubes, switches, nuts and bolts!
Precision-made, finished in durable two-tone
green ename!, complete with card holder.
Available at your dealer's in two sizes—42c
ea, in the small size (illus.), \$1.28 for the large.

*Units interlock rigidly at top, bottom, sides to fit any space.



SOME DEALERSHIPS OPEN

*Once again, enough steel is available to make Multi-Drawers available to new dealers! Write today.

THE CINCINNATI VENTILATING CO. INC. THIRD & MADISON STS., COVINGTON, KY.

EASY TO LEARN CODE

It is easy to learn or increase speed with an instructograph Code Teacher tical method yet developed. For beginners or advanced students, Available to typical messages on all subjects, the property of the Code of the Code



The Instructorraph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators has "acquired the code" with the Instructograph Systems

INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

Get Your F.C.C. LICENSE Quickly!

Correspondence or residence preparation for F.C.C. examinations, Results guaranteed.

An FCC commercial operator license means greater opportunities and higher pay. We are specialists in preparing you, in a MINIMUM OF IME, to pass FCC examinations for all classes of licenses. Beginners get 2nd class license in 5 weeks and 1st class in 3 additional weeks. Write for free booklet.

GRANTHAM SCHOOL OF ELECTRONICS
Dept. 103-B, 6064 Hollywood Blvd., Hollywood 28, Calif.

MINIATURIZING?? Metalclad PRINTED CIRCUIT KIT

For your Electronic Circuit
ad" Conser Clad Phenolic Sheet. Ret Solution. Etch and Instructions.
phenography required, Order direct

TRANSCIRCUITS 1105 W. 42d, Kansas City 3, Kansas

RADIO & TELEVISION NEWS

at the best possible prices. While this is a healthy number of people, they represent only a small segment of the TV set-owning public. It is doubtful whether their purchases of components to service sets represent any serious threat to the stability of service as a

business activity.

Consider the problem of a parts distributor who would like to restrict his sales at dealer net prices to people actually engaged in service as a business. If there is no effective, representative service association in existence in his area, who is he to work with in developing the classifications of recognized service businesses? Also, effective cooperation is a two-way street. If parts distributors sell only to classified legitimate service businesses, these service businesses should buy all of their replacement tubes, parts, supplies, and equipment from the cooperating distributors.

In discussing this problem with a parts distributor recently, your editor was told that this distributor had attempted to work out a restricted sale plan with his service customers. The plan seemed to be working well until a hot-shot parts peddler made a trip through the territory and a number of the protected service accounts loaded up on unboxed replacement tubes that the peddler was selling. Needless to say, this stopped the cooperative plan cold in its tracks.

The ready availability of TV picture tubes at dealer net prices in indiscriminate over-the-counter selling by many parts jobbers has done more than anything else to aggravate service relationships with set owners. Since this is one product for which the use is clearly identified, sales could be confined to properly qualified service operators.

An outstanding example of how stability in service can be achieved through service association-parts distributor cooperation is evident in Columbus, Ohio, where the Associated Radio-Television Service Dealers have worked closely with their set and parts distributors for many years. ARTSD of Columbus is the oldest service business association in the industry. Since its inception, this association has maintained a dynamic attitude that is reflected in the broad scope of the programs they initiate and carry out. One of the most important facets of their program is their quarterly meetings with all local parts distributors to discuss and settle any problems that mutually concern them. These quarterly get-togethers with parts distributors are dinner meetings at which the distributors are the guests of the association. Gripes are freely aired by service businessmen and the parts distributors and steps taken to correct any situation that may adversely affect either the distributors or the local service businesses.

Service Conventions

The Texas Electronic Association is completing plans for the second TV Service Clinic and Electronics Fair to be held at the Adolphus Hotel, Dallas, July, 1954



POWERFUL ALNICO MAGNETS!!!



POLICHED BAR 9/16"x7/32" "HEELING MAGNETS" Set of

ALNICO MAGNET KIT POWER THE Bar, Block, "C." Roc etc. Kit of to assist \$1.9 WRITE FOR LATEST "ALNICO" SUPPLEMENT)

1" FIBREGLASS ACOUSTICAL CABINET LINING RADIO ANTENNAS 1 section, 61 OMED BRASS, With 36" shielded cabl 2.29

115 V. AC ELECTROMAGNET (1) 12, pull, cont. dots 1°C.b. a. a. c. 98c; 6.5.00 Mist Runged all purpose hi-impedance 515 ft. shelided cattle 3.95 °C.MCER' IMPUT TRANSFORMER (116.73.7) C. S.B. carton mike to grid . . cs. 98c; 6.5.00

!!XMAS IN JULY!!

ELECTRONICS PARTS KIT"-LOADED with new & surplus inventory noise & ends. WORTH SEVERAL TIMES THE PRICE! 17 its, or SWITCHES, CONTROLS, SOCKETS, WIRE, TV PARTS TOTAL CONTROLS, SOCKETS, WIRE, TV PARTS TOTAL CONDENSERS, ETC. COLLS, RESISTORAL CONDENSERS, ETC. COLLS, SESSIONAL W. 20 the ... S.2.95

CABINET DRAW SLIDES

5" extension. per pair 2.49
CAHINET LID SUPPORTS (stay hings—holds any sorbe to 70°. Herenze inish. et. 391; 6; 1.58
HS-30 TRANSPORMER only ... es. 591; 10; 5.00
2000 OHM LAR, POTENTIONETER (fedur). ... 55(c. Mw., 3"0.1), tobelite ship.

!!REPAIR YOUR OWN SPEAKERS!!

SPEAKER REPLACEMENT CONES.—An assortment of popular sizes 4" to 12", first, cval. Less. 98 SPEAKER SEPAIS KIT.-Professional assortment of voice Coil Forms, Bings, Spiders, Felt. Chamois Libr., Shim Kit, Cemen & Instructions 2.49 HSSPECIALII-BOTH CONE & REPAIR KITS for ONLY 33.95 DIRECT FACTORY SPEAKER REPAIRS SINCE 1927"



RADIO CORP

SAVE HOURS OF WORK



quickly make round, square, key and "D" openings with Greenlee Radio Chassis Punches

In 11/2 minutes or less you can make a smooth, accurate hole in metal, bakelite or hard rubber with a GREENLES Punch. Easy to operate . . . simply turn with an ordinary wrench. Wide range of sizes. Write for details. Greenlee Tool Co., 1887 Columbia Ave., Rockford, Ill.







CATHODE RA	ar Guara	SPECIALS
G. E.		STAN.BURN *
10BP4A \$14		\$10.20
	10 12LP4	11.90
		A 13.95×
12LP4A 18	78 12QP4	11.90
12QP4A/B1014	12JP4	11.90
		4A 14.50
	75 14CP4	
	.50 15DP4	
15DP4/B1014	16KP	
	.75 16DP4	
	.95 16JP4	or A 17.50%
	.25 16CP4	6 or A 17.50%
	.25 1SFP4	
	20 16WP	
16KP4A	THE RES	
	.35	MA 23.00 x
	AB ANNE	
16LP4A 21	.30	
16WP4A 20	.30	
178P4A 24	.25 178P	
		IA 21.60
17CP4 21	.90 I7GP	
	an IBFP	
		A 24.00
19AP4A 41	OO IBAP	
	50 ITAP	tA 24.90
	OO RECP	
	80 21EP	
	35 21AP	
W C C C C C C C C C C C C C C C C C C C	50 24AP	
QUANT		
		s if you ship them !
		a if you ship them !
FOR BETAILS.		

ANTENNAE SPECIALS	1.9	6	2010
RED DOUBLE "V" Antenna	52 19	\$1.1	18
Police Inserts	2.98	2.1	19
WINDOW CONICALS	4.25	3.2	25
MASTS TO FOOT SWEDGED	1.39	1	29
TV WIRE 43 MIL 300 OHM.		9.95	W Ft. W Ft.
CHASSIS 630 TECH-MASTER Model 1930 with Cascode Tune OPEN FACE CABINET	·	. 514	9.50
PENTRON - Model 973C - 2-aber	N STOCK	Re-	

Model C10 AM-FI Model C500 Will We also carry MASCO	- HOG	Amplific	T. etc. Amp	99.50
Pre-Amps, FM Tunes Sun PM Speaker. S	2 and	WERSTE	R Tape Rec	orders
7 PM Speaker	3.98		XForm	.81
70 Voke	1.98	Cascode	Tuners	14.95
630 Vert., eutput			21.25 mc.	14.91
upright	1.98		inputuner.	
630 Vert., output	1.29		Assembly	let .

20CP4 progressive ... special \$23.95
AUTHORIZED DISTRIBUTORS for gen.
eral Brechtre, Nerread, Yung-Sei, National Union,
De Wald, Regal, Automatic and General Mobers.

De Wald, Regal, Automatic and General Motors, utematic Custem-Built Radios for Plymouth, Pord, hoverclet and many others, always in stock. We carry a Compiled line of HI-FIDELITY and sound equipment. Send us your requests, e aiso carry a compiled inne of hopping makes of dilo Tubes at 80 10 dissount. Also many other specials of the send of

* RADIO and # FLECTRONICS CO. 97 BROADWAY . NIW YORK 19, N.Y

RADIO and TELEVISION ELECTRONICS



in all Technical Phases New Classes (Day and Evening) Start 1st of Dec., Mar., June, Sept. Free Placement Service for Graduates For Free Catalog write Dept. RN

RCA INSTITUTES, INC.
A Service of Radio Corporation of America
350 WEST 4TH ST., NEW YORK 14, N. Y.

RADIOS PHONOGRAPHS TEST EQUIPMENT HI-FI

Write for FREE Brochure RADIO KITS, INC. . 120 Codar St., N. Y. 6 Texas, on August 27, 28, and 29 (Friday to Sunday). The service clinic held in Fort Worth during August, 1953, achieved national recognition as one of the outstanding meetings of its kind in the nation. Subjects to be discussed at the 1954 clinic include color TV, u.h.f., transistors, TV antennas, fair charges for TV service, selling TV service, credits and collections, and bookkeeping systems.

The NATESA annual convention is scheduled to be held in Chicago on September 24th, 25th, and 26th. Although program details have not been announced, the convention will feature a series of clinical sessions on subjects of top importance to service business operators.

Adequate Service Labor Charges

One of the most heartening developments in the independent servicing industry in years is the growing interest among service business operators everywhere in lifting their sights and getting adequate charges for their labor. Letters from readers praising the efforts of this department to stimulate sensible thinking on service practices have come from every section of the country. The three price charts TVL-1 and TVL-2, for TV labor charges, and RPS-1 for radio-phono service charges, are now being used as a pattern by many service groups and as set owner mailing pieces by several service associations.

Information on these charts and other bulletins available from the Bureau may be had by sending a stamped. self addressed envelope to the TTLB Special Services Dept., P. O. Box 1321, Indianapolis, Ind. -30-

Within the Industry (Continued from page 28)

joined Shura-tone Products. Inc. as sales manager . . . DAVID J. BENNETT, vice-president and general manager of station WTPA, has been elected president of Pennsylvania Association of Broadcasters . . . CHARLES A. HANSEN has been appointed manager of the distributor division of Gramer Transformer Corporation of Chicago. He previously held the post of sales manager with Jensen Mfg. Co.

JOSEPH A. HATCHWELL, Mid-Atlantic regional sales manager for Allen B. Du

Mont's TV receiver division, has been promoted to director of service.

bilities include the administration, supervision, and direction of the technical activities of the di-

His new responsi-

vision's service department on a national basis. The department is responsible for service training and follow-through at the distributor, dealer, and independent service organization level.

Servicing Hi-Fi

(Continued from page 57)

to make such repairs to any greater extent than to replace a worn pickup stylus or to cement a damaged loudspeaker cone.

The major electromechanical component in any sound reproducing system which may require any extensive amount of service is the record player and particularly record changer mechanisms. Since the various units of different manufacture generally differ considerably, it is desirable to have available a set of service instructions for the particular unit on which any work is to be done, but there are several rules which can be followed for all types of units.

When first installed, such units should be tested thoroughly for proper operation and performance. Turntables should be level, and the units should float freely when they are mounted on springs. Record changers should be tested through their complete cycle to see that they are operating properly. Turntable speeds should be checked with a stroboscopic disc under standard operating conditions, with the appropriate number of records on the turntable and the stylus on the record. The sound output should be listened to for quality, to insure that there is no excessive distortion or noise introduced through improper performance of the turntable mechanism or the pickup cartridge. Once the unit is in operation, the mechanism should be periodically cleaned and lubricated, with care being taken to avoid excessive lubrication and to prevent any of the lubricant from coming in contact with the motor drive pulley, the idler wheel rubber tire, or the turntable drive rim.

The failures which may occur in record-player mechanisms fall into a number of definite categories and the service procedures depend upon the

specific type of failure.

1. Turntable rotation failure—the motor should be checked to see that it receives power. If there is voltage at the motor, check to see if it is binding anywhere due to damaged or frozen bearings, or to gummed oil and foreign material between its armature and pole pieces. The idler wheel should turn properly and make contact with the turntable drive rim. The turntable should be checked to see that it is not binding and that its bearings are not defective.

2. Improper operation during record change cycle-the records should be visually inspected for correct size, evidence of warping, damage, size of center-hole, and correct run-in and cutoff grooves. Spring tensions should be checked, as well as the adjustments of clutches, cams, and trip levers. The center post should be inspected for evidence of damage or bending.

3. Incorrect tone arm indexing and

OUARTZ CRYSTALS

FT-243-.093" PIN DIA .- . 486" PIN SPC

HAM AND GENERAL USE . GUARANTEED

1015 6150 6650 7400 8400 2125 8175 7000 7425 8425 3500 8200 7225 7440 8430 3640 8440 7055 8075 8475 375 8447 7150 8075 850 3735 8447 7150 8075 8525 3735 8447 7150 8075 8525 3800 6500 7150 8125 8573 6000 6550 750 8125 8573 6005 6507 7150 8125 8573 6007 6507 7150 8125 8574 6075 6060 7325 8240 7150 6075 6517 7150 8175 8175 6075 6607 7325 8240 7150 6075 6517 7150 8175 8175 6175 66175 7150 8175 6175 66175 7150 8175 6175 66175 7150 8175 6140 6640 7375 8380

49c each - 10 for \$4.00

99cen. 10 for \$8.00

r frequency—FT 241A for 3, Lattice Fitter etc., .093* 3, 486* SPC, marked in Chan-Nos. 0 to 79, 54th Harmonic 270 to 389, 72nd Harmonic ed below by Fundamental quencies, fractions omitted.

FT1718 BC-610 2 Banana Plugs 3/4" SPC

BC746 TUNING UNITS, CHAN-NELS 10 AND 12 -foundation coils and condener for 80 meter VF0 or exciter—less stals SEE ARTICLE BY SEE ARTICLE BY W3PPQ IN MARCH '54 CQ.

add 20c postage for every 10 crystals (orless)

49c each-18 for 54.86 99c each - 10 for \$8.00 Spec.-200 KC without halder-39c, 3 for \$1.00

Seec -- 200 KC or 500 KC in FT241A Holder \$1.79 ca.



STAY ON THE AIR an ONAN Electric Plant



Model 10EL, 10KW A.C. When storms, floods, or fires interrupt

electricity and force you off the air, you lose listeners and income. Guard against loss, assure vital public service during emergencies by installing an Onan Electric Plant. Onan Standby Electric plants serve many network and private stations. Gasoline driven automatic models to 50,000 watts.

PORTABLE ELECTRIC PLANTS Supply A.C. power for broad-casting at scene of events. Light in weight. Can be car-ried by hand or in trunk of car. A.C. models: 400 to 3,500 watts.

Write for FREE Folder

D. W. ONAN & SONS INC. University Minneapolis 14, Minnesota needle pressure-spring tensions and the adjustment of level and guide pin assemblies should be checked. The tone arm counterbalance spring should be adjusted for the correct needle pressure, and the tone arm bearing should be checked for binding.

4. Rumble, wow, or slow speed of rotation-check for damaged or worn rubber rim or flat spots on idler wheel, damaged or poorly lubricated motor or turntable bearings, slipping of idler wheel due to weak spring tension or to oil on rubber rim, record slipping on record below due to warping, records not properly aligned on turntable.

5. Noise and squeaks-rubber idler wheel may be bumpy or out of round. If a squeak is due to the records rubbing against the center-post, it may be removed by lightly coating the centerpost with wax or Vaseline to eliminate friction.

6. Hum, distortion, lack of outputcheck for shorted or open pickup leads or shielded cable, defective pickup cartridge or stylus, or leakage through output plug.

If the procedures outlined are followed in the installation and servicing of the electronic and mechanical components, then the sound reproduction of the system will be maintained at the standards to which it was designed.

R.F. in Audio Systems

(Continued from page 45)

control can be reduced by shunting a resistor across one side of the control and ground. The resistor should be five to ten times the control impedance. A small condenser, perhaps 50 µµfd., can be tried instead of the resistor. It may also help to insert a 2 or 3 millihenry shielded choke in series with the control. Such remedies should always be followed by a check on the frequency response and other performance characteristics of the unit.

The writer was aided in the preparation of these articles by data furnished by broadcast personnel, manufacturers, and other agencies and individuals too numerous to acknowledge by name. However, particular thanks are due Dr. Halley Wolfe, co-author of "Elements of Sound Recording" for his advice on the filter shown in Fig. 2 and other points, to his publisher, John Wiley and Sons, for permission to use illustrations from the book, and to Mr. Robert B. Monroe of CBS, who kindly read the manuscript and offered many valuable suggestions.

REFERENCES

1. Augustadt & Kannenberg: "Longitudinal Noise in Audio Circuits," Audio Engineering, January and February 1950.

2. Fragne & Wolte: "Elements of Sound Recording," John Wiley and Sons, page 193.

3. Hicks, H. J.: "Principles and Practice of Radio Servicing," McGrav-Hill Book Company, page 123, Second edition.

4. Langtord-Smith, F.: "Fadiotron besimer's Handbook," Radio Corporation of America, page 616, Fourth edition.

5. Maxwell, Ken: "FM Interference," RADIO & TELEVISION NEWS, February 1951.

BUILD 15 RADIOS

AT HOME With the New Improved 1954\$ 1095

Progressive Radio "EDU-KIT"

NOW INCLUDES SIGNAL TRACER and

CODE OSCILLATOR . ABSOLUTELY NO KNOWL-EDGE OF RADIO NEC-ESSARY

· NO ADDI-TIONAL PARTS NEEDED . EXCELLENT

BACKGROUND FOR TELEVISION . SCHOOL INQUIRIES INVITED

. FREE SOLDERING IRON . 10-DAY MONEY-BACK GUARANTEE

WHAT THE PROGRESSIVE RADIO

WHAT THE PROGRESSIVE RADIO
"EQU-KI!" OFFERS YOU
The "Edu-Ki!" offers you a Home Radio Technician
Course at a rock-batten grice. You will learn how to
identify Radio Symbols and Diagrams; how to build radies, using regular radio schematics; how to wire and
solder in a grofessional manner. You will learn how to
ageriate Receivers, Transmitters, and Audio Amplifers.
You will learn how to service and trouble-shoot radios,
you will learn code. You will exceed the
precisionies.

education in Radio, worth many times the small price
you will.

THE KIT FOR EVERYONE It is not necessary that you have even the slightest background in science or radio. The "Edu-Kil" is used by young and old: by radio schools and clubs: by Armed Ferces personnel and veterans for training and rehabilitation. No instructor is required. Instructions are compete, simple and clear. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD PROGRESSIVE TEACHING METHOD
The "Edu-Kii" uses the principle of "Learn by Deing." Therefore you will build radion, gerform job,
and conduct experiments to illustrate the principles
which you learn. You begin by learning the function
and theory of each of the radio parts. Then you build
a simple radio. Gradually in a progressive manner, you
will find yourself constructing more advanced multi-tube
radio sets, and doing work like a professional fladio
Technician. The "Edu-Kii" Instruction Books are excedingly clear in their explanations, photographs and
diagrams. These sets operate on 105-125 V. AC-DC. An
adaptor for 210-250 V. AC-DC is available.

adaptor for 240-250 V. AC-DC in available.

The Progressive Rodio "EDU-KIT" is Complete You will receive every part necessary to build fifteen different radio sets. Our kits contain tubes, tube sockets, chassis, variable condensers, decretolytic condensers, paper condensers, resistors, tine condensers, paper condensers, resistors, tine condensers, paper condensers, resistors, tine condensers, resistors, tine condensers, resistors, tine condensers, mica condensers, paper condensers, resistors, tine condensers, tine condensers, resistors, tine condensers, tine condensers, resistors, resistors, resistors, resistors, resistors, resistors, tine condensers, resistors, resistors, tine condensers, resistors, resistoresistors, resistors, resistors, resistors, resistors, resistors,

TROUBLE-SHOOTING LESSONS Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will be taught to recognize and repair troubles. You will build and learn to operate a professional bignal and learn to use if for radio repairs. While you are tearning in this practical way, you will be able to do many a repair job for your neighbors and friends and chirge fees which will far exceed the cost of the "Edu-Kit." Our Consultation Service will help you with any technical problems which you may have.

Electrical & Radio Tester * Electric Soldering Iron * Back on Television * Radio Trouble-Shoot-ing Guide * Consultation Service * Quizzes * F. C. G. Training

	AT	TRAC	TIVEL	YG	IFT	PA	CKE	D	
	PROG	RESS	IVE	"EC	U-	KIT	5"	INC	
ŗ	UNION	AVE	BKLY	FN. 1	11.	N.Y	. D	EPT.	RN-31
4			-		-	-			

MAIL TODAY-Order shippe 10-Day Money-Back Guarante	d e.	same i	day AL	received.
Send "Edu-Kil" Postpaid.	ij	enclose	full	payment
of \$19,95 (U.S.A. only).	8	enclose	full	payment

of \$20-\$1. Postpaid, I enclose full payment of \$20-\$5 (Dustide U.S.A.).

210-250 V. Adapter for "Edu-Kit"—\$2.50.
Send "Edu-Kit" (C.D. I will pay \$19.95 plus postage. (U.S. only.)

I wish additional information describing "Edu-Kit." No obligation.

Send me FREE Radio-TV Servicing Literature.

Name Address

PROGRESSIVE "EDU-KITS" INC. 497 Union Ave., Sklyn. 11, N.Y., Dept. RN-31

CRYSTALS =

ALL CRYSTALS TESTED FOR ACTIVITY BE-FORE SHIPMENT AND GUARANTEED TO OSCILLATE! Numbers listed are fundamental frequencies with fractions omitted.



FT-243 CRYSTALS

Lots	of	10 a	r more	. Each		. 69c
Lots	of	5 or	more.	Each.		.79c
Indi	idi	ully.	Each			.99c

1110	2450	2715	2995	3310	6373	7500	7980	
1129	2455	2720	3005	3320	6375	7510	7990	
1150	2460	2725	3010	3340	6405	75.29	8000	
1195	7465	2730	3015	3410	6406	7530	8006	١
1525	24.70	2740	3020	3420	6425	7540	8008	
1900	2475	2745	3025	3455	6440	7550	8010	
1915	2480	2750	3030	3465	6450	7560	8016	1
1930	2485	2755	3035	3510	6473	7570	8020	1
1940	2490	2760	3040	35.25	6475	75.80	80.25	
1950	2495	2765	3045	3550	6500	7590	8030	
1965	2505	2770	3050	36.55	6506	7600	80.33	1
1977	2510	2775	3055	3790	6525	7610	8040	1
1980	2515	2780	3060	3825	6540	7620	8041	
1985	25.20	2785	3065	3885	6550	76.30	8050	1
2010	25.25	2790	30.70	3940	6573	7640	8058	1
2015	25.30	2795	30.75	3955	65.75	7650	8060	
2017	25.35	2815	3080	3980	6600	7660	8066	
2020	2545	2825	3085	3990	6606	7666.7	80.70	1
2025	2550	2830	3090	6000	6625	7670	80.73	1
2035	2557	2835	1095	6006	6640	7680	80.75	
2040	2560	2840	3100	6025	6650	7690	8083	1
2055	2565	2845	3105	6040	7000	7700	8100	١
2060	25 70	2850	3110	6042	7006	7710	8108	
2065	25.75	2855	3115	6050	70.25	7720	8110	
2090	25.80	2860	3120	6073	70.40	7730	8116	ı
2105	2585	2865	3125	6075	7050	7740	8125	1
2125	25.90	2870	3130	6100	7073	7750	8 (30	
2130	25.95	2875	3135	6106	70.75	7760	B133	
2135	26.00	2880	3140	6125	7100	7770	8140	1
2140	2603	2885	1145	6140	7106	7780	8141	
2145	2605	2890	3150	6142	7125	7783 3		
2155	2610	2895	3155	6150	7140	7790	B160	
2165	2615	2900	3160	6173	7150	7800	R163 4	ď
2175	2520	2905	3165	6175	71.73	7810	H166	1
2180	26.25	2910	31.70	6185	71.75	7820	8170	
2195	26.30	2915	3175	6200	7200	7830	R173	
2300	26.35	2920	3180	6206	7206	7840	0818	
2305	2640	2925	3185	6225	7225	7850	8183	
2320	2645	2930	3190	6235	7240	7860	R190	
2350	2650	2935	3195	6240	1213	7870	8191	
2355	2655	2940	3200	6250	7/75	7800	8200	
2360	26+0	2945	3202	6273	7300	7890	R206	
2365	2665	2950	3205	6275	7306	7891.7	8208	
2370	26.75	2955	3210	6300	7325	7900	8220	
2375	2680	2960	3220	6306	7340	7910	H225	
2390	2685	2965	3225	6315	7350	7920	-	
2415	2690	2970	1230	6325	7375	7930		
2430	2695	2975	3235	6335	7400	7940		
2435	2700	2980	3240	6340	7406	7950		
2440	2705	2485	3290	6350	7425	7960		
2442	2710	2990	3300	6362	7440	7970		
FAAR	25.80	2000	2290	2346	- 240			

MISCELLANEOUS & SHIP BAND

	FREQUENCIES
81.95	KC, Octal tube type (Used in SCR-584
200	KC in FT-241 holder
200	KC. Type 9C-15 in octal tube base type
Mini	holder
327.8	KC. No. D-168342. (Used in TS-102/
	AP) 9.95
500	KC in FT-241 holder 1.99
1000	KC. in FT-211 holder 2.49
1000	KC, type DC-0, in octal tube base type
	holder
2000	KC in Ff-243 holder
2174	
2182	KC, in DC-34 holder
2500	KC. in FT-243 holder 1.99
2632	KC in FT-213 holder 2.99
2637	KC. in FT-243 bolder 2.99
2638	KC, in DC-34 holder 2.99
2638	KC. in FT-243 holder 2.99
2670	KC. in FT-243 holder 2.99
2647	KC. In FT-143 holder 2.99
2670	KC. in DC-34 holder 2.99
2738	KC. in type 1-C holder 2.99
2738	KC, in Ff-243 holder 2.99
2738	
3000	KC in FT-243 holder
3003	KC in FT-243 holder 299
3008	KC in FT-243 holder 2.99
3103	KC. in FT-243 holder 2.99
3188	KC in FT-243 holder 2.99
20103	KC. in FT-243 holder 2.99
3198	KC. in FT-243 holder 2.99
3203	KC in FT-243 holder 2.99
5000	KC in FT-243 holder 1.99
10,00	O KC. Type SR-5 Bliley, in CR-1 holder 1.99

SEE OUR ADS!



NOTE: MINIMUM ORDER \$2.50. ALL ORDERS MUST BE ACCOMPANIED BY CHECK, CASH OR MUST BE ACCOMPANIED BY CHECK, CASH OR BUYER and SAICE EAS. INCLUDE APPROX. 5c. PER CRYSTAL FOR POSTAGE. DEALERS, JOBERS: WRITE FOR SPECIAL QUANTITY DISCOUNTS. Hers subj. to prior table & change of price


U. S. CRYSTALS, INC. 805 S. Union Ave. Los Angeles 17, Gal.

NEW EQUIPMENT FOR THE AUDIO TECHNICIAN

CUSTOM CHASSIS

Scott Radio Laboratories, 1020 N. Rush Street, Chicago, Ill. has released a new radio chassis which has been designed for custom installation.

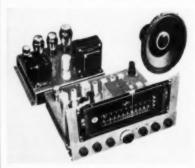The Series 1000 has a custom AM-FM tuner and associated amplifier. The chrome-plated chassis mounts the



tuner of superheterodyne design with r.f. preamp. The new unit has seven controls including station selector, separate bass and treble tone compensators, and AM sensitivity control.

The power amplifier is built on a separate chrome-plated chassis and supplies power for the tuner. Coverage is from 50 to 20,000 cps with pushpull 6L6 output. The unit comes optionally equipped with a 15" specially matched coaxial speaker.

CONDENSER MICROPHONE

Frank L. Capps & Co., Inc., 20 Addison Place, Valley Stream, N. Y. is in production on a new condenser microphone, the Model CM 2001.

The new unit is designed specifically for hi-fi enthusiasts and professionals. Although the microphone houses a self-contained preamplifier, it is only 1½" in diameter, 6" long, and weighs 12 ounces.

The microphone has a frequency response of 30 to 15,000 cps, ± 3 db. It is omnidirectional and free from angular discrimination, it is blastproof and unaffected by moist atmospheres. It comes complete with cable and power supply,

"ULTRA-LINEAR" TRANSFORMER

Aero Products Company, 369 Shurs Lane, Philadelphia 28, Pa. is now offering its Model TO-330, an "Ultra-Linear" output transformer designed for push-pull parallel "Ultra-Linear" operation of tubes of the KT-66 type.

The new high-power unit has a bandwidth of ± 1 db from 10 to 100,000 cps for the transformer alone and permits the construction of a Williamson-type power amplifier providing 60 watts of output at less than 1% IM

distortion from four KT-66 output tubes.

Data on the TO-330 and circuitry illustrating its application are available on request.

MULTICHANNEL MIXER

Berlant Associates, 4917 W. Jefferson Blvd., Los Angeles 16, California is now offering a 4-channel high-level mixer which can handle any combination of audio inputs and feed any type of output circuit.

By means of plug-in accessories, the basic high-impedance mixer can be adapted to accommodate low-impedance microphones, variable reluctance pickups, and high-level signal sources such as tape recorders, tuners, crystal pickups, etc. Any of these can be mixed in any desired combination.

The new MCM-2 has a built-in power supply which makes it independent of other equipment and insures low hum and high signal-to-noise ratio.

FENTON "ADAPHONE"

Fenton Company, 15 Moore St., New York 4, N. Y. is now offering a small instrument, the "Adaphone," which permits the hard-of-hearing to hear radio or television programs with perfect clarity and comfort at normal loudspeaker volume.

The unit is devised so that the listener can adjust the volume to his individual requirements without disturbing others with normal hearing. A built-in audio volume compression cir-



cuit automatically compresses loud passages so essential in some cases of deafness. By alternating output sockets from normal to high tone response, a low cut of near 6 db per octave can be achieved.

HARTLEY TAPE SYSTEM

H. A. Hartley Co. Inc., 521 E. 162nd Street, New York 51, N. Y. is now offering a tape recorder which has three motors and 3% and 7½ ips speeds.

By means of specially-designed recording and playback heads, flat and undistorted response from 50 to 12,-000 cps is obtainable at the 7½ ips speed. The tape deck is normally supplied with three heads for erase, recording, playback and simultaneous monitoring. Two tracks can be recorded so the unit can be equipped for binaural recording on a custom basis.

The company will supply complete specifications on the new recorder and details on companion accessory units upon request.

TAPE CUTTER-SPLICER

Yale Industries Corp., 82-09 251st Street, Bellerose 26, N. Y. has developed a new cutter-splicer for magnetic recording tape which is said to be easier to operate than conventional

The TS-4 cuts two rounded indentations in the tape splice which leaves



the edges of the tape, which contact parts of the recorder, entirely free from adhesive. This particular unit is designed to handle standard 1/4" wide tape. Splicers for other tape widths are available on special order.

NEW COAXIAL SPEAKER

Stephens Manufacturing Corporation of Culver City, California is in production on a new 12-inch coaxial speaker, the 122AX.

A 2-inch voice coil operates the 12inch diaphragm from a fully enclosed magnet structure using 11/2 pounds of Alnico V, thus providing faithful performance down to 40 cps. Coupled through a 5000 cps high-pass filter network are a "Dural" diaphragm and a 1-inch voice coil giving smooth response up to 18,000 cps.

A heavy die-cast aluminum frame and concentric mounting recesses allow exact voice coil clearance for maximum efficiency. Copper voice coils are used to approach the ideal ratio of conductor mass to that of the moving system.

Nominal impedance is 12 ohms, power capacity is 20 watts. The speaker measures 51/2" deep by 121/4" o.d. Shipping weight is 12 pounds.

ELECTRODYNAMIC PICKUP

Electro-Sonic Laboratories, 3215 36th Avenue, Long Island City 1, New York is in production on a new phonograph pickup of the electrodynamic type which is designed for hi-fi sound systems.

The output is flat from 20 to 10,-000 cps and has a slight rising characteristic to 20,000 cps, depending on the

record material.

A tiny loop of fine wire, wound on a Permalloy armature, is mounted between the pole pieces of a small but powerful Alnico magnet. To one end of the supporting shaft is attached a

Let MILTON S. KIVER Help You Prepare For U.H.F.-TV, Color And...



Easy to TRAIN AT HOME This Practical Way!

Men with the right training in Television Servicing are in big demand... pull down big pay. T.C.I. TRAINS YOU RIGHT with easy-to-follow technical training designed by servicemen, for servicemen? You learn practical, professional type Television Servicing without leaving your present job. Included are money-making returns your present job. Included are money-making extras such as set conversion, master antenna installation, U.H.F.TV NTSC Color System and field servicing short cuts. You can start earning Television money after the first few lessons. You learn to test, trouble shoot and repair all types of TV sets the proven, practical way!

HERE'S HOW YOU GET EXPERIENCE!

You train on your own large screen modern television receiver, furnished as part of your course. This set is yours to keep! As an optional feature you can get two weeks of actual field experience out on service jobs and on the repair bench for Chicago's largest independent servicing organization. You learn Television Servicing by actually doing Television Servicing to you get the practical know-how you need to qualify for BIG MONEY in this fast-growing field! Age is no barrier, Many TCI students are over 401.

T.C.I.

ACT NOW! Mail coupon for FREE Catalog and SAMPLE LESSON. Write TODAY!

E

COMMUNICATIONS INSTITUTE

605 W. Washington Blvd., Dept. BC, Chicago 6, Ill.



YOU GET and keep modern large screen Television receiver.

YOU DO actual testing, servicing, trouble shooting and repairing

BEGINNERS! LEARN ABOUT NEW BASIC TY COURSE! You don't need rading experience for you don't need rading and the factorial, home-study and the factorial for the factorial for the factorial factorial for the factorial facto

MAIL NOW FOR FREE BOOKLET

MILTON S. KIVER. President TELEVISION COMMUNICATIONS INSTITUTE 605 W. Washington Blvd., Dept. BC Chicago 6, III.

Rush full facts on practical TV training. I am not obligated. Salesman will not call. Veterans: Address

City Zone State DEGINNERS check here for information on Basic Television Course.

World's Only Recorder of its Kind WALKIE-RECORDALL 8-LB SELF POWERED BATTERY RECORDER

AUTOMATIC UNDITICITIO Records naiselessly in or out of classe RECORDING us to Any bristcase, centraining hidden mine with 197CCS UP within white, riding, fring, Centrarces, lectures of it ADUUS citation, 2-way phone. Fernancest, unafter voict activated this, indeed recording at any 3 central control of the Control of th

ACTORY REPAIRS ON ALL MAKES AND TYPES OF

TEST EQUIPMENT

Write Dept. 5 for BIG NEW FREE Catalogue GENERAL ELECTRONIC DIST. CO. 98 PARK PLACE, NEW YORK 7, N. Y.



LAFAYETTE made a terrific deal with one of the leading manufacturers of recording tape pastace pastace to supply us with their regular twice our price. WE GUAR-ANTEE ABSOLUTE SATISFACTION OR YOUR MONEY BACK. The finest, preferation of theorems of playings. Bed Oxide Base in a smooth, uniform coating: greater signal strength; with maximum fidelity; uniform frequency response from 9-15,100 cps.

1200 FT. REEL

Genuine Plastic Base

RECORDING TAPE

AFAYETTE made a territ

CHANNEL VHF 3 TUBE TV BOOSTER CHANNEL VHF 3 TUBE TV BOOSTER
Features a new low-noise cancade chrouitpully automatic — no tunine. Best for all
TV risers.

Best for all channels

at through 13. Low noise factor (approximately 6). Automatically turned on and off
by the TV set. Concealed behind TV receiver.

Mount it and forget it. Employs new 6BKT-A
tube for snow-free reception with new high
gain-low noise TV receivers. 3-tube circuit
includes two GIG tubes in push-pull, crossneutralized RF amplifier circuit. All-metal
cabinet, brown hammertone finish. U/L acproved. Tudistorted sound and picture on all
12 channels. Engineered for maximum rerformance. Sive 9'x 8'x 8'x 8'x 8'x

MODEL ABV VHF-TV BOOSTER.

PRECISION DRAFTING SET

II Pieces—Fitted Felt-Lined Case
Made in Germany, of leavy brass, nickel
plated and polithed, instruments include 51." Compass with perceit and sinvider, three 31." sidewheel bow dividers
with needle point, pan point and principoint. 5" Ruling per, extra handle for
pen or pencil, capsule with extra leads.
Infectionapability of these many parts
makes this on acceptionally veraltic set.
verift levice our price!

Set 2.15

Radio DEPT. RG

Write for free catalog. NEW YORK, N. Y. 100 Sixth Ave. BRONX, N. Y. 542 E. Fordham Ri MEWARK, N.J. 24 Central Ave PLAINFIELD N.J. 139 West 2nd St. BDSTON, MASS. 110 Federal St.

Editors and Engineers

RADIOTELEPHONE

Now, in one convenient volume, complete study-guide questions with clear, concise answers for preparation for all U.S.A. commercial radiotelephone operator's license examinations.



Book No. ELE-RL1 \$3.75"

"Plus any fex.

Send three cent stamp for circular with detailed contents of books listed.

8	u	۲	1	į	3	Ċ	L	1	۲	c	ı	Ī	ŧ	ŀ	9	I	i	Ĺ	II	1	U	7	0	R	
		0					101																		
0						A	8		H	1				A	R	Ü	A	Ü				A			

Concord	A PAYOR HOLD N 1
Concord	
VEE DX YAG	15
Less 74	4
Manufacturers (Post!
It may sound like brag	ging buy of the
made the most sensation decade, and we're pass	ing the savings on to
DX 4 and 8 element all	aluminum yagis that
manufacturer's cost. ***	th Auges so order
lection of all channels	realf of an adequate
early and assure you supply of yagis at give	8 Element
4 Element	Vee-DX Long John Yagis
Channel 7,8,9	Channel 5
List \$8.50	\$7.95 EACH
\$1.98 EACH	57 50 Lots of 3
\$1.75 Lets of 3	Channel 9,10,13
FREE	\$4.50 ea. \$4.15 Lets of 3
FREE!NEW 195	COVERN
listing of all rour	
SPECIAL VALUE	S WITH CONCORD
Dept N 7	المالات
CONCORD RADIO	MINIMUM
20% deposit with C.O.D.	
NAME	
ADDRESS	
CITY_ ZO	NE STATE
CONCORD RADIO	

NEW YORK 7, N. Y. . Digby 9-1132

light arm about 3/16" long, the free end of which holds a sapphire or diamond stylus.

This item is being handled through electronic jobbers.

TAPE "CONSOLE"

A newly-designed extension loudspeaker, housed in a cabinet which converts the company's portable pushbutton tape recorder into a console, has been introduced by *Radio Corpora*tion of America, Camden, N. J.

The unit is finished in polished mahogany and has a compartment into which the tape recorder can be placed for use or storage. The bottom section of the cabinet contains the company's "accordion"-edge extended range speaker and matching baffle.

The cabinet measures 29" high, 21" wide, and 16" deep with a beveled, picture frame edging around the front. Most of the front is covered with brown grille cloth in a gold criss-cross pattern.

SPEAKER KIT

De Mar Products Company, P.O. Box 1449, Chicago 90, Illinois is now offering a speaker kit for service technicians and audiophiles.

The kit consists of two 6½-inch, extended-range speakers and an output transformer to match the set. The speakers have a frequency response from 50 to 12,000 cps.

"ULTRA-LINEAR" AMPLIFIER

Sonex, Inc., 245 Sanson St., Upper Darby, Pa. is offering a new power amplifier which uses the "Ultra-Linear" circuit in a Williamson arrangement and features the Acrosound output transformer designed expressly for this type of circuitry.

The amplifier has frequency response flat \pm .5 db from 10 to 100,000 cps,



according to the company. It is rated at 25 watts and furnishes 20 watts at less than 1% intermodulation distortion. The amplifier is furnished with matched KT-66 tubes and matched resistors are used in the parts of the circuit that require balancing.

PHILCO SPEAKER

Philo Corporation of Philadelphia has announced a new 10" speaker which can be used with all singlespeaker radio phonographs.

Offered as a separate unit, it can be operated as an auxiliary speaker in combination with the set speaker. A special three-way switch, included in the new kit, permits manual operation

of each speaker separately or together. In addition, there is a 30-foot



extension cord which makes the new unit flexible for use almost anywhere within the home as well as outdoors.

The kit is being marketed through the company's regular distributors.

NEW PICKUP ARM

Pickering & Company, Oceanside, Long Island, N. Y. has developed a new pickup arm for manual turntables, the Model 190D.

A re-engineered version of the Model 190, the new unit requires less mounting space while retaining the low vertical mass, static and dynamic balance, lack of arm resonance, and low friction of the original design.

The arm requires a 17"x17" motor board for mounting.

NEW E-V SPEAKERS

Electro-Voice, Inc., Buchanan, Michigan has added two new concentrictype 12" and 15" triaxial, three-way speakers to its line.

The new units combine the company's "Super-Sonax" very high frequency driver, "Radax," treble propagator, and large bass cone into one compact, concentric assembly.

Response is 30 to 15,000 cps in the company's "Regency" or "Aristocrat" enclosures. A full half-section, m-derived crossover network minimizes distortion products. The 12" unit is the Model 12TRX while the 15" unit is the Model 15TRX. Bulletin No. 204, giving full details, is available on request.

REGENCY AMPLIFIER

The Regency Division of I.D.E.A., 7900 Pendleton Pike, Indianapolis 26, Ind. has added a moderately-priced unit to its audio amplifier line.

The Model HF-150 includes a preamplifier and power supply. It incorporates five controls for bass, treble, loudness, level control and record compensation, and input selection. It has a rated output of 12 watts and a frequency response of 20 to 40,000 cps ± ½ db. It is finished in gold-anodized aluminum.

STROMBERG SPEAKER

The Sound Equipment Division of Stromberg-Carlson Company, Rochester 3, N. Y. is offering a new 8" conetype speaker, the Model RF-460.

OTONS RADIO GEAR

268—FILAMENT TRANSFORMER: Input 120V 60 cycles, 6 Volt output tapped at 2 & 4 volts, 10 amp. \$2.00 ca,

269 TERMINAL BLOCK, 3"x6", Western Elec., 50c ea.

#71—TRANSMITTER FILTER CHOKE, 3 Hys at 320 MA . . . \$1.50 ca.

272—RA-37 TELETYPE RECTIFIER. Input 110 AC, Output 130V DC, 1 amp....\$5.00 ea,

#273—OUTPUT TRANSFORMER AND LOW PASS FILTER, Pr. 10.000 ohms. Sec: 4 ohms, pass freq. from 410 cycles to 2000 cycles. #1.50 ca.

275—LIP OR THROAT MIKE........... 25c ca.

278—GRAB BAG ASSORTMENT, odds & ends of resistors, condensers, etc., five pounds...\$1.00

ALL PRICES F.O.B. MEMPHIS, TENN

Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% deposit on all C.O.D.'s please. Money-back guar-

ARMY SURPLUS OUTLET

91 North Second St.

Memphis 3, Tenn.



T-V CLARIFIER

Removes annoying signals that cause picture distortion in TV sets due to FM, amateurs, shortwave, diathermy, ignition and adjacent channels. Ghosts, lines, herringbone patterns, tears and wavy effects are eliminated or reduced simply by turning the two control knobs on this new type interference eliminator.

- No technical knowledge needed
 Traps unwanted signals
- Fastens to screws on back of set Easy to tune. Stable

- Small, mechanically rugged Necessary with every TV installation PRECISION

ELECTRONICS, INC. 9101-Rv King St., Franklin Park, III. Please rush Free Bulletin on T-V Clarifier Address

Zone State

Frequency response is from 50 to 13,000 cps, power handling capacity is 10 watts, impedance is 8 ohms, and flux density is 13,000 gausses. The speaker pan is fine wrinkle, silvergray over cadmium plate while the magnetic structure is cardinal red. It can be used in applications where the speaker must fit into wall or ceiling enclosures, portable speaker cases, bookshelves, etc.

TAPE SPLICER

Tech Laboratories, Inc., 14 E. Edsall, Palisades Park, N. J. now has available a small model recording tape splicer, the "Editall, Jr."

This model was designed for use with home recorders as well as with portable professional equipment where weight and compactness are important, The block is made of duraluminum. It has no clips or mechanical parts to get out of order.


V.T.V.M. FOR AUDIO

Freed Transformer Company, Inc., 1715 Weirfield St., Brooklyn 27, N. Y. is offering its Model 1060 high-impedance v.t.v.m. which is especially suited to tuned circuit measurements at audio and ultrasonic frequencies.

Input impedance is 50 megohms in parallel with 25 µµfd. capacity. Accuracy is 2 per-cent on all ranges with full-wave average reading meter calibrated in r.m.s. Frequency coverage is from 10 cps to 30 kc. The meter also includes five voltage ranges. The 4" meter is suppressed zero protected against overload.

END-TABLE CABINET
Components Corporation, Denville, N. J. has announced an end-table cabinet for use with its professional model, three-speed turntable. The cabinet also provides space for an amplifier and record storage in addition to the turn-

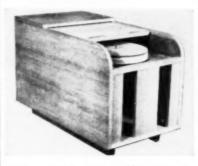A roll top allows the record to be covered during playing. A fixed top



section at the rear provides room for a lamp and other accessories. It is available in either blonde or mahogany finishes, with or without the turntable.

STEPHENS CABINET

Stephens Manufacturing Corporation, 8538 Warner Drive, Culver City, Cal. is marketing a new type of speaker cabinet, the "Cavalcade."

Designed to produce full volume, the cabinet permits direct radiation





Specially Designed for Operating Standard A.C. Electric Shavers in Automobiles, Buses, Trucks, Boats, and Planes.

Glove Compartment

PLUGS INTO CIGARETTE LIGHTER RECEPTACLE ON DASH

BUTPUT TYPE 6-SPB 115 velts 12.95





Household ELECTRICITY Anywhere in your own car!

Plugs into Cigarette Lighter Receptucle on Dash

50 - AND UP LIST PRICE



ATR INVERTERS . . .

especially designed for operating standard 110 volt A. C.

- . TAPE RECORDER
- . WIRE RECORDERS
- . DICTATING MACHINES
- . ELECTRIC RAZORS

See your jobber or write factory today for complete information AMERICAN TELEVISION & RADIO CO. Saint PAUL I. MINNESOTA - U.S. A.





FINGER STOCK

Electrical Weather-Stripping by Eimac -Now Available!

Silver-plated, spring alloy, preformed finger stock especially suited for electrical "weatherstripping" for TVI - proofing cabinet access doors, etc. Also ideal for making coaxially constructed tube connections and many other uses. Available in

widths.

 Write for new Eimac Catalogue Summary showing Eimac tubes and other accessories.

17/32", 31/32", and 11/4"



EITEL - McCULLOUGH, INC. San Bruno, California from the loudspeaker and employs the company's full-expanding dual exponential horn for rear horn loading.

Available in either blonde or mahogany finish, the cabinet is of modern design.

CORNER HORN

Product Development & Research, 2365 Le Forge Road, Ypsilanti, Mich. has developed a new corner horn featuring vertical design for greater utilization of wall surfaces.

Designed for a 12" speaker, with additional space for a tweeter, this ex-



ponential horn has a top opening to take advantage of unobstructed wall space. The horn is 36 inches high, 24 inches wide with a triangular shelf 14 inches below the top formed by the 'V" in the design. Back surfaces are slanted at the bottom to clear molding and quarter round. It is available in assembled or kit form.

5-WATT AMPLIFIER

Electronic Crafts Co., 74 Cortlandt St., New York, N. Y. is now marketing a 5-watt a.c. amplifier with built-in preamp for use with reluctance or crystal type pickups. The small, compact unit is designed for paging systems, intercoms, record players, or other sound systems.

The Model RL-5 uses three tubes and features a power outlet for a motor, a two-connection terminal strip for a 3.2 ohm speaker, and a built-in

output transformer

ULTRASONIC SPEAKER

Ultrasonic Corporation, 640 Memorial Drive, Cambridge 39, Mass. has announced a new low-cost, compact speaker, the U-26.

The new 1/2 cubic foot U-26 provides high acoustic efficiency with only 2 watts. The U-26 is designed for 4 ohm speaker while the U26A is for 16 ohms.

The cabinet, available in either blonde or mahogany finishes, measures 13" wide, 19" deep, and 1014" high.

CUSTOM CONVERTER

Carter Motor Company, 2641 N. Maplewood Ave., Chicago 47, Ill. has introduced a custom converter for hi-fi installations.

This new 500 watt unit, #DR1025-C5PX, is designed to deliver 125 volts

MEN! THIS IS IT!

Nothing like these "Q.T." Cartoon Booklets, ever! REAL COLLECTOR'S ITEMS!



2. Toots and Jasper
3. Title the Soiler
4. Lord Pushbottom & Emma
5. Villain & Little Nell and others.

ACT NOW!

TITILLATING MOVELTIES WITH ORDER

Q.T. SALES

Bex 8516, Dept. 726 Hollywood 46, Calif.

CRYSTALS! COMPLETE SET-80 CRYSTALS

COMPLETE SET—120 CRYSTALS 370-516 Kc., ct \$9.95 IERATOR: 12 V. 35 A. Used cond. V. TRANSFORMER, Drl. 110 @ 2 amp EXTRA! See Our Ad in April '94 Radio News

400 MICA CAPACITORS. Asserted. Mounted 10 to a stree. All 400 ARW-2 REMOTE CONTROL RECEIVER. New . \$27.50 All merchandise sold as is. Write for quantidiscountal litems subject to prior sale. Send for FREE Catalogue! J. J. GLASS ELECTRONICS CO.

It's P.A.R.T.S. for PARTS!

CARTER GENEMOTOR

\$17.95

w, guaranteed! Appro THE CONTRIVENS ASSOSTMENT: Unused Approximately 110 per 10. A great bay.

St. 1206 BEACON BECEIVEN The Lazy User: 200 per 10 atto NC. Votume control. HF gain resulted. 24-22 NEW NEW NEW NOTE: 10 per MICA CONDENSERS ASSORTMENT: Uni

P-A-R-T-S, INC.

2005-15 Empire Ave., Burbank, Calif. PHONES: Victoria 9-2834 Thornwall 2-5349



MOVIES ON APPROVAL

Most entertaining 8MM DANCE FILMS for home movie shows. Write today movie shows. Write today and we'll send you a 50-ft. SMM FILM - POSTPAID-ON APPROVAL. (Return film and 25c within 5 days without obligation, if it's not worth more than \$1.50 we ask). BON BONICA NEWSREEL CLUB, 6516-RT Selma Avenue, Hollywood 28. California.

PREPARE FOR A GOOD JOB!

BROADCAST ENGINEER COMMERCIAL OPERATOR (CODE) RADIO SERVICING

Television Servicing

(Approved for Veterans) SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE 1425 EUTAW PLACE, BALT, 17, MD.

RADIO & TELEVISION NEWS

a.c. with 120 volts d.c. input and a load of only 50 watts. Due to the regulation of the converter, the voltage would only drop to about 105 volts with 110 volts d.c. input and full 250 watt load. These a.c. limits coincide with equipment ratings.

Frequency control with frequency meter is included allowing the operator to adjust to exactly 60 cycles for record players and tape recorders. A filter is available for noise-free radio reception.

BINAURAL TUNER

Browning Laboratories, Inc. Winchester, Mass. is in production on a new tuner designed specifically for binaural reception which provides simultaneous reception of AM and FM broadcasts.

The Model RJ48 also provides either AM or FM high-fidelity reception or independent reception of two different programs with speakers located in different rooms. Provision is made for the use of tape recorders. Detailed information is available from the manufacturer.

TUNER-AMPLIFIER

Freed Electronics and Controls Corp., 200 Hudson St., New York 13, N. Y. has re-entered the audio field with the release of its P-717 AM-FM tuner and amplifier.

Marketed under the Freed-Eisemann tradename, the new chassis provides a.f.c. of the FM circuit, terminated in a Foster-Seely limiter-discriminator. Multi-purpose tubes are used to give 15-tube performance. Response of the unit is 20 to 20,000 cps ± 1 db at full output. Audio output is 10 watts at less than 1.5% distortion. A preamp for variable reluctance phono pickups, treble and bass controls, full record compensation, and a jack for a tape recorder are also included.

TURNER LAPEL MIKE

The Turner Company, 909 17th St., N.E., Cedar Rapids, Iowa is now offering a new and improved lapel microphone, the L-100.

This new crystal unit weighs only 1



ounce without the cable. An adjustable, rubber-padded clip permits the microphone to be clipped anywhere. Frequency response is 50 to 10,000 cps,

.R.T. TUBES 70% 10 90%

ALL NJRT TUBES ARE BRAND NEW AND **FULLY GUARANTEED FOR ONE YEAR**

Туре	Price	Type	Price	Type	Price	Type	Price	Type	Price
1A7GT	.45	6ALS	.39	6BZ7	.95	6W4GT	.45	12Vegr	.86
183GT	.67	6AQ5	.39	604	.39	SWEGT	.45	12X4	.31
INSGT	.38	6AQ6	.36	6086	.45	6X4	.39	198666	1.15
11.4	.50	6AQ7	.68	60066	1.15	6X5GT	.35	1978	.75
INSGT	.62	SARS	.45	6F6	.45	786	.40	25BQ6GT	.75
1R5	.48	6ASS	.50	6H6	.83	7×6	.58	25L6GT	.41
185	.40	SATS	.39	6.15	.40	71.7	.77	25W4GT	.45
114	.48	GAU4GT	.70	6.16	.50	12AL5	.40	35A5	.41
104	.48	6AU5	.82	SKEGT	.39	12ATG	.35	3585	.36
105	.40	6AU6	.45	6L6	.62	12AT7	.65	35C5	.34
1 X 2	.65	SAVE	.39	6R7	.49	12AU6	.38	35L6GT	.45
3A4	.45	GAX4GT	.59	654	.39	12AU7	.58	35W4	.45
3Q4	.48	6BA6	.40	658GT	.51	12AV6	.50	35Z5GT	.45
3Q5GT	.48	6BA7	.57	#SA7GT	.41	12AV7	.60	45	.53
354	.48	6BC5	.49	6SB7Y	.76	12AX4GT	.55	SOBS	.41
3V4	.50	6806	.45	65C7	.59	12AX7	.55	SOCS	.41
SU4G	.55	GBEG	.39	65D7GT	.39	1.2BA6	.40	SOLGET	.51
SY3GT	.39	6BFS	.55	6SK7GT	.39	12BA7	.57	79L7GT	1.07
SY4G	.39	6BG6G	1.20	65L7GT	.49	12BE6	.41		.42
6AB4	.42	6886	.45	6SN7GT	.55	1.2BH7	.65	76	
6AF4	.92	GBJG	.41	65Q7GT	.37	12BY7	.65	81	1.25
SAFS	.75	6BK7	.89	6TB	.78	12027	.65	117L7GT	1.15
6AG5	.49	6BL7GT	.65	6U7	.56	125L7GT	.49	117P7GT	1.39
GAH4	.67	GBQGGT	.77	SUB	.59	125N7GT	.50	11723	.31
GAKS	.59	6BQ7A	.92	GVGGT	.48	125R7met	.55	807	1.25

T.V. PIX TUBE BRIGHTENER

\$1.39 PEE-WEE "HIDE-A-WAY" ANTENNA

HI-PO TV RECTIFIER TUBES LAST LONGER

Makes Picture brighter, lorger

HI-PO 567 TO REPLACE \$1.39 TO REPLACE \$1.95

FREE FIVE 1L4 TUBES INDIVIDUALLY CARTONED LIST \$11.25 WITH EVERY ORDER OF \$25.00 OR MORE.

Many 7 volt types not listed. All tubes individually boxed. For orders under \$10 add \$1 handling charge. Tubes offered subject to prior sale. Prices subject to change. All orders shipped F.O.B. 25% deposit on c.o.d. shipments.

SEND FOR FREE TUBE LISTING



NEW JERSEY TELEVISION SUPPLY CO.

Sole Distributor of NJRT Tubes 906B WESTFIELD AVE., ELIZABETH, N. J. EL. 3-6166

In DETROIT it's AARON ELECTRONICS

6025 Mt. Elliott, Detroit 11, Michigan



TG-34-A CODE KEYER-115

SUPREME METER = 5918 Heat

TRIUMPH SWITCH ASS'Y Model G. Str. 27.
8 pos_compl. wired w all volt multiplie

CHANGE OVER RELAY - DPDT

CARDWELL 7 GANG TUNING CONDS TVI SO to 1 does over the SOX contains 2" to \$2.95 on \$2.95 o 250, WITH ORDER BAL INCL. POSTAGE C.O. MICHIGAN RESIDENTS ADD 300 SALES TAK

HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO AND TELEVISION REPAIRMEN, SERVICEMEN AND STUDENTS

2 VOLS, 6 COMPLETE \$1 AO. A UDLELS T.V.-RADIO SERVICE LIBRARY— Highly Endorsed—1001 Facts—Over 1552 Pages— 625 Illustrations, Diagrams of Parts. Presents Impor-tant Subjects of Modern Radio, Television, Indus-trial Electronics, F.M., Pub-lie Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc.



IT PAYS TO KNOW!

The Basic Principles—
Construction—Installation
Operation—Repairs—
Trouble Shooting, Shows
How to get Sharp, Clear
T.V. Pictures, Install Aerials—How to Test, Explains
Color Systems, Methods of
Conversion, Terms, etc. Includes Ultra High Frequency (U.H.F.)—Valuable for Quick Ready Reference & Home Study, Tells How to Solve T.V.
& Radio Troubles—Answers Your Questions.

Get this Information for Yourself.

Get this Information for Yourself,
7 DAY TEST—ASK TO SEE IT!
-----MAIL ORDER-----

AUDEL, Publishers, 49 W. 23 St., N.Y. 10, N.Y. Mail AUDELS T. V. RADIO SERVICE LIBRARY 2 Vols. 56 on 7 days free trial. If O. R. I will recent \$1 in 7 days and \$1 monthly until \$6 is paid, Other wises I will return thom.

Name	
Address	
Occupation	
Employed by	



PRICES SLASHED FAR BELOW WHOLESALE!

rd brands only! One of largest stocks in We sell-buy-trade. WRITE FOR FREE OG JUST OFF PRESSES.

IAS	.70	DBLB	.BO	4525	.61
184	1.00	6K7	.75	SOLGGT	.69
1A7	.85	61.6	1.50	8.3	.95
105	.80	61.7	.95	OAZ	.95
106	1.00	6N7	.95	082	.91
107	1.00	654	.60	1021	3.50
1021	1.00	65A7	.80	2051	3.9
ILA4	.90	65C7	.95	2021	1.1
14.06	.90	65FS	.90	2526	3.2
SENS	.90	6SF7	1.00	282	.61
INSGT	-65	6567	.79	3597	1.9
184	.90	65H7	.75	3GP1	1.9
1×2A	.90	6517	.60	3HP7	2.9
306	.49	6587	.60	SAPI	3.2
304	.60	65L7GT	.75	SEPA	
10907	.80	65N7GT	.85	SEP7	3.2
354					1.9
574	.65	65Q7	.55	12AY7	.50
	3.40	6587	.70	1148	.4
5046	.70	6557	.90	304TL	6.9
5 V 4	1.00	6577	.65	701A	4.5
5×4	.65	GTS	.75	807	1.5
SYJGT	.65	GUM	1.00	609	2.9
5 Y 4 G	.95	SVEGT	.70	BILA	3.4
GA7	1.00	6W4GT	.60	813	7.9
SAGS	.75	6X4	.60	822	6.5
GACF	.90	6760	.85	830B	1.9
6AG7	1.20	7AG7	.85	MEGA	8.30
GAKS	.75	7C4	.90	8728	1.9
GALS	.55	707	.90	878	2.0
GAQS	.65	717	1.00	922	1.3
6AQ6	.75	7 N 7	.90	923	1.3
GATE	.45	1246	.85	931A	4.5
BUAR	.70	12AT7	.95	935	5.5
GAVSGT	1.10	12AU7	.95	954	.3
6846	1.00	12ANAGT	.85	955	.4
68666	1.60	1208	.80	956	.4
6HH6	.70	1286	.62	957	.4
6816	.70	1215	.60	938A	.4
6C4	.60	1287			.6
614	4.50	1288	.80	959	1.5
616	.70		.59	1619	.3
606		125C7	.89	1625	. 3
6C6	.95	125F7	.99	2050	1.3
656	.85	125H7	.70	2051	.9
	1.10	125L7GT	.92	5654	3.5
6F7	1 00	125N7GT	.BO	5614	1.5
6FBG	1.00	12507	.65	9001	1.30
6666	.85	125R7	.49	9002	.81
6N6	.65	25LGGT	.69	9003	1.2
616	-65				

add sales tax. Add postage to order, der \$5.00.

2		SP	ECIAL!	VACI	MUL	CAPACI	TORS	
6	6	mmfd.	30 KV	10.00	50	mmfd.	40 KV	14.50
10	548	mmfd	$20\mathrm{KV}$	10.00	100	mmfd.	10KV	12.00
000	50	mmfd.	$32\mathrm{KV}$	12.50	100	mmfd.	$20\mathrm{KV}$	14.00



ELECTRONICS Dept. A-F 7552 Melrose Ave Los Angeles 46, California

output level is 52 db below 1 volt/ dyne/ sq. cm, pickup pattern is essentially non-directional. The unit is supplied with a 20-foot attached singleconductor, shielded cable. The case is light-grey plastic.

A similar unit, but without the clip and with a 7 foot cable, is being offered as the Model 100.

NEW "FOLD-A-FLEX"

Angle Genesee Corporation, 107 Norris Drive, Rochester 10, N.Y. is now in production on the Model 33 "Fold-a-flex" speaker enclosure.

The new unit permits compensation for every speaker system, every room, and every acoustical condition. By means of a simple adjustment, it be-



comes a folded horn, infinite baffle, or bass reflex enclosure.

Provision is made for either a 12" or 15" speaker. A sealed compartment at the top is provided for tweeters and mid-range speakers with space available for a crossover network. It can be used with a single speaker originally and later expanded to a 2or 3-way system.

Standard finishes for the Model 33 are hand-rubbed blonde oak and mahogany. Custom finishes are also available. Dept. RN will supply full details on request.

SOUND PACKAGE

Asco Sound Corporation, 115 West 45th Street, New York, N.Y. is now offering a new sound package which has been designated as "High-Fi in Miniature.'

The system comprises the new Brociner "printed circuit" Mark 12 amplifier and an imported Lenco record player.

The new unit can be attached to any quality speaker system. Compact in design, the unit is an integration of the Brociner amplifier which includes all of the controls ordinarily found only on expensive units and the Lenco record player, of Swiss precision make, which is designed to play 33, 45, and 78 rpm records.

Set within a typical phonograph enclosure, the over-all unit measures 9" high, 16" wide, and 1314" deep. It is currently available in ebony, black lacquer, cherry mahogany, and natural birch finishes. -30-

Magnetic Recording

(Continued from page 59)

company failed and the stock became worthless. A Danish company was formed in 1909, and dissolved in 1916 without having manufactured a single machine. For some years after the "Telegraphone's" commercial failures, magnetic recording disappeared from the public eye and ear.


In the middle twenties a man with a wire recorder and a remarkable ability at persuasion obtained backing from German financiers and formed a company known as the Telegraphic-Patent-Sundikat. He was Kurt Stille and the company's purpose was that of selling licenses to manufacture magneticrecording equipment. Some say it was a modified American "Telegraphone." By dramatic salesmanship he succeeded in selling them to companies who actually went ahead and did manufacture the machine.

About 1930 a motion picture promoter named Blattner bought the right to manufacture Stille's machine for entertainment purposes. Blattner, however, used a steel tape. He named his machine the "Blattnerphone." It was used quite extensively by the British Broadcasting Company. It is believed that the "Blattnerphone" was the first magnetic tape machine to be used in the Western Hemisphere when the Canadian Broadcasting Corporation installed it in their Montreal offices for delayed broadcasts.

The "Blattnerphone" used a steel tape about 3/1000th of an inch thick, approximately a quarter inch wide, and required operating speeds of 3 to 6 feetper-second. It was discarded eventually for technical and economic reasons. It had only slightly better frequency range than the original Poulsen machine, noise was high, the reels were unwieldy and quite expensive.

Kurt Stille sold a license for the manufacture of dictating and telephone recording equipment to a Karl Bauer who formed the Echophone Company. Its product was called the "Dailygraph." It was the first magnetic wire recorder to use a magazine instead of separate reels, considerably simplifying operation. A number of different models were manufactured, the least expensive of which cost approximately \$600.00. The "Dailygraph" had good acceptance. In 1932, Bauer sold the Echophone Company to the International Telephone and Telegraph Company. It was then resold to the C. Lorenz Company in Germany who completely redesigned and marketed the machine under the name of "Textophone." This new recorder was placed on the market in 1933, about the time Hitler came to power. The Gestapo bought the "Textophone" in large quantities and gave magnetic recording a big commercial boost. The Lorenz Company also marketed a magnetic steel tape recorder which they called the "Stahltonmachine," and in

SUPER TV BARGAINS

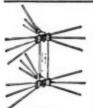

Fringe Master MOTORLESS DIRECTRONIC

NO GHOSTS
NO INTERFERENCE
ELECTRONICALLY
BERMED
NO MOTORS NEEDED

Model AN-519. 18-rice nearl, stacked array provides sparkling reception in city or fringe-all chamnels in all directions. Serviceman's kit provides 18 hi-tensil aluminum elements. 6-position birectronic Beam Selector. 1 set matched stacking hars. 75' TRLX Cable, universal U-Clamp.

To with

\$16.95

Tremendous Conical Bargain 2-Bay 16-Element Array \$4.99 LOTS OF 3 (ith Hi-Rand Adapters, Sturdy

29 Elements.
SINGLE LOVE . \$5.30 EACH
This conical 2-bay 16-element
array provides ultra-fine fringe
reception. Includes sixteen 3s
inch airplant type aluminum elements, including helmin adapters
fiels and its complete with one
pair of stacking bars to each
teed in earlow of three 16-element

\$1.95 set

Single 16-element arrays, separately bexed your cost \$5.30 each 3 Two-Ray Arrays per carton without Tie Rods \$13.50 carton 4 Bay Ultra-Fringe Stacking Assembly for

UHF CORNER REFLECTOR
ONLY \$2.99 EACH IN SINGLE LOTS
LOTS OF 6 \$2.50 EACH


This hi-gain URF Corner Reflector can only be offered you at this low, low price for a short time. 8 to 11 db gain across URF band, Order Model F-6,

NEW SPRING-SUMMER CATALOG AVAILABLE

Do not remit more than complete purchase price. Pay ahipping charges on receipt of goods. 25% deposit on all C.O.D. orders, please, Money-back guarantee.

National Electronics
OF CLEVELAND
THE HOUSE OF TV VALUES

ATLAS RADIALS

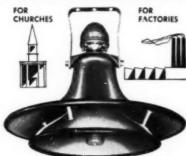





With uniform 360° coverage, non-resonant construction, and 100% storm-proofing, ATLAS Radial Driver Unit Projectors often solve the most difficult sound problems—are excellent for reproduction of speech, chimes and music. For complete details on Radials and the famous ATLAS line of Public Address and Microphone Stand Equipment . . .

WRITE NOW for FREE Catalog 553



1935 the German Broadcasting Company adopted it.

While all of these business exchanges and maneuvers were going on, another German, by the name of Pfleumer, developed the forerunner of the modern magnetic tape recorder. He conducted experiments with magnetic recording mediums consisting of paper or plastic tapes coated with powdered magnetic materials. His first efforts were somewhat crude and the results were a sandpaper-like roll of tape.

However, in 1931, several large research organizations, one of which was I. G. Farben, undertook the development of his idea. They designed and constructed a magnetic tape of paper with a very fine powdered coating and a recorder which could produce the best results yet obtained. They called it the "Magnetophone."

At its first demonstration in 1935 at the German Annual Radio Exposition in Berlin, the "Magnetophone" made a hit. The "hit" was due primarily to the astonishingly low cost of the "Magnetophone" magnetic recording tape which cost only 15 cents-per-minute as compared to \$1.00 per-minute for steel tapes. The new magnetic recording material was also less unwieldy. Very little information concerning the "Magnetophone" was available from that time until the end of World War II.

When the Allies entered Germany they discovered that the Nazis had continued to work on magnetic recording despite severe shortages of manpower and material. The equipment showed a remarkably high degree of development for both broadcast and military applications. Magnetic powder-coated tapes had been greatly improved and the "Magnetophone" had been redesigned to take fuller advantage of their capabilities.

American industry and research and development companies continued where the "Magnetophone" had left off, bringing magnetic recording tapes and equipment to their present low cost, long life, astonishing fidelity, and have so simplified their operation that the youngest child can, with brief instructions, make and play back his own, instantaneous magnetic tape recordings.

J. R. Bauserman (right) director of the bureau of vehicles in the Virginia Division of Motor Vehicles, presents a special license plate for mobile W4RSB to Joseph A. Johnson, owner of the station while Vernon McCoy, another ham, checks gear.



Quality Features TUNG-SOL PICTURE TUBES



Gun made of best grade non-magnetic steel.

Glass bead type assembly is stronger both mechanically and electrically—gives greater protection against electrical leakage.

Rolled edges in gun minimize corona.

Custom built stem with greater spacing between leads assures minimum leakage.

Low resistance of outside conductive coating minimizes radiation of horizontal oscillator sweep frequency.

Double cathode tab provides double protection against cathode circuit failure.

Selected screen composition resists burning (X pattern).

Rigid control of internal conductive conting provides utmost service reliability.

Designed for use with single or double field ion trap designs.

One-piece construction of parts assures better alignment.

Maximum dispersion of screen coating assures uniform screen distribution.

Tung-501 makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle.

TUNG-SOL



You Can Build A Reputation On Tung-Sal Quality



3.1-3	mos.			No.											 24	3
4-5.3	mes.	W	ith	Tub	68				*					8	-	.9
5.3-7	mes.	W	ith	Tub	618			2 6	*		10	*	 *	×	. 5	-9
T-20	ARC	5		7												. 19
E.A	Cont	WILL	T	ubes	. 1	Q4	to l	1.5	65.	13	×		F	y s	19	.9

ARC-5 OR 274-N RECEIVERS . 519.95

COMMA	ND REC	EIVERS	AS H	i, DO 1	HOT \$3.95
C-456	274-N I scel, Co	dodulat	or, Les	a Dyna	ffice:
-tr. 1 mm	n. Used	Luss	Tubes	N	ow 22.50
	s. With	Tubes			sed 7.95
6 men		Tuties.			
-6 mcs.	s. Like	New year			22.50

Plus All Accessories Needed For Above, Conversion Dope Available On Request. NEW SIG. CORPS RELEASE

SCR-183 12 V. RECEIVER AND TRANSMITTER
Covers Marine as Well as Aircraft and Park
With Proper Coll.

YOUR NAME ON OUR MAILING LIST FOR

COLUMBIA ELECTRONIC SALES



- TRACES TV SIGNALS AND VOLTAGES LOCATES DEFECTIVE COMPONENTS
- REQUIRES NO ADDITIONAL EQUIPMENT

ELECTRONICS CO. . Dept. 215, Queens Village, N. Y.

RADIV ENGINEERING27 MONTHS

Hadio engineering is a big field. There's room for you in it—If you're good. Get first class training at Indiana Tech. Intensive, specialized course, including strong basis in mathematics and electrical engineering, advanced radio theory and design, television, electronics. Mostern laboratories. Low rate. Also 8.8. DEGREE 810.27 MONTHS in Aeronautical, Chembal, Civil, Electrical and Mechanical Engineering. G.J. Government approach. Easier September, Decomber, March, June, Wayne while you are studying

INDIANA TECHNICAL COLLEGE 974 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. Engineering Degree in 27 months as checked.

Radio-Television
Civil Mechanical

SAVE SSS THOUSANDS OF BARGAINS Send Stamp for our

GIANT CATALOG

UNITED RADIO CO. SOA MARKET ST. NEWARK, N. J.

MANUFACTURERS' LITERATURE

The various listings presented in this section are for your convenience. The builetins, unless otherwise indicated, are available to all our readers. For prompt attention write directly to the manufacturer for this literature.

RADIO RECEPTOR DATA

Radio Receptor Co., Inc., 251 W. 19th Street. New York 11. N. Y. now has available for free distribution two new publications

Bulletin No. 177 is a comprehensive 24-page catalogue describing the company's "Seletron" selenium rectifiers. Fully illustrated with voltage curves. circuitry, tabular matter, and product applications, it devotes considerable space to an expanded tabulation of power rectifiers.

The second publication, Bulletin No. G-23, covers the company's line of germanium diodes and germanium transistors. The catalogue is illustrated with charts, voltage curves and diagrams, and product application data.

Either or both of the bulletins will be sent to engineers on request.

HI-FI EQUIPMENT

The Goody Audio Center, 235 W. 49th St., New York 19, N. Y. has published its first annual catalogue covering high-fidelity equipment.

The 88-page booklet, completely illustrated, lists the firm's entire selection of phono equipment, tuners, amplifiers, speakers, cabinets, and tape recorders. The booklet not only has a complete index but also lists items alphabetically by manufacturer within each major grouping.

OIL-FILLED CONDENSERS

Industrial Condenser Corp., Dept. RTN, 3243 N. California Ave., Chicago 18, Ill. has issued a four-page brochure on its line of tubular oil-filled conden-

Catalogue 1134 pictures and describes the company's "G" and "H" series which cover a capacity range from 5 to 8 ufd.

FACILITIES BROCHURE

Barnes & Reinecke, Inc., 230 E. Ohio St., Chicago 11, Ill. has outlined the scope of its engineering activities in a new brochure which is free on request.

The company offers engineering, research, development, design, and testing facilities, all of which are pictured and described in the booklet.

WINDINGS AND COILS

Jeffries Transformer Company, 1710 E. 57th St., Los Angeles 58, California has issued a comprehensive bulletin illustrating its line of typical coils and

The publication covers applications, manufacture, conductivity and resistivity, complete magnet wire characteristics table, tables on temperature coefficient of resistance, current, h.p., kw and kva etc

TV TRANSFORMER REPLACEMENTS

Application data on 38 new television transformer replacements is included in three bulletins, 485, 486, 487, just issued by Chicago Standard Transformer Corp., Addison and Elston Streets, Chicago 18, Ill.

The new Stancor replacements include 23 power transformers, 8 vertical output transformers, 5 width and linearity controls, 1 deflection yoke, and 1 filter choke. The power transformers are replacements for Motorola, Philco, RCA, Zenith, Silvertone, and other companies' original components.

RECTIFIER HANDBOOK

The Rectifier Division of Sarkes Tarzian, Inc., Bloomington, Ill. is now offering copies of its new, revised "Selenium Rectifier Handbook."

The 72-page book includes a revised selenium rectifier replacement guide and treats the different types of selenium rectifiers in some detail. Suggestions for applications and engineering data complete the book. The price is \$1.00 a copy.

MICROPHONE CHAPT

Since microphone sensitivity ratings are often specified in different systems, Shure Brothers, Inc. 225 W. Huron St., Chicago 10, Ill. is offering a "Microphone Sensitivity Conversion Chart" and explanatory guide.

The easy-to-read nomograph shows the relationship between open-circuit voltage response, open-circuit power response, and the RETMA sensitivity rating. The chart is designed for use by those engaged in buying, selling, installing or using microphones. Relative ratings can be determined in a few seconds. Copies of the chart are available on request.

ELECTRAN TRANSFORMERS

The Electran Manufacturing Co., 1901 Clybourn Ave., Chicago 14, Ill. has issued a 6-page folder which illustrates and describes its line of custommade transformers, reactors, chokes, special windings, and electronic de-

The folder incorporates a check list for those considering electrical or electronic components. Please specify Bulletin No. 55R when writing for this publication.

WIRE DATA

Columbia Wire & Supply Co., 2850 Irving Park Road, Chicago 18, Ill. has

COMMUNICATIONS RECEIVERS



COMPLETE KIT-This kit is complete COMPLETE KIT—This kit is complete with every part necessary to assemble into a finished receiver, including tubes and cabinet. Chassis is punched and marked. Mount the parts, wire it, align it and you have a fine receiver of commercial appearance, that can't be beat for 3 or 4 times the price. Parts layout, schematic diagram and alignment instructions are supplied.

Shpg. wright 45 Ibs. Shipped express only. F. G.E. Complete Kit 59 Kit Price to change without notice.

YAGI TV ANTENNAS

Camburn types VB-4 (Channel 4) and VB-5 (Channel 5) at way below the regular \$4.95 price. Either type only.

Write for new FREE Radio Surplus Catalog-

BOULEVARD ELECTRONICS, INC.

Mail Order Address: 1229 W. Washington Blvd., Chicago, III. Store Address: 4054 W. Belmont Ave., Chicago, III. RADIO AND TELEVISION SUPPLIES



mediately on contact.

LUBRICATES! . . . one drop eliminates scratch, hum and noise. PROTECTS1 . . . assures continued top

performance. Perfect Contact Restorer—cleans & restores volume controls, band switches, push button assemblies, electrical contacts. NO NOISE is not a carbon tet solution.



ELECTRONIC CHEMICAL CORP. 813 Communipaw Ave., Jersey City 4, N. J. issued a 36-page catalogue which lists the company's basic and well as new wire items

Designed to provide complete data for jobbers and manufacturers, this illustrated catalogue is available without charge.

PRINTED CIRCUIT DATA

Centralab, Division of Globe-Union, Inc., 900 E. Keefe Ave., Milwaukee 1, Wis. is now offering a new "Printed Electronic Circuit Guide." No. 3.

This 16-page brochure contains manufacturers' listings showing the usage of various printed circuits, circuit schematics showing printed circuit replacement of standard components. and a catalogue of printed circuits now available in the company's line.

TRANSISTORIZED CIRCUITS

P. R. Mallory & Co., Inc., North Tarrytown, N. Y. has issued two new booklets of interest to transistor engi-

The booklet, "Power Requirements for Transistor Circuits," is an 8-page bulletin written by the chief engineer of the company's battery division.

The other publication provides technical information on the firm's mercury cells and batteries for transistor circuit applications. This 6-page bulletin describes and pictures the units in the company's line designed especially for applications involving limited space and extremes in operating conditions.

Either or both of these publications are available on request. -30-

PHOTO CREDITS

Credit

Page

31 (right)Westinghouse Electric Corp. 35.... Stanford Research Institute 36 (left)...Zenith Radio Corporation 36 (second from left)..... 36 (center), 46Radio Corporation of America 36 (second from right) Sparks-Withington 36 (right) Stewart-Warner Corporation 43.....Tele-Beam Industries 44 (top)Altec-Lansing 44 (center)Cornell-Dubilier 44 (bottom) Heath Company 55...Allen B. Du Mont Laboratories 64......Universal Radio DX Club & Television Service Associations

ERRATA

In the article "A Transistorized Light-Beam Communications System" which appeared in the May issue, the emitter-current limiting resistor in Fig. 1 is shown as a 15,000 chm unit. This value should be 1500 chms.

Since publication of the article "Community TV" in our May issue, we have been informed that the community TV system in Reno will use single-channel amplifier strips throughout, employing automatic gain con-trol at every third amplifier, rather than broad-band amplifiers.

In addition, the total cost of the Williams ort, Pa. operation was over a quarter of million dollars rather than \$31,000.

You Can Become an

CTRICAL ENGIN

with a Bachelor of Science Degree IN 36 MONTHS



Major in Electronics or Power at Milwaukee School of Engineering

Everyone knows the tremendous opportunities ahead in electrical engineering. The expanding field of color television alone is one example. In addition to the demand for engineers, thousands of engineering technicians are needed. The Milwaukee School of Engineering can prepare you to become an engineer in 36 months or an engineering technician in 12 to 18 months. It'll pay you to look into it today. No obligation.

Technician and Service Courses - 12 to 18 months

In 12 months you can be a radio technician. An additional 6-month course qualifies you as a radio-television technician with an Associate in Applied Science degree. Or you can earn an industrial electronic technician certificate in 12 months.

These technician courses form the first third of the program leading to a B.S. Degree in Electrical Engineering. Twenty-one subjects in electronics, electronic engineering, and electronic design in this course.

Also offered are: radio-television service course (12 mos.); electrical service course (6 mos.); general preparatory and refresher



Faculty of specialists — 50,000 former students — Annual enrollment from 48 states and 23 foreign countries — Non-profit institution — 51st year of service — Course approved for veterans — Residence courses only.

MILWAUKEE SCHOOL OF ENGINEERING

MILWAUKEE SCHOOL OF ENGINEER Dept. Rh. 754. 1025 N. Milwaukee Street Milwaukee I, Wisconsin	
Bend me Free illustrated booklet on tunities in Electrical Engineering or Free trated booklet on careers in Radio TV.	
I am interested in	
Name Age	
Address	
CityZone State.	
If veteran, indicate date of discharge.	

DIAMONDS OR RHINESTONES?

How many times have you been fooled by cheap, imitation jewelry (or tubes) that looked like the "yeal" thing?

Too often cheap grices and extravagant claims have fooled the buyer into purchasing these imitations, instead of the genuine article.

Barry Electronics sells First Quality, Fully Guaranteed, individually boxed, Standard Brand tubes, Our tubes do not have to be "set or meter checked.", . . They are from original, sealed cartons from the five leading tube manufacturers.

Cheap imitations such as seconds, rewashed bar-gains, and off brands result in unnecessary call-backs, expenses, and loss of customer good will. . . . can place your confidence in our New, First y, fully guaranteed STANDARD BRAND Quality,

ASK FOR FREE NEWS BULLETIN AND HANDY-ORDER FORM

Tube Orders Over \$25.00, with full remittence, PREPAID to you in U.S.A.

RECEIVING TUBES

KE	CEIAIMO IOI	JE2
Type Not	Type Met	Type Net
OA295	BAKSOT .1.25	78878
	68675	70429
082 VR90 82		708 69
OC3 VRIOS 91	6866 74	78539
QD3 VR150.89	68E6 72	767 85
074 0744 55	68F594	7 F F R G . 1.55 7 H 7 7 Q 7 N 7 9 S
1A7GT77	68969 . 1.89	78770
187GT 77 183GT 90	68G6G . 1.89	7N795
1827 11.50		70798
183GT .90 1827 11.50 189GT .77 1L4 .60 1L6 .95	6816 . 85 68K5 . 95 68K7A 1.15 68L7QT 1.20	7Q798 7×790
1L4 60 1L6 95 1LAG 1.10 1L84 1.10		12AT655 12AT7105
	68L7GT 1.20 68N6 1.20 68Q6GT 1.27 68Q7A 1.23	12AT71.05
1LAN1.10	68N6 . 1.20	12AU665 12AU784
11.00	endent 1.27	12AV655
11.86 1.10 11.84 1.10 11.85 1.10 1N9GT .95 184 .65 185 .75	6847A 1.22	12AV655
184 65	68Y50 1.75	12AW688
18575	6877 1.28	12AX490
	604 56	
174 70 104 75	60650	12AY7 . 1.75
1U475	6C8675	12AZ792
104	6CD6G1.80	
1V1.03	6CL61.10	128AG70
1 v	6CU6 2.10	128A670 1280675
182890	08N6 120 68Q6GT 127 68Q7A 127 68K7GT 126 68K7GT 126 66K7 166 66K6 56 6CM6 79 6CL6 160 6CL6 210 6CU6 79 6F4 350	128E672 128H7 . 1.00
28235	6F43.50	128Y7 . 1.05
2×235	606 .75 6F4 3.50 6F5 68 6F5GT 68	12877 . 1.10 12877 . 1.10 12587
	6F5GT68	12587 69
30489	6F6G80	
304		12507 80 125H7 63
395GT90 38475	606085	1258763
31.490	6H6 52	
3V475	6G6G85 6H652 6J4 (RCA) .4.95	125J7
5AW4 1.50 5R4GY 1.50	6/555	125K7 69 125L7GT 65
584GY 1.50	616 80	
5V4097	61775 6K6GT65	125Q7QT63 125R769 125X7GT 1.10
	6K6GT65	125X7GT 1.10
5K4G79	6L6G 1.10	1457 76
5Y3GT48	6L6GA . 1.10	
52378	6L6M1.45	
523	6L760	258Q6GT 1.35 25L6GT 70
	6N7M70	25L6GT70
6A8795 6AC7114	egrat so	25W4GT .70
6AC7 1.14 6AD7G 1.85	654 63	252575
SAU/4 . 1.85	657M98 65A7 69	
6AG578 6AG7110	65A769 65C788	
6AG7 1.10	ASDIGT BO	26A7GT 4.50 26C61.25
GAHSGT49	65C7 88 65D7GT 80 65G7 66	26061.75
	65H798	28D71.55
6616 1.30	88.17 68	358572
6AKS-W 1.50	65K769	3585 70 35C5 72 35LGGT .70
6AKS-W 1.50	65L7GT . 65 65N7GT . 79	35C572
		35L6GT . 70
6ALS 60		35W4 45
6AN4 . 1.60	6T41.35	352370 3525GT50
6ANS . 3.65 6AQS72 6AQ673	6TR99	35ZSGT50 50A575
680673	6V36 1.30	5085 70
6855 75	SVSGT 67	50CS72
6A\$5 .75 6A\$6 .2.65	6W4GT65	SOLGET70
	SWEGT 82	80 66
GATGSR	6W4GT65 6W6GT82 6X5GT52 6X81.00	81
6AU4GT 1.00	6×8 1 00	83V1.15
6AT6 58 6AU4GT 1.00 6AU5GT 1.15 6AU6 63	7A775	84 6Z4 . 65
6AU669	7A869	
SAVSGT 1.10	78675	11726 . 1.00
6AV6 57		16204.50
DEREST	78776	. 5042 1.00

SPECIAL PURPOSE TUBES

Write fer our complete listing of Xmtg., Industrial, Special-Purpose and Crystal Diodes. We stock over 2,000 types at excellent prices.

Above is only a partial listing of our huge stock. Types not listed may be ordered at approx. the same savines. Many new special purpose types in stock.

AUTHORIZED DISTRIBUTORS CBS-HYTRON EIMAC WESTINGHOUSE

ORIGINAL JOBBERS' BOXED TUBES IN STOCK-LATE DATES, at WHOLESALE PRICE LEVELS!

TWO-COLORED TUBE CARTONS, with new Safety Partitions, Presents Tube Breakage. This Super-Gloss Red and Black Carton is the Out Distinctive Box Available Today! Minimum: 100 any one size, Quantity prices on request.

 SIZE
 EACH

 Miniature
 (6AU5, 6AL5, etc.)
 \$.01

 GT
 (6SN7, 6W4, etc.)
 .0125

 LARGE GT
 (1HEL 6HQGGT, etc.)
 .015

 LARGE G
 (5U46, 0HGGG, etc.)
 .02

Terms: 25% with order, balance C.O.D. Il merchandise guaranteed. F.O.S., N.Y.C. PHONE: REctor 2-2562

ARRY ELECTRONICS CORP. 136-F LIBERTY ST. N. Y. 6, N. Y.

JULY 1954

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

Aron Electronics	. 115 . 111 . 115 . 67 . 26 . 90 . 119 . 127 . 81 . 125 . 3 . 9 . 123 . 117 . 122 . 1111 . 104 . 6 . 8 . 8 . 8 . 8 . 8 . 8 . 9 . 9 . 104 . 105 . 105
Acro Products Co. 86 Acros Products Co. 109 Airex Radio Corp. 100 All Channel Antenna Corp. 76 All Channel Antenna Corp. 76 All Channel Antenna Corp. 13 American Microphone Co. 107 American Microphone Co. 107 American Television & Radio Co. 121 Amplifier Corp. of America 113 Arkay Radio Kits, Inc. 116 Arkay Radio Kits, Inc. 116 Arrow Sales, Inc. 82 Ashe Radio Co. Walter 65 Ashe Radio Co. Walter 65 Associated Industries 122 Audei Publishers 123 Baltimore Technical Institute 124 Bell Telephone Laboratories 24 Bell Telephone Laboratories 24 Bell Telephone Laboratories 28 Bonica Newsreel Club 122 Boulevard Electronics, Inc. 127 Burstein-Applebee Co. 124 CBS-Hytron 19 Cannon Electronics Corp. 76 Cannon Electronics Corp. 126 Centralab 216 Centralab 217 Centralab 218 Centralab 219 Centralab 219 Centralab 210 C	. 115 . 111 . 115 . 67 . 26 . 90 . 119 . 127 . 81 . 125 . 3 . 9 . 123 . 117 . 122 . 1111 . 104 . 6 . 8 . 8 . 8 . 8 . 8 . 8 . 9 . 9 . 104 . 105 . 105
Airex Radio Corp. All Channel Antenna Corp. All Channel Antenna Corp. All Channel Antenna Corp. All Channel Antenna Corp. American Microphone Co. American Microphone Co. American Television & Radio Co. Amplifier Corp. of America Amplifier Corp. of America Arkay Radio Kits, Inc. Arkay Radio Kits, Inc. Army Surplus Outlet. Artisticus Outlet Outlet. Artisticus Outlet. Antional School of Engineering. Amusical Masterpice Society, Inc., The. Artisticus Outlet. Artisticus Outlet. Artisticus Outlet. Antional School of P. Radio Corporation, The. Artisticus Outlet. Artisticus Outlet. Antional School of P. Radio Corporation of America Outleto	.115 .67 .26 .90 .119 .127 .81 .93 .111.125 .3 .9 .123 .117 .124 .111.104 .6 .88 .121 .84 .96 .117
Allied Radio Corp. 13 Allied Radio Corp. 13 American Microphone Co. 107 American Television & Radio Co. 121 Amplifier Corp. of America 113 Arkay Radio Kits, Inc. 116 Army Surplus Outlet 121 Army Surplus Outlet 121 Ashe Radio Co. Walter 65 Associated Industries 122 Allas Sound Corp. 125 Audie Publishers 123 Baltimore Technical Institute 122 Berlant Associates 28 Bell Telephone Laboratories 24 Bell Telephone Laboratories 24 Berlant Associates 28 Bonica Newsreel Club 122 Boulevard Electronics, Inc. 127 Burstein-Applebee Co. 124 CBS-Hytron 19 Cannon Electric Company 78 Cannon Electric Company 78 Cannon Electronics Co. 166 Communications Company, Inc. 176 Century Electronics Co. 166 Communications Equipment Co. 94 Communications Equipment Co. 94 Radio Corporation ARadio Corp. Mattison Television & Radio Corp. McGraw-Hill Book Co. 16c. 167 Mattison Television & Radio Corp. McGraw-Hill Book Co. 16c. 166 Mattison Television & Radio Corp. 121 Mattison Television & Radio Corp. 121 Mattison Television & Radio Corp. 122 Mattison Television & Radio Corp. 124 McGraw-Hill Book Co. 16c. 186 McGraw-Hill Book Co. 16c	. 67 26 90 119 127 81 93 . 11 125 . 3 9 . 123 . 117 . 122 . 111 . 104 6 . 88 . 121 . 84 . 96 . 117
Allied Radio Corp. American Microphone Co. American Television & Radio Co. Amplifier Corp. of America. Arkay Radio Kits, Inc. Army Surplus Outlet. Army Surplus Outlet. Ashe Radio Co., Walter. Ashe Radio Co., Inc. Bussical Masterpiece Society, Inc., The. National Company. National Electronice of Cleveland. National Radio Institute. National Radio Institute. National Radio Institute. National Radio Institute. National Schools. New Jersey Television Supply Co. Onan & Sons, Inc., D. W. P-A-R-T-S, Inc. Palley Supply Co. Precision Electronics Corp. Premier Radio-TV Supply Prentice-Hail, Inc. Progressive "Edu-Kits", Inc. Quietrole Company Q. T. Sales. Collins Audio Products Co., Inc. 8 W Electronics. RCA Institutes, Inc. Progressive "Edu-Kits", Inc. RCA Institutes, Inc. RCA Institutes	. 26 . 90 . 119 . 127 . 81 . 93 . 111 . 125 . 3 . 9 . 123 . 117 . 122 . 111 . 104 . 6 . 88 . 121 . 84 . 96 . 117
American Microphone Co. American Television & Radio Co. Amplifier Corp. of America Amplifier Corp. of America Arkay Radio Kits, Inc. Arkay Radio Kits, Inc. Arkay Radio Kits, Inc. Arrow Sales, Inc. Ashe Radio Co. Arrow Sales, Inc. Bassociated Industries Atlas Sound Corp. Associated Industries Alas Sound Corp. Associated Industries Alas Sound Corp. Astional Company Antional Company Antional Electronics of Cieveland Antional Schools National Electronics of Cieveland National Schools National Schools National Schools National Electronics of Cieveland National Schools National Company	. 26 . 90 . 119 . 127 . 81 . 93 . 111 . 125 . 3 . 9 . 123 . 117 . 122 . 111 . 104 . 6 . 88 . 121 . 84 . 96 . 117
American Television & Radio Co. 21 Amplifier Corp. of America 113 Amplifier Corp. of America 113 Arkay Radio Kits, Inc. 116 Army Surplus Outlet 121 Army Surplus Outlet 121 Ashe Radio Co. Walter 65 Associated Industries 122 Atlas Sound Corp. 125 Atlas Sound Corp. 125 Baltimore Technical Institute 122 Barry Electronics Corp. 128 Beil Telephone Laboratories 24 Beil Telephone Laboratories 24 Berlant Associates 28 Bonica Newsreel Club 122 Boulevard Electronics, Inc. 127 Bourstein-Applebee Co. 124 CBS-Hytron 19 Candler System Co. 76 Cannon Electric Company 78 Canton Electronics Corp. 126 Centrury Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co. The 114 Cleveland Institute Of Radio Electronics 77 Collims Audio Products Co. Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Corp. 80 Communications Company, Inc. 18 Communications Equipment Co. 94 Communications Company 18 Communications Company 16 Communications Company 16 Communications Company 17 Communications Company 17 Communications Company 18 Communications Company 19 Communications Company 19 Communications Company 10 Communications C	.119 .127 .81 .93 .11 .125 .3 .9 .123 .117 .122 .111 .104 .6 .88 .121 .84 .96 .117
Arkay Radio Kits, Inc.	.127 , 81 . 93 . 11 .125 . 3 . 9 .123 .117 .122 .111 .104 . 6 . 88 .121 . 84 . 96 . 117
Army Surplus Outlet. 121 Moss Electronic Distributing Co., Inc. . 82 Arrow Sales, Inc. 82 Musical Masterpiece Society, Inc., The Ashe Radio Co., Walter 65 Associated Industries 122 National Company . 1 National Electronics of Cieveland National Schools National Schools National Schools National Schools National Schools New Jersey Television Supply Co. Mational Schools New Jersey Television Supply Co. National Schools New Jersey Television Supply Co. New Jersey Television New Suck Televisio	, 81 , 93 , 11 , 125 , 3 , 9 , 123 , 117 , 122 , 111 , 104 , 88 , 121 , 84 , 96 , 117
Arrow Sales, Inc. 82 Ashe Radio Co. Walter 65 Associated Industries 122 Atlas Sound Corp. 125 Audei Publishers 123 Baltimore Technical Institute 122 Berry Electronics Corp. 126 Bell Telephone Laboratories 24 Berlant Associates 28 Bonica Newsreel Club. 122 Bonica Newsreel Club. 122 Boulevard Electronics, inc. 127 Burstein-Applebec Co. 124 CBS-Hytron 19 Candder System Co. 76 Cannon Electric Company 78 Capitol Radio Engineering Institute 25 Centralab. 21, 68, 75, 113 Century Electronics Corp. 27 Cincinnati Ventilating Co., The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co., Inc. 87 Collumbia Electronics Corp. 89 Columbia Electronics Corp. 89 Columbia Electronics Corp. 186 Communications Company, Inc. 186 Communications Equipment Co. 94 Radio Captsmen, Inc., The Radio Television News Book Service	. 93 . 11 . 125 . 3 . 9 . 123 . 117 . 122 . 111 . 104 . 6 . 88 . 121 . 84 . 96 117
Ashe Radio Co., Walter 65 Associated Industries 122 Audei Publishers 123 Baltimore Technical Institute 122 Barry Electronics Corp. 128 Bell Telephone Laboratories 24 Berlant Associates 28 Bonica Newsreel Club. 122 Boulevard Electronics, Inc. 127 Boulevard Electronics, Inc. 127 Bousevard Electronics, Inc. 127 Bousevard Electronics, Inc. 127 Candier System Co. 124 CBS-Hytron 19 Candier System Co. 76 Cannon Electric Company 78 Canton Electronics Co. 124 Centralab. 21, 68, 75, 113 Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co., The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co., Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Sales 126 Communications Company, Inc. 18 Radio Carfsmen, Inc. 25 Communications Equipment Co. 94 Radio Television News Book Service 120 National Company National Electronics of Cieveland. National Electronics Ocips National Electronics Supply Co. Pak Flectronics Co. Pak Electronics Corp. Precision Electronics Corp. Precision Electronics Corp. Precision Electronics Corp. Prentice-Hail, Inc. Progressive "Edu-Kits", Inc. 25 Collins Audio Products Co., Inc. 85 Columbia Electronics Sales 126 Communications Company, Inc. 18 Radio Carfsmen, Inc., The Communications Equipment Co. 94 Radio Television News Book Service	. 11 .125 . 3 . 9 .123 .117 .122 .111 .104 . 6 . 88 .121 . 84 . 96 . 117
Astociated Industries Allas Sound Corp. Allas Sound Corp. Baltimore Technical Institute Bell Telephone Laboratories Bell Telephone Laboratories Berlant Associates Bonica Newsreel Club Bory Electronics, Inc. Bory Electronics Co. Bory Elec	.125 .3 .9 .123 .117 .122 .111 .104 .6 .88 .121 .84 .96 .117
Atlas Sound Corp. Audei Publishers 123 Baltimore Technical Institute 124 Barry Electronics Corp. 128 Bell Telephone Laboratories 24 Berlant Associates 26 Bonica Newsreel Club 122 Boulevard Electronics, Inc. 127 Burstein-Applebee Co. 124 CBS-Hytron 19 Candier System Co. 27 Cannon Electric Company 27 Cannon Electric Company 28 Cannon Electronics Corp. 29 Cantury Electronics Co. 21 Centralab 21, 68, 75, 113 Centralab 22, 68, 75, 113 Centralab 23, 75, 113 Centralab 24 Centralab 25 Collins Audio Products Co., Inc. 26 Channel Master Corp. 27 Cincinnati Ventilating Co., The. 114 Cleveland Institute of Radio Electronics 27 Collins Audio Products Co., Inc. 28 RCA Institutes, Inc. 29 Collimbia Electronics Sales 26 Communications Company, Inc. 29 Communications Company, Inc. 29 Communications Company, Inc. 21 Radio Television News Book Service	3 9 123 117 122 111 104 6 88 121 84 96 117 98
Baltimore Technical Institute 122 Barry Electronics Corp. 128 Bell Telephone Laboratories 24 Berlant Associates 28 Bonica Newsreel Club. 122 Bonica Newsreel Club. 122 Bonica Newsreel Club. 122 Burstein-Applebee Co. 124 Burstein-Applebee Co. 124 CBS-Hytron 19 Candier System Co. 76 Cannon Electric Company 78 Capitol Radio Engineering Institute 25 Centralab. 21, 68, 75, 113 Centralab. 21, 68, 75, 113 Centry Electronics Corp. 27 Cincinnati Ventilating Co., The 114 Cleveland Institute of Radio Electronics 77 Cincinnati Ventilating Co., The 114 Cleveland Institute of Radio Electronics 77 Collims Audio Products Co., Inc. 87 Collims Audio Products Co., Inc. 87 Communications Company, Inc. 18 Communications Company, Inc. 19 Communica	. 9 .123 .117 .122 .111 .104 .6 .88 .121 .84 .96 .117
Baltimore Technical Institute. 122 Barry Electronics Corp. 128 Bell Telephone Laboratories 24 Berlant Associates 28 Bonica Newsreel Club. 122 Boulevard Electronics, Inc. 127 Bourstein-Applebee Co. 124 CBS-Hytron 19 Candler System Co. 76 Cannon Electric Company. 78 Canton Electronics Company. 18 Centralab. 21, 68, 75, 113 Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co. The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co. Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Sales 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Radio Carftsmen, Inc., The Communications Equipment Co. 94 Radio Television Supply Co. 94 P-A-R-T-S, Inc. 9 Palley Supply Co. 9 Pall	.123 .117 .122 .111 .104 .6 .88 .121 .84 .96 .117
Barry Electronics Corp. Bell Telephone Laboratories 24 Berlant Associates 28 Bonica Newsreel Club 122 Boulevard Electronics, Inc. 27 Bourstein-Applebee Co. 124 CBS-Hytron 19 Candler System Co. 76 Cannon Electric Company 78 Capitol Radie Engineering Institute 27 Centralab 21, 68, 75, 113 Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co. The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co. Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Corp. 186 Communications Company, Inc. 186 Communications Company, Inc. 186 Communications Equipment Co. 94 Radio Craftsmen, Inc., D. W. P-A-R-T-S, Inc. P-A-R-T-S, Inc. Peak Electronics Co. Peak Electronics Corp. Precision Electronics Corp. Precision Electronics Premier Radio-TV Supply Prentice-Hail, Inc. Progressive "Edu-Kits", Inc. Quietrole Company Q. T. Sales. RCA Institutes, Inc. 29 Columbia Craftsmen, Inc., The Radio Carporation of America Communications Company, Inc. 18 Radio Television News Book Service	. 122 . 111 . 104 . 6 . 88 . 121 . 84 . 96 . 117
Berlant Associates 28 Bonica Newsreel Club. 122 Boulevard Electronics, Inc. 127 Bourstein-Applebee Co. 124 CBS-Hytron 19 Candler System Co. 76 Cannon Electric Company. 78 Capitol Radio Engineering Institute 25 Centralab. 21, 68, 75, 113 Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co. The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co. Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Corp. 89 Columbia Electronics Sales 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Radio Craftsmen, Inc., The Communications News Book Service.	. 122 . 111 . 104 . 6 . 88 . 121 . 84 . 96 . 117
Bonica Newsreel Club. 122 Boulevard Electronics, Inc. 127 Boulevard Electronics, Inc. 127 Burstein-Applebee Co. 124 CBS-Hytron 19 Candler System Co. 76 Cannon Electric Company. 78 Canton Electronics Co. 76 Cannon Electric Company. 78 Capitol Radio Engineering Institute. 25 Centralab. 21, 68, 75, 113 Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co. The. 114 Cleveland Institute of Radio Electronics. 77 Collins Audio Products Co. Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Sales. 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Radio Television News Book Service.	.111 .104 . 6 . 88 .121 . 84 . 96 .117
Boulevard Electronics, Inc. 127 Burstein-Applebe Co. 124 CBS-Hytron 19 Candler System Co. 76 Cannon Electric Company 78 Capitol Radio Engineering Institute 25 Centralab. 21 68 75 113 Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co. The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co. Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Sales 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Radio Captsion News Book Service .	. 104 . 6 . 88 .121 . 84 . 96 .117
Burstein-Applebee Co. 124 CBS-Hytron 19 Candier System Co. 76 Cannon Electric Company 78 Capitol Radio Engineering Institute 25 Centralab 21, 68, 75, 113 Centralab 21, 68, 75, 113 Centralab 21, 68, 75, 113 Centralab 22, 68, 75, 113 Centralab 21, 68, 75, 113 Centralab 22, 68, 75, 113 Centralab 21, 68, 75, 113 Centralab 22, 68, 75, 113 Centralab 21, 68, 75, 113 Centralab 22, 68, 75, 113 Centralab 21, 68, 75	. 6 . 88 .121 . 84 . 96 .117
CBS-Hytron 19 Platt Electronics Corp. Candler System Ce. 76 Precision Electronics Cannon Electric Company. 78 Premier Radio-TV Supply. Capitol Radio Engineering Institute. 25 Premier Badio-TV Supply. Centralab. 21, 68, 75, 113 Century Electronics Ce. 26 Channel Master Corp. 27 Cincinnati Ventilating Co., The. 114 Cleveland Institute of Radio Electronics. 77 Collins Audio Products Co., Inc. 85 Collumbia Electronics Corp. 89 Columbia Electronics Sales. 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Radio Craftsmen, Inc., The Communications News Book Service.	. 88 .121 . 84 . 96 .117
Candler System Co. 76 Cannon Electric Company 78 Capitol Radie Engineering Institute 2 Premier Radio-TV Supply 2 Centralab 21, 68, 75, 113 Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co., The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co., Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Sales 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Communications Equipment Co. 94 Radio Television News Book Service	. 121 . 84 . 96 .117
Cannon Electric Company. 78 Capitol Radio Engineering Institute. 25 Centralab. 21, 68, 75, 113 Century Electronics Ce. 126 Channel Master Corp. 27 Cincinnati Ventilating Co., The. 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co., Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Sales. 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Capitol Radio Television News Book Service.	. 84 . 96 .117
Centralab	. 117
Century Electronics Co. 126 Channel Master Corp. 27 Cincinnati Ventilating Co., The. 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co., Inc. 85 Columbia Electronics Corp. 89 Columbia Electronics Sales. 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Communications Equipment Co. 94 Communications News Book Service.	. 98
Channel Master Corp. Cincinnati Ventilating Co., The 114 Cleveland Institute of Radio Electronics 77 Collins Audio Products Co., Inc. 85 Collins Audio Products Corp. 89 Columbia Electronics Corp. 89 Columbia Electronics Sales 126 Communications Company, Inc. 18 Communications Equipment Co. 94 Communications Equipment Co. 94 Communications Reguipment Co. 94 Comm	
Cincinnati Ventilating Co., The	. 122
Collins Audio Products Co., Inc	
Columbia Electronics Corp. 89 Radiart Corporation, The	
Columbia Electronics Sales	
Communications Company, Inc	
Communications Equipment Co	
Constant Police	
Concord Radio	. 79
Corona Radio & T.V. Co	
Coyne Electrical School	
De viy recunical institute 3	
Delco Radio Corporation	
Editors & Engineers, Ltd	
Electronic Chemical Corp	
Electronic Instrument Co., Inc. (EICO) Standard Surplus	
Electron Tube Wholesalers, Inc	
Electro-Voice	
Fair Radio Sales. 95 Supreme Publications	
Fairchild Recording Equipment Corp 105 Sylvania Electric Products, Inc	. 7
Fisher Radio Corporation	.130
G & G Radio Supply Co	. 86
G & H Wood Products Co	
G. L. Electronics, Inc	
General Electric Co	
Goodheart, R. E	
Grantham School of Electronics	
Greenlee Tool Co	
H & H Electronic Supply, Inc	
Harjo Sales Co	
Harvey Radio Company, Inc	
Menchaw Padie Supply 103	
Hughes Research and Development	
Laboratories	
Indiana Technical College	
Instructograph Company	
Wholesale Radio Parts Co., Inc.	.101
J. J. Glass Electronics Co. 122 Windsor Electronic Tube Co. 122	
JSH Sales Co124	
Jones & Laughlin Steel Corporation 14 Zingo Products	. 86

Rate 50c per word. Minimum 10 words

RADIO ENGINEERING

COMPLETE radio, electronics theory & practice: television; broadcasting; servicing; aviation, ma-rine, police radio. 12 or 18 months. Catalog. Val-paraiso Technical Institute, Dept. N, Valparaiso.

FOR SALE

DIAGRAMS—Radio \$1.00; record changers, re-corders \$1.25. Television with service data \$2.00. Where model unknown, give part numbers. Kra-mer's Radio Service, Dept. 853, 36 Columbus Ave., New York 23, N. Y.

TAPE Recorders, Tapes, Accessories, Unusual Values, Dressner, 624-R East 20th St., N.Y.C. 9. FREE: Get our monthly electronic lists. Dick Rose, Everett, Wash.

CODE practice oscillators New, guaranteed, \$4.00 postpaid. Stout, 2241 E. Broadway, Muskegon,

TELEVISION Receivers, \$30 up. W4. South Randolph, Arlington 4, Virginia.

TV-FM antennas, All types including UHF, Mounts, Accessories, Lowest prices, Wholesale Supply Co., Dept. II, Lunenburg, Mass.
AN/Apr.4, other "APR.", "ARR.", "TS.", "LE.," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment, Describe, price in first letter. Engineering Associates, 434 Patterson Rd., Dayton 9, Ohio.

5,000-6J5 TUBES, (Army). Rough but new, tested. 5 for \$1, postpaid. Guaranteed. Holt Radio, 10659 Magnolia, North Hollywood, Calif.

CUSTOM made high-fidelity speaker enclo utility cabinets. Wilmington Cabinet Company, Box 394, Wilmington, North Carolina.

MANUFACTURERS Surplus. 60 note triple stacked shunt keying mechanisms. Octave wired isolating resistor to each palladium contact. 2 types, Great. 16° -8° -4°. Swell, 8° -4° -2°5′ Make your own electronic organ with these basic units. \$10.00 each. Minshall-Estey Organ, Inc., P.O. Box 537, Brattleboro, Vermont.

ALUMINUM tubing, angle and channel, plain and perforated sheet. Willard Radcliff, Fostoria, Ohio. HEARING Aids. Zeniths, Western Electrics. Re-conditioned. Make miniature transmitters or re-ceivers. Complete with ear piece and cords, \$16.00 each. Gloria Davis, 12 Oak Drive, Great Neck,

SPECIAL on tape recorders and tape. Brush "Sound Mirror" tape recorder model No. RK 442—brand new (sealed carton). \$129.75. Regularly priced at \$259.50. Brush 1200" plastic tape on 7" metal reels—\$2.50 each. Regularly priced at \$5.50. Asco Sound Corp., 115 West 45 Street, New York, N. Y.

VanSICKLE displaying all National Receivers, of-fers big trades, easy terms. W9KJF, 1320 Calboun, Ft. Wayne, Indiana.

TOWER TRUCK Telescoping tower for TV reception surveys. Mounted on 4 wheel drive army personnel carrier. Extends to 70 feet. Truck and tower \$300.00 F.O.B. M. & M. T. V. Co., 7 Maple Ave., Morristown, N. J.

COMPLETE speaker reconing service, inventories over \$500.00 distributor's cost; closeout \$200.00. Selling first come first serve basis. Radio Labora-tories, 215 King Street, Charleston 5, S. C.

TELEVISION sets \$22 up. Jones TV, 1115 Rambler, Pottstown, Pa

"DIAGRAMS for repairing radios \$1.00. Record-Changers \$1.50. Television \$2.00. Give Make, Model. Diagram Service, 672-RN, Hartford 1,

WANTED

WILL buy all ART-13/type T-47A \$200.00 ART-13/type T-47 \$150.00. BC-318 unmodified \$65.00. BC-318 modified \$50.00. APN-9 \$200.00. ARC1 Radio \$200.00. BC-312 Receiver \$60.00. BC-342 Beceiver \$60.00. Ship Via Express C.O.D., Sub-ject to Inspection to H. Finnegan, 49 Washington Ave., Little Ferry, N. J.

WANTED: Selsyns type 3—\$40.00 each; Size 1 and other sizes will advise; Torque Units, Ampli-dynes, Autosyns, Tubes. Subject to Inspection Electro, 50-58 Eastern Ave., Boston 13, Mass.

Electro, 59-58 Eastern Ave., nosion 19, mass. TUBES wanted, Highest prices paid, 1P21, 2C40, 3B24, 3C22, 3C45, 3B21A, 3E29, 4C35, 5C22, 3047H & TL, WE, 447A, 4507H & TL, 715B & C, 723AB, 726B & C, 807, 810, 813, 829B, 832A, 5691, 5992, 5693 All 2J-2K & 4K Series, Sub-miniature & receiving types. Send your List. Phone Rector 2—5245, "Tab", 111 Liberty St., N. Y, 6, N. Y. 572E ET-CEMENTETER, trace sond-receive 9.

"TELETYPEWRITERS, tape send-receive or re-ceive only, Model 14, any quantity or condition. Box 540, Radio & Television News."

CORRESPONDENCE COURSES

USED correspondence Coutses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Ala.

PASS amateur theory exams. Check yourself with sample FCC-type questions & novice & general class examinations. All for only 50c. American Electronics, 1203½ Bryant Ave., New York 59,

USED Correspondence Courses and Educational books Bought, Sold, Rented. Catalog Free. Edu-cational Exchange, Summerville, Ga.

MISCELLANEOUS

ALL makes speakers repaired. Amprite Speaker Service, 70 Vesey St., New York City 7.

BUILD your own electronic organ or miniature electronic brain. Jim Kirk, Webeg, 1552 Church St., San Francisco 14, Calif.

TEST Equipment Repaired and calibrated by fac-tory staff. All makes. Solar, Simpson, Triplett, Heath, etc. Immediate service. Bouglas Instru-ment Laboratory, 176 Norfolk Avenue, Boston 19.

POPULAR ELECTRONICS Watch for August **RADIO & TELEVISION NEWS**

A SWEET OSCILLOSCOPE DEAL

ASB-7 Radar Indicator Unit: For conversion to test scope or for use as modulation monitor. Has standard test-scope CR tube, B Cent, V Cent, Brill, Foe, Gain, and range selection switch. External power source was used. Tubes: 4-6AC7, 3-6H6, 1-5BP1. \$9.95.

ASB RECEIVER: Freq. range: 510-555 MC. With tubes. New, Reduced to	
ASB TRANSMITTER: Freq. range: 510-555 MC, Complete with tubes, Only	4.95
ASB POWER SUPPLY: New	4.95

ASB ANTENNA SWITCHING UNIT, New. 2.95

BC-929 Contains power supply 110 V. 400 cycles, has 7 tubes such as 3CP1, brand new, complete \$14.95 with tubes, Each ...

ARC-5/R-28 2 MTR RCVR-2 meter superhet, also lutely one of the BRS-T available today! Times from 100 to 156 mes, in four cristal channets, (familiconverted to continuous tuning.)

[17.9] \$17.95

T-23 ARC-5 Transmitter for above, 100-156 MC, Complete w/Tubes, Used exc.\$29.95

RL-42 Reversible beam rotator motor 8500 rpm, attached to gear reduction box which drops speed to 120 rpm.

BEAM ANTENNA SELSYN TRANSMIT- \$12.00

w Freq. Crystals—FT 241 A for SSB, lattice fil-r, 1-2" spc. 54th harm channels listed by fund. Fractions omitted.

See previous Radio-TV News Issues for frequencies

49c each 10 for \$3.00

Command Equipment (274N-ARC5, ATA)

190-550 KC	\$14.95
La-a me	14.95
3-6 mc 5.95	9.95
5-9 mc 5.95	9.95
3-Rec. Rack	1.50
3-Control Head	2.50
BC 458 Transmitter 4.95	6.95
459 Transmitter 7.95	12.95
456 Modulator 1.95	3.95

Hundreds of items in stock. WRITE FOR NEW BULLETIN AND PRICES. Shipments F.O.B. warehouse. 20% Deposit on orders. Minimum order 55.00. Illinois residents, add regular sales tax remittance. Prices subject to change without

R W ELECTRONICS

Dept. N. 2430 S. Michigan Ave. Chicago 16, III. PHONE: Calumet 5-1281-2-3

FOR YOUR CONVENIENCE
www. West Coast Representative
ELECTRONICS TRADING POST Venice Blvd. Los Angeles, Calif. Phone: Richmond 7-4104

BROADCAST BAND-DIREC. TION FINDER and AERO

Ideal for Use in Boats, etc.

MN-26-C Hemote Controlled Navira-tional Direction finder and commu-nications receiver. Manual DF in any one of three freq. bands, 130 to 1500 KC, 24 V. Self contained dynamotor supply. Complete instal-lation, including receiver, control office control. Left-Right Indicator, plays, on line and fixe, shafts, oper, is math.

ALL UNIT	-				-		-				-			=0
MN-36-V	1.50	to 3.	25 1	66.	11.25	0.03	- 63	9.75	K	£.	13.	. 6		
to 7 m	REVIRCI	cles.	674.0	mp.	kram	alla	a t, i e	171					49	50
MN-26-C	alone	like	e ne	w									24	.95
MH-26-Y	as is	less	6 talls	08							, ,		4	.95
MN-20-E	Loop.	Bri	box	New										.95
MN-52 C	ank s	irive	. 54	156										.80
MN-26LB	Rece	iver	080	. fr	eu.	1.5	0-1	2	0	K	c.		9.	En
2.9-6m	e											q	3.	วบ

T-26 Telephone chest unit with F-1 Western El \$1.59 HS-23 Hendset, used \$1.89 new 4.50 M8-30, miniature headset. Used \$1.49, new 2.49 Threat Mike-T-30......tew .98 Lip Mike-Navy Type .98

T-45 Lin Mike, New .. RS38 Navy type carbon mike exc.ea. TS Handset with F I unit 2.45 J-38 or J-47 Telegraph key.....rach 98c 5BP1, 5FP7, 4AP10, 5AP1

OIL CONDENSERS 8 mid. oil condensers ee 600 VDC 98c ARB NAVY RECEIVER 198 KC

\$19.95 to 5 MC. Used, exc. BC-375 TRANSMITTER with TUS

AN/APR5A Airborne superhet radar search rec. Freq range 1000 to 3000 MC. Rec. has a 10 MC IF band aidth operating from 80/115 VAC, single phase 60 to 2600 cps, and one amp, at 26 VDC-

TUNING UNIT -- se.

complete with tubes AN APTS TRANSMITTER operates mer a freq. of 300 to 1100 MC; output 30 Watts. The carrier freq. is noise-modulated with effective random noise freq. up to 2 MC. Complete with tubes \$99.50

1-122 SIGNAL GENERATOR RF signal 15 to 25 MC and 90 to 125 MC; modulated at 400 cps. or 625 cps. Power Supply 100 to 135 VAC, 25 to 60 cps. \$49.50 NEW

8C669 Crystal Controlled Radio Receiver and 50 Watt Transmitter-freq. range 1700 to 1400 KC \$89.50 complete with tubes, new \$69.50 Used, exc. (F.O.B. Calif.)

129

\$49.50

INDUSTRIALS WRITE ON YOUR LETTERHEAD FOR POWER RECTIFIER CATALOG CHUCK MODEL 200 III-TORQUE OFWARTAN UL Appd. 2400RPM II-5 Volt AC-DC motor. Geared Chuck & Key. self-aligning—alliese—Ball Thrust Bearing. II-5 Volt AC-DC motor. Geared Chuck & Key. self-aligning—alliese—Ball Thrust Bearing. Model 4000 les Teril 125 RPM. Proverful II-5V AC-DC Motor w-9 drillsdease. 329.95 Model 1000 Streed Saw 14PP Ad)45-322.35 Grade, Crease Cut 810.95 Reg. Self-aligning—aligni SELENIUM RECTIFIERS THAT'S A BUY NUMECHRON Fleet TV-ClockBille, Walnut. 18. Special Lie, Walnut. 18. AUDIO COMPONENTS AUDIO COMPONENTS Electronoice triplay curt. \$1.98 RFX050 GE Rowed ... \$1.98 GE RFX040.78 Goldtone \$5.25 GE RFX041.MG Goldtone \$5.25 GE RFX041.MG Goldtone \$5.25 GE RFX053.001 & GOld diamonds \$2.38 RF3010 Bull. 6014 c.003 diamonds \$2.38 RF3010 Bull. 6014 c.003 diamonds \$2.38 RF3017 Bull. 6014 c.003 diamond \$2.38 RF3018 Bull. 6014 c 00 OHM Twinex 65M nuty, Durable. 00 Feet 000 Ft \$11.95; 5000 00 OHM Twinex 100: \$1.39 to 14VDC at 12 amps... to 28VDC at 4 amps... to 28VDC at 2 amps... to 28VDC at 2 amps... to 28VDC at 24 amps... to 28VDC at 50 amps... c 28VDC at 50 amps... C "TAS" feet delivery SPEC 100 Feet 31.95; 5000 Ft \$50 300 OMM Twines 1005Mi stra 100 OF 15.20 inco \$24 100 OF 15.20 inco \$24 100 OF 15.20 inco \$24 100 OF 15.20 inco \$25 100 OF 15.2 HIGH CURRENT PWR SUPPLIES 000 Variable 0-28VDC. Complete Control of the Control o 106 WATT SEC PHOTOFLASH KIT-106 WATT SEC PHOTOFLASH KIT— 106 WATT SEC PHOTOFLASH KIT— 122 MFPL/50 V Total 103W Seechs. Resistors, capacitors, capacitors, Resistors, capacitors, Resistors, capacitors, Resistors, capacitors, Resi RECTIFIER APMINS Primary 113V 80 C4-24-36V 4 condary 0-9-12-18-24-36V 4 Amp ... \$6.75; 2 \$28-55 12 Amp ... \$1.575; 2 \$28-55 2 N 12Volts /2 Augs ... \$1.58 2 N 12Volts /2 Augs ... \$1.58 2 N 12Volts /2 Augs ... \$1.58 4 Amp ... \$7.95 RECTIFIER CHOKES 4 Amp ... \$7.95 MICA CONDENSERS D TRANSFORMES TRANSFORMES ALL 115V 60CVC 1NPUTS SBOOV 2088A, 0.3V 6A, 2.5V BALL 115V 60CVC 1NPUTS SBOOV 2088A, 0.3V 6A, 2.5V SBOOVT 1808A, 2.2 5V 28, 288, 3 for 315 SBOOVT 1888A, 2V 25, 3V 28, 288, 3 for 315 DIGITIE FIRST 100 MA, 3V 2.3A, 3V 1A DIGITIE FIRST 3 400 MB, 2.5V THORDARD 2V 71A, 4V 1A, 4V 1A, 4V 1A COUNTY 700 A, 5VCT 1A, 3V 1A SBOOVT 508A, 2V 1A, 3, 3V 1A SBOOVT 508A, 4V 1A, 4V 1A, 5V 1A SBOOVT 508A, 6V 1A, 4V 1B 1B, 1B, 5V, 1B, 5V SBOOVT 508A, 6V 1A, 4V 1B 1B, 1B, 5V, 1B, 5V SBOOVT 508A, 6V 1A, 4V 1B 1B, 1B, 5V, 1B, 5V SBOOVT 508A, 6V 1A, 4V 1B 1B, 1B, 5V, 1B, 5V SBOOVT 508A, 6V 1A, 4V 1B 1B, 1B, 5V, 1B, 5V SBOOVT 508A, 6V 1A, 5V 1A, 5V 1A, 5V 1A SBOOVT 508A, 6V 1A, 6V 1A, 5V 1A, 5V 1A SBOOVT 508A, 6V 1A, 6V 1A, 5V 1A, 5V 1A SBOOVT 508A, 6V 1A, 6V 1B, 5V 1A, 5V 1A SBOOVT 508A, 6V 1A, 6V 1B, 5V 1B, 5 TRANSFORMERS Variable 1tC Power Sun-ply, Full Wave Rectifica-tion, floodwift filter Condeinser, fused, Rated Model 2DCF, \$12.98 Model 4DCF, \$20.98 OIL CONDENSER 10 MFD \$1.75 ea. Case dimensions, not including insulators 41.5H x 3% W x 114.7D, Smaller Quantities, special V Write for TUBES U. S. A. INFRARED SNOOPERSCOPE A caps at 600, 100 & 15V; 1 P25 Infrared tube. SPECIAL S BRITISH SNOOPERSCOFE dark 2° diameter image of the sensitivity Willemite screen M-1 vibrator supply brator 4000VDC power samply rescope kit includes 1P25 M-1 power definition and the second date & definition of the second date & 25 of 2

THAT'S AUY

nesperson nesperson of the second of the sec

Heavy Buty Transforms.
Heavy Buty Transforms.
Heavy Biow toreh. Instant light no east a 7712 Blow toreh. Instant light no 53.75



Boost your converter sales



Give Your Customers

their choice

...with two Mallory converter styles

Mallory . . . and only Mallory . . . offers you both types of ALL-CHANNEL UHF CONVERTERS—one designed to fit inside any TV set and the other to be used on or beside any set.

The New Mollory '188' Conceoled Converter is mounted inside the TV set... out of sight! All that shows is a clear plastic selector dial and switch. Installation is easy. A bracket and four screws are supplied to mount the unit on either side or at the top in wood cabinets. For plastic or metal cabinets, the converter may be mounted on the fiber-board rear enclosure.

Both the Mollory '188' and the Mollory '88' Cabinet Model give the same trouble-free performance, that has made Mallory the leading converter in every area since the start of UHF telecasting.



No radiation problem! Mallory Converters contain specially designed components to prevent troublesome interference from radiation—a problem common to low quality converters which can ruin TV reception over a wide area.

Give yourself greater Converter Sales . . . By giving your Customers Their Choice of Mallory Converters.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA